
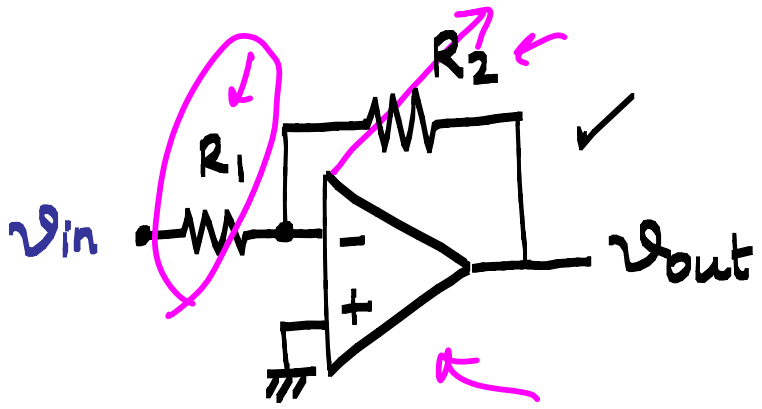


BRIEF CONTACT WITH AMPLIFIER DESIGN


INVERTING AMPLIFIER

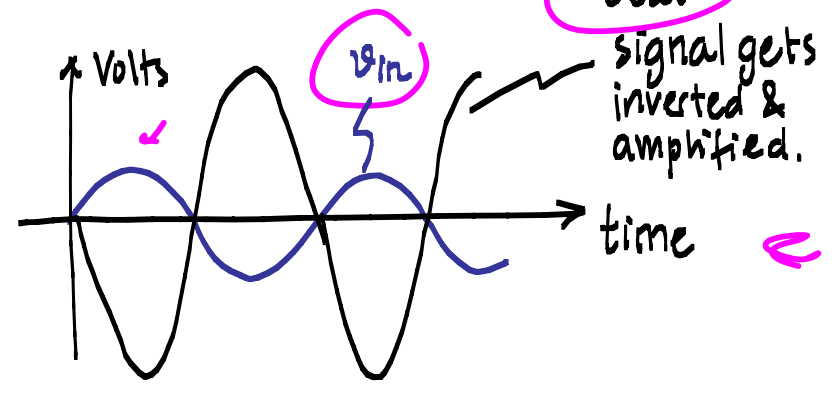


$$\text{Gain: } \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$



NON-INVERTING AMPLIFIER

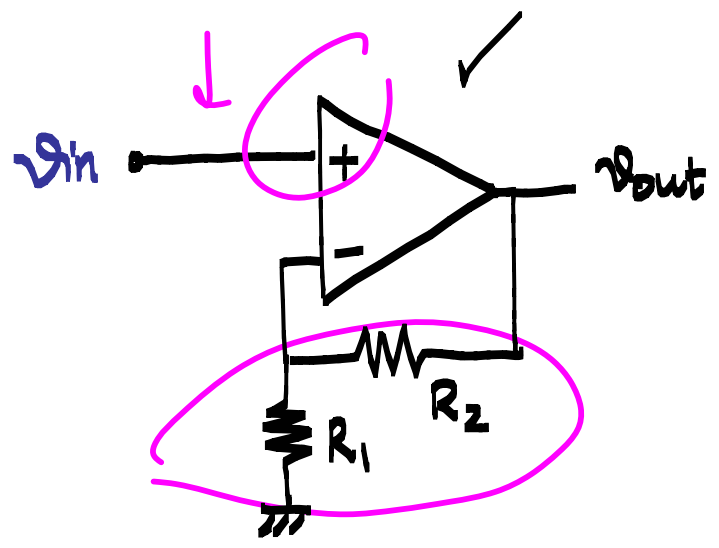

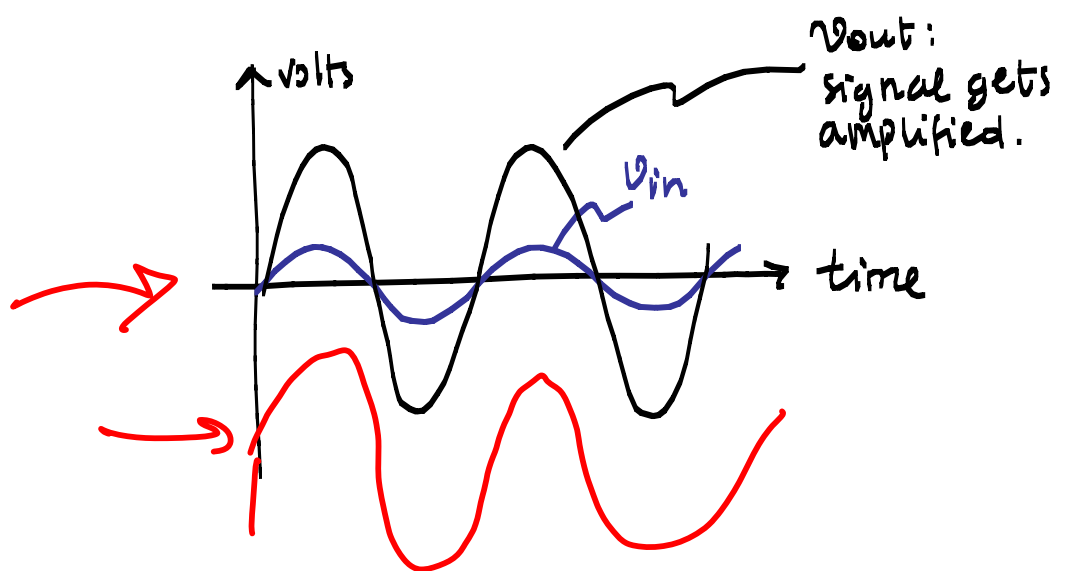
$$\text{Gain: } \frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$$



BRIEF CONTACT WITH AMPLIFIER DESIGN

ADDER

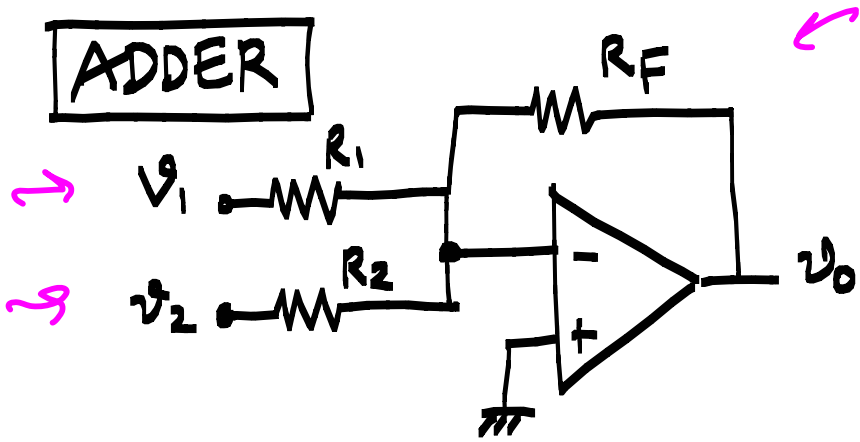


$$v_o = v_1 \left(-\frac{R_F}{R_1} \right) + v_2 \left(-\frac{R_F}{R_2} \right)$$

Use this topology to amplify the sum of two signals




DIFFERENTIAL AMPLIFIER

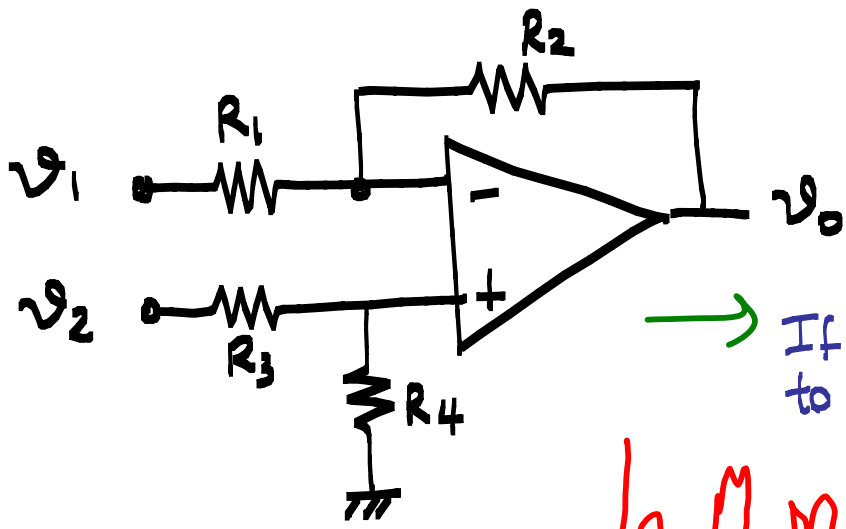


$$v_o = v_2 \left[\frac{R_4}{R_3 + R_4} \right] \left[1 + \frac{R_2}{R_1} \right] - v_1 \frac{R_2}{R_1}$$

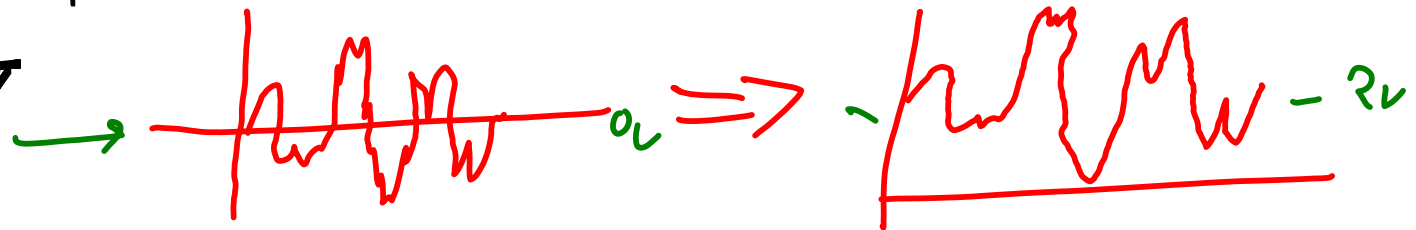→ If v_2 is a DC value, you could use this topology to add an OFFSET to a signal ←




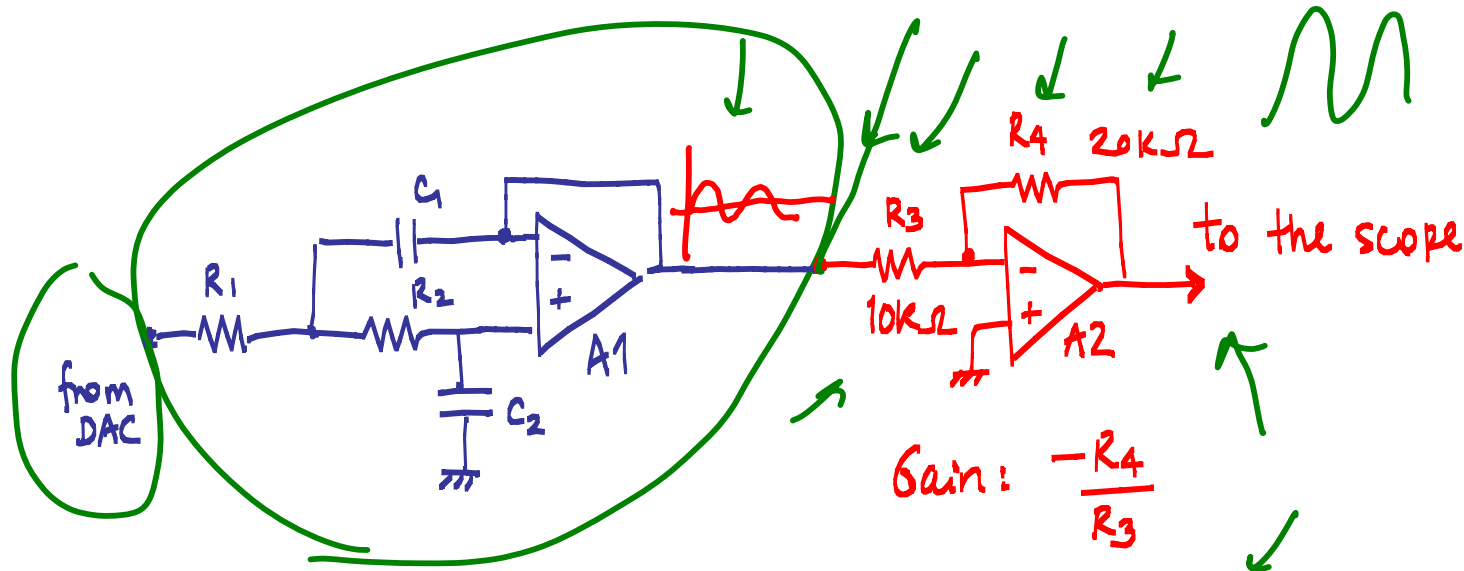So, for instance, how would a filter followed by an amplifier look like?



In this one resistor R_3 poses a load to amplifier A1. It's important to consider that for the power requirements of R_3 (hence, R_3 can't be small)

$$\text{Gain: } -\frac{R_4}{R_3}$$

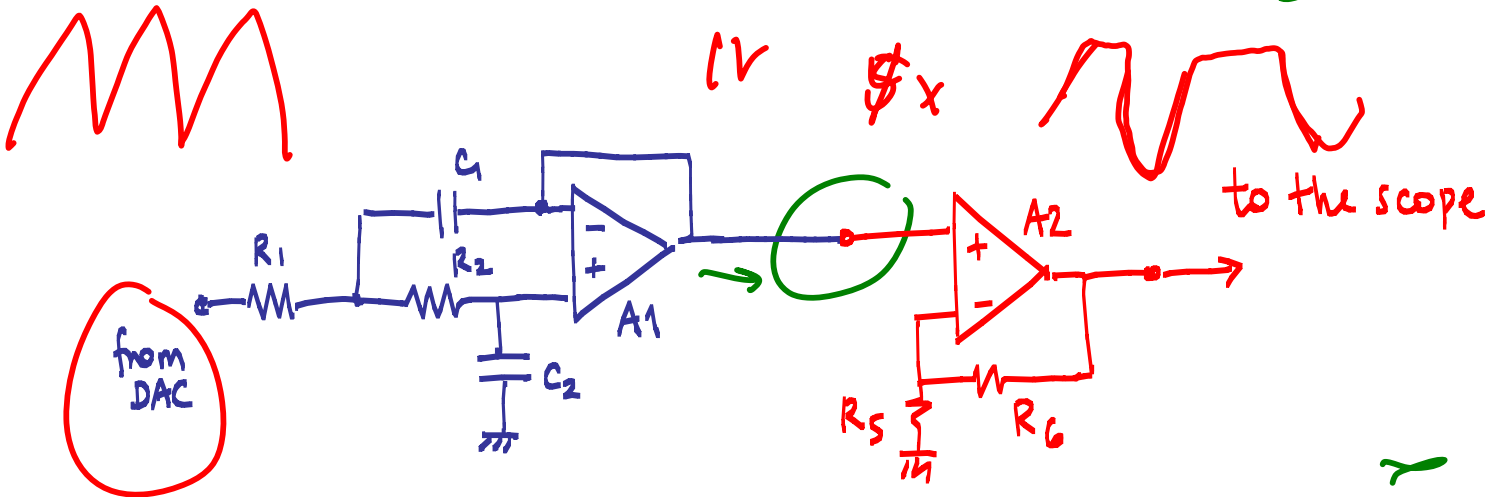

In this one no load effect is imposed on A1 but if resistors R_5 & R_6 are small then A2 will have to provide the current for them.

$$\text{Gain: } 1 + \frac{R_6}{R_5}$$

$$\text{For gain of 2: } R_6 = R_5$$