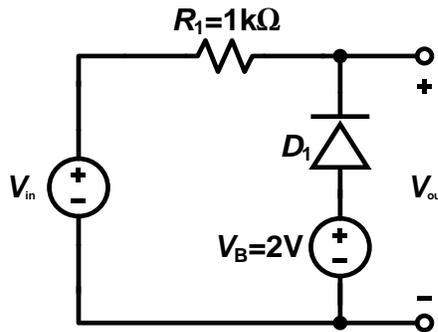


Name: \_\_\_\_\_

**EXAM #1 EXTRA POINTS***All work is to be your own - show your work for maximum partial credit.*

1. For the circuit shown below, assume *a constant voltage diode* model (i.e.  $V_{D,on}=0.8$ ):



- (a) Plot input/output characteristics (i.e.  $V_{out}$  vs  $V_{in}$  plot).

- (b) Find the current flowing through the resistor when the input is a DC source of 1V (i.e.  $V_{in} = 1V$ ).

(c) In part (a), the input is given by  $V_{in}(t)=V_p\sin(\omega t)$ , where  $V_p=5V$  and  $\omega=2\pi\cdot 60$  rad/s. Plot input and output waveforms,  $V_{in}(t)$  and  $V_{out}(t)$  respectively as a function of time,  $t$ .