

HW #2

- 1) **Turn in Textbook problems** 2.11, 2.13, 2.15, 2.27.
- 2) Solve problem **2.19** using iteration as well as the load-line analysis (graphical) method discussed in class. You may use any software (Matlab etc.) to plot the diode I-V characteristics.

Solve on your own (no need to turn in): 2.10, 2.12, 2.16, 2.24.