

HW #3

- 1) **Textbook problems** 3.3, 3.9 (b,d); 3.11(b,d); 3.15 (a, b); 3.37.
- 2) Do textbook problems 3.41 and 3.45 and simulate them using Cadence (use diode model D1N4002 as in the examples provided on the ECE310 server).