

HW #6

- 1) **Textbook problems:** 17.1, 3, 5, 7, 13, 17, 19, 21, 25, 27. You will find the values of transistor parameters in the textbook at the beginning of the problem set.
- 2) Solve textbook problems 17.57 and 17.61.
- 3) Using Cadence, plot g_m vs V_{GS} , and r_o vs V_{DS} for several values of V_{GS} , for the NMOS ($18\mu/0.18\mu$) as well as the PMOS ($36\mu/0.18\mu$). Explain the behavior observed in these curves.
Hint: Use the derivative operator `deriv()` in ADE calculator tool for the plots, as shown in the tutorial.

Solve on your own (Don't turn these in): 17.2, 4, 6, 8, 14, 16, 18, 20, 24, 28.