

HW #9

- 1) **Textbook problems:** Textbook problems 5.3 (a,c); 5.7, 5.11, 5.17, 5.21, 5.35, 5.37, 5.39 (a,b), 5.55, 5.65. Use nominal base-emitter voltage $V_{BE,nom} = 0.7V$ if needed.