

ECE 310 MICROELECTRONICS I

EXAMPLES

VISHAL SAXENA
VSAXENA@UIDAHO.EDU

RAFAEL AKIO ALVES WATANABE
ALVE8348@VANDALS.UIDAHO.EDU



FIGURE 2-31 IV CURVE

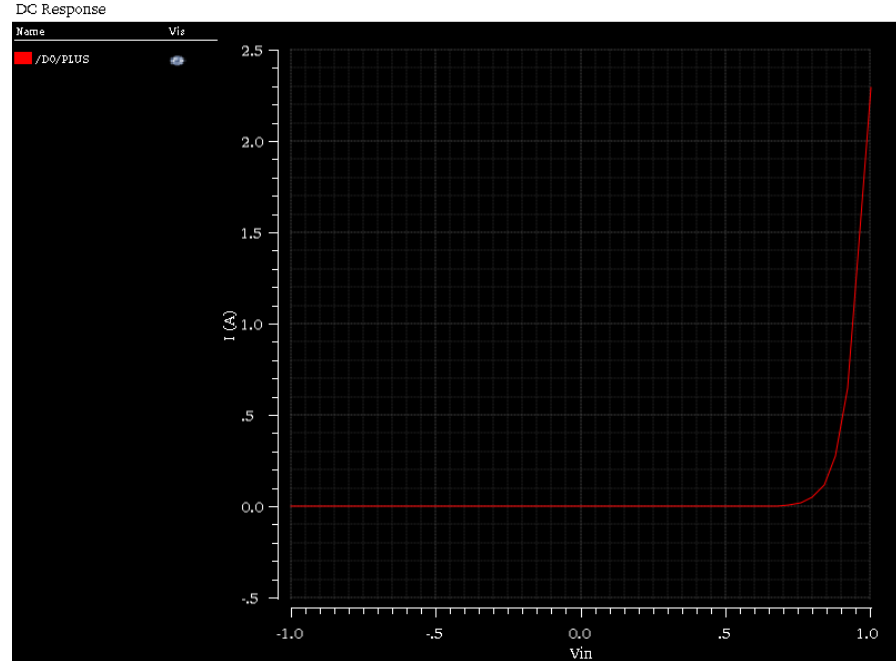
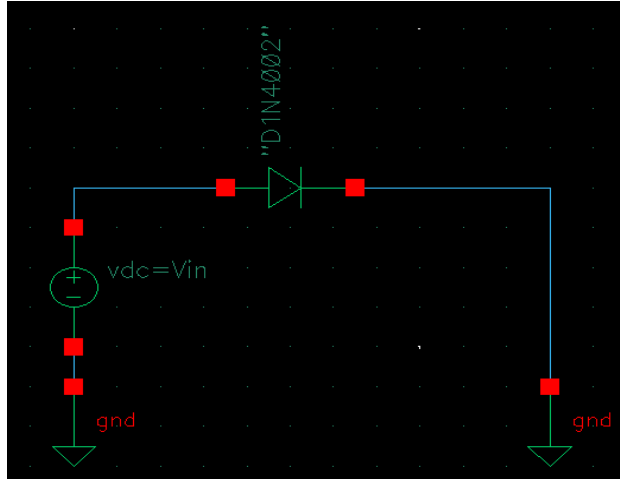


FIGURE 2 – LOAD LINE

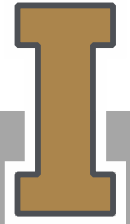
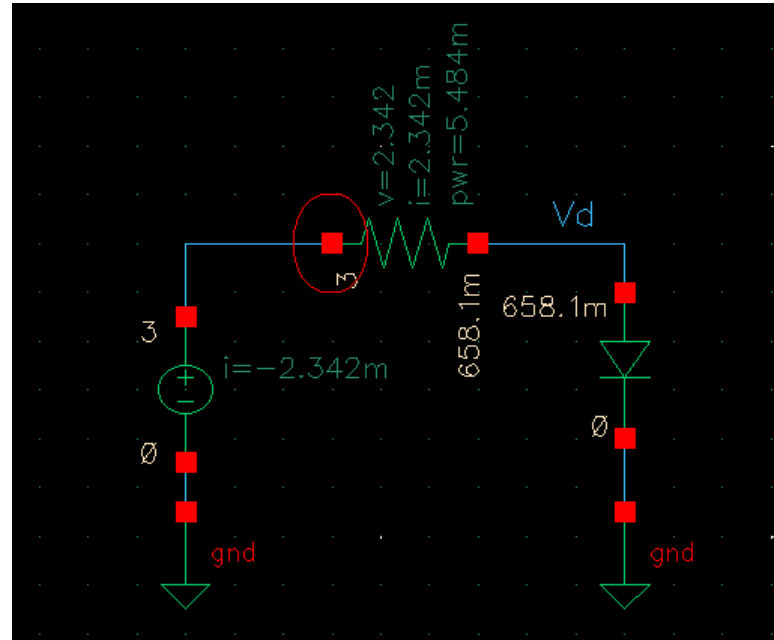


FIGURE 2 – REVERSE RECOVERY


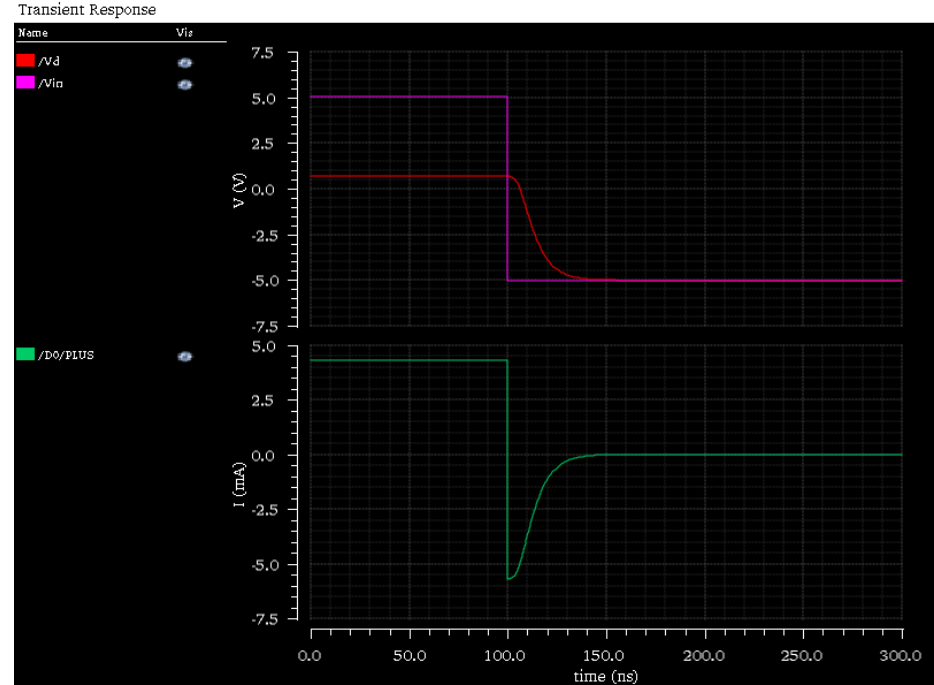


FIGURE 3-57 VOLTAGE DOUBLER

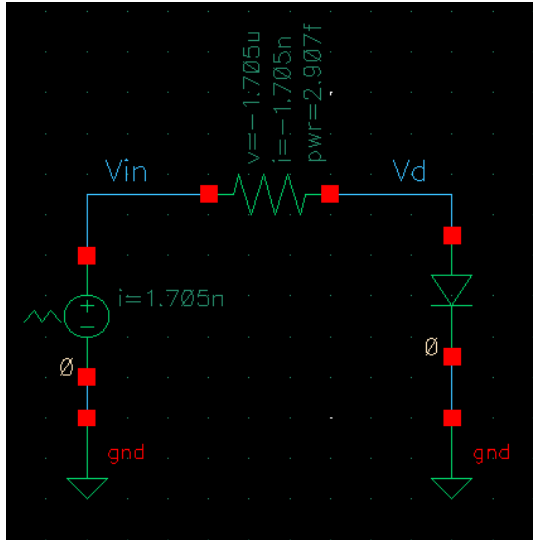