

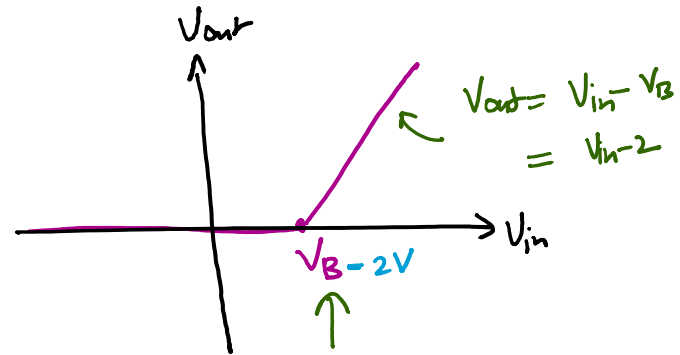


ECE 310 - Lecture 12

Wednesday, February 7, 2018 10:27 AM


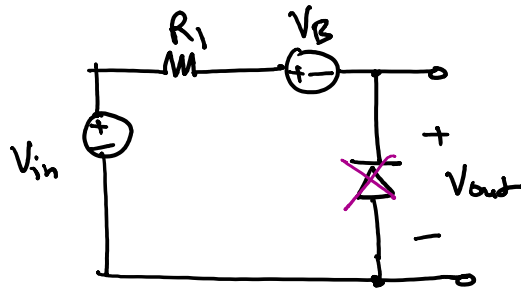


c) Ideal Diode

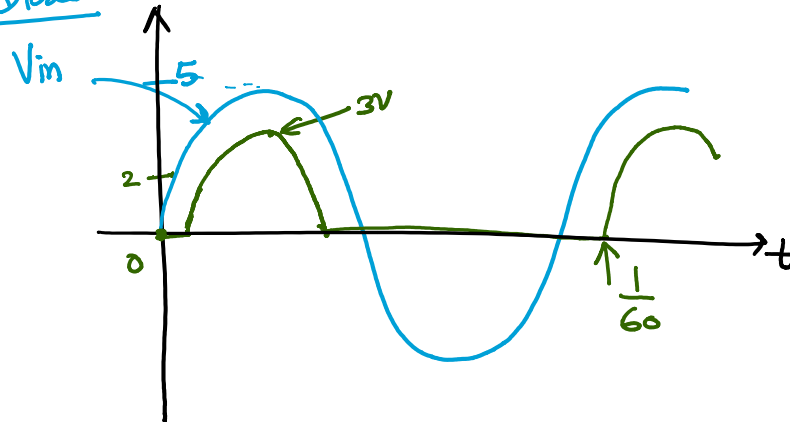

EXAM I is
ON Feb/12
Monday.

Half-Wave Rectifier

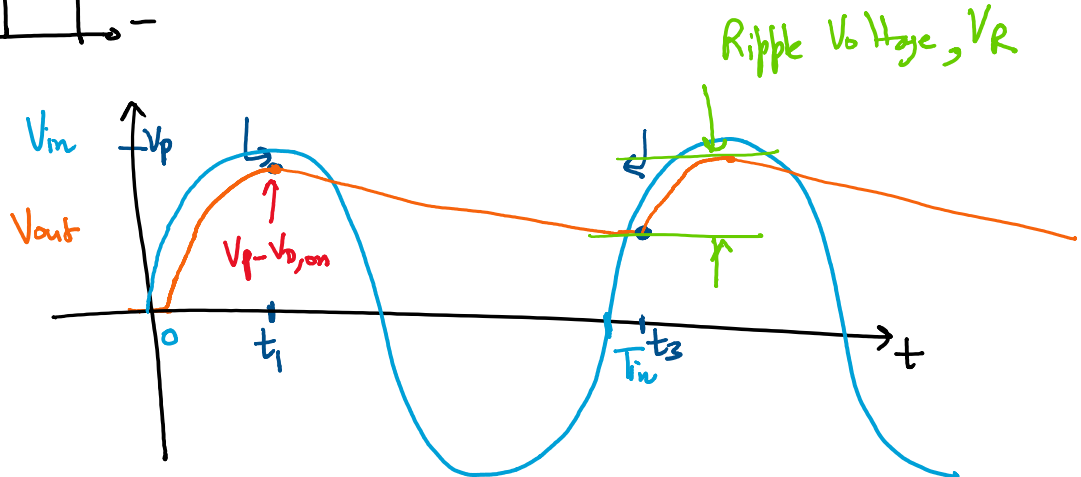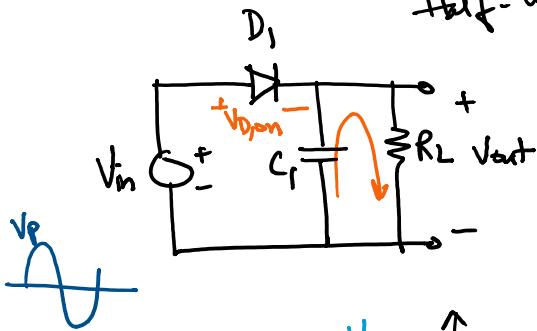

$$V_{out}(t) = (V_p - V_{d,on}) e^{-t/R_L C_1}$$

$$\tau = R_L C_1$$

time constant


Taylor Expansion

$$e^{-t/R_L C_1} \approx 1 - \frac{t}{R_L C_1}$$

$$t \ll R_L C_1$$

$$\Rightarrow V_{out}(t) \approx (V_p - V_{d,on}) \left(1 - \frac{t}{R_L C_1} \right)$$
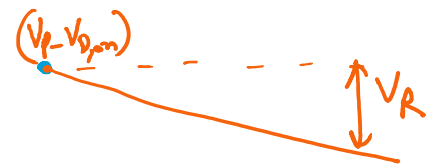
$$= \underbrace{(V_p - V_{d,on})}_{\text{initial condition}} - \underbrace{\frac{(V_p - V_{d,on})}{R_L C_1} \cdot t}_{\text{drop}}$$



$$V_R = \frac{V_p - V_{d,on}}{R_L} \cdot \frac{T_{in} - \Delta T}{C_1}$$

ΔT is the time when D_1 is ON, and charging the capacitor

for small ripple, $\Delta T \ll T_{in}$

$$V_o \approx \frac{V_p - V_{d,on}}{R_L} \cdot \frac{T_{in}}{C_1}$$

$$V_R \approx \frac{V_p - V_{D,on}}{R_L} \cdot \frac{T_{in}}{C_1}$$

$$V_R = \frac{V_p - V_{D,on}}{R_L C_1 \cdot f_{in}}$$

$$V_R \approx \frac{I_L}{C_1 f_{in}}$$

$f_{in} \leftarrow$ input frequency

$$I_L = \frac{V_p - V_{D,on}}{R_L} \in \text{max load current}$$

$$PIV \approx 2V_p$$

for Bridge Rectifier:

$$V_R \approx \frac{1}{2} \cdot \frac{V_p - 2V_{D,on}}{R_L C_1 f_{in}}$$

\Rightarrow FW has half the ripple than half wave rectifier

max reverse bias voltage across a

$$\text{diode} = V_p$$

$$PIV \approx V_p \quad (\text{NOT } 2V_p!)$$