

# ECE 310- Lecture 13

Thursday, February 8, 2018 1:12 PM

Half wave Rectifier:

$$PIV \approx 2V_p$$

$$V_R \approx \frac{V_p - V_{D(on)}}{R_L C_1 f_{in}} = \frac{I_L}{C_1 f_{in}}$$

← peak load current

Full-wave Rectifier:

$$PIV \approx V_p$$

$$V_R \approx \frac{1}{2} \frac{(V_p - 2V_{D(on)})}{R_L C_1 f_{in}} = \frac{I_L}{C_1 f_{in}}$$

Diode Peak Current:





$$I_p \approx \frac{V_p}{R_L} \left( R_L C_1 \omega_{in} \sqrt{\frac{2V_{in}}{V_p}} + 1 \right) \quad \leftarrow \text{Page 92-93}$$

$$R_L C_1 \uparrow \Rightarrow I_p \uparrow$$


$$\text{Book Ex } \underline{3.28} \Rightarrow I_p = 577 \text{ A} \leftarrow \text{Too large!}$$

Read Book Examples: 3.27 & 3.28

# Section 3.5.2

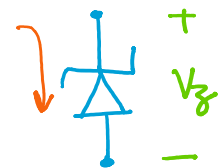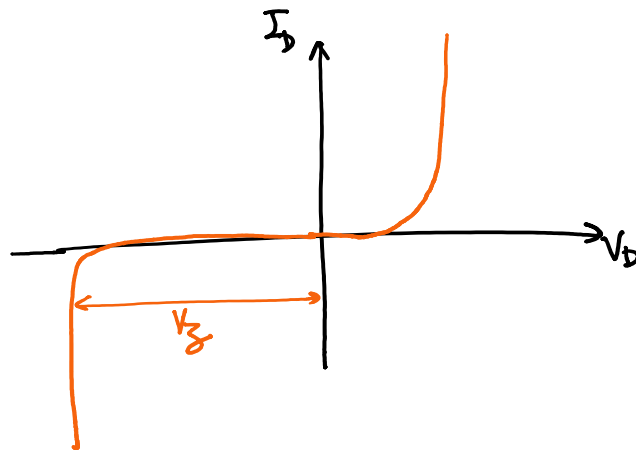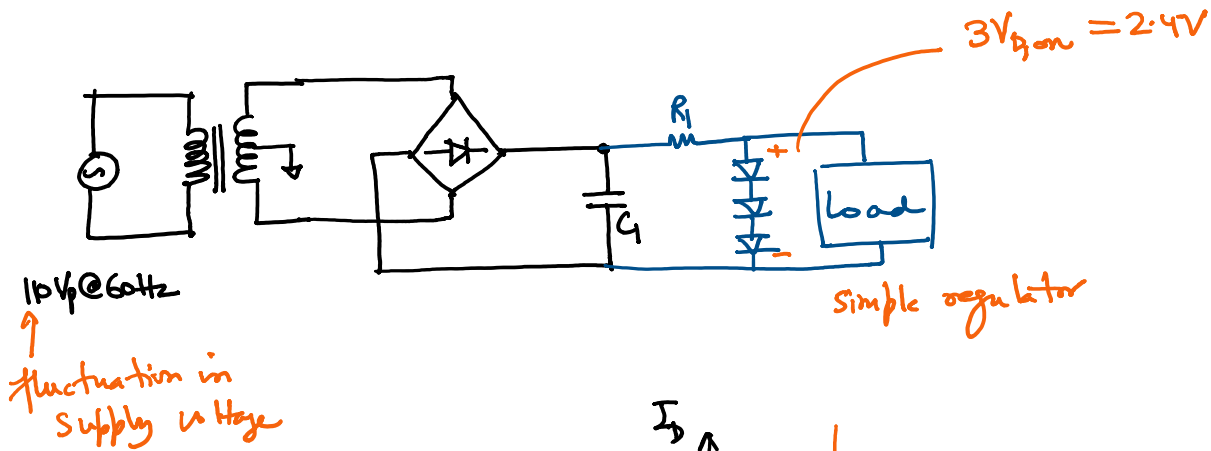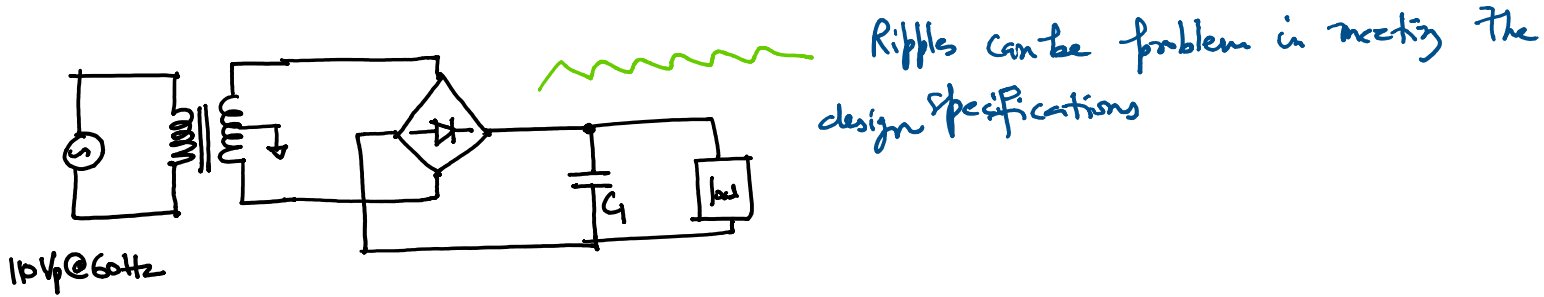

Can use zener diode as a regulator




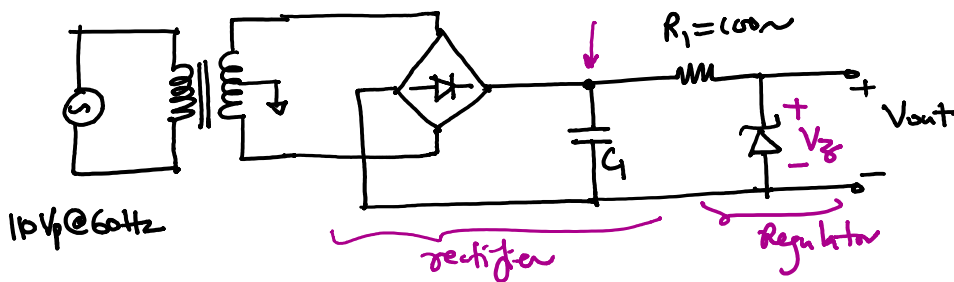


Read on your own: 3.5.2 → Voltage Regulators  
Limiting Circuits

Read on your own:

3.5.2 → Voltage Regulators  
3.5.3 → Limiting Circuits  
3.5.4 → Voltage Doublers.

# Small signal operation of a Diode:

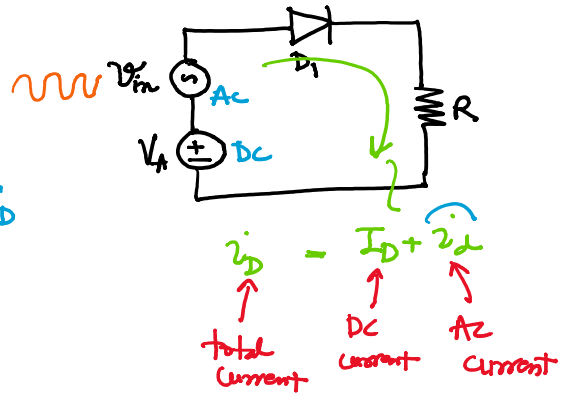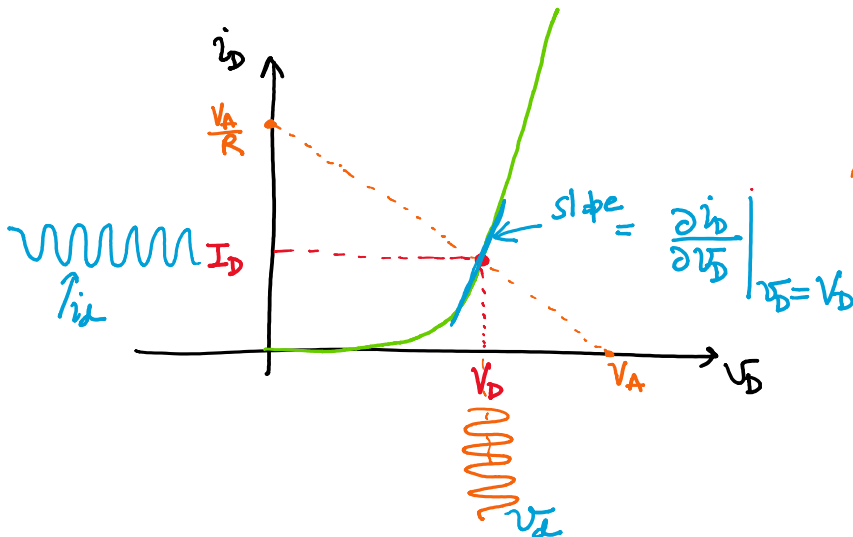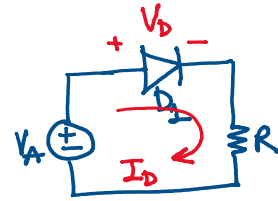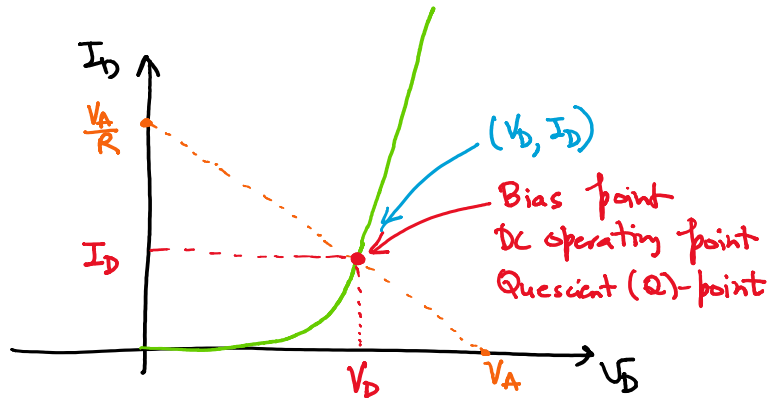

input voltage  $\Rightarrow V_A + v_{in}$

Diode voltage  $\Rightarrow v_D = V_D + v_d$

Diode current  $\Rightarrow i_D = I_D + i_d$

how does  $i_d$  relate to  $v_d$

$$\Delta i_D = \left. \frac{\partial i_D}{\partial v_D} \right|_{v_D = V_D} \cdot \Delta v_D$$

$$\Rightarrow i_d = \left( \left. \frac{\partial i_D}{\partial v_D} \right|_{v_D = V_D} \right) v_d \leftarrow \text{Small signal voltage (ac)}$$

Small signal

$i_a = \left( \frac{\partial i_D}{\partial v_D} \right)_{v_D = V_D} v_a$  ← Small signal voltage (ac)  
 ← Small signal current

$$\frac{\partial i_D}{\partial v_D} = \frac{\partial}{\partial v_D} \left( I_S e^{\frac{v_D}{nV_T}} - 1 \right) = \frac{1}{nV_T} \cdot I_S e^{\frac{v_D}{nV_T}} \stackrel{= i_D}{\approx}$$


$$= \frac{i_D}{nV_T}$$

$$\left. \frac{\partial i_D}{\partial v_D} \right|_{v_D = V_D} = \frac{I_D}{nV_T} = \frac{I_D}{V_T} \text{ for } n=1$$

↑ dimension of conductance  $\equiv g_a \triangleq \frac{1}{r_a}$


$$i_a = g_a v_a = \frac{v_a}{r_a} \rightarrow r_a = \frac{V_T}{I_D}$$

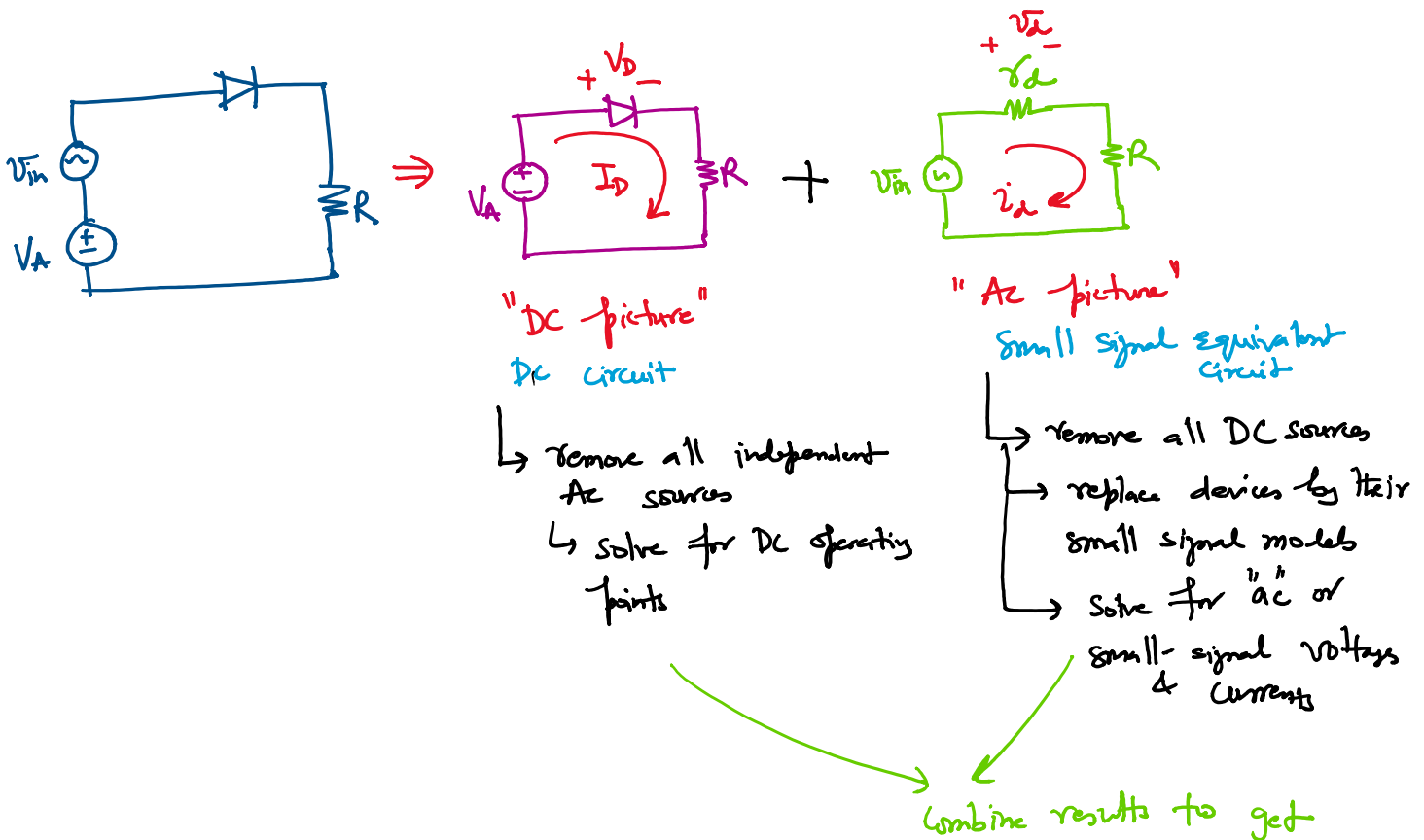Diode behaves like a linear resistor for small signal inputs



Combine results to get final answers.

"Small signal Analysis" method








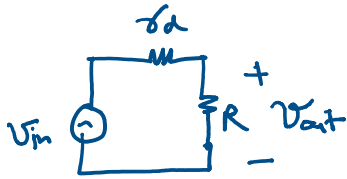










$$V_{out} = V_{in} \cdot \frac{r_d}{r_d + R}$$

$$V_{out} = I_D R$$

$$\text{Total output voltage} = \underbrace{I_D R}_{\text{DC}} + \underbrace{V_{in} \cdot \frac{r_d}{r_d + R}}_{\text{AC}}$$



## Clipping + Clamping :

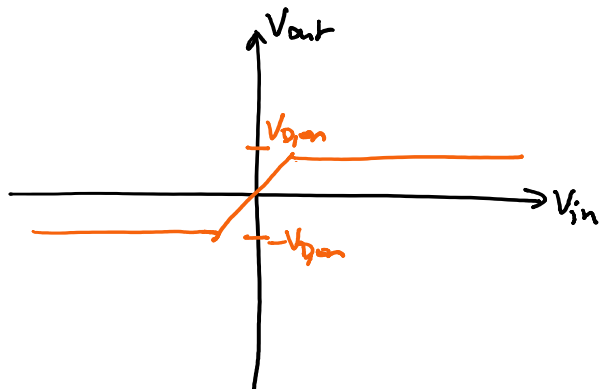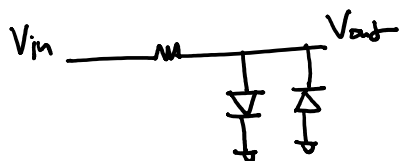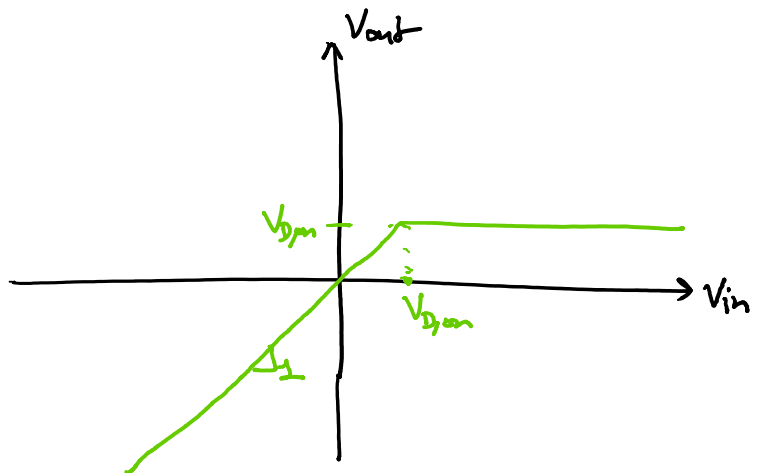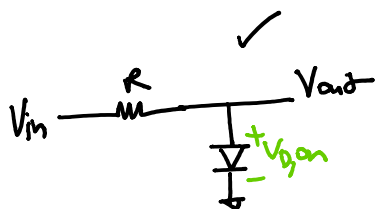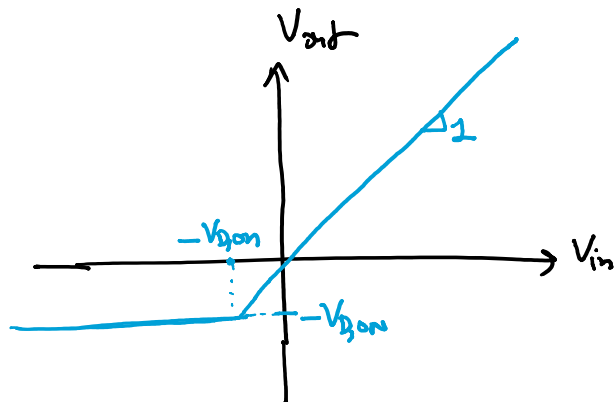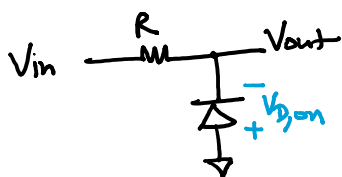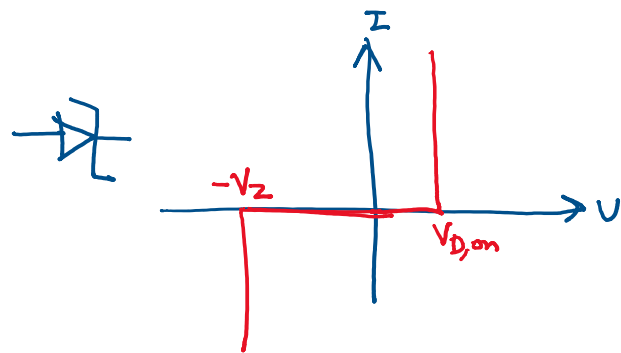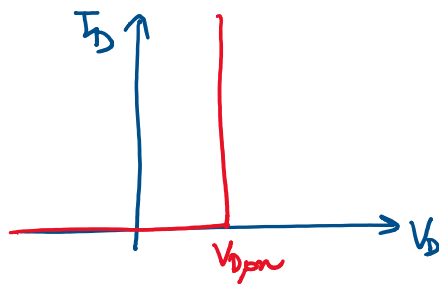

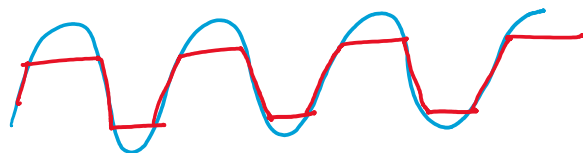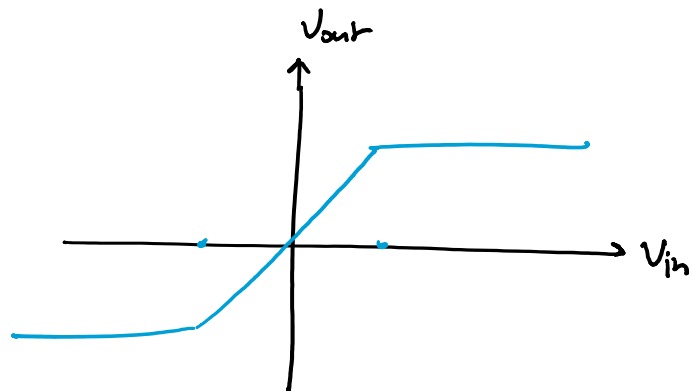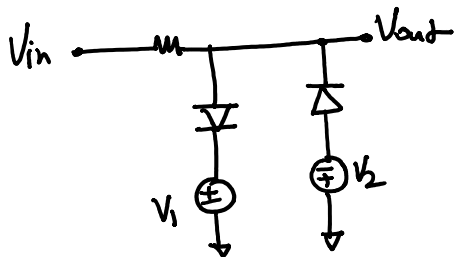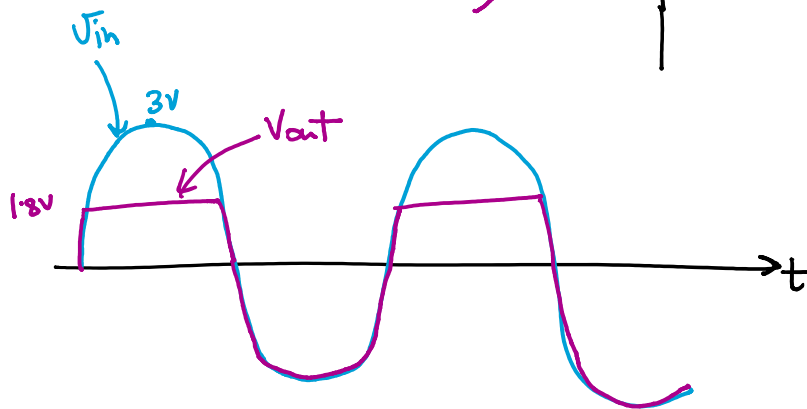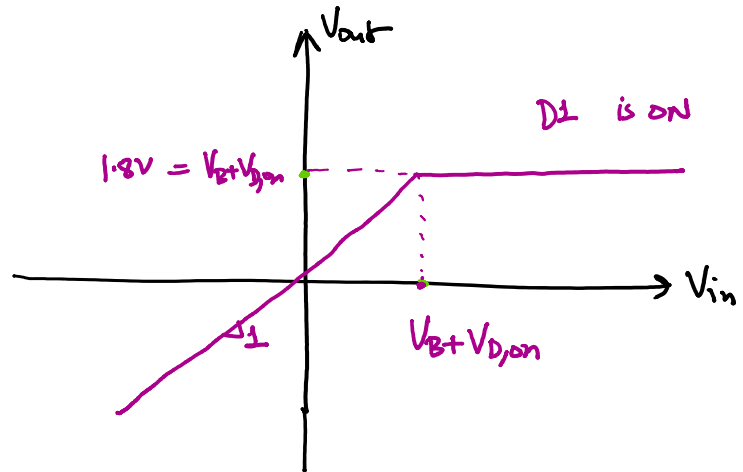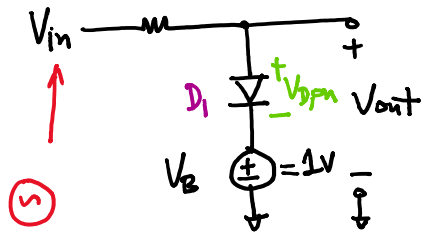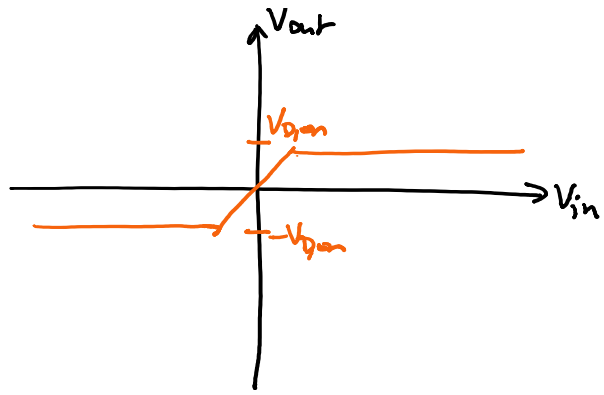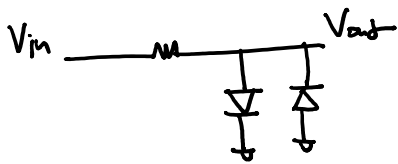




Ex 3.12

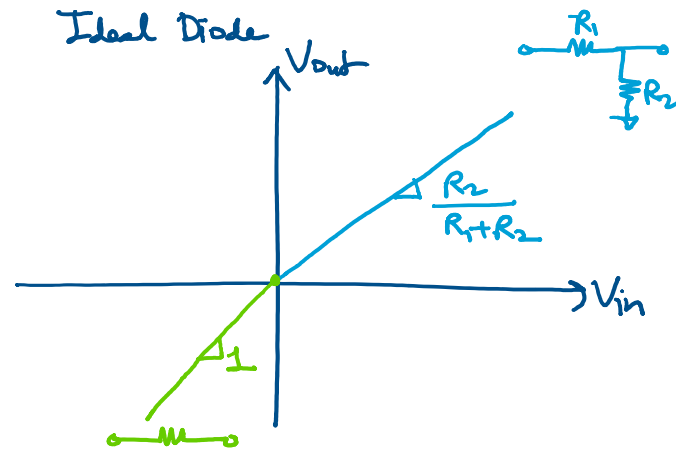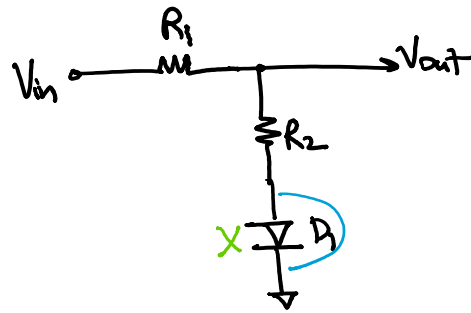


a) for  $V_{in} < V_{D_{on}}$ ,  $D_1$  is off  $\Rightarrow V_{out} = V_{in}$

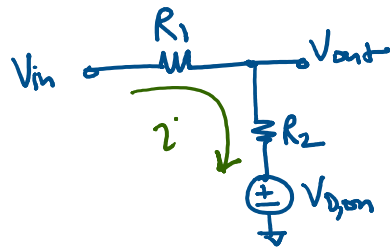b) for  $V_{in} > V_{D_{on}}$ ,  $D_1$  is ON  $\Rightarrow$



$$i = \frac{V_{in} - V_{out}}{R_1} = \frac{V_{out} - V_{D_{on}}}{R_2}$$
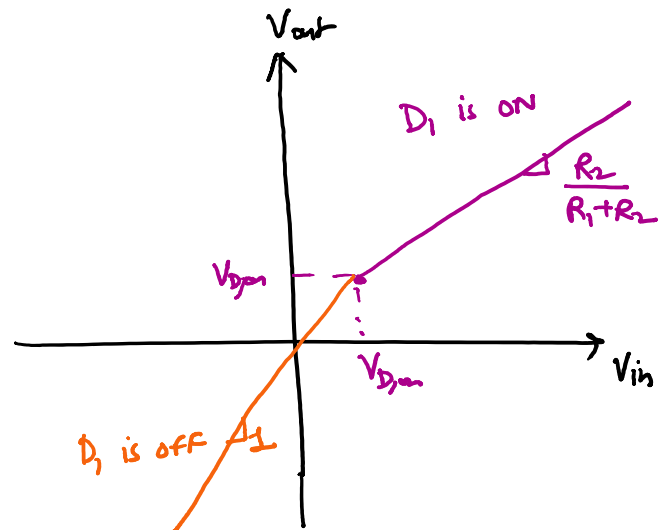
$$\Rightarrow V_{out} = \frac{\frac{R_2}{R_1} V_{in} + V_{D_{on}}}{1 + \frac{R_2}{R_1}}$$



\* Do Ex 3.15 & 3.16 on your own

Concludes Chapter 3.

\* Start with chapter 6 on wednesday.