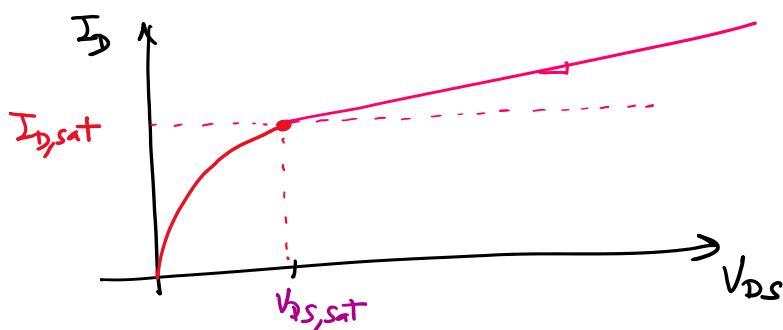


ECF 318 - Lecture 18


Monday, February 26, 2018 10:33 AM



$$V_{GS} > V_{THN}$$

$$V_{DS,sat} = V_{GS} - V_{THN}$$

Channel Length Modulation (CLM)

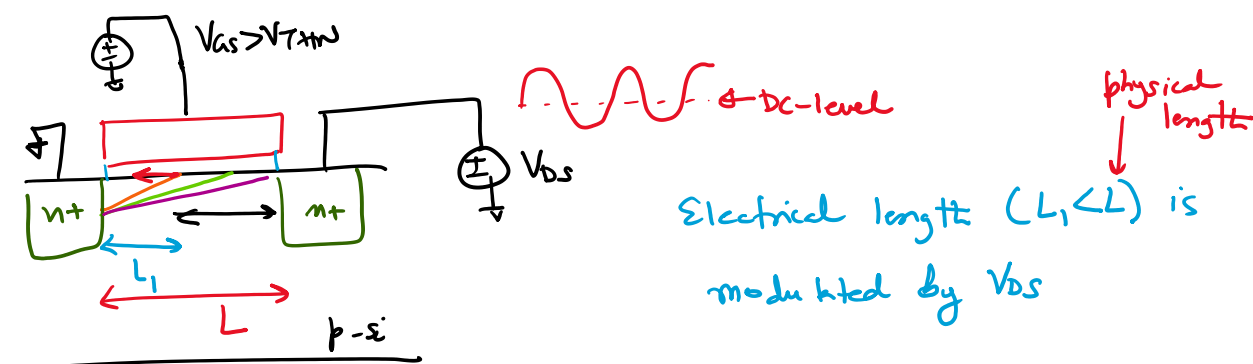

$$V_{DS} \uparrow \Rightarrow L_1 \downarrow \Rightarrow I_D \uparrow \quad \Leftarrow \text{Short-channel MOSFETs } L < 1\mu\text{m}$$

Sat:
$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{THN})^2$$

\uparrow
 $I_{D,sat}$

If we want to include "CLM" into saturation I_D equation


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{THN})^2 (1 + \lambda V_{DS})$$

\swarrow curve fitting parameter

$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{THN})^2 \cdot \lambda V_{DS}$ \Leftarrow some textbooks use this

$$\lambda \propto \frac{1}{L}$$

ΔL is now
comparable to L

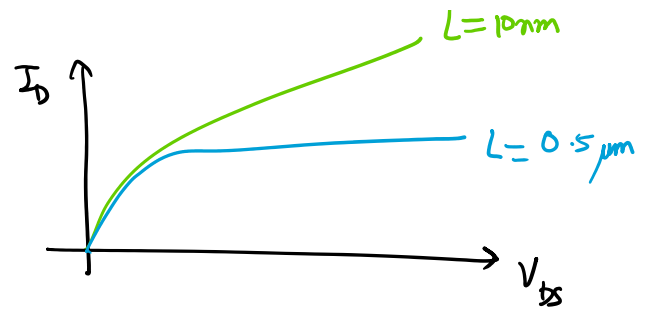

180nm CMOS
 $(L_{min} = 180nm)$
 $V_{DD} = 1.8V$

Ex 6.6

Calculate bias current of M_1


$$K_n = \mu_n C_{ox} = 100 \frac{\mu A}{V^2}$$

$$V_{THN} = 0.4V$$

$$\frac{W}{L} = \frac{2\mu m}{0.18\mu m}$$

$$V_{GS} = 1V > 0.4V$$

$$\Rightarrow \text{ON}$$

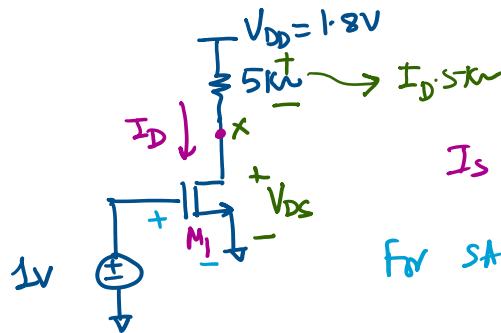

Is M_1 SAT or TRIODE Region?

for SAT: $V_{DS} \geq \underbrace{V_{GS} - V_{THN}}_{V_{DS,sat}}$

* Assume M_1 is in SAT

$$I_D = \frac{1}{2} K_n \frac{W}{L} (V_{GS} - V_{THN})^2$$

$$= 200 \mu A$$

$K_n = \mu_n C_{ox}$
 \uparrow Transconductance parameter of the NMOS.

for hand calculations $\lambda = 0$

Go back and verify the assumption of SAT.

$$V_{DS} = V_{DD} - I_D \cdot R_D$$

$$= 1.8 - 200 \mu A \times 5k\Omega$$

$$= 0.8V$$

$$V_{DS,sat} = 1 - 0.4 = 0.6V$$

$\therefore V_{DS} > V_{DS,sat}$ M_1 is really in SAT.


$$I_D = 200 \mu A$$

$$V_{DS} = 0.8V$$

Ans.

$$ax^2 + bx + c = 0$$
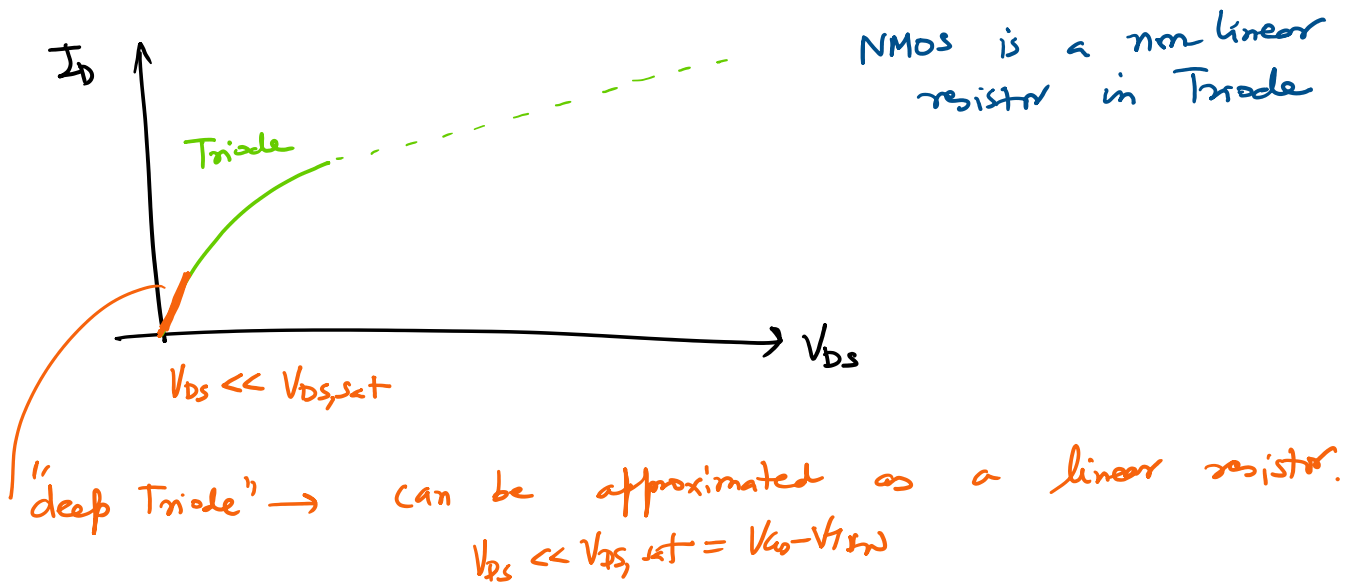
$$x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$



$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{dd} - V_{thn}) V_{gs} - \frac{V_{gs}^2}{2} \right] \rightarrow \textcircled{1}$$

ON resistance

$$R_{on} = \frac{\partial V_{gs}}{\partial I_D} = \left[\frac{\partial I_D}{\partial V_{gs}} \right]^{-1} = \frac{1}{\mu_n C_{ox} \frac{W}{L} [V_{dd} - V_{thn} - V_{gs}]}$$

R_{on} depends upon $V_{gs} \rightarrow$ non linear resistance



But for $V_{gs} < (V_{dd} - V_{thn})$


In Deep Triode

$$\rightarrow R_{on} \approx \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{dd} - V_{thn})} = \frac{1}{K \frac{W}{L} (V_{dd} - V_{thn})}$$

Resistance that depends upon V_{gs}

\Rightarrow voltage controlled Resistor

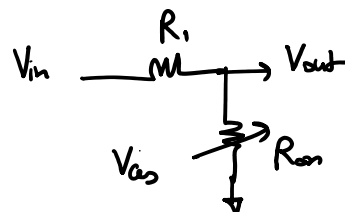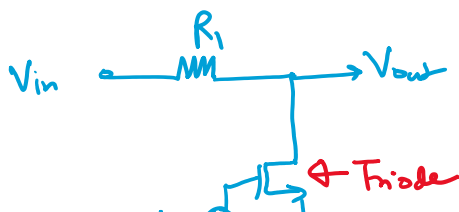


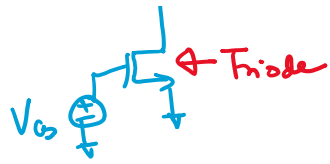


$$\frac{V_{out}}{V_{in}} = \frac{R_{on}}{R_{on} + R_1}$$


programmable voltage divider
 $R_{on} = R_{on}(V_{gs})$

Small-Signal Model

Monday, February 26, 2018 11:07 AM

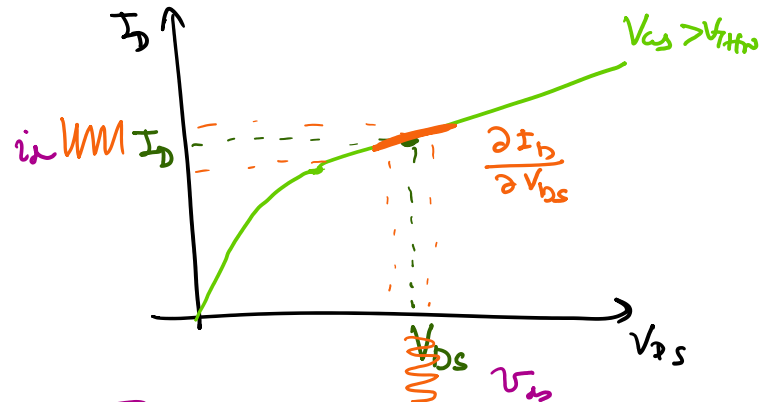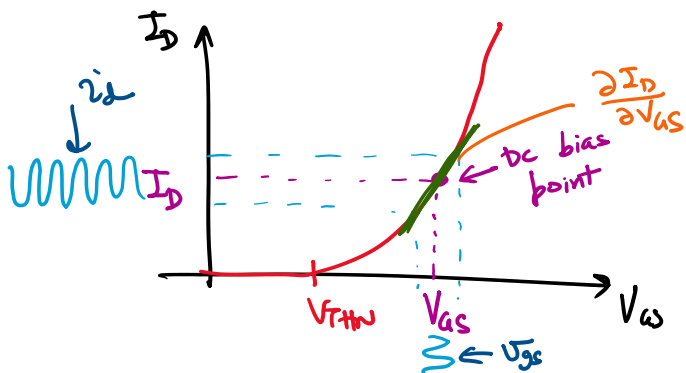

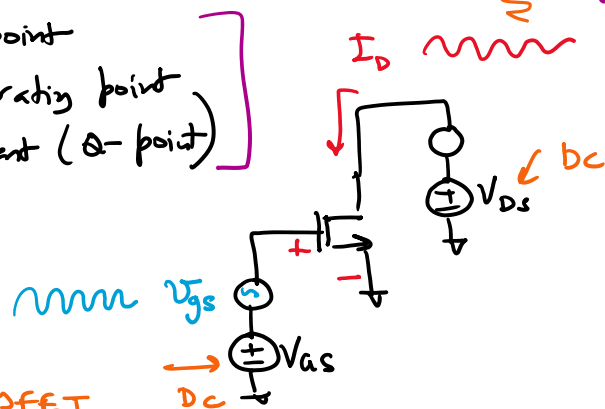$(V_{GS}, V_{DS}, I_D) \Leftarrow$ Bias point
DC operating point
Quiescent (Q-point)



Transconductance of the MOSFET

$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DS}=V_{GS} \leftarrow \text{DC bias point}}$$

$v_d = g_m v_{gs} \rightarrow \textcircled{1}$ $\rightarrow g_m$ depends upon the bias point

output resistance

$$r_o = \left[\frac{\partial I_D}{\partial V_{DS}} \right]^{-1}$$

$$r_o = \frac{1}{\lambda I_{D,sat}}$$


$$I_D = \underbrace{\frac{1}{2} k_p n \frac{W}{L} (V_{GS} - V_{TH})^2}_{I_{D,sat}} (1 + \lambda V_{DS})$$

$$= I_{D,sat} (1 + \lambda V_{DS})$$

$v_d = \frac{v_{gs}}{r_o} \rightarrow \textcircled{2}$

Small signal parameters $\Rightarrow g_m, r_o$

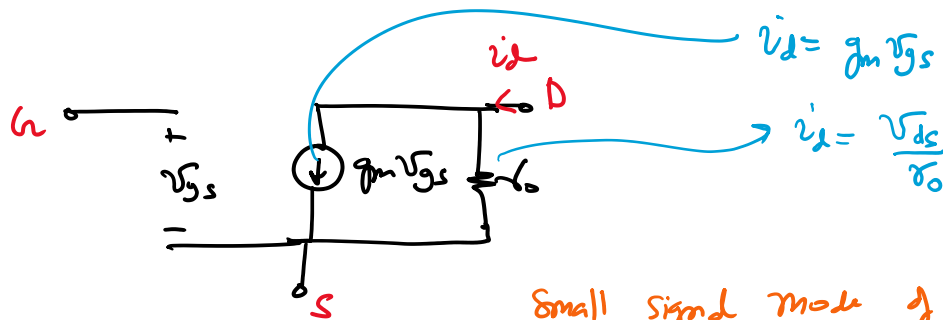\rightarrow can relate small change in input to other currents & voltages in the MOSFET circuit.



Small signal model of NMOS in Saturation.