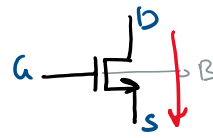



ECE 310- Lecture 19

Sunday, February 25, 2018 9:26 PM


NMOSFET \rightarrow NFET or NMOS in short





Current: $D \rightarrow S$

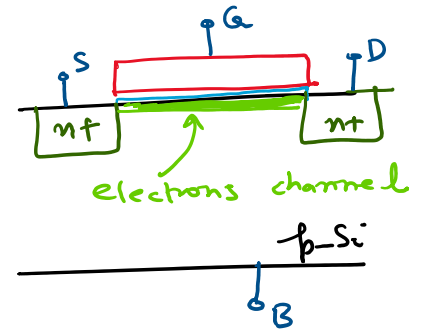

PMOSFET \rightarrow PFET or PMOS

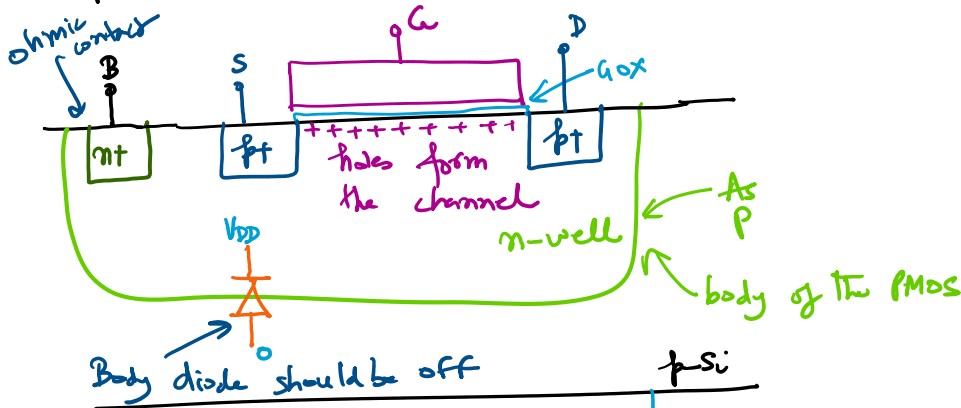


Starting material \rightarrow p-doped Si

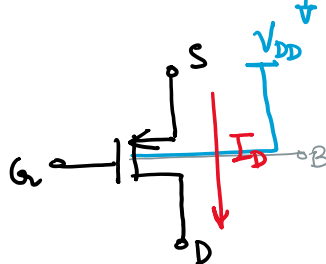
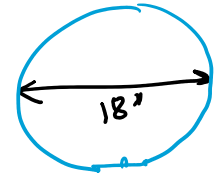


Current always flows from Source to Drain
 $S \rightarrow D$

PMOS body is connected to the highest p-potential on chip
 \rightarrow supply voltage, V_{DD}





$V_{DD} \rightarrow$ supply voltage

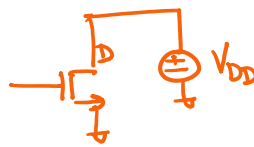

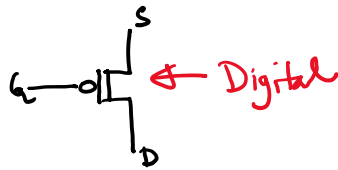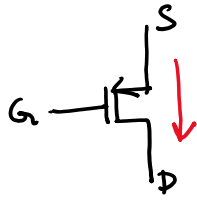

$V_{THP} \leftarrow$ Threshold voltage
 \hookrightarrow -ve number

All positive convention :

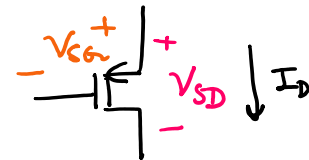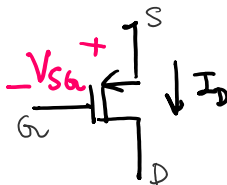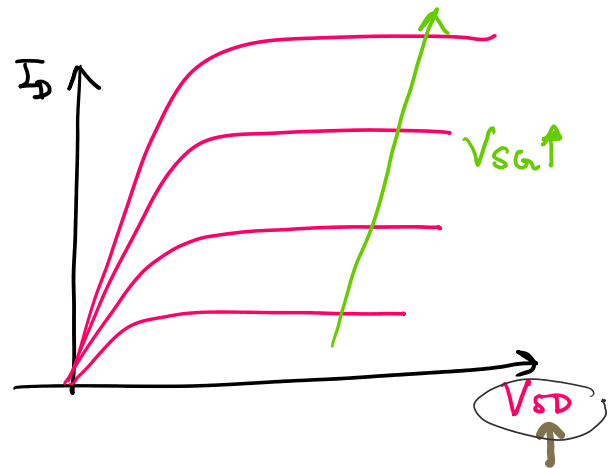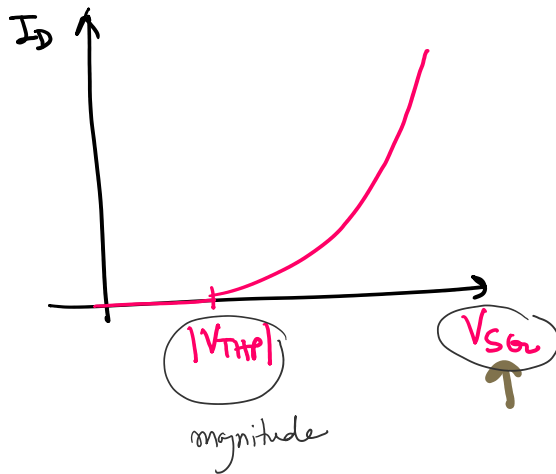

We use the magnitude of $|V_{THP}|$.

$$I_D = \begin{cases} 0 & V_{SG} < |V_{THP}| \quad \text{CUTOFF} \\ \mu_p C_{ox} \frac{W}{L} [(V_{SG} - |V_{THP}|) V_{SD} - \frac{V_{SD}^2}{2}], & V_{SD} < V_{SD, \text{sat}} \quad \text{TRIODE} \\ \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{THP}|)^2, & \text{SATURATION} \end{cases} \quad V_{SG} > |V_{THP}|$$


$$V_{SD, \text{sat}} = V_{SG} - |V_{THP}|$$

$$V_{GS} \rightarrow V_{SG}$$


- PMOS Equations

NMOS Equations $\xrightarrow{\begin{matrix} V_{GS} \rightarrow V_{SG} \\ V_{DS} \rightarrow V_{SD} \end{matrix}}$ PMOS Equations
 $V_{THN} \Rightarrow |V_{THP}|$
IV curves look similar

PMOS small signal model

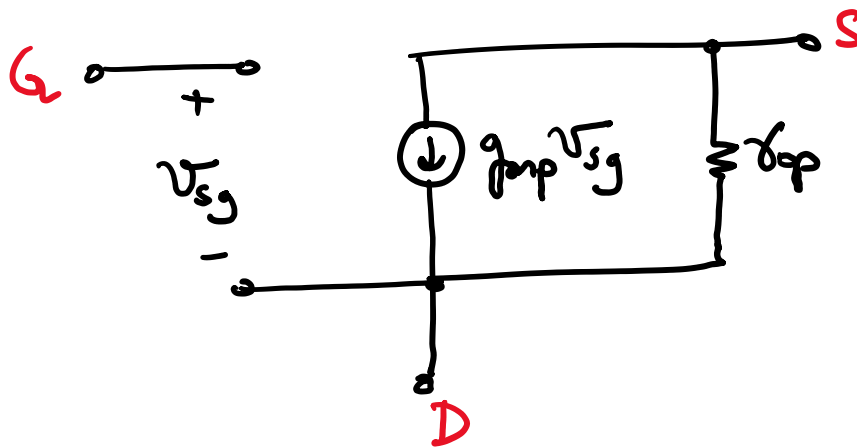

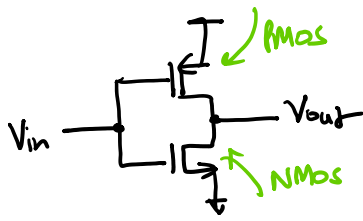CMos Technology : CMOS \Rightarrow Complementary MOS




\Rightarrow



CMos inverter (NOT gate)



8086 from
Intel

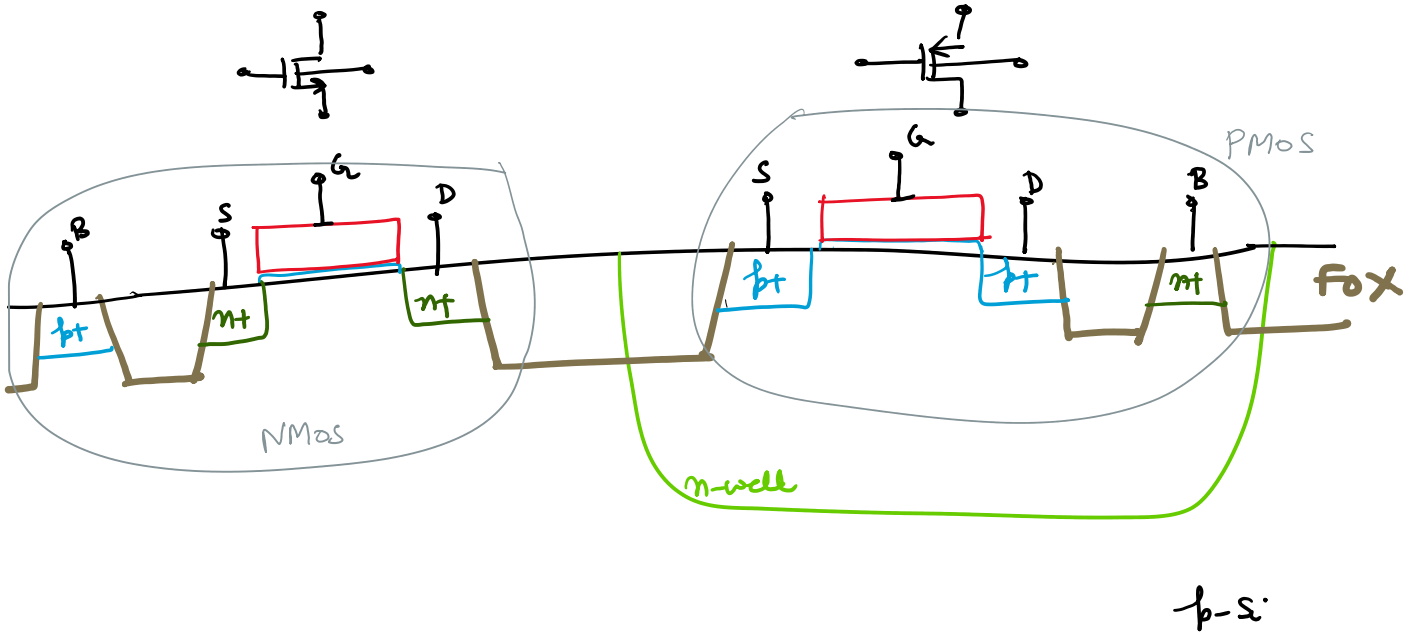

"Diode Connected MOSFETs"

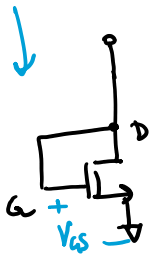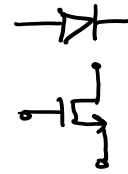


diode connected NMOS

if $V_{GS} > V_{THN} \Rightarrow ON$

$$V_{DS} = V_{GS} > (V_{GS} - V_{THN})$$

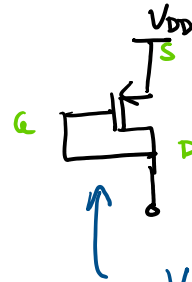\Rightarrow if the NMOS diode is ON, its always in Saturation!



Diode connected PMOS

$$V_{SD} = V_{SG} > (V_{SG} - |V_{THP}|)$$


\Rightarrow PMOS diode is always ON in SAT.

& never in TRIODE

Chapter 16 [clone of chapter 7] of the Textbook

Monday, February 26, 2018 12:22 AM

CMOS amplifiers:

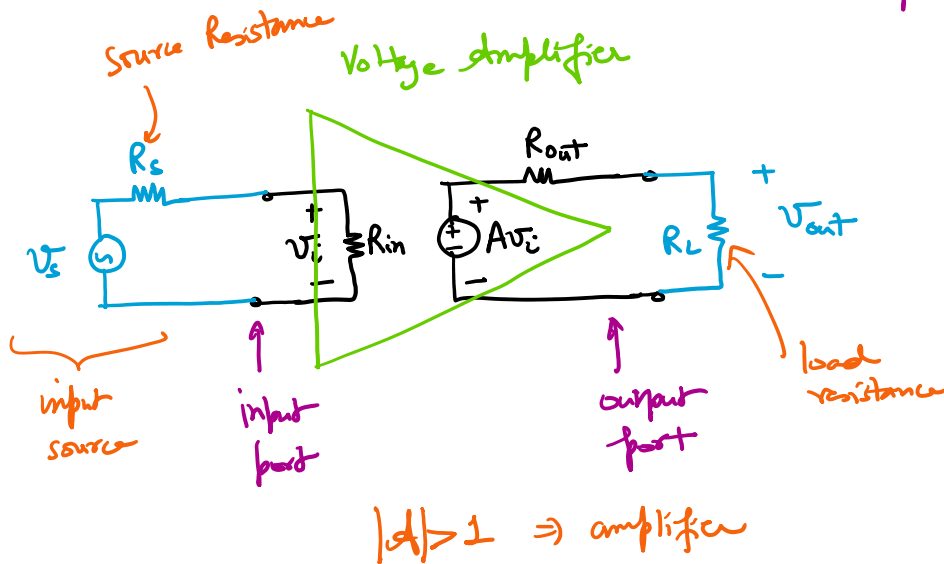

Ideal voltage amplifier:

→ At the input, the circuit must operate as a voltmeter
 * sense the input voltage without disturbing the previous stage (shouldn't "load" the previous stage)

$$V_i = \frac{R_{in}}{R_{in} + R_s} \cdot V_s \Rightarrow R_{in} = ?$$

$$= \frac{1}{1 + \frac{R_s}{R_{in}}} V_s = V_s \quad \text{if } \boxed{R_{in} \rightarrow \infty}$$

→ Similarly for an ideal voltage amplifier, we desire

$$\boxed{R_{out} \rightarrow 0}$$

all of the output voltage must appear across the load.

$$R_{in} \rightarrow \infty, R_{out} \rightarrow 0$$


$$R_{in} \rightarrow \infty, R_{out} \rightarrow 0$$

$$V_{out} = A \left(\frac{R_{in}}{R_s + R_{in}} \right) \left(\frac{R_L}{R_{out} + R_L} \right) V_s \Rightarrow AV_s \text{ iff } \begin{matrix} R_{in} \rightarrow \infty \\ R_{out} \rightarrow 0 \end{matrix}$$

* Important to estimate / analyze input & output impedances of amplifiers


(or analyze) How to measure input and output impedances?

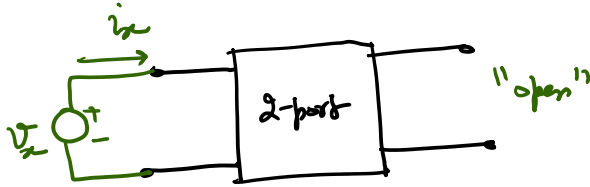open the output port & find small signal $\frac{v_x}{i_x} \triangleq Z_{in}$





$Z_{in} \equiv R_{in} = \frac{v_x}{i_x}$ ← input impedance

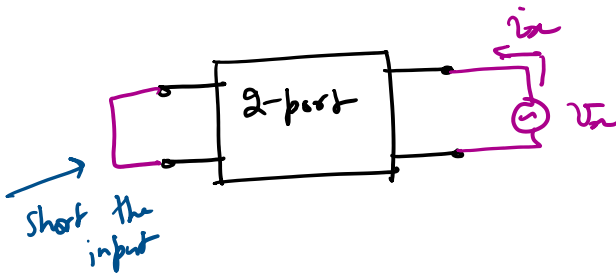Short the input port and find small signal $\frac{v_x}{i_x} \triangleq Z_{out}$







$Z_{out} \equiv R_{out} = \frac{v_x}{i_x}$

Examples

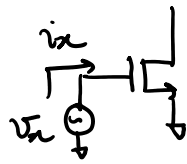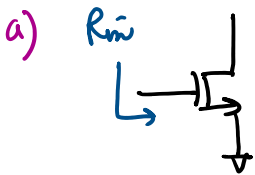


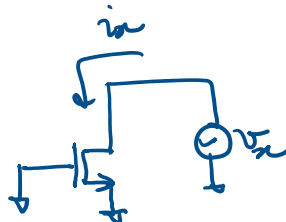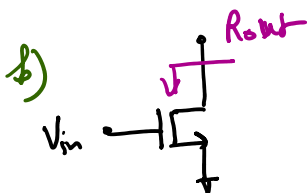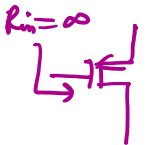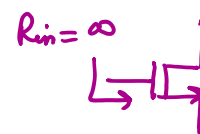At low frequencies, gate is insulated $\Rightarrow i_x = 0$
 $\Rightarrow R_{in} = \frac{v_x}{0} = \infty$




R_{out} , "looking into" the drain



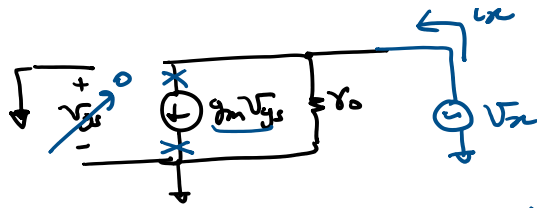

\Rightarrow

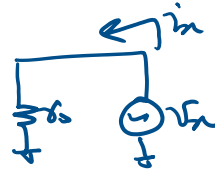

$$\Rightarrow v_x = i_x r_o$$

$$\Rightarrow R_{out} = \frac{v_x}{i_x} = r_o$$

