
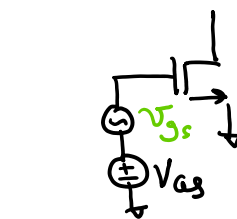


ECE 310 - Lecture 21

Monday, March 5, 2018 10:28 AM

MOS Transconductance

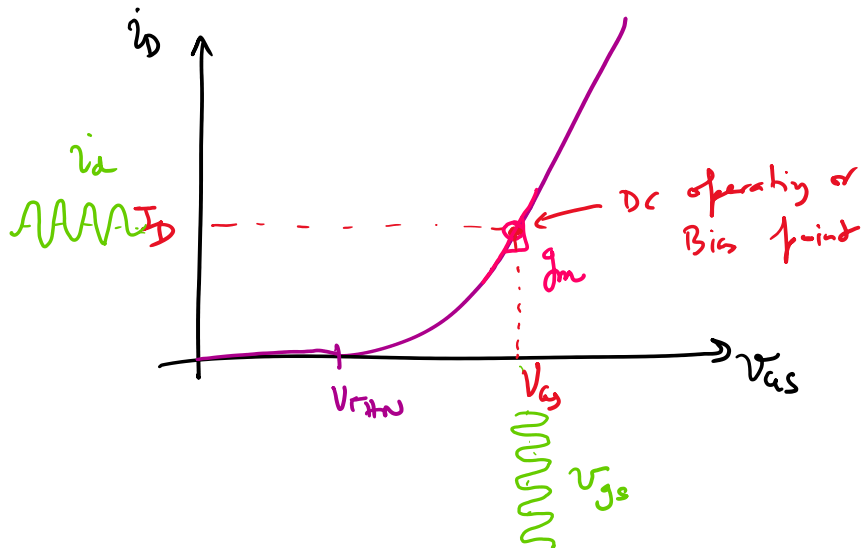

AC current
 $\downarrow$
 $i_d = g_m v_{gs}$ AC voltage
 Small-signal

$g_m \Rightarrow$ slope of $I_D - V_{GS}$ curve at the DC bias point
 $\rightarrow$ valid in SATURATION Region

$$i_D = \frac{1}{2} k_p n \frac{W}{L} (V_{GS} - V_{TN})^2$$

ignore CLM
 $\lambda \Rightarrow$

$$g_m = \left. \frac{\partial i_D}{\partial V_{GS}} \right|_{V_{GS} = V_{GS}} = \frac{1}{2} k_p n \frac{W}{L} \cdot 2 (V_{GS} - V_{TN})$$

$$g_m = k_p n \frac{W}{L} (V_{GS} - V_{TN}) = \beta V_{OV}$$

* $g_m \propto \frac{W}{L}$

* $g_m \propto (V_{GS} - V_{TN})$ for fixed W/L

$\downarrow$
 $g_m \propto k_p n \frac{W}{L} V_{OV}$
 $V_{OV} = V_{GS} - V_{TN}$
 overdrive voltage

Square Law Equation
 $I_D = \frac{1}{2} k_p n \frac{W}{L} (V_{GS} - V_{TN})^2$

$$g_m = K_p n \frac{W}{L} (V_{GS} - V_{THN})$$

$$= \left(K_p n \frac{W}{L} \right) \sqrt{\frac{2I_D}{K_p n W/L}}$$

$$I_D = \frac{1}{2} K_p n \frac{W}{L} (V_{GS} - V_{THN})^2$$

Recast

$$V_{GS} - V_{THN} = \sqrt{\frac{2I_D}{K_p n W/L}} \rightarrow \textcircled{A}$$

$$g_m = \sqrt{2 K_p n \frac{W}{L} \cdot I_D}$$

$$= \sqrt{2 \beta_n I_D}$$

$$\text{Beta } \beta_n = K_p n \cdot \frac{W}{L}$$

$$g_m = \left(K_p n \cdot \frac{W}{L} \right) (V_{GS} - V_{THN})$$

$$\Rightarrow g_m = \frac{2I_D}{V_{GS} - V_{THN}}$$

$$g_m = \frac{2I_D}{V_{OV}}$$

$$I_D = \frac{1}{2} K_p n \frac{W}{L} (V_{GS} - V_{THN})^2$$

$$\Rightarrow K_p n \frac{W}{L} = \frac{2I_D}{(V_{GS} - V_{THN})^2} \rightarrow \textcircled{B}$$

Various forms of $g_m \leftarrow \left\{ \frac{W}{L}, V_{GS} - V_{THN}, I_D \right\}$

I_D is variable
 W/L is constant
 $V_{GS} - V_{THN}$ is variable

$$g_m = \sqrt{2K_p n \left(\frac{W}{L} \right) I_D}$$

$$g_m = K_p n \left(\frac{W}{L} \right) (V_{GS} - V_{THN})$$

$\rightarrow g_m \propto (V_{GS} - V_{THN})$

I_D is variable
 W/L is variable
 $(V_{GS} - V_{THN})$ is constant

$$g_m = \frac{2I_D}{V_{GS} - V_{THN}}$$


I_D is constant
 W/L & $V_{GS} - V_{THN}$ are variable

$$g_m = \sqrt{2K_p n \frac{W}{L} I_D}$$

$$g_m \propto \sqrt{W/L}$$

$$g_m = \frac{2I_D}{V_{GS} - V_{THN}}$$
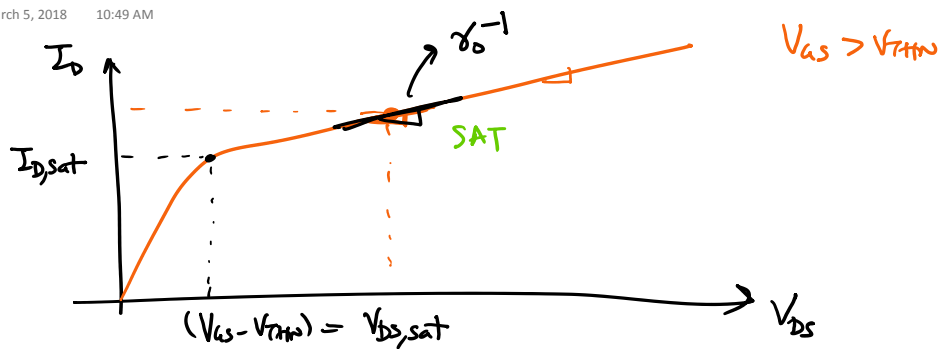
$$g_m \propto \frac{1}{(V_{GS} - V_{THN})}$$



in SAT:

$$I_D = \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_{TTH})^2 [1 + \lambda V_{DS}]$$





channel length modulation

output conductance


$$g_o = g_{ds} = \left. \frac{\partial I_D}{\partial V_{DS}} \right|_{V_{GS} = V_{DS}} = I_{D,sat} \cdot \lambda$$

output resistance $\Rightarrow$



$$r_o = \frac{1}{\lambda I_{D,sat}}$$

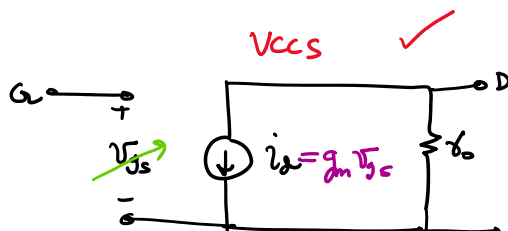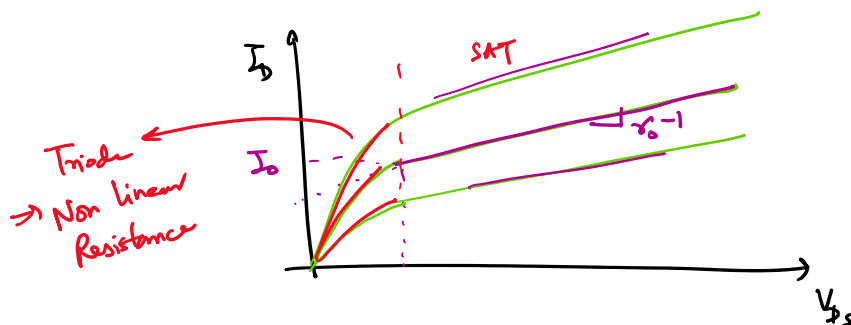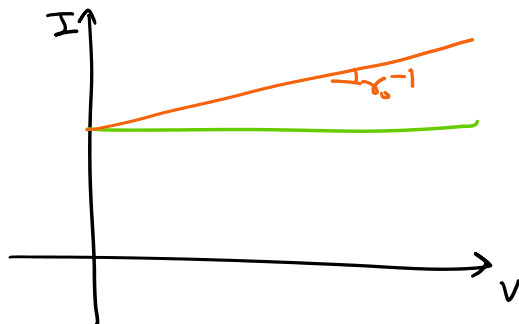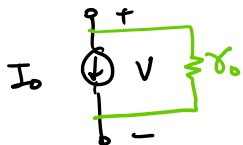

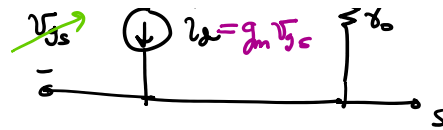Voltage Controlled Current Source (VCCS) with an output resistance




(VCCS) with r_o
output resistance

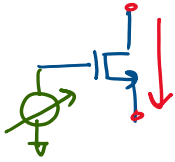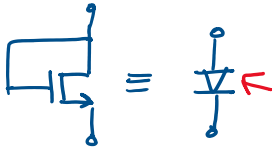

$$g_m = \begin{cases} \beta V_{ov} \\ \sqrt{2\beta I_D} \\ \frac{2I_D}{V_{ov}} \end{cases}$$

$$r_o = \frac{1}{\lambda I_{D, \text{sat}}}$$
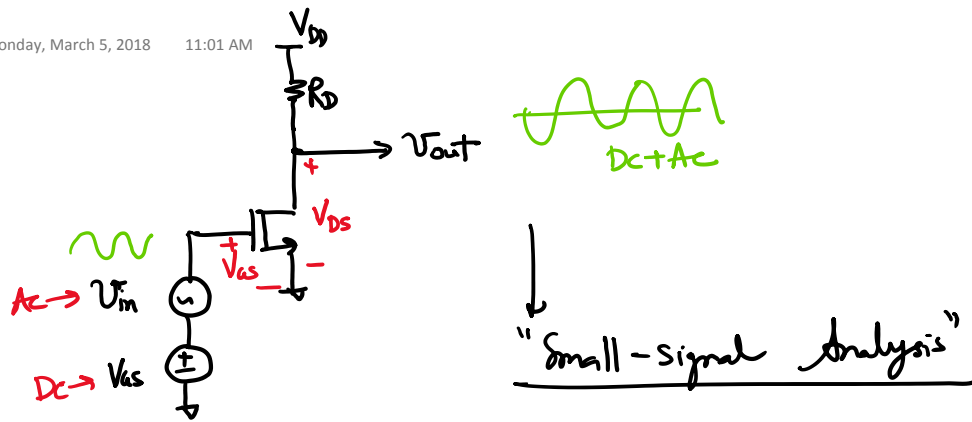
$$A_v = g_m r_o \leftarrow \text{maximum small-signal gain we can get from the transistor (NMOS)}$$



Procedure:

1) Look at the "DC picture (equivalent circuit)"

↳ Solve for the DC operating (or bias) points

↳ all AC voltages are shorted all AC current sources are opened

2) from DC analysis $\Rightarrow$ small-signal parameters $\Rightarrow g_m, r_o, \dots$

3) Analyze small-signal equivalent circuit (AC picture) of the circuit (linear circuit analyze).

↳ All devices are replaced by their small signal models

↳ All indep. DC voltage sources are shorted & DC current sources are opened





↳ obtain small signal gains input/output resistances for the circuit

4) final voltages & currents are superposition of DC & AC quantities.

... .. disturb the DC bias conditions

- * Small signal shouldn't disturb the DC bias conditions
↳ 10% variation could be a rule of thumb.

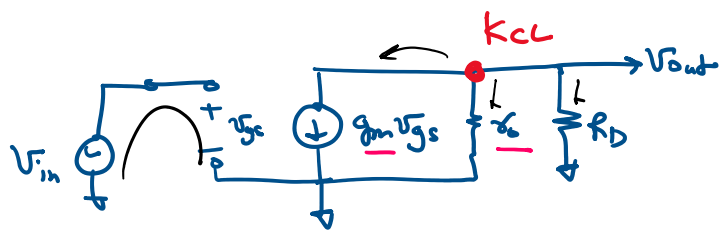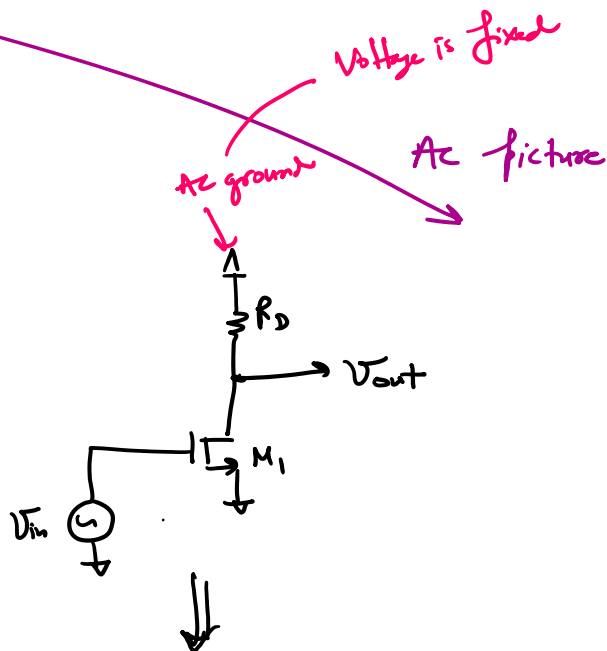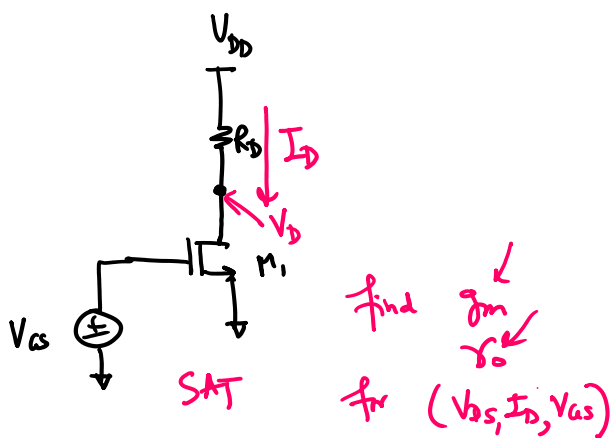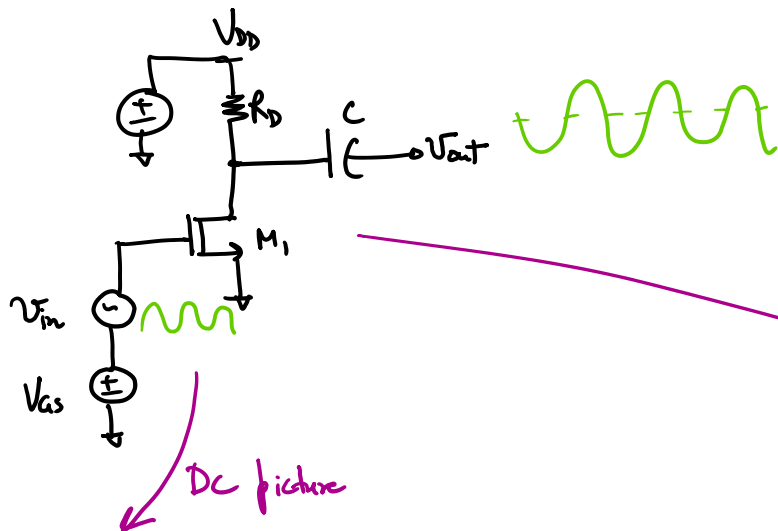$\text{---}(\text{---}) \Rightarrow \begin{matrix} \text{DC} & \text{open} \\ \text{AC} & \text{short} \end{matrix}$



$$V_{gs} = V_{in}$$

$$\text{KCL: } g_m V_{in} + \frac{V_{out}}{r_o} + \frac{V_{out}}{R_D} = 0$$

$$\Rightarrow V_{out} \left(\frac{1}{r_o} + \frac{1}{R_D} \right) = -g_m V_{in}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = -g_m (r_o \parallel R_D)$$

$$\frac{V_{out}}{V_{in}} = -g_m(r_o \parallel R_D)$$

Small signal voltage gain

$$A_v = \frac{V_{out}}{V_{in}} = -g_m(r_o \parallel R_D)$$

Let's say $R_D \rightarrow \infty$

$$A_v = -g_m r_o \rightarrow \text{max gain from NMOS}$$

Let's say $R_D \ll r_o$

$$A_v = -g_m R_D$$