
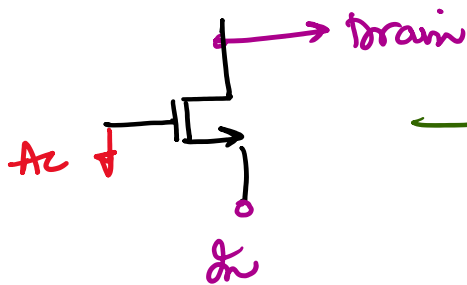



Monday, March 26, 2018 10:28 AM

Common Source Amplifier



↳ CS with source degeneration

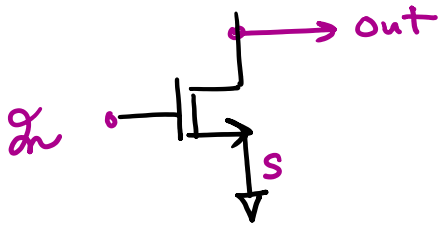

→ Common Gate amplifier

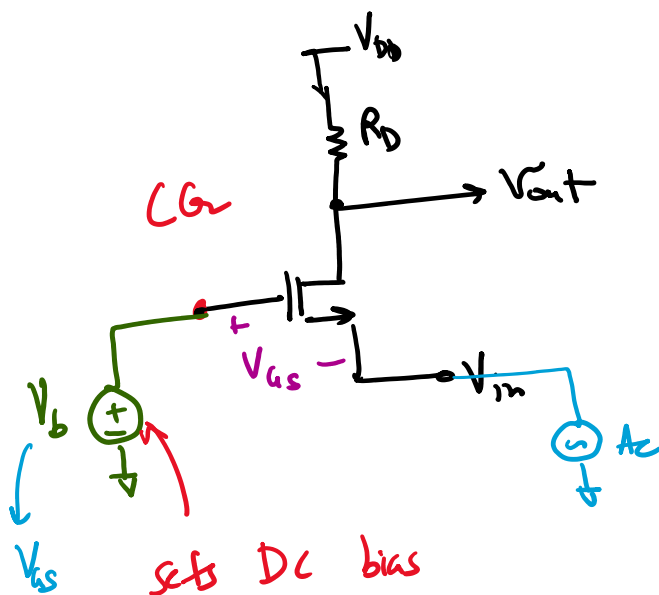

for the NMs

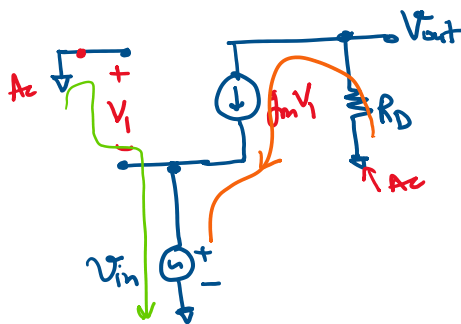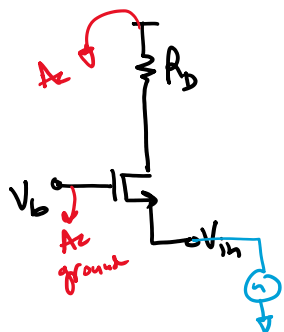

$$V_1 = V_{gs}$$

Here, $\lambda = 0$

KVL \rightarrow

$$V_1 = -V_{in} \rightarrow \textcircled{1}$$


\rightarrow

$$V_{out} = -g_m V_1 R_D \rightarrow \textcircled{2}$$



$$\Rightarrow V_{out} = -g_m R_D (-V_{in}) = + g_m R_D V_{in}$$

$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = \boxed{+ g_m R_D} \rightarrow$$

+ve gain
non-inverting
gain

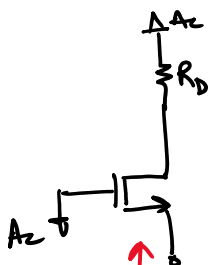

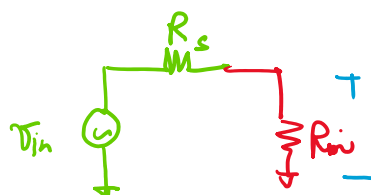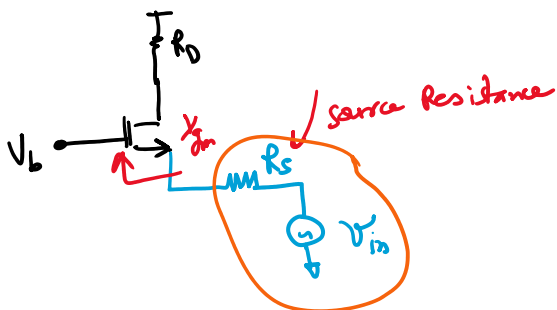$R_{in} \approx \frac{1}{g_m} \ll \text{Small impedance, } 100 \sim k\Omega$




CS: $R_{in} \rightarrow \infty \Rightarrow$ No issue



CD: $R_{in} \approx \frac{1}{g_m} \Rightarrow$ Voltage Divider

Not a great voltage amplifier


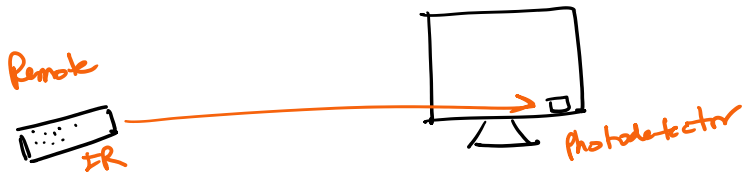
Not a great voltage amplifier
due to low R_{in}



Current amplifier

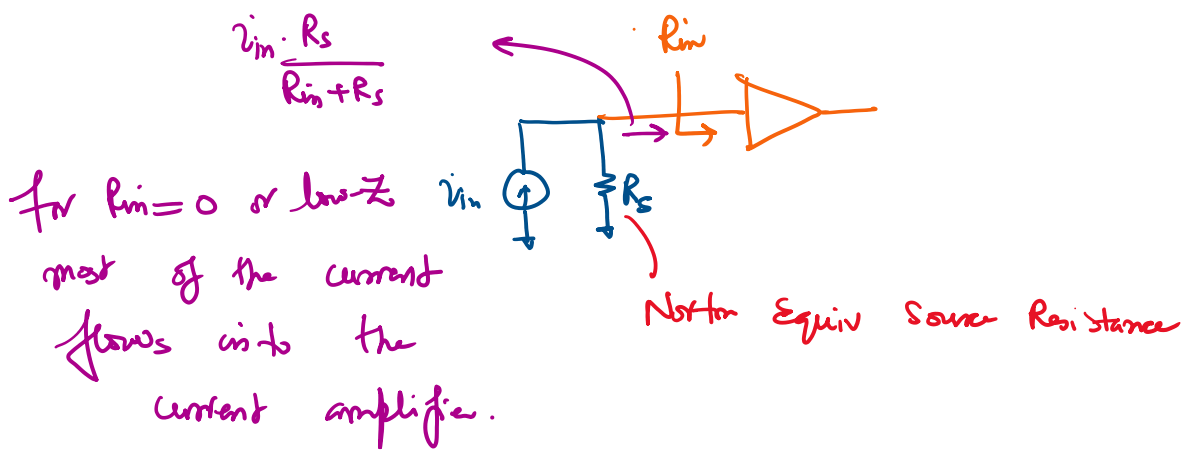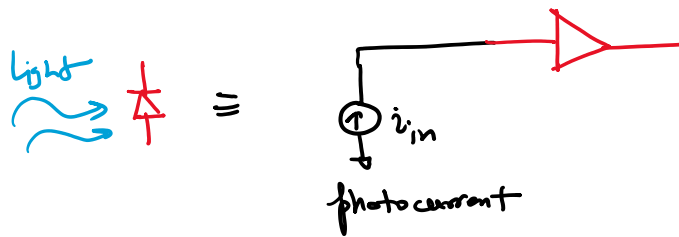

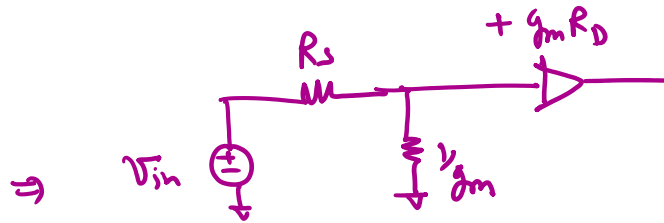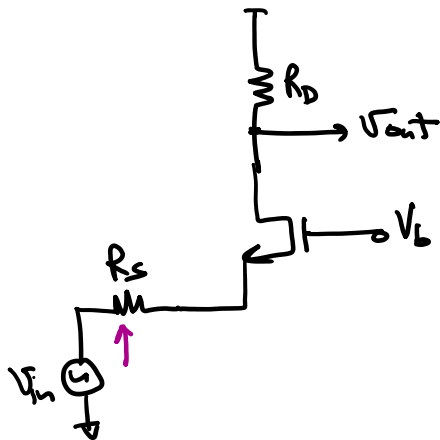
C_A is Excellent for current amplifier applications!





$$\frac{V_{out}}{V_{in}} = \frac{g_m R_D \cdot \frac{1}{g_m}}{\frac{1}{g_m} + R_s} = \frac{R_D}{\frac{1}{g_m} + R_s} = + \frac{g_m R_D}{1 + g_m R_s}$$

Do Book Examples 17.22, 23, 24, 28, 34 & 35.

Ex. CG with biasing

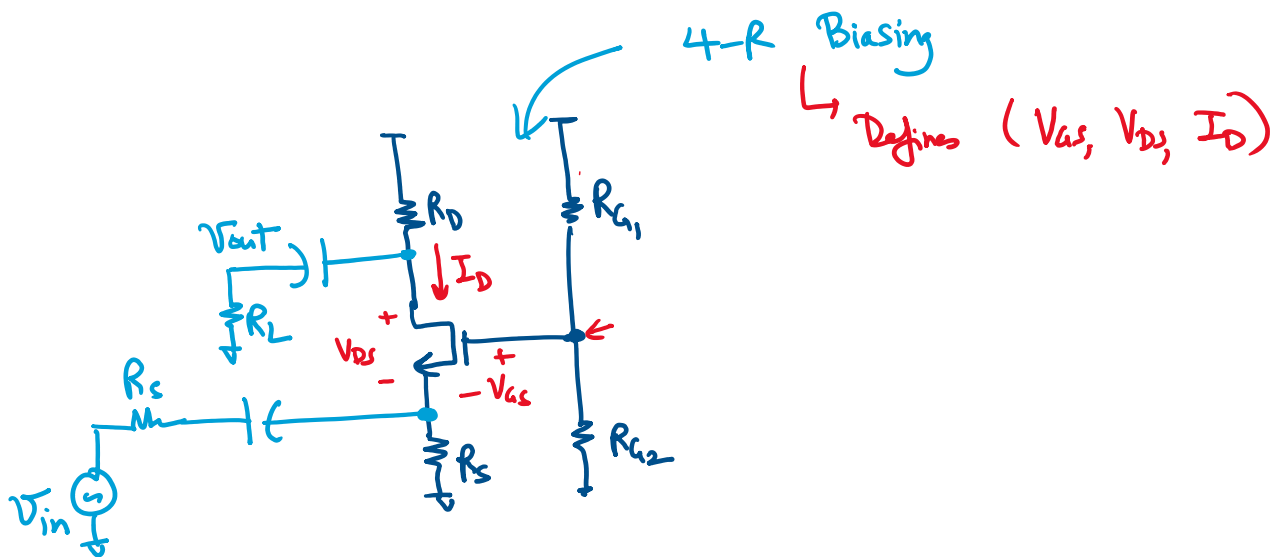


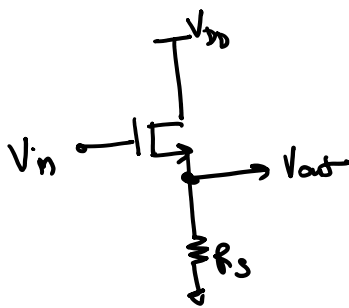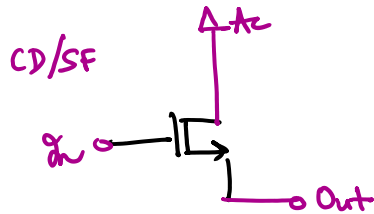Common Drain \Rightarrow Source follower (SF)



Small signal (Ac) Equivalent Circuit

Ans

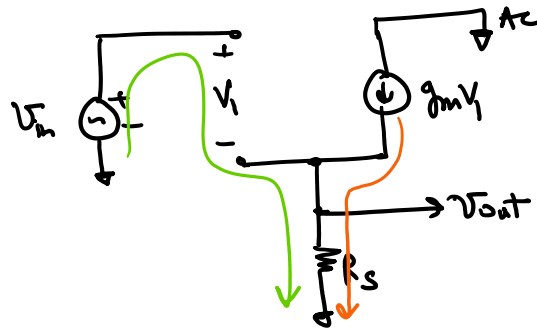

KVL:

$$V_1 = v_{in} - v_{out} \rightarrow \textcircled{1}$$

\Rightarrow :

$$v_{out} = g_m V_1 \cdot R_S \rightarrow \textcircled{2}$$

$$\Rightarrow v_{out} = g_m R_S [v_{in} - v_{out}]$$



$$\Rightarrow v_{out} (1 + g_m R_S) = g_m R_S v_{in}$$

⇒



$$A_v = \frac{V_{out}}{V_{in}} = \frac{g_m R_s}{1 + g_m R_s} = \boxed{\frac{R_s}{R_s + \frac{1}{g_m}}} \leq 1$$

$$0 < A_v < 1$$



;)

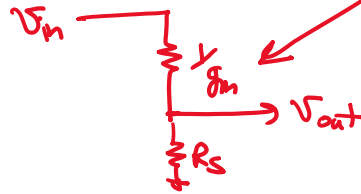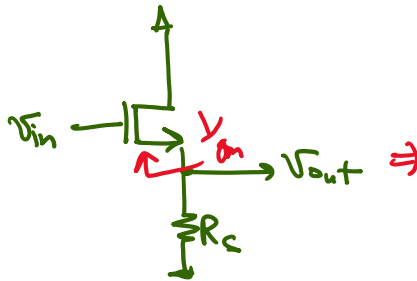

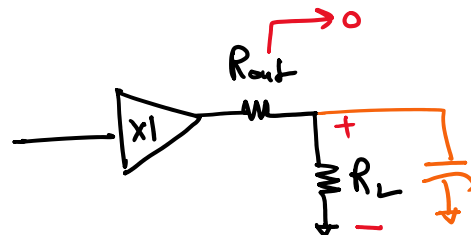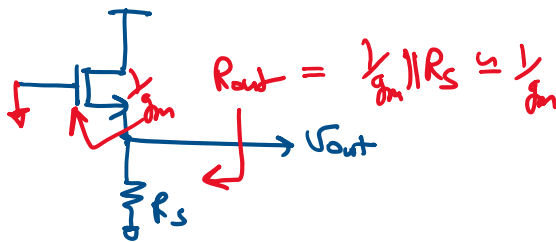
output impedance, $R_{out} = \frac{1}{g_m} \Rightarrow$ low impedance




Voltage Buffer (VB)

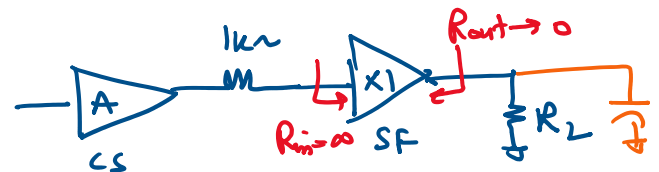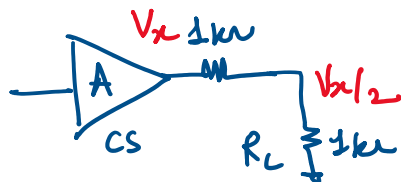

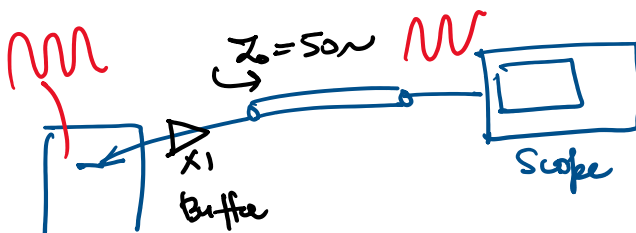VB is used to isolate load from a high gain amplifier







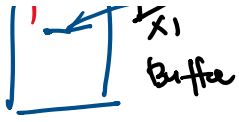

Scope

Excellent as a Voltage Buffer!

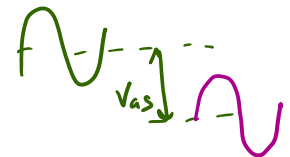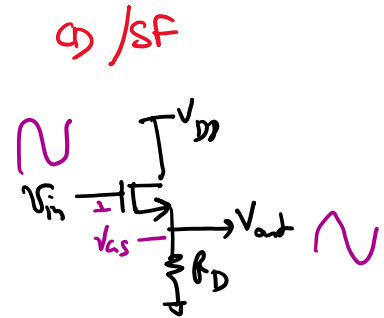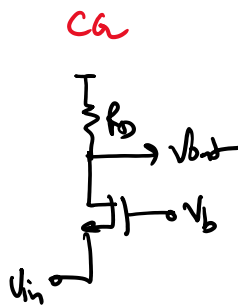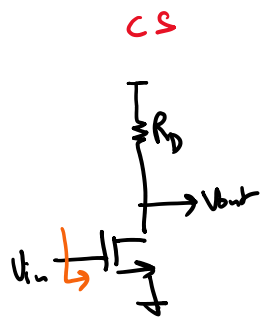Summary of MOS Amplifier Stages (chapter 17)



on your follow the input

$$A_v = \frac{R_D}{\frac{1}{g_m} + R_D}$$

$$R_{in} \rightarrow \infty$$

$$R_{out} = \frac{1}{g_m} \rightarrow 0 \text{ (low)}$$

Voltage Buffer

$$A_v = -g_m(R_D || r_o)$$

$$R_{in} \rightarrow \infty$$

$$R_{out} \approx R_D || r_o$$


Voltage Amplifier

$$A_v = +g_m(R_D || r_o)$$

$$R_{in} \approx \frac{1}{g_m} \text{ (low)}$$

$$R_{out} = R_D || r_o$$

Current Amplifier
" Buffer


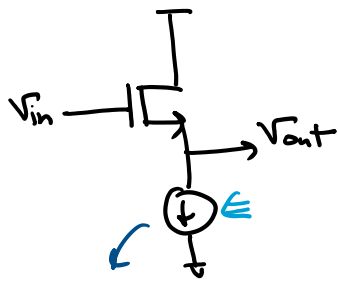


$$A_v = \frac{V_{out}}{V_{in}} = \frac{R_s}{R_s + \frac{1}{g_m}} = \frac{1}{1 + \frac{1}{g_m R_s}} \approx 1$$

$R_s \rightarrow \infty$

Gain of (1)

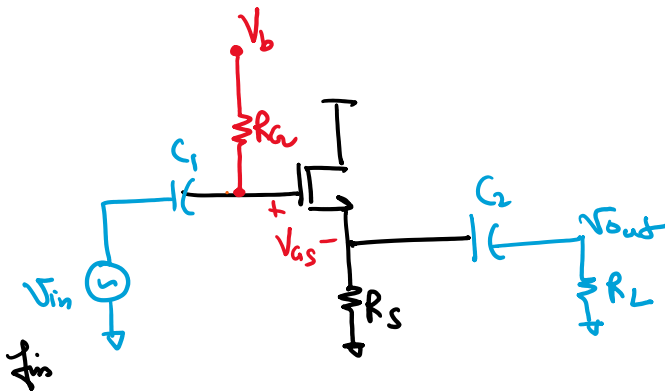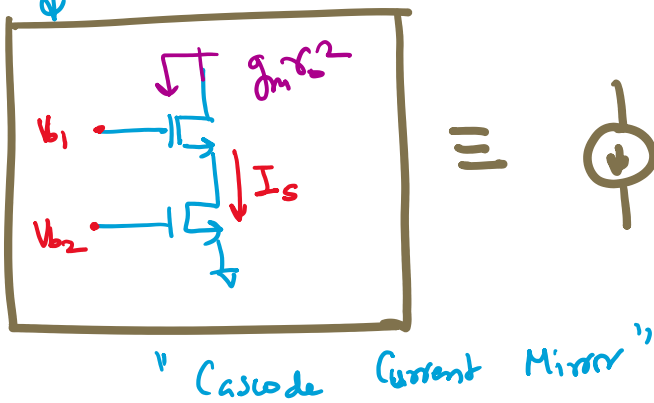$R_s \Rightarrow$ output resistance of the current source (ideally ∞)



$$\tau = R_s C_1 > \frac{10}{f_{in}}$$