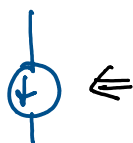


Current Mirrors

Section 9.2.3


Chapter 9



Assume $\lambda = 0 \Rightarrow r_o \rightarrow \infty$


$$I_{ref} = \frac{1}{2} k_n' \left(\frac{W}{L}\right)_{ref} (V_x - V_{thn})^2$$
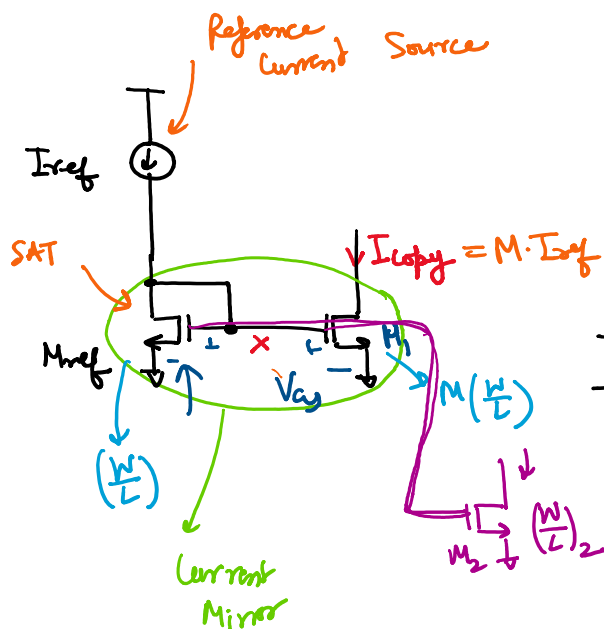
$$I_{copy} = \frac{1}{2} k_n' \left(\frac{W}{L}\right)_1 (V_x - V_{thn})^2$$




$$\frac{I_{copy}}{I_{ref}} = \frac{(W/L)_{copy}}{(W/L)_{ref}} \Rightarrow \frac{W_{copy}}{W_{ref}} \Big|_{L=\text{same}}$$

Also if lengths were the same $= L$


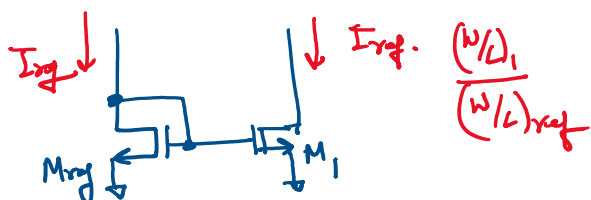


Ex.

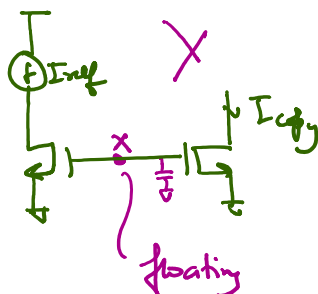



I_{copy} is poorly defined

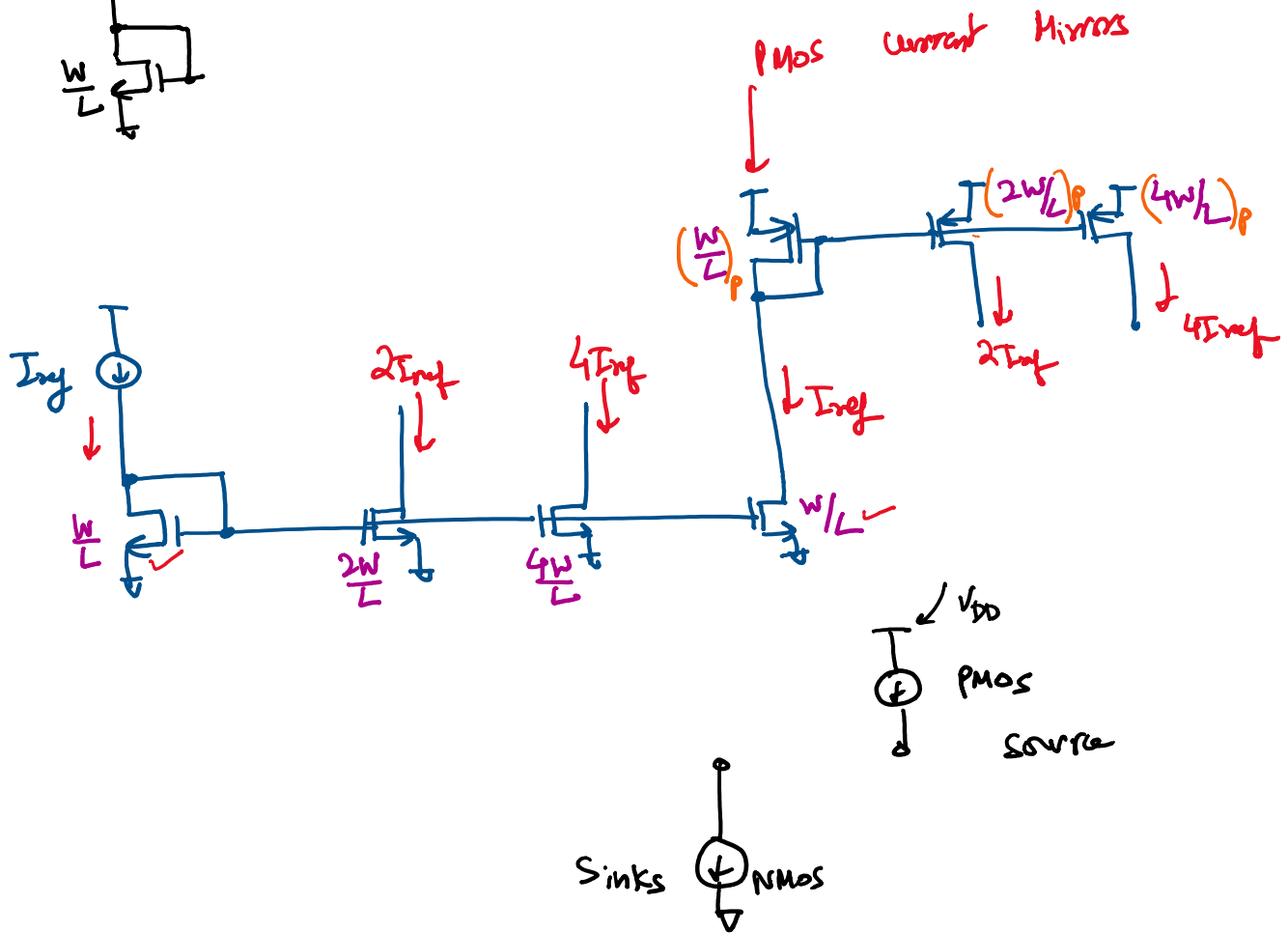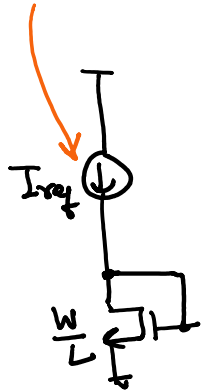410/415 Bandgap Reference
 ↳ Current reference independent of T_{env} , V_{DD} variations, and device variations



$\lambda \neq 0$


I_D, V_{DS} curve

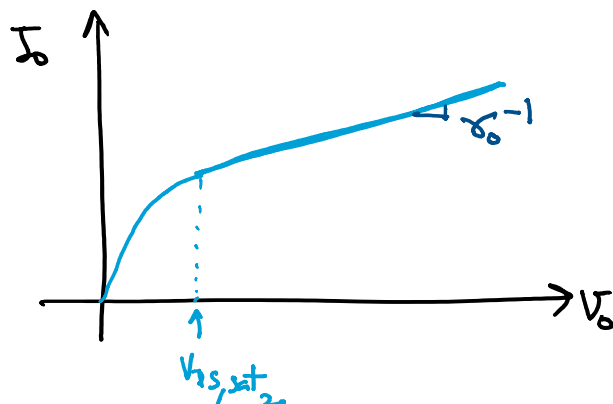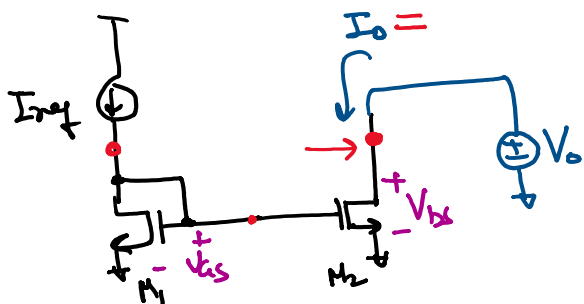

Variation in current (I_O) due to finite λ or CM

$$V_{GS1} = V_{GS2}$$

$$V_{DS1} = V_{DS2}$$

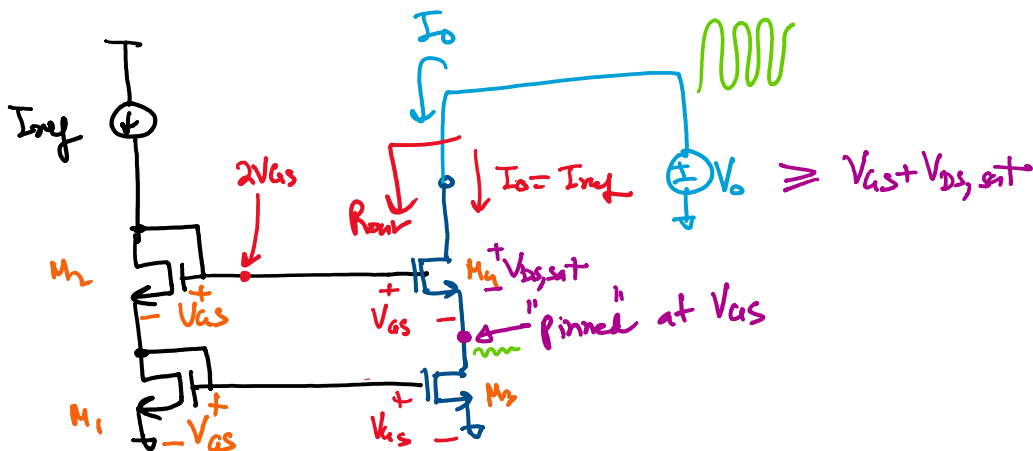


All Transistors are identical

By Cascoding

$$R_{out} \propto g_m r_o^2 \Rightarrow \infty$$

" Cascode Current Mirror


Output resistance is very high

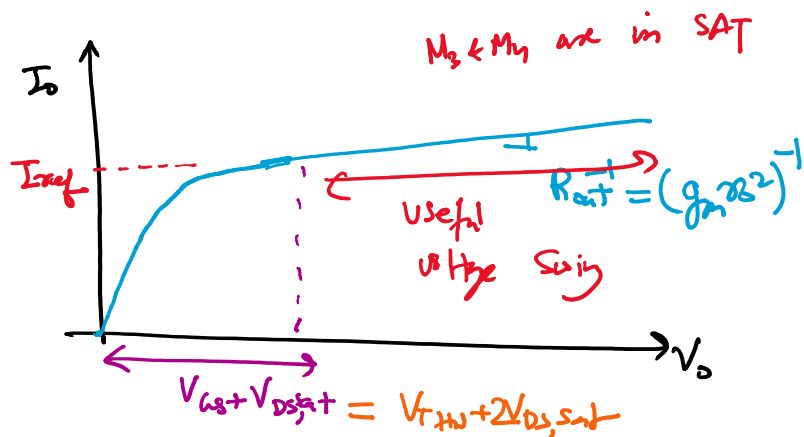


$$R_{out} \approx \infty$$


" Cascode Current Mirror

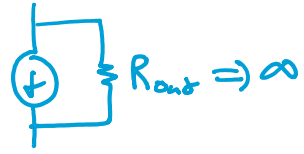Better Current Mirror but
with reduced voltage headroom"



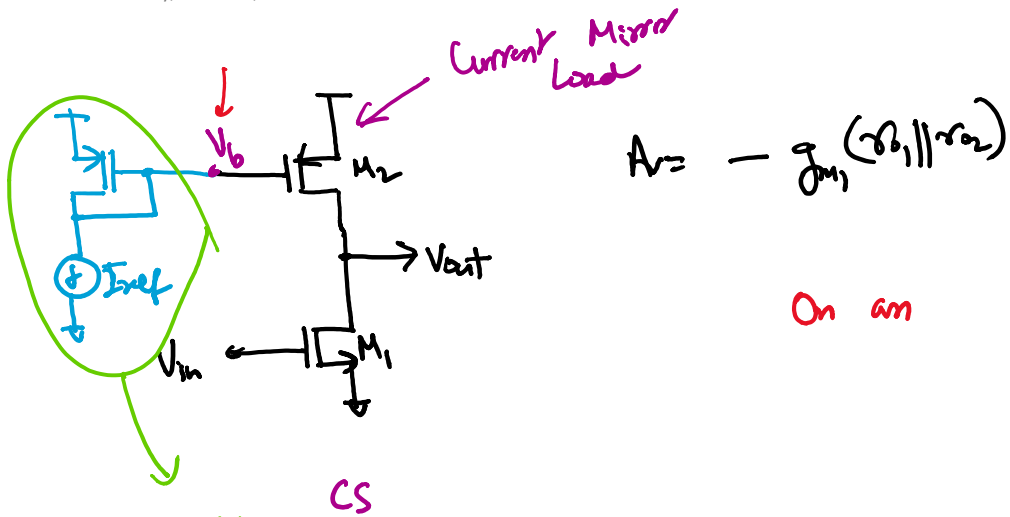

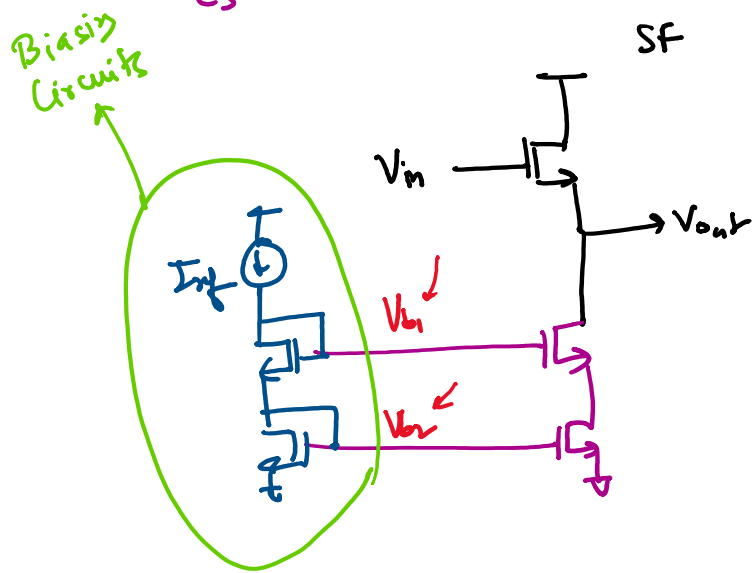
On an "Mixed-Signal" IC
Mask-biasing is done using
Current Mirrors.



5G

Bipolar Junction Transistors
(BJTs)



BiCMOS



Wifi

2.4GHz, 5GHz

fcc \Rightarrow 2.8 GHz
60 GHz
70
90
100 GHz

mmWave

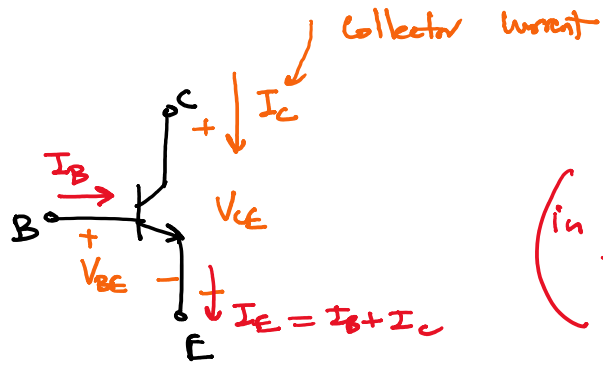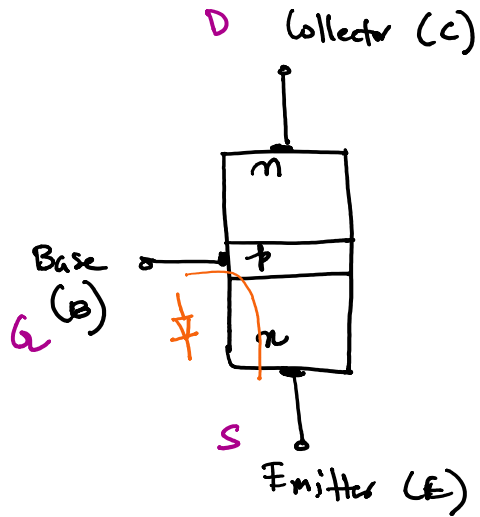Bipolar \rightarrow both type of carriers (holes & electrons) are responsible for current flow.



(in a MOSFET $I_G = 0$)

