

ECF 310 - Lecture 28

Monday, April 2, 2018 10:34 AM

Ex. 17-28


Design a CS stage for $av=5$

$R_{in} = 50k\Omega$, Power Budget = 5mW

$$K P_n = \mu_n C_{ox}' = 100 \frac{\mu A}{V^2}$$

$$V_{T_{NMOS}} = 0.4V \quad 0.5V$$

$$V_{DD} = 1.8V$$

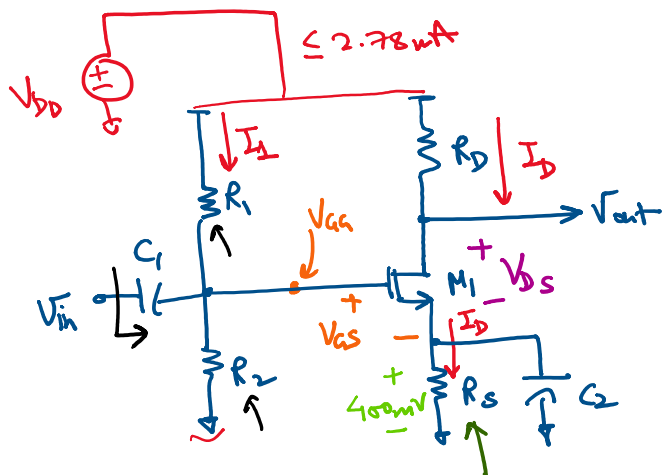

* Assume voltage drop of 400mV across R_S


C_1, C_2 are large for AC coupling.

$$\text{Total current } (I_D + I_1) \leq \frac{P}{V_{DD}} = \frac{5mW}{1.8V} = \boxed{2.78mA}$$

initial guess: Lets allocate $\boxed{I_D = 2.7mA}$ leaving $80\mu A$ for I_1

$$R_S = \frac{400mV}{2.7mA} = \boxed{148\Omega}$$

* Gain

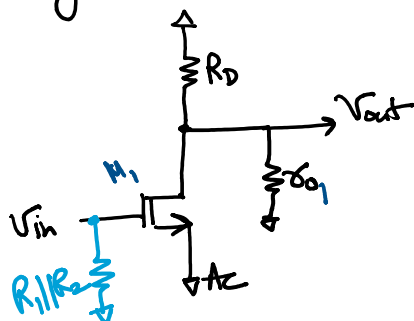

$$av = -g_{m1} (R_D || r_{o1})$$

$$\approx -g_{m1} R_D$$

$$\lambda \Rightarrow \Rightarrow r_o = \frac{1}{\lambda I_{D_{bias}}} \rightarrow \infty$$

AC picture

$$av = -g_{m1} R_D = -5$$

$$\boxed{g_{m1} R_D = 5}$$

Let's choose $V_{GS} = 1V \Rightarrow g_m = \frac{2I_D}{V_{GS} - V_{THN}} = \frac{2 \times 2.7mA}{1 - 0.5} = \boxed{\frac{1}{92.6\Omega}}$

$R_D = \frac{5}{1/g_m} = \boxed{463\Omega}$

* M_1 is in SAT

$I_D = \frac{1}{2} K_n \cdot \left(\frac{W}{L}\right) (V_{GS} - V_{THN})^2$
 $\swarrow$ $2.7mA$ $\searrow$ $(0.5)^2$

$\boxed{\frac{W}{L} = 218}$

Now, verify if M_1 is in SATURATION.

$V_{DS} > V_{DS,sat} \rightarrow V_{GS} - V_{THN} = 0.5V$

$V_{DS} = 1.8 - 2.7mA (R_D + R_S)$
 $= 0.150V$

M_1 is in TRIODE $\therefore$

* We have chosen an excessively large R_D & R_S values.

$5 = g_m \times R_D$

$R_D \downarrow 2\times$

$g_m \uparrow 2\times$

$g_m = \sqrt{2K_n \left(\frac{W}{L}\right) I_D}$
 $\swarrow$ $2\times$ $\searrow$

$\frac{W}{L} = \cancel{218} \xrightarrow{4\times} 864$

↓
2x

↓
4x

$$\frac{W}{L} = 218 \rightarrow \infty$$

$$g_m = \sqrt{2 \mu_n \left(\frac{W}{L}\right) I_D} = \frac{1}{463 \Omega}$$

$$\Rightarrow V_{GS} - V_{TH} = 250 \text{ mV}$$

$$\rightarrow V_{GS} = \boxed{0.75 \text{ V}}$$

Check for saturation

$$V_{DS} = V_{DD} - I_D \times (R_D + R_S)$$

$$= 1.8 - 2.7 \text{ mA} \left(\frac{463}{2} + 148 \right) = 0.775 \text{ V}$$

$$V_{DS} = 0.775 \text{ V} > V_{DS,sat} = 250 \text{ mV}$$

↳ M_1 is in SAT

$$V_{GS} = 750 \text{ mV}$$

$$\frac{W}{L} = 864$$

$$I_D = 2.7 \text{ mA}$$

$$R_D = \frac{463}{2}$$

$$R_S = 148 \Omega$$

$$V_{GS} = 750 \text{ mV} + 400 \text{ mV} \Rightarrow 1.15 \text{ V} = V_{DD} \times \frac{R_2}{R_1 + R_2}$$

$$1.8 \times \frac{R_2}{R_1 + R_2} = 1.15 \text{ V} \rightarrow \textcircled{1}$$

$$R_{in} = 50 \text{ k}\Omega$$


$$R_{in} = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2} = 50 \text{ k}\Omega \rightarrow \text{C}$$


 Solve $R_1 + R_2 = (\quad)$
 $> 50 \text{ k}\Omega$


$$I_1 = \frac{V_{DD}}{R_1 + R_2} \leq 80 \mu\text{A}$$

Ex. 17.38

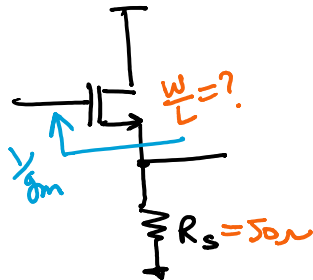Design a source follower to drive a 50 Ω load with a voltage gain = 0.5 and a power budget of 1mW.


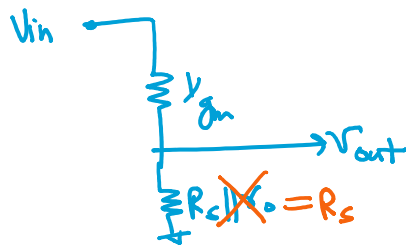
$$I_D = \frac{P}{V_{DD}} = \frac{1 \text{ mW}}{1.8 \text{ V}} = \boxed{5.26 \text{ nA}}$$



$$A_v = \frac{V_{out}}{V_{in}} = \frac{R_s}{g_m + R_s} = 0.5$$

$$\frac{50}{g_m + 50} = 0.5$$

$$\boxed{g_m = \frac{1}{50 \Omega}}$$

$$g_m = \sqrt{2 \beta I_D} = \sqrt{2 K_n \left(\frac{W}{L}\right) I_D}$$

$$\text{Solve for } \frac{W}{L} = \underline{\underline{360}} \text{ Ans.}$$


$$I_D = 1 \text{ mA}$$

$$g_m \uparrow 2 \times$$


on . .

$$g_m = \sqrt{2\beta \textcircled{I_D}} = \frac{2\textcircled{I_D}}{V_{GS} - V_{TH}}$$


$V_{GS} = \text{const.}$

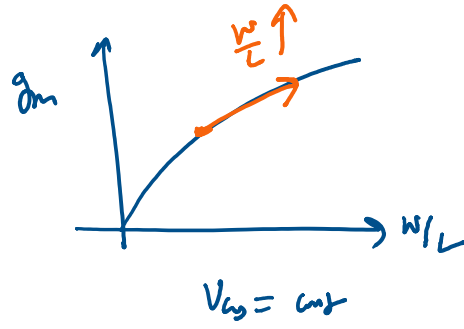

$\frac{W}{L} = \text{const.}$

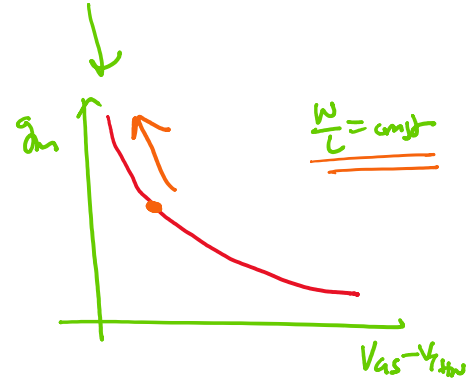


Ex. 17.40

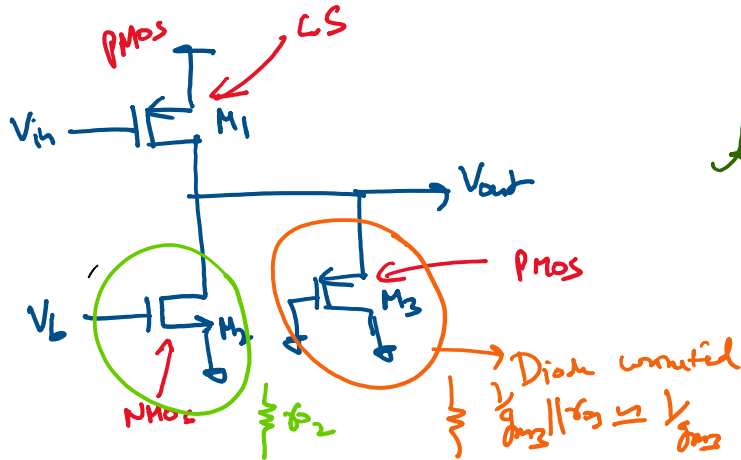

Av2?

Av picture.

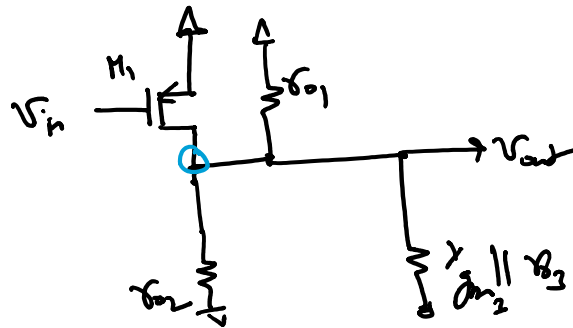

$$A_v = -g_{m1} R_L$$

$$= -g_{m1} r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m3}} \parallel r_{o3}$$

$$\approx -\frac{g_{m1}}{g_{m3}}$$

$$\frac{1}{g_m} \ll r_o$$