
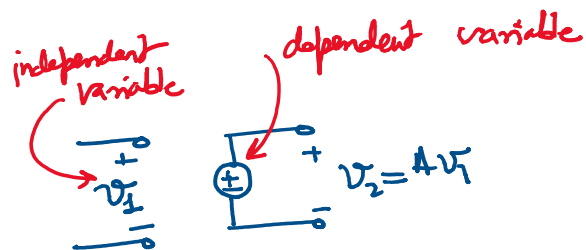


Dependent Sources

voltage controlled voltage source
VCVS

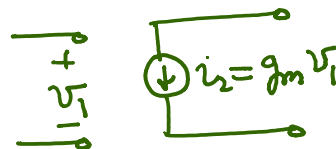


VCCS




two-port
components

CCCS

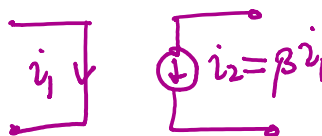

CCVS

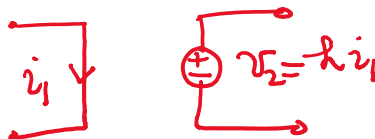


Dependent sources can model the microelectronic devices.

Thevenin and Norton Equivalents

- * Thevenin & Norton theorems greatly simplify algebra and provide insight into the circuit


Thevenin's Theorem:

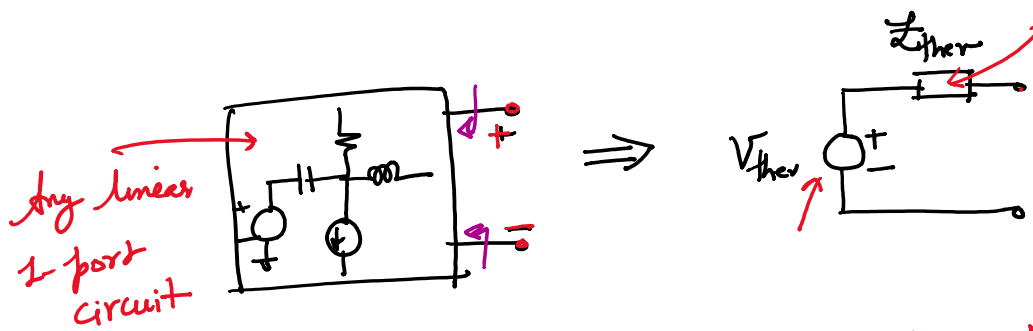A linear one-port network can be replaced by an equivalent circuit consisting of one voltage source in series with an impedance



- * V_{th} is obtained by leaving the output open and calculating the open circuit voltage at this port.
- * Z_{th} is determined by setting ALL independent voltage and current sources to zero and then calculate the impedance between the two nodes.
 - Short ALL independent voltage sources
 - Open ALL independent current sources
- * Be careful with dependent sources

Ex.

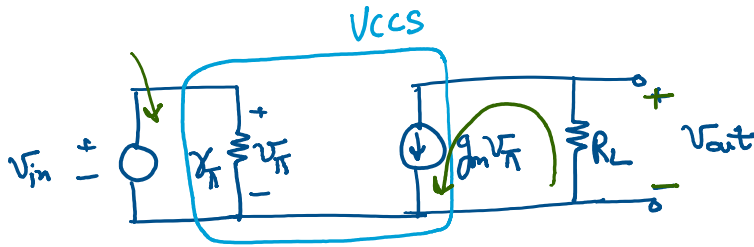

* $V_{th} \Rightarrow$ open circuit voltage at the output



$$V_{out} = -g_m V_{gs} R_L$$

$$V_{gs} = V_{in}$$

$$\Rightarrow \boxed{V_{th} = -g_m V_{in} R_L}$$


* for Z_{th} calculation, we set $V_{in} = 0$ and apply a test voltage source V_x at the output port

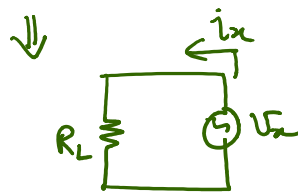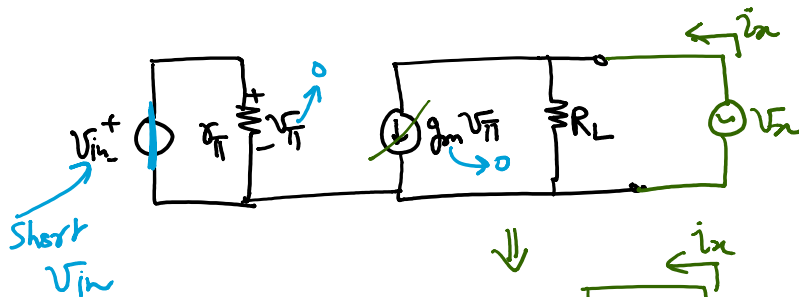\rightarrow determine the current, $i_x \Rightarrow Z_{th} = \frac{V_x}{i_x}$



$$\Rightarrow \frac{V_x}{i_x} = R_L$$


$$Z_{th} = R_{th} = R_L$$

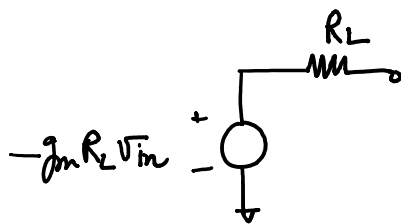


Thevenin Equivalent Circuit

Exercise \Rightarrow Repeat Ex 1.9 & 1.10

Norton's Theorem :

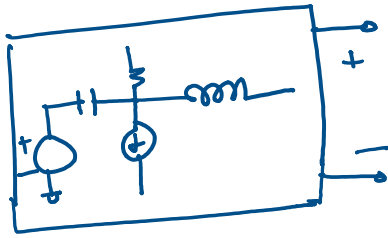

\Rightarrow

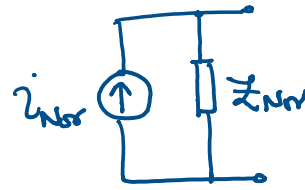


Norton Equivalent Circuit


* $Z_{Nor} \equiv R_{Nor}$ is calculated as the same way as the Z_{Thev}
 \rightarrow set ALL indep sources to zero and calculate the impedance at the output port.

* The equivalent current, i_{Nor} , is obtained by shorting the output port and computing the "short circuit" current that flows through it.


Ex.

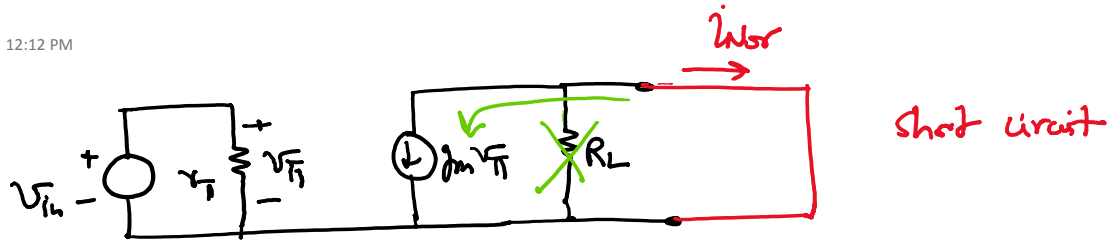
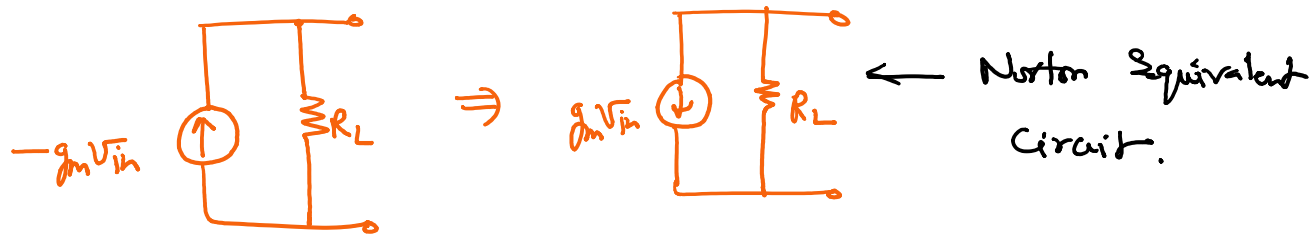
$$i_{Nor} = -g_m V_{\pi} = -g_m V_{in} \quad Z_{Nor} = Z_{ther} = R_L$$



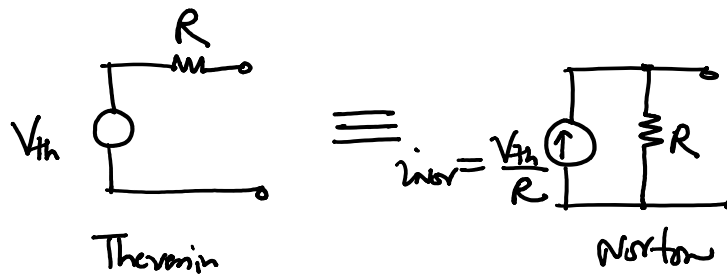
$$V_{ther} = i_{Nor} \cdot Z_{ther} = i_{Nor} \cdot Z_{Nor}$$




See Ex. 1.12

Ex.

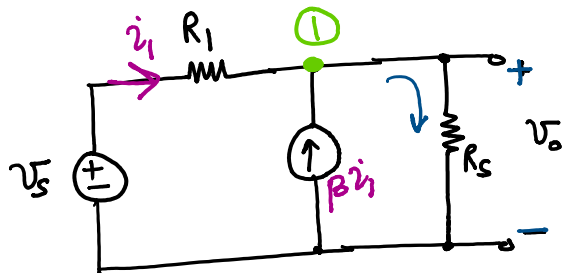

$$\beta = 50, R_1 = 20\text{ k}\Omega, R_S = 1\text{ k}\Omega$$

Find Thevenin Equivalent circuit

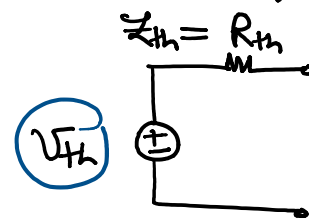

$V_{Th} \Rightarrow$ open circuit voltage at the output terminals

Apply KCL at node ①

$$\beta i_1 + i_1 - \frac{V_o}{R_S} = 0 \longrightarrow \textcircled{1}$$

$$i_1 = \frac{V_S - V_o}{R_1} \longrightarrow \textcircled{2}$$


Eliminate i_1 in Σ eq. ① and ②:


$$(\beta + 1) \left(\frac{V_S - V_o}{R_1} \right) - \frac{V_o}{R_S} = 0$$

$$\Rightarrow \frac{(\beta + 1)}{R_1} V_S = \left[\frac{\beta + 1}{R_1} + \frac{1}{R_S} \right] V_o$$

$$\Rightarrow \boxed{V_{Th} = V_o = \frac{(\beta + 1) R_S}{(\beta + 1) R_S + R_1} \cdot V_S} = 0.718 V_S$$

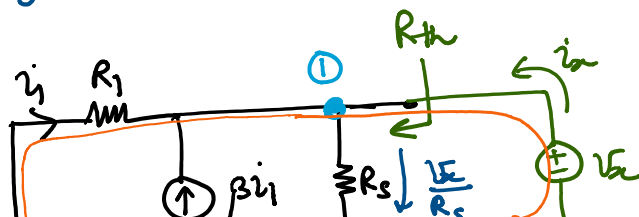for calculating $R_{Th} \Rightarrow$ short indep voltage sources



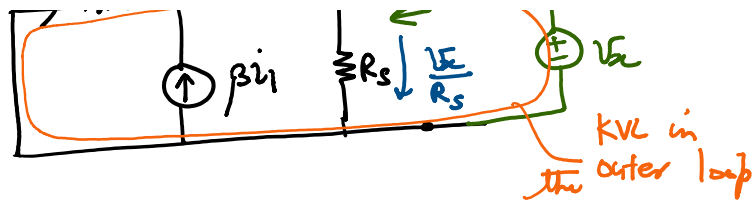

Apply KCL at ①:

$$i_x + i_1 + \beta i_1 - \frac{V_x}{R_s} = 0$$

$$\Rightarrow i_x + (\beta+1)i_1 - \frac{V_x}{R_s} = 0 \longrightarrow \textcircled{1}$$

Need to eliminate i_1

Taking KVL in the outer loop we get

$$-V_x - i_1 R_1 = 0$$

$$\Rightarrow i_1 = -\frac{V_x}{R_1} \longrightarrow \textcircled{2}$$

from eq. ① & ② we get,


$$i_x - (\beta+1)\frac{V_x}{R_1} - \frac{V_x}{R_s} = 0$$

$$\Rightarrow i_x = V_x \left[\frac{\beta+1}{R_1} + \frac{1}{R_s} \right]$$

$$\Rightarrow R_{th} = \frac{V_x}{i_x} = \frac{1}{\frac{\beta+1}{R_1} + \frac{1}{R_s}} = \boxed{\frac{R_1 R_s}{(\beta+1)R_s + R_1}}$$

$$= \frac{\frac{R_1}{\beta+1} \times R_s}{R_s + \frac{R_1}{\beta+1}} = R_s \parallel \frac{R_1}{\beta+1}$$
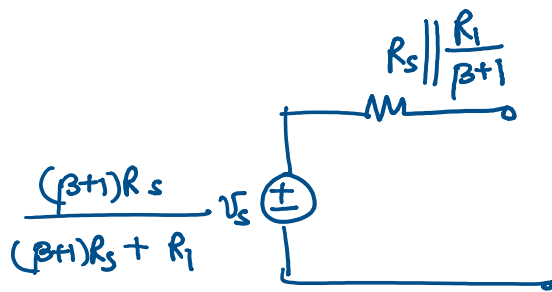
$$\boxed{R_{th} = R_s \parallel \frac{R_1}{\beta+1} = 282 \Omega}$$




Norton Method

$$R_{nor} \equiv R_{thor} = R_2 \parallel \frac{R_1}{(\beta+1)}$$

find i_{nor}

\Rightarrow short-circuit output current

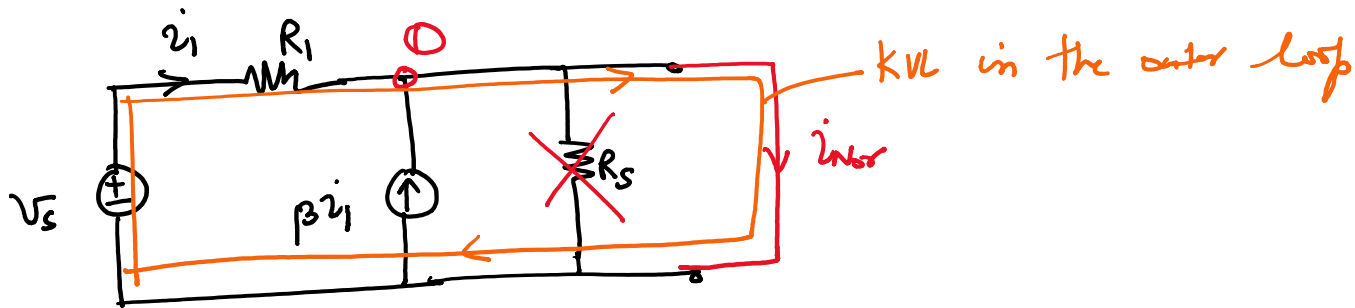

KCL at node ①

$$-i_{nor} + \beta i_1 + i_1 = 0$$

$$\Rightarrow i_{nor} = (\beta+1) i_1 \longrightarrow \text{①}$$


\uparrow Need to find i_1

KVL in the outer loop


$$-V_s + i_1 R_1 = 0$$

$$\Rightarrow i_1 = \frac{V_s}{R_1} \longrightarrow \text{②}$$

from ① & ② \Rightarrow $i_{nor} = (\beta+1) \frac{V_s}{R_1}$ = 2.55 mA

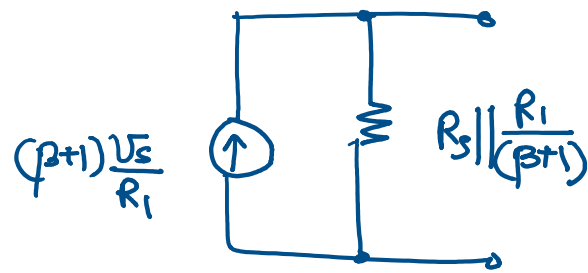

Ex.3

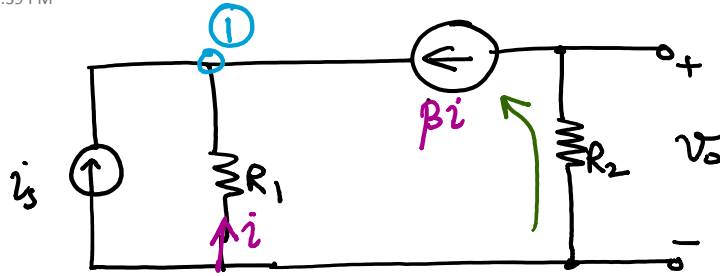

open circuit voltage at the output

$$v_o = -\beta i R_2 \rightarrow \textcircled{1}$$

KCL at node ①


$$i_s + i + \beta i = 0$$

$$\Rightarrow i = -\frac{i_s}{(\beta+1)} \rightarrow \textcircled{2}$$

from ① & ② we get

$$v_o = \frac{\beta R_2}{\beta+1} \cdot i_s \Rightarrow \boxed{V_{th} = \left(\frac{\beta}{\beta+1}\right) i_s R_2}$$

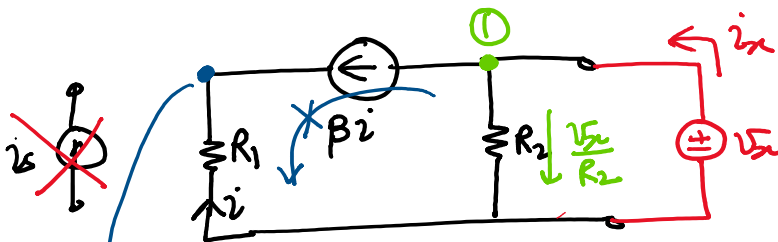for R_{th} , open " i_s " \Rightarrow independent current source



$$R_{th} = \frac{v_x}{i_x}$$

we have $i = \beta i$
 $\Rightarrow i = 0$


we have

$$\Rightarrow i = 0$$

$$\text{KCL at } \textcircled{1} \Rightarrow i_x - \frac{V_x}{R_2} - \cancel{pi} = 0$$

$$\Rightarrow \frac{V_x}{i_x} = R_2$$


$$\Rightarrow \boxed{R_{th} = R_2}$$

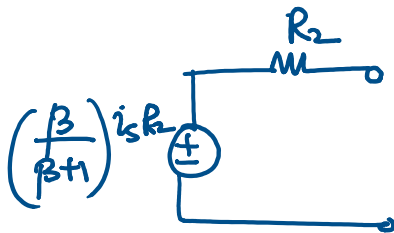

Thevenin equiv. circuit

\equiv
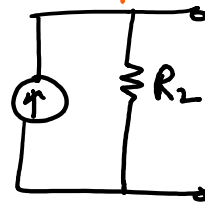
$$\left(\frac{\beta}{\beta+1}\right)i_s$$



Norton equiv. circuit.

$$i_{nor} = \frac{V_{th}}{R_{th}} = \left(\frac{\beta}{\beta+1}\right)i_s$$