

ECE 310 - Lecture 2

Note Title


8/23/2011

Basic Circuit Theorems

① Kirchoff's Laws

Kirchoff's current law (KCL) states that the sum of currents flowing into a node is zero.

$$\sum_j I_j = 0$$

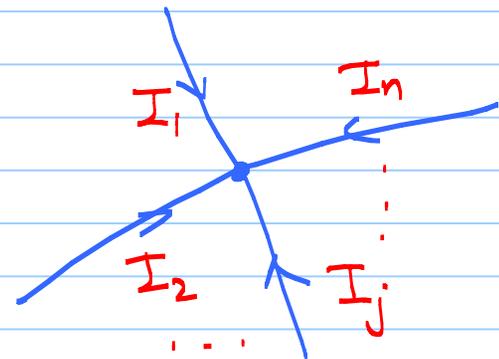


* Kirchoff's Voltage Law (KVL) states that the sum of voltage drops around any closed loop in a circuit is zero.

$$\sum_j V_j = 0$$


Trick to apply KVL:

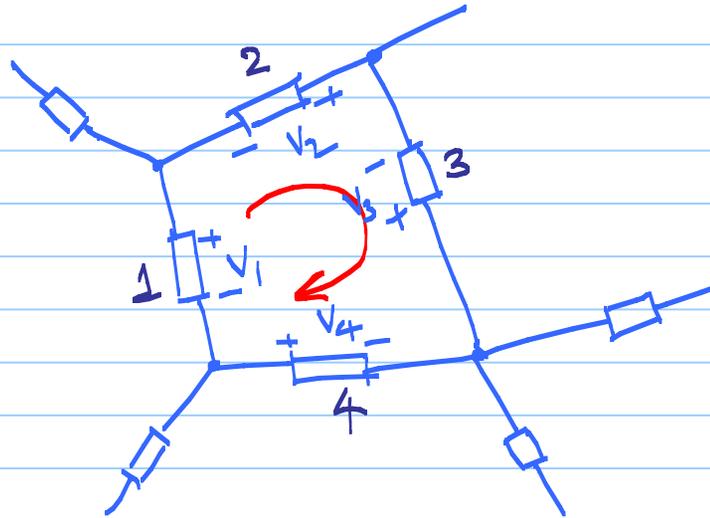- * Traverse along the loop
- * put down the sign you encounter first
- * the sum of all voltages in the loop is zero.



$$-V_1 - V_2 - V_3 - V_4 = 0 \Rightarrow V_1 + V_2 + V_3 + V_4 = 0$$

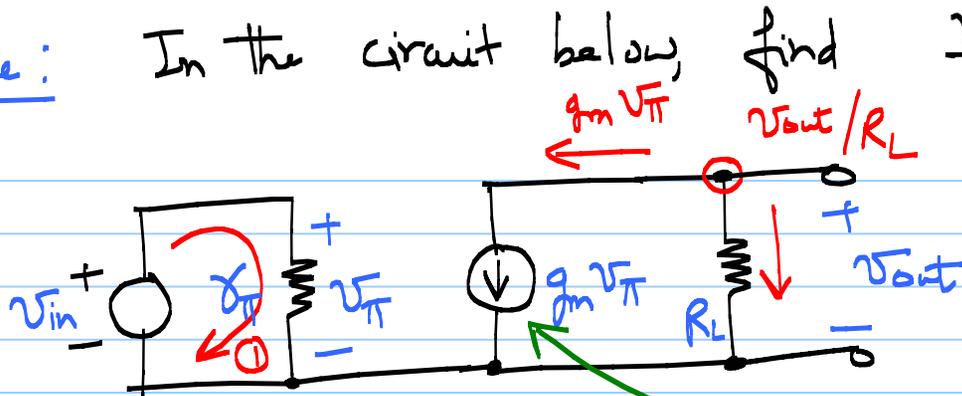Example: In the circuit below, find $\frac{V_{out}}{V_{in}}$



* KVL in loop ① \Rightarrow

$$-V_{in} - V_{\pi} = 0$$

$$\Rightarrow \boxed{V_{in} = V_{\pi}}$$

Voltage controlled current source (VCCS)

* KCL at the output node yields

$$\Rightarrow -g_m V_{\pi} - \frac{V_{out}}{R_L} = 0$$

-ve sign as the currents are leaving the node

$$\begin{aligned} \Rightarrow v_{out} &= -g_m v_{\pi} \cdot R_L \\ &= -g_m R_L v_{in} \end{aligned} \quad \because v_{\pi} = v_{in}$$

$$\Rightarrow \boxed{\frac{v_{out}}{v_{in}} = -g_m R_L}$$

↳ an amplifier $|g_m R_L| > 1$.

↳ -ve sign means that the signal is inverted.

HW: Repeat Textbook examples 1.6 & 1.7


Thevenin and Norton Equivalents

Thevenin and Norton theorems greatly simplify the algebra and provide insight into the circuit.

Thevenin's Theorem:


"A linear one-port network can be replaced with an equivalent circuit consisting of one voltage source in series with one impedance."

Any (linear)
2-port
circuit

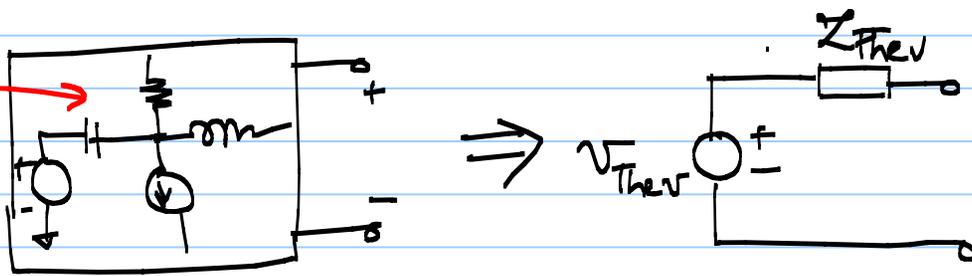



* The equivalent voltage, V_{Ther} , is obtained by leaving the port "open" and computing the voltage created by the actual circuit at this port.

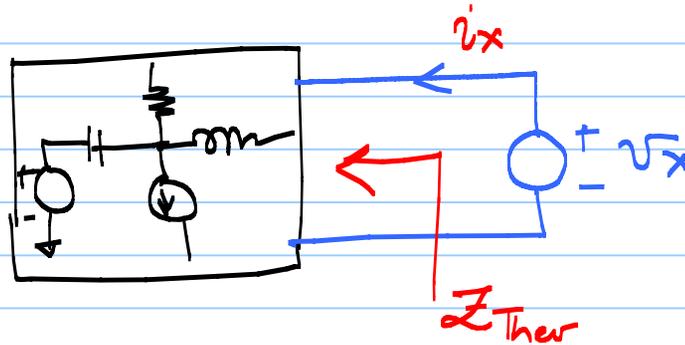* The equivalent impedance Z_{Ther} is determined by setting all independent voltage and current sources in the circuit to zero, and then calculating the impedance between the two nodes



'Short' the independent voltage sources
&
'open' the independent current sources
* Careful with dependent sources

Example :

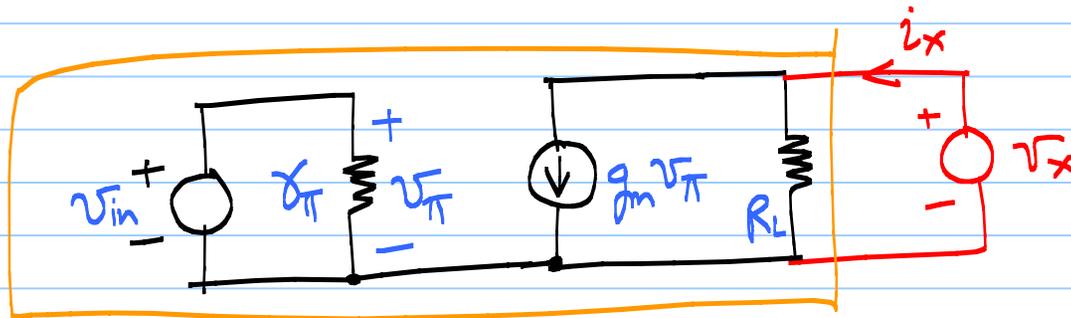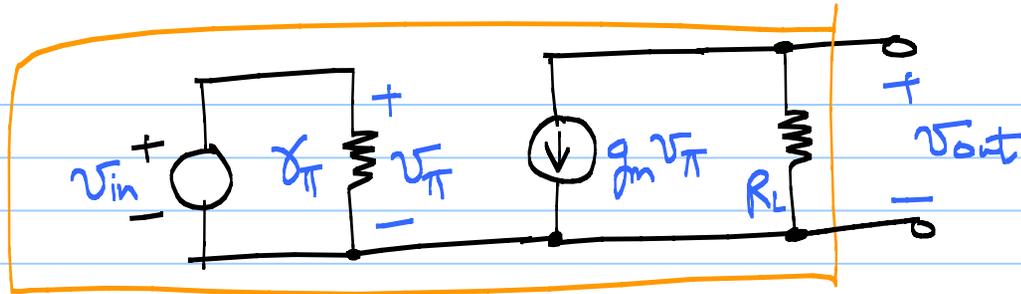

Here,
$$v_{Thev} = v_{out} = -g_m R_L \cdot v_{in}$$

* To calculate Z_{Ther} , set $V_{in} = 0$, and apply a test voltage source V_x across the output port


↳ determine the current drawn, i_x , at the output port

$$\Rightarrow V_{\pi} = 0$$

⇒ impedance at the output port ⇒ R_L

$$\Rightarrow i_x = \frac{V_x}{R_L}$$

$$\Rightarrow R_{Ther} = R_L$$

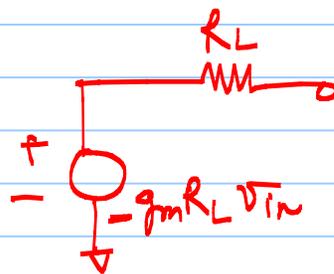



← Thevenin equivalent circuit

HW: Repeat Textbook Ex. 1.9 & 1.10


Norton's Theorem :

" A linear one-port network can be represented by one current source in parallel with one impedance".

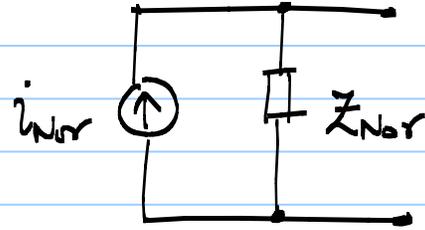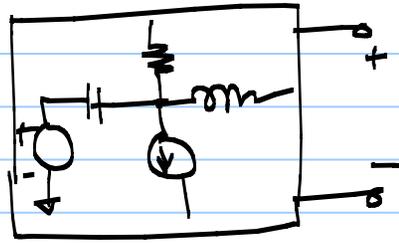- * The equivalent current, i_{Nor} , is obtained by shorting the port of interest and computing the current that flows through it.
- * The equivalent impedance, Z_{Nor} , is found the same way as in Thevenin's theorem.
 - ↳ set all independent sources to zero and calculate the impedance at the output port



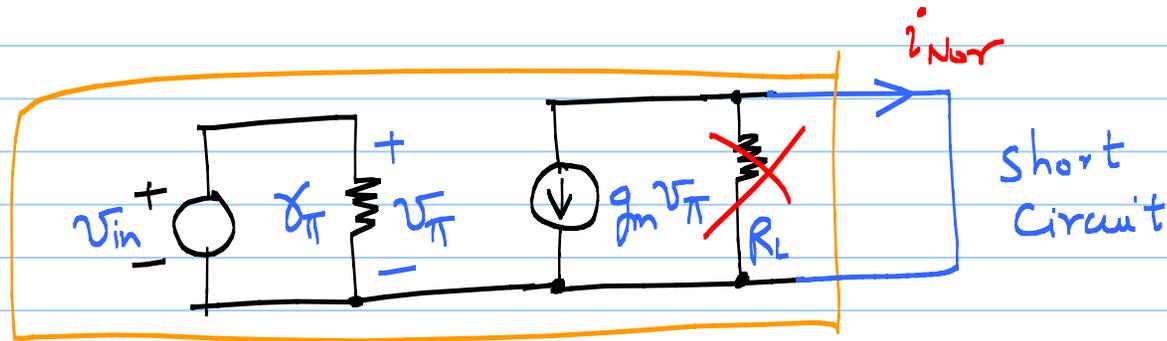Example: short the output port and find the short-circuit current, i_{Nsc}




\Rightarrow due to the short the resistance has no effect
 \hookrightarrow remove it

\Rightarrow KCL at the output node

$$\Rightarrow i_{Nsc} = -g_m v_{\pi} = -g_m v_{in}$$

* from previous example, $R_{Nur} = R_{Thev} = R_L$


⇒

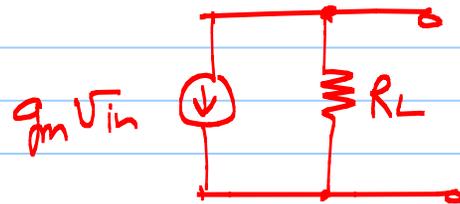

← Norton Equivalent circuit

hw: Repeat Textbook Example 1.12

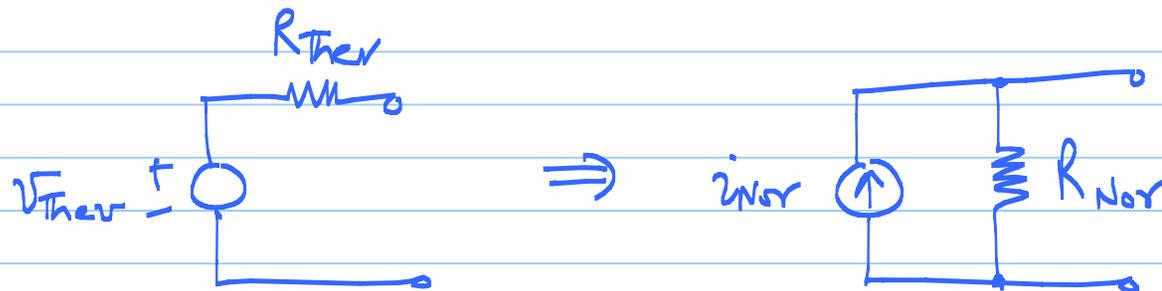Conversion between Thevenin and Norton Circuits



$$i_{Nor} = \frac{V_{Thev}}{R_{Thev}}$$
$$R_{Nor} = R_{Thev}$$