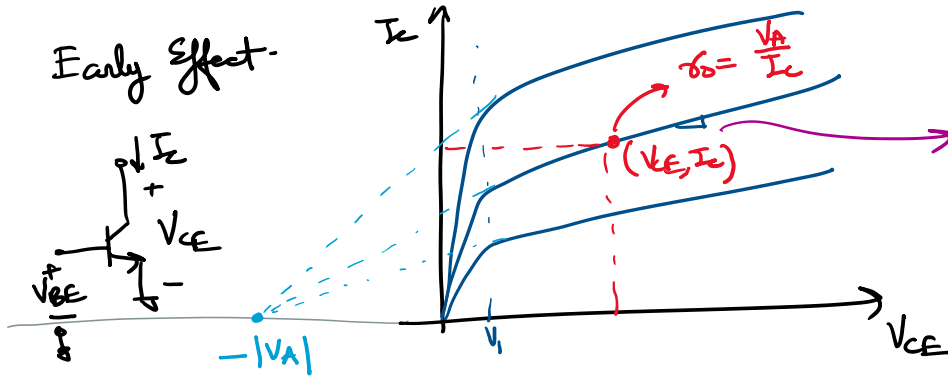


ECF 310 - Lecture 30.

Thursday, April 5, 2018 5:32 PM

Early Effect.



$$\phi = \left(\frac{\partial I_C}{\partial V_{CE}} \right)^{-1} = \boxed{\frac{V_A}{I_E}}$$

(V_E, I_E)

$$\phi_0 = \frac{V_A}{I_C}$$

$$I_C \approx I_S e^{\frac{V_{BE}}{nV_T}} \left(1 + \boxed{\frac{V_{CE}}{V_A}} \right)$$

$$\frac{V_{BE}}{nV_T} \rightarrow n=1 \text{ for our Book}$$



BJT Small-signal Model

$$\boxed{r_o = \frac{I_c}{V_A}} \text{ : BJT}$$


→ $\frac{1}{\lambda I_D}$ for MOSFETs

$$g_m = \left(\frac{\partial i_c}{\partial V_{BE}} \right) \bigg|_{(V_{BE}, I_c)} = \frac{\partial}{\partial V_{BE}} \left(I_s e^{\frac{V_{BE}}{V_T}} \right) = \frac{I_s}{V_T} e^{\frac{V_{BE}}{V_T}} \rightarrow I_c$$
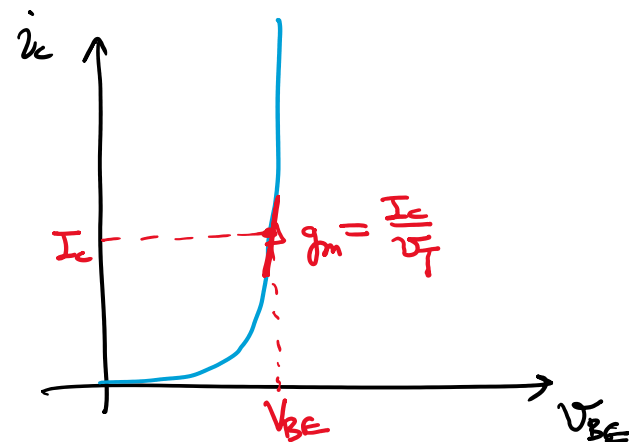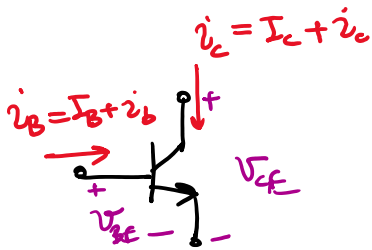
$$\Rightarrow \boxed{g_m = \frac{I_c}{V_T}}$$



π -Model of BJT

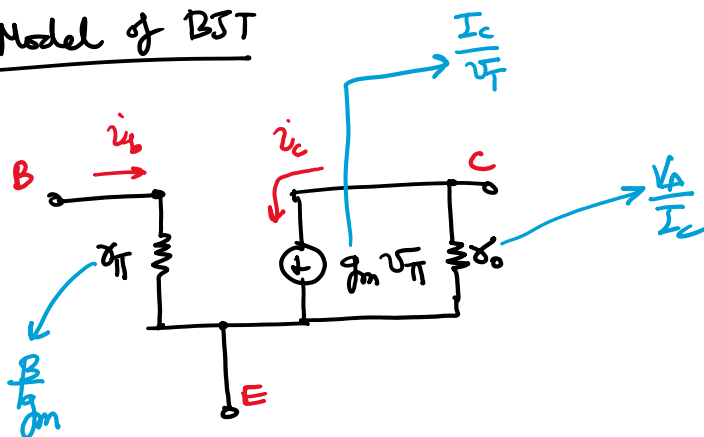

$$i_b = \frac{i_c}{\beta} = \frac{g_m V_{\pi}}{\beta}$$

$$\Rightarrow i_b = \left(\frac{g_m}{\beta} \right) V_{\pi}$$


$$\Rightarrow i_b = \frac{V_{\pi}}{r_{\pi}}$$

$$\boxed{r_{\pi} = \frac{\beta}{g_m}}$$

Small signal BJT Model

Small signal BJT model


π -Model :

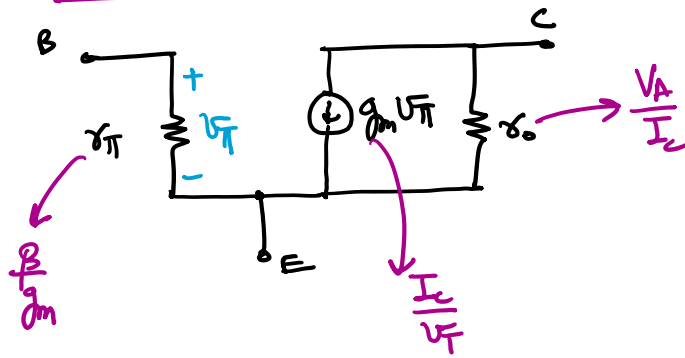

$$I_S = 3 \times 10^{-16} \text{ A}, \beta = 100, V_A = \infty$$

$$V_T = 26 \text{ mV}$$

Ex 4.10 :

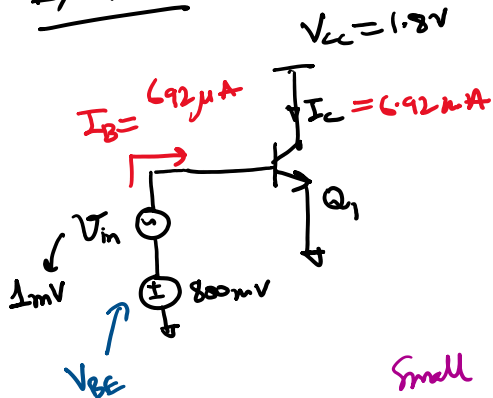


Find small-signal (A_v) circuit

$$I_C = I_S e^{V_{BE}/V_T} = 3 \times 10^{-16} \exp\left(\frac{0.8}{0.026}\right)$$

$$\Rightarrow I_C = 6.92 \text{ mA for } V_{BE} = 0.8 \text{ V}$$

Small signal parameters
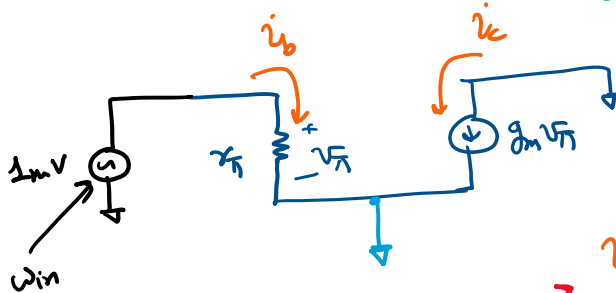
$$\begin{cases} g_m = \frac{I_C}{V_T} = \frac{6.92 \text{ mA}}{26 \text{ mV}} = \frac{1}{3.75 \Omega} \\ r_{\pi} = \frac{\beta}{g_m} = 375 \Omega \\ r_o = \frac{V_A}{I_C} = \infty \end{cases}$$



$$V_A \rightarrow \infty \Rightarrow r_o \rightarrow \infty$$

Small signal currents

$$i_c = g_m v_{\pi} = g_m v_{in} = 267 \mu\text{A}$$

$$i_b = \begin{cases} \frac{i_c}{\beta} \\ \frac{v_{\pi}}{r_{\pi}} \end{cases}$$




$$\frac{v_{\pi}}{r_{\pi}} = \frac{1 \text{ mV}}{375 \Omega} = 2.67 \mu\text{A}$$

total current $\Rightarrow$

$$i_c = I_C + i_c \sin(\omega t)$$

$$i_b = I_B + i_b \sin(\omega t)$$

PNP BJT

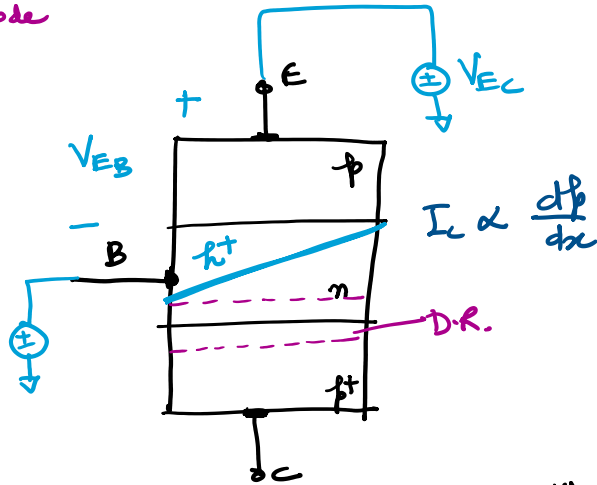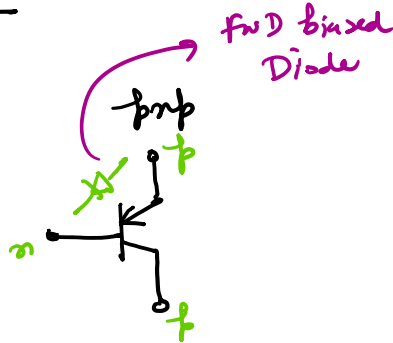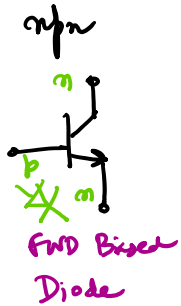



$$I_c = I_s e^{V_{EB}/V_T}$$

$$I_B = \frac{I_c}{\beta}$$


$$\alpha = \frac{\beta}{\beta + 1}$$

With Early Effect:
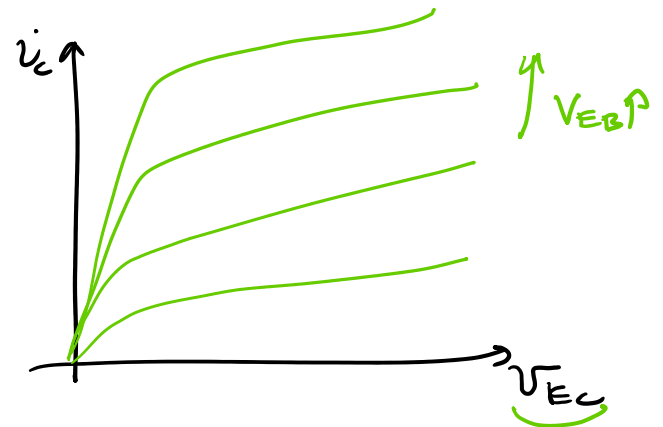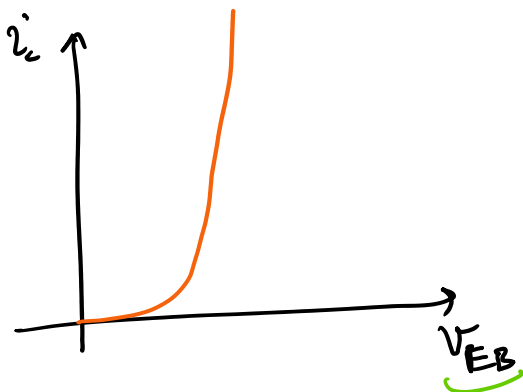
$$I_c = I_s e^{(V_{EB}/V_T)} \left(1 + \frac{V_{EC}}{V_A} \right)$$




PNP Small-Signal Model

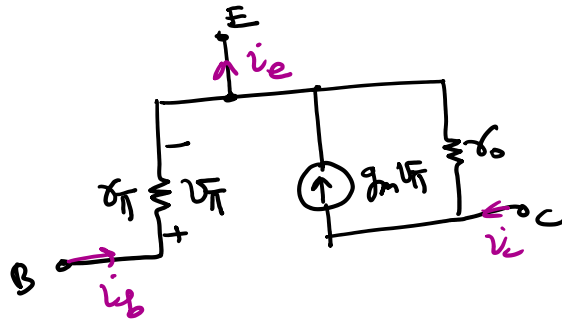


Read Section 4.6.3
in the Textbook

NMOS $\longrightarrow$ npn BJT

PMOS $\longrightarrow$ pnp BJT

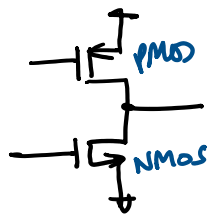


CMOS

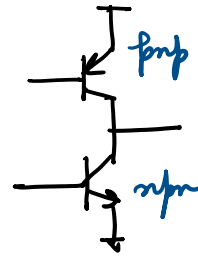

BJTs


Chapter 5: Bipolar Amplifiers

CS

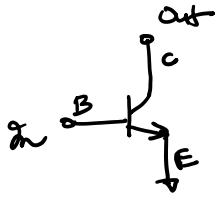


Common-Source
(CS)

CG

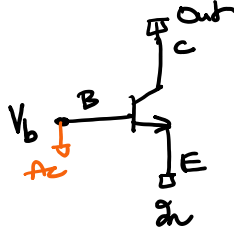




Common Gate
(CG)

CD/SF

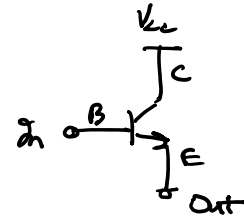

Common Collector (CC)
Emitter follower Circuit

Input resistance looking into the Base

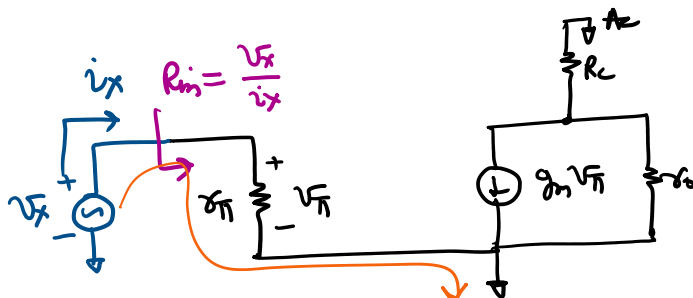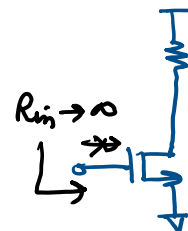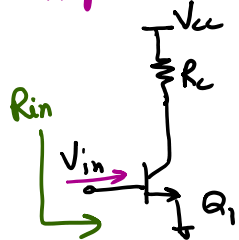


KVL:

$$v_x = i_x r_{\pi} \Rightarrow r_{in} = \frac{v_x}{i_x} = r_{\pi} = \frac{\beta}{g_m} = \frac{\beta r_e}{I_c}$$


$$r_{in} = \frac{\beta}{g_m}$$

for a large $r_{in} \Rightarrow \beta \uparrow$ or $I_c \downarrow$


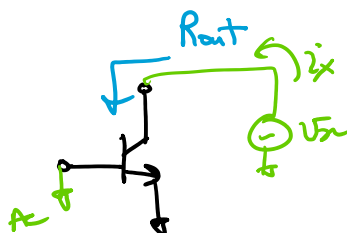
* Output resistance looking into the collector





$$R_{out} = r_o = \frac{V_A}{I_c}$$

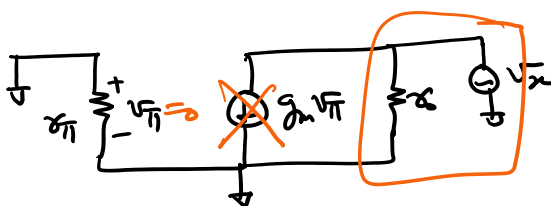

* Resistance looking into the emitter

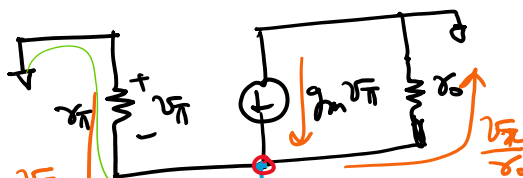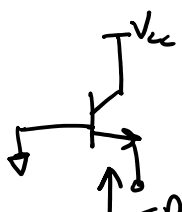

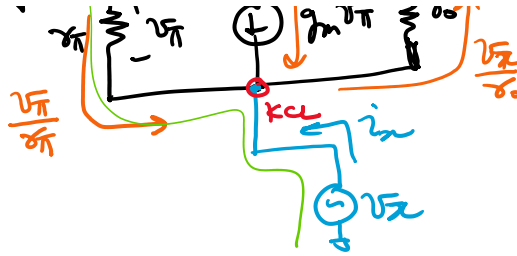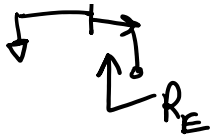

$$v_{\pi} + v_x = 0 \\ \Rightarrow v_x = -v_{\pi}$$

Kel:

$$i_x + \frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} - \frac{v_x}{r_o} = 0$$

$$i_x = v_x \left[\frac{1}{r_{\pi}} + g_m + \frac{1}{r_o} \right]$$

$$\Rightarrow R_E = \frac{v_x}{i_x} = \frac{1}{g_m + \frac{1}{r_{\pi}} + \frac{1}{r_o}}$$

$$R_E \approx \frac{1}{g_m}$$

$$R_E = \frac{1}{g_m + r_{\pi}^{-1} + r_o^{-1}} \approx \frac{1}{g_m}$$

Since $r_{\pi} = \frac{\beta}{g_m} \gg \frac{1}{g_m} \quad \therefore \beta \gg 1$

also $r_o \gg \frac{1}{g_m}$