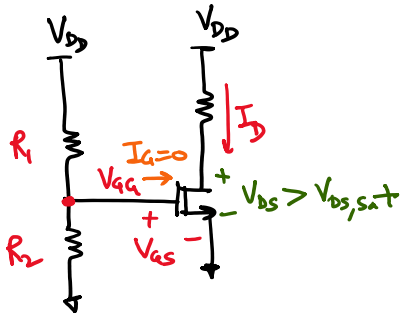


ECE 310 - Lecture 31

Friday, April 13, 2018 10:29 AM

Resistive Divider Biasing:



$(V_{GS}, V_{DS}, I_D) \leftarrow$ DC operating point


$\rightarrow g_m, r_o$

THz

300 GHz - 1 THz

InP, GaAs BJTs

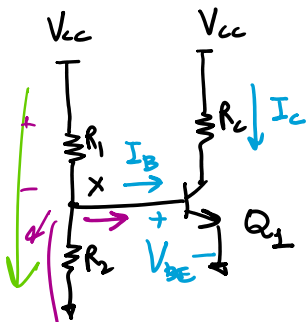Ignoring $I_B \approx 0$ (assuming $I_B \ll I_C$)



$$V_x = \frac{R_2}{R_1 + R_2} V_{CC} = V_{BE}$$

$$I_C = I_S e^{(V_{BE}/V_T)}$$

$$V_T = \frac{kT}{q} = 26 \text{ mV} @ 300 \text{ K}$$

$$I_S = 10^{-17} \text{ A}, \beta = 100, R_1 = 17 \text{ k}\Omega, R_2 = 8 \text{ k}\Omega, V_{CC} = 2.5 \text{ V}$$

$$V_x = 2.5 \times \frac{8 \text{ k}\Omega}{25 \text{ k}\Omega} = 0.8 \text{ V}$$

$$I_C = I_S e^{V_{BE}/V_T} = 231 \mu\text{A}$$

V_{DS}

$$V_{CE} = V_{CC} - I_C \times R_C = 1.345 \text{ V}$$

$$V_{BE} = 0.8 \text{ V}$$

$\therefore V_{CE} > V_{BE} \Rightarrow Q_1$ is in FA Region

$$\beta = 100$$

Ex 5.8

$$V_x = V_{CC} - \left(\frac{V_{CC}}{R_1 + R_2} + I_B \right) R_1$$

$$I_B = \frac{I_C}{\beta} = \boxed{2.3 \mu A}$$


for I_B to be negligible, we need

$$I_B \ll \frac{V_{CC}}{R_1 + R_2}$$

$$\frac{2.5}{25k}$$


$$2.3 \mu A \ll 100 \mu A$$

Burning power here

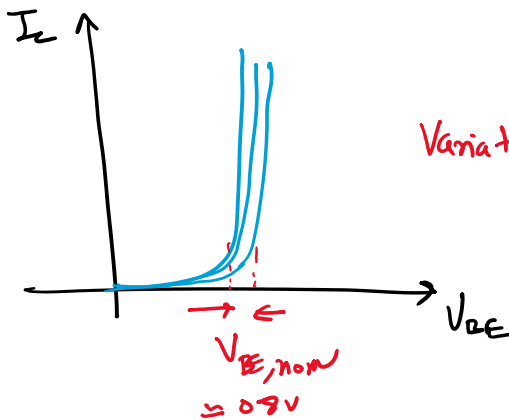

Variations in BJT nominal $V_{BE} \Rightarrow V_{BE, nom} \approx 0.8V$

4-Resistance Biasing

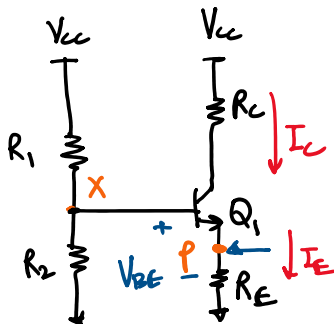

If Q_1 is in FAR $\Rightarrow \beta \gg 1$

assume I_B can be neglected ($I_B \approx 0$)
 $I_E \approx I_C$

$$V_P = V_X - V_{BE} \rightarrow \textcircled{1}$$

$$I_E \approx I_C = \frac{V_P}{R_E} = I_s e^{V_{BE}/V_T} \rightarrow \textcircled{2}$$


Solve for V_{BE}, I_C

$$\frac{V_X - V_{BE}}{R_E} = I_s e^{V_{BE}/V_T}$$

$$\frac{V_X - V_{BE}}{R_E} = I_S e^{V_{BE}/V_T}$$

$V_{BE} = ?$


✗ Use load line

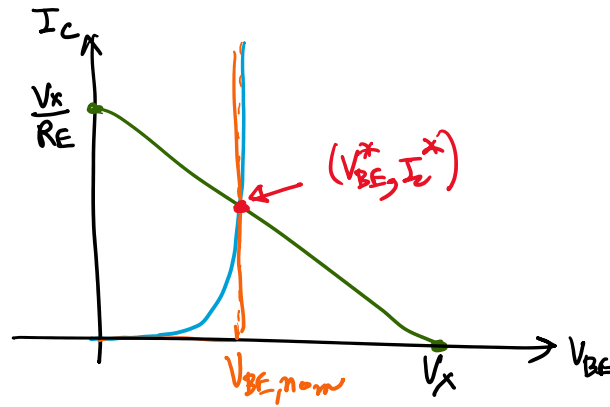

✗ For MOSFET, we used to solve quadratics
 ↳ here, we have exponential equation

if BE junction is forward-biased, we can assume that
 $V_{BE} \leq V_{BE, nom} = 0.8V$

$$S_C \Rightarrow 0.5V + 0.8V$$

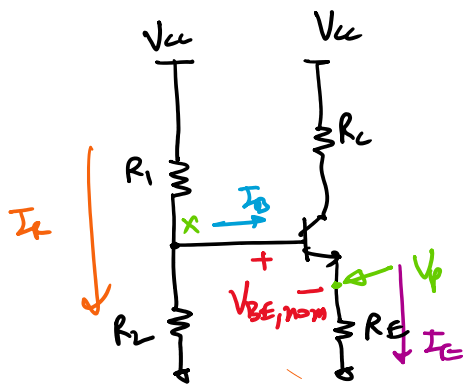

$$V_p \approx \overbrace{V_{CC} \cdot \frac{R_2}{R_1 + R_2}}^{1V} - \overbrace{V_{BE, nom}}^{0.8V}$$

$$I_E = \frac{V_p}{R_E} = \frac{0.2V}{1k\Omega} = 200\mu A$$

↓
 1mA

check whether Q_1 is in $f_A R$

$$V_{CE} > V_{BE}$$

↓


$$V_{CC} - I_E R_E$$

$$\uparrow$$

$$= I_E$$

$$I_B = \frac{I_E}{\beta}$$

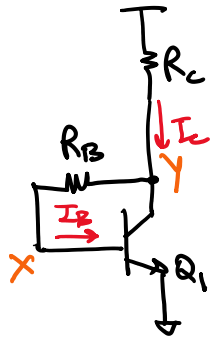$R_E \Rightarrow$ desensitizes I_E wrt manufacturing variations in $V_{BE, \text{nom.}}$



$$V_X = V_Y - I_B \cdot R_B$$

$\uparrow$ $\uparrow$
 V_{BE} V_{CE}

$$V_{BE} < V_{CE}$$

* Q_1 is always in **FAR**



$$V_Y = V_{CC} - I_C R_C \longrightarrow \textcircled{1}$$

$$\text{Also, } V_Y = I_B R_B + V_{BE} \longrightarrow \textcircled{2}$$


$$= R_B \frac{I_C}{\beta} + V_{BE}$$

~~① & ②~~ give


$$I_C = \frac{V_{CC} - V_{BE}}{R_C + \frac{R_B}{\beta}}$$

for lower sensitivity to $\beta' \Rightarrow R_C \gg \frac{R_B}{\beta}$

CE Amplifier

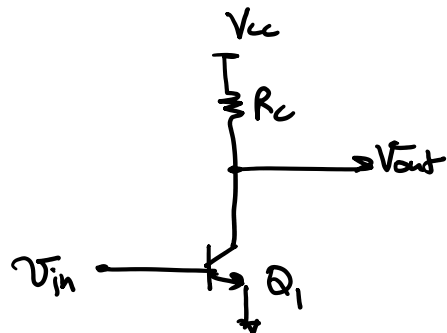

$$A_v = \frac{v_{out}}{v_{in}} = ?$$

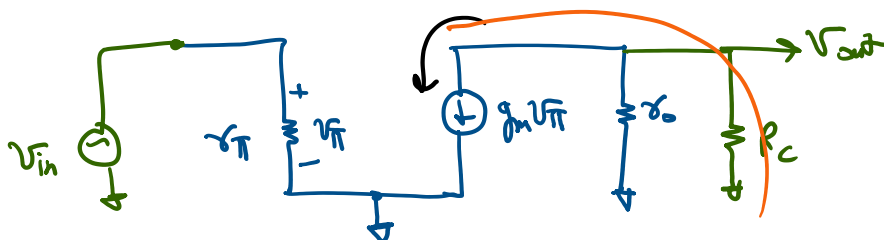

$$v_{out} = -g_m v_{\pi} (r_o || R_C)$$

$$= -g_m v_{in} (r_o || R_C)$$

$$r_o = \frac{V_A}{I_C}$$

$$A_v = \frac{v_{out}}{v_{in}} = \boxed{-g_m (r_o || R_C)}$$

CE with Emitter Degeneration

