


EE 310 - Lecture 34.

Friday, April 20, 2018 10:30 AM

Problem 5.52 (c)


$$V_{CC} = 2.5V, I_D = 8 \times 10^{-16} A, \beta = 100, V_A \rightarrow \infty.$$

$$V_{BE, \text{nom}} = 0.7V$$

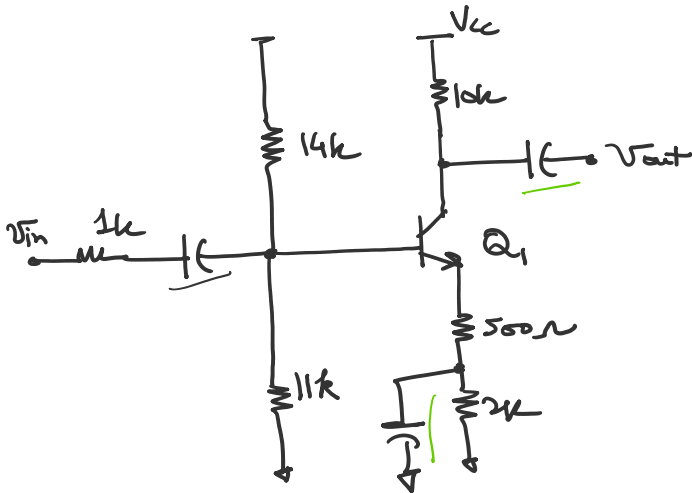

DC picture:

$$\beta = 100$$

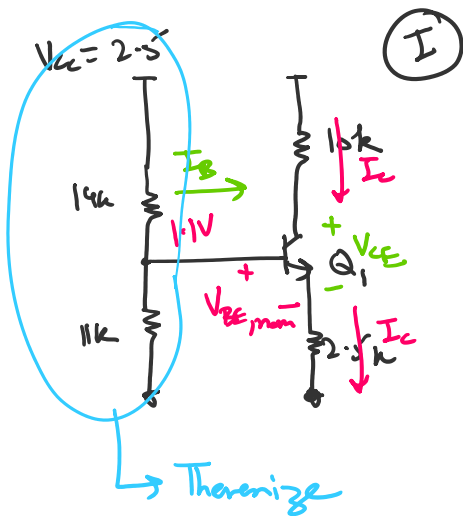

Ignore base current:


$$I_C \approx I_E = \frac{1.1 - 0.7}{2.5k} = \boxed{0.16 \text{ mA}}$$


$$V_{CE} = 2.5 - 0.16 \text{ mA} (12.5k) = \underline{0.5V} \leftarrow \text{SAT.}$$

$$g_m = \frac{I_C}{V_T} \quad r_o \rightarrow \infty$$

$$r_{\pi} = \frac{\beta}{g_m}$$

II Not ignoring base current

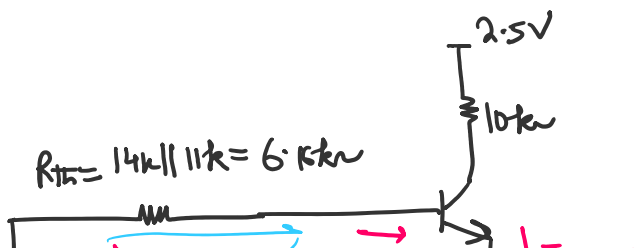

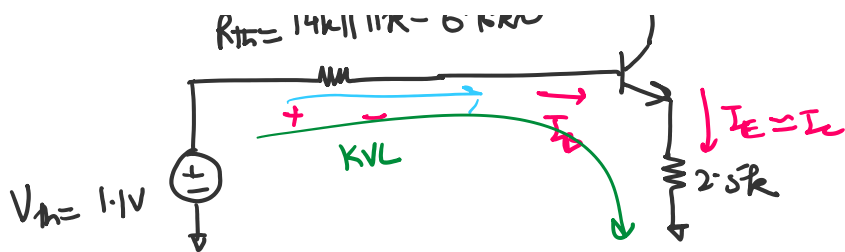

$$V_{th} - I_B \cdot R_{th} - V_{BE, nom} - I_C \cdot 2.5k = 0$$

$$I_B = \frac{1.1V - V_{BE, nom} - I_C \cdot 2.5k}{6.16k\Omega}$$


$$I_C = \beta I_B = \frac{100 (1.1 - 0.7 - I_C \times 2.5k)}{6.16k\Omega}$$

$$I_C = 0.156 \mu A$$

$$g_m = \frac{I_C}{V_T} = \frac{0.156 \mu A}{V}$$

$$r_{\pi} = \frac{\beta}{g_m} = 16.67 k\Omega$$

AC picture:

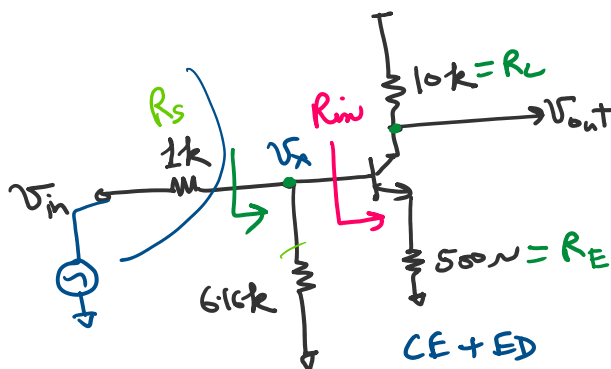

$$\frac{V_{out}}{V_{in}} = \left(\frac{V_x}{V_{in}} \right) \times \left(\frac{V_{out}}{V_x} \right)$$

$$R_{in} = r_{\pi} + (\beta + 1) R_E$$

$$= 16.67k + 101 \times 0.5k$$

$$= 16.67k + 101 \times 0.5k$$

$$= 67.17k$$

$$\frac{v_z}{v_{in}} = \frac{R_{in} \parallel 6.15k}{1k + R_{in} \parallel 6.15k} = 0.85$$

$$\frac{V_{out}}{V_{in}} \approx - \frac{g_m R_c}{1 + \left(\frac{1}{g_m} + g_m\right) R_E}$$

$$\approx - \frac{R_c}{\frac{1}{g_m} + R_E}$$

$$= -59.82$$

$$\because \beta \gg 1$$

$$A_v = 0.85 \times (-59.82) = -50.84$$

$$20 \log_{10}(\downarrow) = 21.3$$

$$\text{Input Resistance} \Rightarrow R_{in} \parallel 6.15k = 5.64k$$


Chapter 8 - Operational Amplifiers (Opamps)

Friday, April 20, 2018 10:56 AM

MOSFETs
BJTs
JFETs

Ideal opamp:

Differential inputs

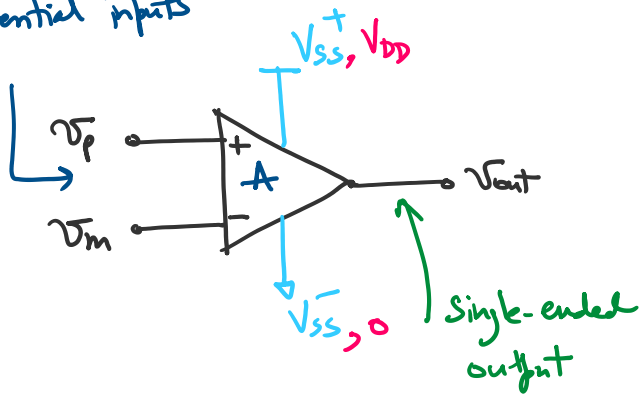


low-frequency idealized model

$$v_{out} = A(v_p - v_m)$$

$\uparrow$ finite $0 < < V_{DD}$
 $\downarrow$ $A \rightarrow \infty$

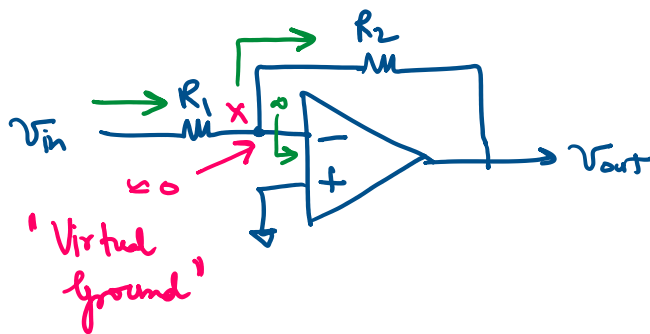for finite $v_{out} \Rightarrow v_p \approx v_m$





$$\frac{v_{in}}{R_1} = \frac{(v_{in} - v_{out})}{R_2}$$

$$\frac{v_{in}}{R_1} = -\frac{v_{out}}{R_2}$$


$$\Rightarrow \frac{v_{out}}{v_{in}} = -\frac{R_2}{R_1} \quad \text{very precise}$$

$\hookrightarrow$ independent of A

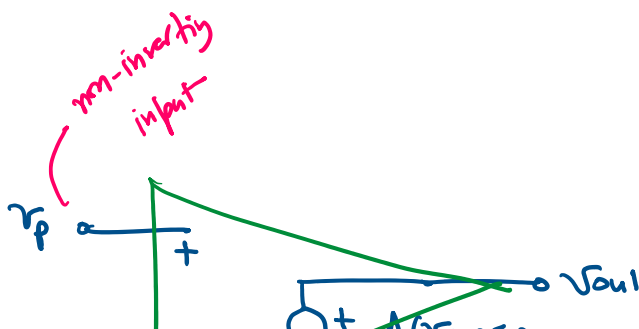

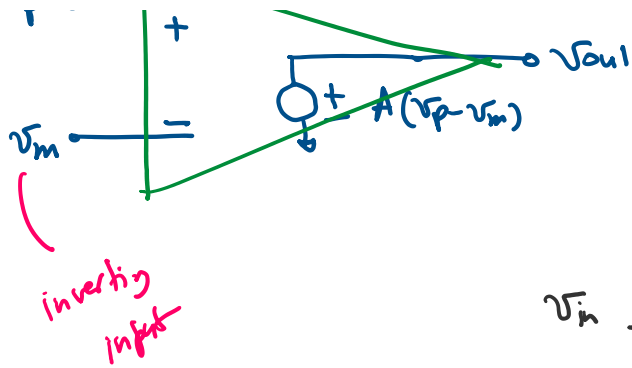

Control system

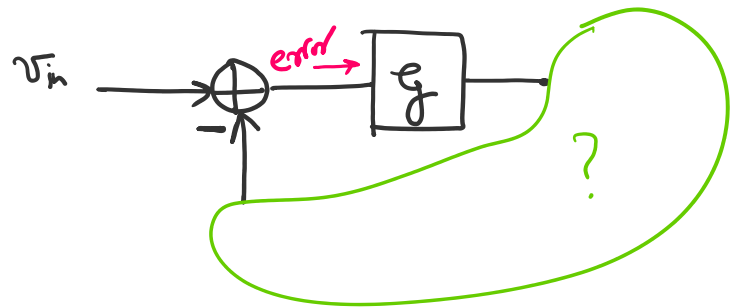

Ideal opamp:

- * $A \rightarrow \infty$
- * $R_{in} \rightarrow \infty$
- * $R_{out} \rightarrow 0$
- * infinite speed $\rightarrow \infty$ bandwidth