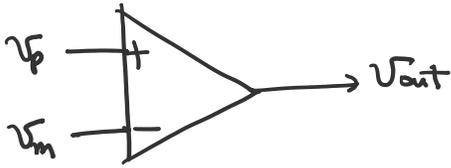


EECE 310 - Lecture 35

Monday, April 23, 2018 2:08 AM




$$v_{out} = A_o (v_p - v_m)$$


Annotations: An arrow points from v_{out} to the word "finite". An arrow points from A_o to the symbol ∞ . An arrow points from $(v_p - v_m)$ to the equation $v_p \approx v_m$.

Also,
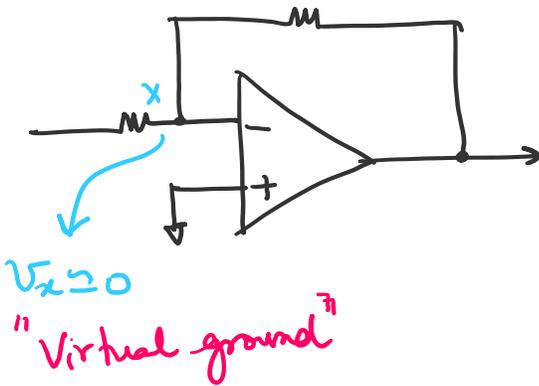
$$v_p - v_m = \frac{v_{out}}{A_o} \rightarrow 0 \quad \text{as } A_o \rightarrow \infty$$



Unity Gain Buffer

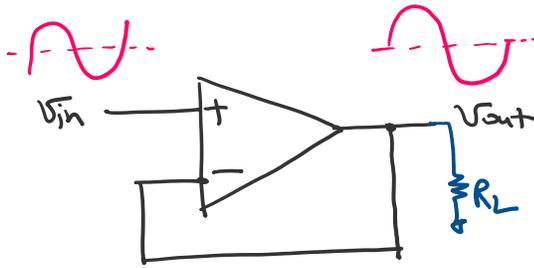

$$V_{out} = A_o (V_{in} - V_{out})$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{A_o}{1 + A_o} = \frac{1}{1 + \frac{1}{A_o}}$$

$$= \left(1 + \frac{1}{A_o}\right)^{-1} \approx 1 - \frac{1}{A_o} \rightarrow 1 \text{ as } A_o \rightarrow \infty$$

Unity gain as $A_o \rightarrow \infty$

Voltage Buffer using an opamp.

Let $A_o = 1000$
 $\hookrightarrow 20 \log_{10}(1000) = 20 \times \log_{10}(10^3)$
 $= 20 \times 3 = \underline{60 \text{ dB}}$


\downarrow $V_{in} = 2V$

$$V_{out} = \frac{1}{1 + \frac{1}{1000}} = 0.999V$$

error $\Rightarrow 0.001V$

\Rightarrow larger the opamp gain \Rightarrow smaller is the error

Negative feedback amplifier:

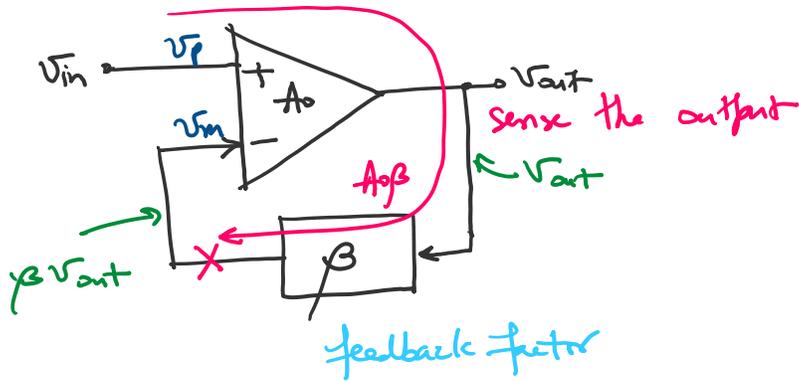

Typically
 $0 \leq \beta \leq 1$
 \hookrightarrow precise

$$\Rightarrow V_{out} = A_0 (v_p - v_m)$$

$$= A_0 (V_{in} - \beta V_{out})$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{A_0}{1 + A_0 \beta} = \frac{1}{\beta} \cdot \frac{1}{1 + \frac{1}{A_0 \beta}}$$

$$= \frac{1}{\beta} \cdot \left(1 + \frac{1}{A_0 \beta}\right)^{-1}$$

$$\approx \left(\frac{1}{\beta}\right) \left(1 - \frac{1}{A_0 \beta}\right)$$

Very precise gain set by β

for loop gain $A_0 \beta \gg 1$

Here:

$A_0 \beta \leftarrow$ open loop gain

$\frac{A_0}{1 + A_0 \beta} \leftarrow$ closed loop gain

$\approx \frac{1}{\beta} \leftarrow$ independent of A_0 for $A_0 \beta \gg 1$


$$\frac{V_{out}}{V_{in}} \approx \frac{1}{\beta} \left(1 - \frac{1}{A_0 \beta}\right) = \frac{1}{\beta} (1 - \epsilon)$$

precision 1. finite gain

$$\frac{V_{out}}{V_{in}} \approx \underbrace{\frac{1}{\beta}}_{\text{precision}} \underbrace{\left(1 - \frac{1}{A_o\beta}\right)}_{\text{error due to finite gain}} = \frac{1}{\beta} (1 - \epsilon)$$

$\epsilon \Rightarrow$ error due to finite gain

Non-inverting amplifier:

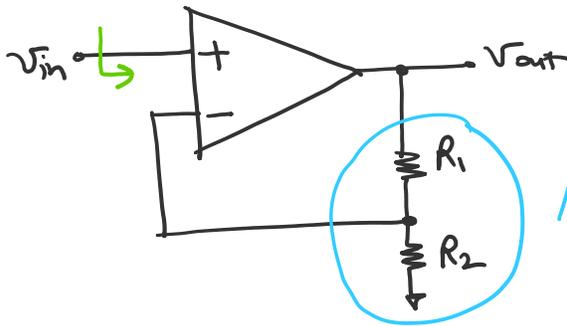

$$\beta = \frac{R_2}{R_1 + R_2} \Rightarrow \frac{1}{\beta} = \frac{R_1 + R_2}{R_1} = \boxed{1 + \frac{R_2}{R_1}}$$

closed loop gain

$$\frac{V_{out}}{V_{in}} = \frac{1}{\beta} \cdot \left(1 - \frac{1}{A_o \beta}\right)$$

$$= \underbrace{\left(1 + \frac{R_2}{R_1}\right)}_{\text{ideal closed-loop gain}} \cdot \left[1 - \underbrace{\left(1 + \frac{R_2}{R_1}\right) \cdot \frac{1}{A_o}}_{\text{gain error}}\right]$$

ideal closed-loop gain

gain error

If $A_o \beta \gg 1$ then

$$\boxed{\frac{V_{out}}{V_{in}} \approx 1 + \frac{R_2}{R_1}}$$


non-inverting amplifier

$$R_1 = 1k\Omega, R_2 = 1k\Omega \\ \Rightarrow \text{gain} = 10$$

\Rightarrow This gain is precise as it only depends upon the resistor ratio
 \hookrightarrow very precise

Input impedance = ∞ for an ideal opamp.

Inverting amplifier :

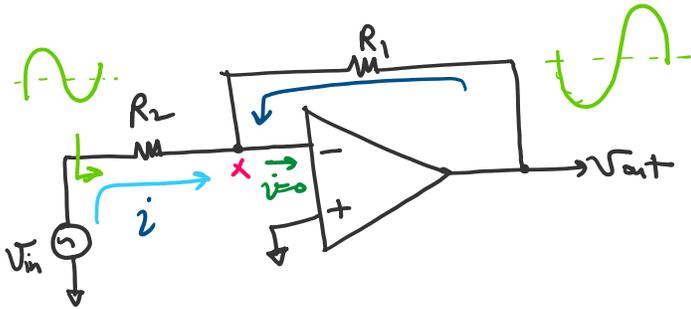

$$i = \frac{V_{in} - V_x}{R_2} = \frac{V_x - V_{out}}{R_1} \rightarrow \textcircled{1}$$

$$V_{out} = A_o (V_p - V_m) \\ = A_o (0 - V_x)$$

$$\Rightarrow V_x = -\frac{V_{out}}{A_o} \rightarrow \textcircled{2}$$

from ① & ②

$$\frac{V_{out}}{R_1} = -\frac{V_{in}}{R_2} + \frac{V_x}{R_2} + \frac{V_x}{R_1} \\ = -\frac{V_{in}}{R_2} - \frac{V_{out}}{A_o} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\Rightarrow \frac{V_{out}}{R_1} + \frac{V_{out}}{A_o R_1} \left(1 + \frac{R_1}{R_2} \right) = -\frac{V_{in}}{R_2}$$

$$\Rightarrow V_{out} \left[1 + \frac{1}{A_o} \left(1 + \frac{R_1}{R_2} \right) \right] = -\frac{R_1}{R_2} \cdot V_{in}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = -\frac{R_1}{R_2} \cdot \frac{1}{1 + A_o \left(1 + \frac{R_1}{R_2} \right)}$$

$$= -\frac{R_1}{R_2} \cdot \frac{1}{1 + A_o \beta}$$

for $A_o \beta \rightarrow \infty$

$$\frac{V_{out}}{V_{in}} \approx -\frac{R_1}{R_2}$$

$$V_x \approx 0 \text{ for } A_0 \rightarrow \infty$$

Node X is the virtual ground

$$\leftarrow \text{inverting gain is } -\frac{R_1}{R_2}$$

* Input impedance is R_2

↳ lower impedance than ∞

Q. What happens if we have finite opamp gain

$$\frac{V_{out}}{V_{in}} \approx \frac{1}{\beta} \cdot \left(1 - \underbrace{\frac{1}{A_0\beta}}_{\epsilon}\right) \quad \text{for loop-gain } A_0\beta \rightarrow \infty$$

$\epsilon \rightarrow 0$

$$\text{for large closed-loop gain} = \frac{1}{\beta}$$

⇒ β is small


⇒ $A_0\beta$ is smaller than A_0

⇒ higher closed-loop error ($\epsilon = \frac{1}{A_0\beta}$) for
a higher closed loop gain $\frac{1}{\beta}$.

higher closed-loop gain ⇒ higher error.

* higher precision ⇒ high $A_0\beta$ ⇒ high A_0 ⇒ more power in the opamp.

Voltage Adder :

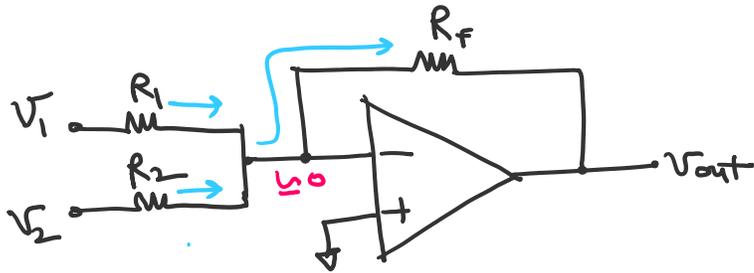

KCL at x

$$\Rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_{out}}{R_F} = 0$$

$$\Rightarrow V_{out} = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

$$= -g_1 \cdot V_1 - g_2 \cdot V_2$$

\downarrow $g_1 = \frac{R_F}{R_1}$ \downarrow $g_2 = \frac{R_F}{R_2}$

if $g_1 = g_2 = 1$

$$V_{out} = -(V_1 + V_2)$$