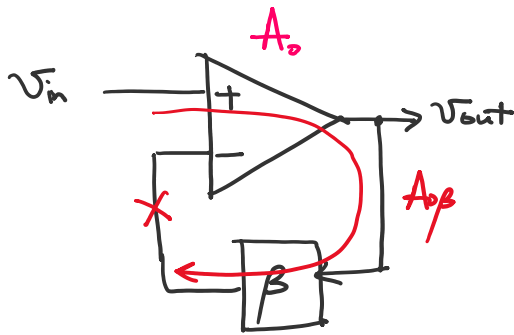


ICE 310- Lecture 36

Wednesday, April 25, 2018 10:35 AM



$\beta \rightarrow$ precise

$$0 \leq \beta \leq 1$$

open-loop gain
(loop gain) = $A_o\beta$


closed-loop gain $\frac{V_{out}}{V_{in}} = \frac{A_o}{1 + A_o\beta}$

$$(1+x)^{-1} \approx 1-x$$

$$= \frac{1}{\beta} \left(1 + \frac{1}{A_o\beta}\right)^{-1}$$

$$= \boxed{\frac{1}{\beta}} \left(1 - \frac{1}{A_o\beta}\right)$$
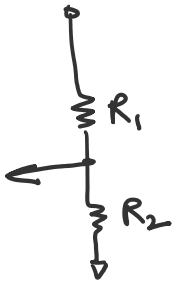
$$1 - \epsilon \rightarrow \epsilon = \frac{1}{A_o\beta}$$




$$\beta = \frac{R_2}{R_1 + R_2}$$

higher closed-loop gain $\Rightarrow \frac{1}{\beta} \uparrow$


$\Rightarrow \beta \downarrow$

$A_{\beta} \downarrow$

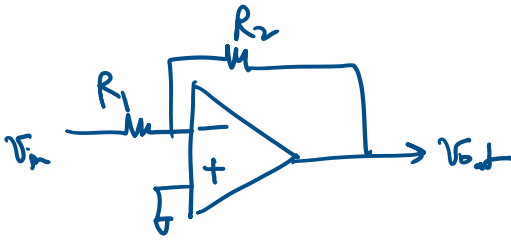


inverting
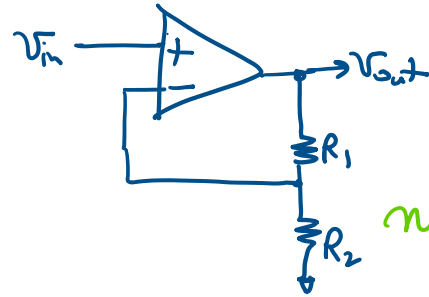
$$\frac{V_{out}}{V_{in}} = - \frac{R_2}{R_1}$$



noninverting

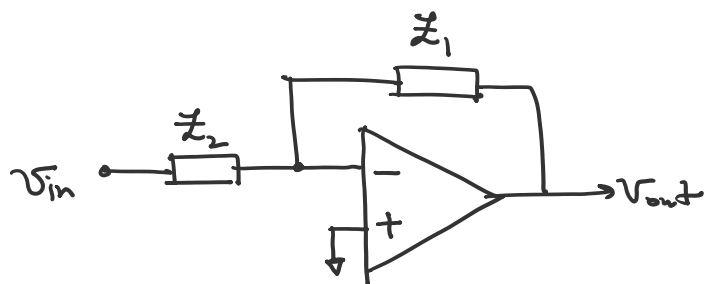
$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$$



inverting topology

$$\frac{V_{out}}{V_{in}} = -\frac{Z_1}{Z_2}$$

Integrator

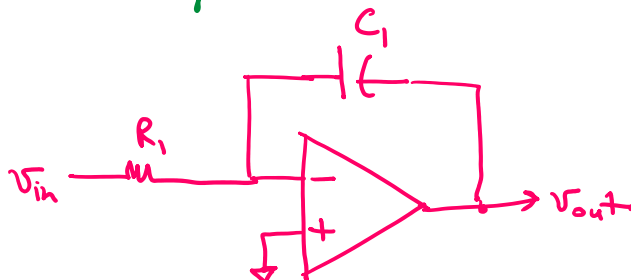


$$Z_1 = \frac{1}{sC_1}, \quad Z_2 = R_1$$

$$\frac{V_{out}}{V_{in}}(s) = -\frac{Z_1}{Z_2} = -\frac{1}{sR_1C_1}$$



$$= -\frac{\omega_1}{s}$$

$$\omega_1 = \frac{1}{R_1C_1}$$

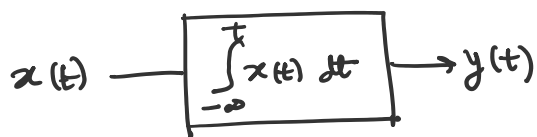

$$X(s)$$

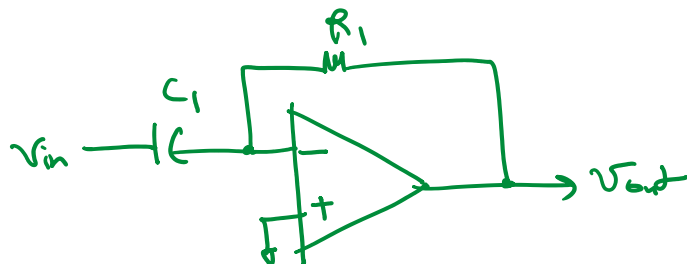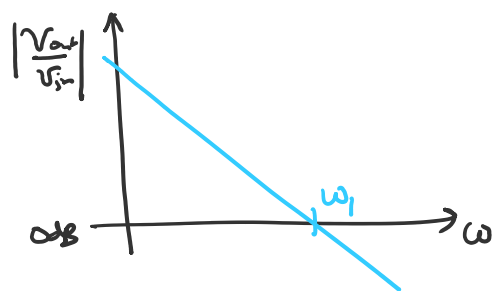
$$Y(s) = \frac{X(s)}{s} - \int_{-\infty}^0 x(t) dt$$



$$\frac{V_{out}}{V_{in}} = -\frac{R_1}{1/sC_1} = -sR_1C_1$$

L → ...
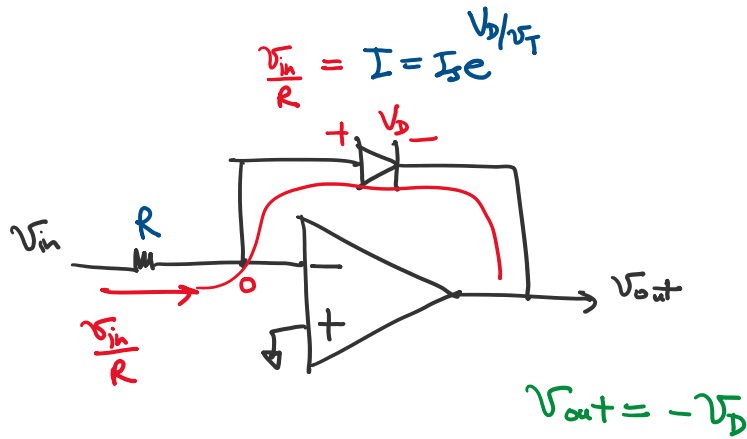
$$\frac{V_{out}}{V_{in}} = - \frac{1}{V_{sc1}} = - \frac{1}{V_{sc1}} \rightarrow \text{Differentiator}$$




$$\frac{V_{in}}{R} = I_s e^{V_b/V_T}$$

$$\Rightarrow \frac{V_{in}}{R} = I_s e^{-V_{out}/V_T}$$

$$\Rightarrow \left(\frac{V_{in}}{I_s R} \right) = e^{-V_{out}/V_T}$$

$$\Rightarrow -V_T \ln \left(\frac{V_{in}}{I_s R} \right) = V_{out}$$



logarithmic circuit

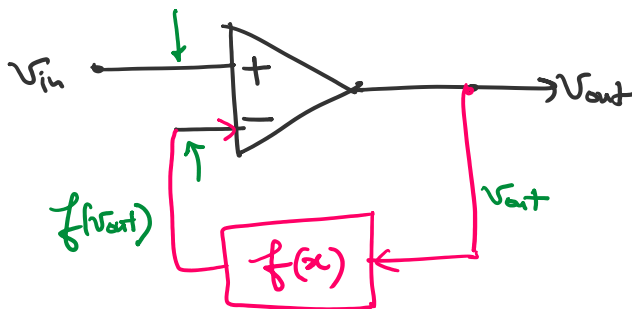



$$V_{in} = f(V_{out})$$

$$\Rightarrow V_{out} = f^{-1}(V_{in})$$

Opamp Non-idealities:


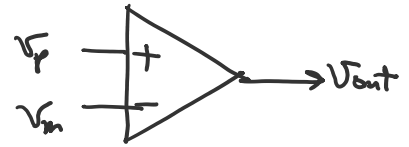
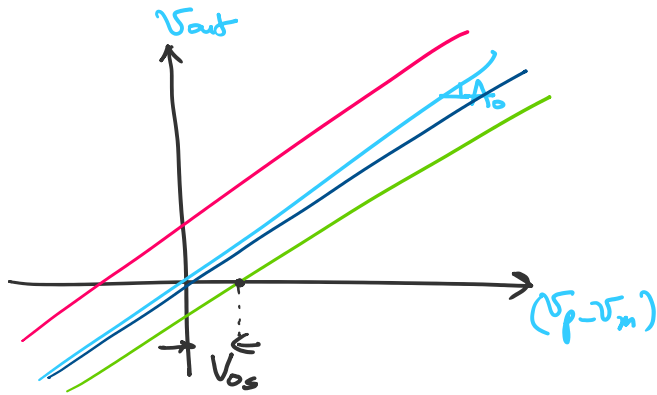


$$V_{out} = A_0(V_p - V_m)$$

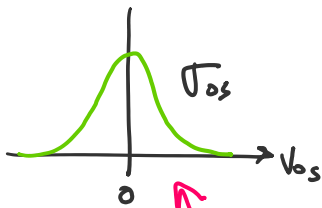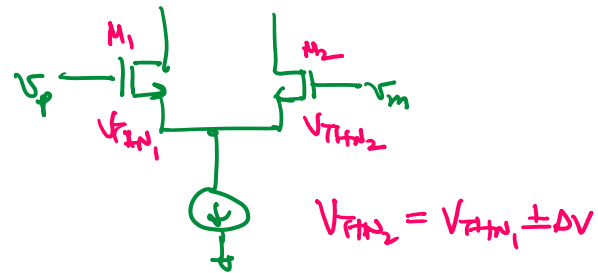

OFFSET Voltage

↳ Random variation from chip to chip

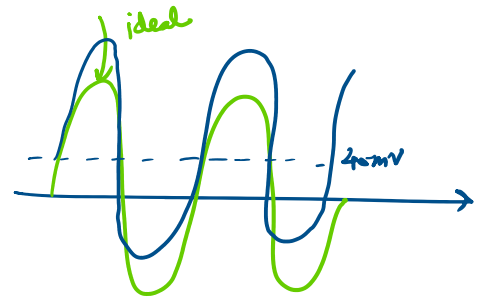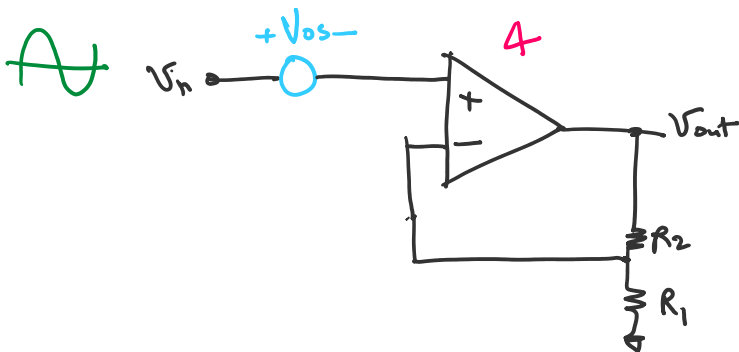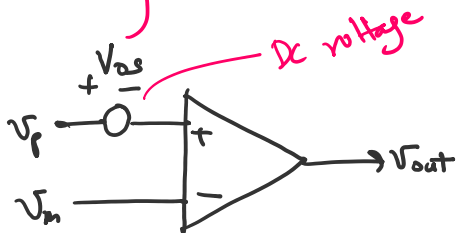

$$V_{out} = \left(1 + \frac{R_2}{R_1}\right)(V_{in} + V_{os})$$

$\uparrow$
10mV

... T_{10mV}

↳ effect is also amplified

↳ accuracy limitation)