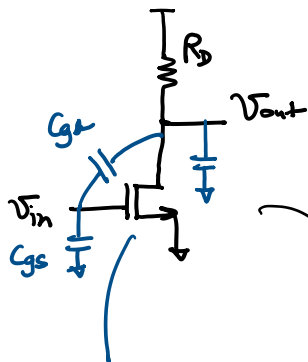


EE 310- Lecture 37



Monday, April 30, 2018 10:25 AM

Opamps:

$$A_v = -g_m(r_o \parallel R_D) \approx -g_m R_D \quad \text{for } R_D \ll r_o$$



"parasitic capacitances"

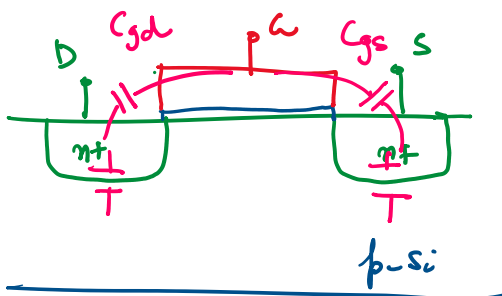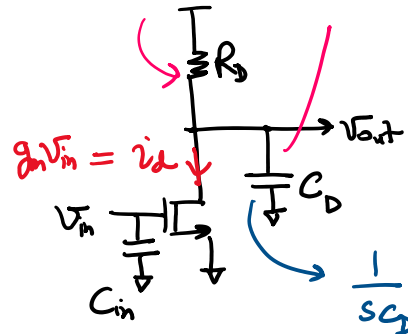

$$\frac{V_{out}}{V_{in}} = ?$$

$$\begin{aligned} \Rightarrow V_{out} &= -i_d \left(R_D \parallel \frac{1}{sC_D} \right) \\ &= -i_d \cdot \frac{R_D \cdot \frac{1}{sC_D}}{R_D + \frac{1}{sC_D}} \\ &= -i_d \cdot \frac{R_D}{1 + sR_D C_D} \end{aligned}$$

$$\boxed{\frac{V_{out}}{V_{in}}(s) = - \frac{g_m R_D}{1 + sR_D C_D}}$$

low-frequency gain

no zero
1 pole

roots are
zeros


$$P(s) = \frac{N(s)}{D(s)}$$

↓ roots are

Single-pole Transfer function

Single-pole Transfer function

$D(s)$
↓ roots are poles

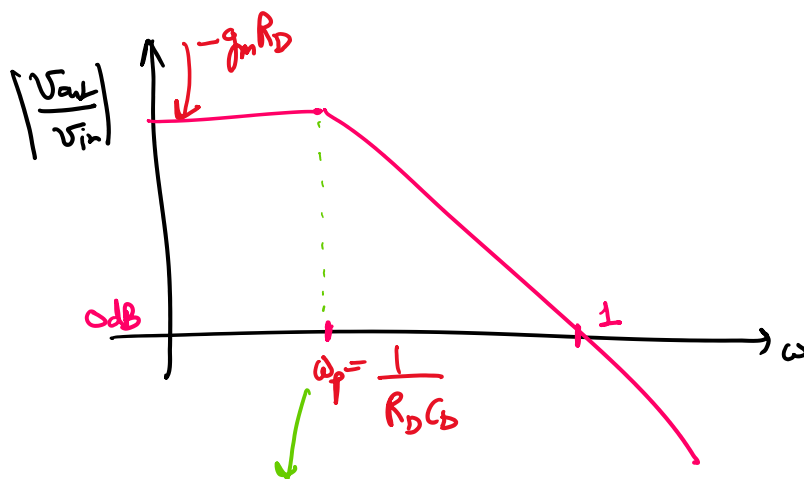

$$1 + s R_D C_D = 0$$

$$\Rightarrow s = j\omega_p = -\frac{1}{R_D C_D}$$

$$\omega_p = \frac{1}{R_D C_D}$$

3dB Bandwidth of the CS amplifier.


Any Amplifier will have finite bandwidth

↳ finite speed.

frequency Response of Amplifiers → ECE 410

Opamp speed limitations :


Single-pole model

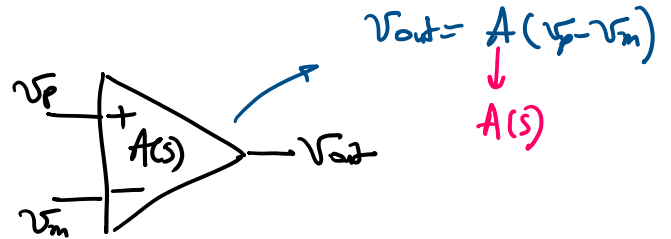

$$A(s) = \frac{A_0}{1 + s/\omega_p}$$

DC gain $\rightarrow A_0$
 pole $\rightarrow \omega_p$

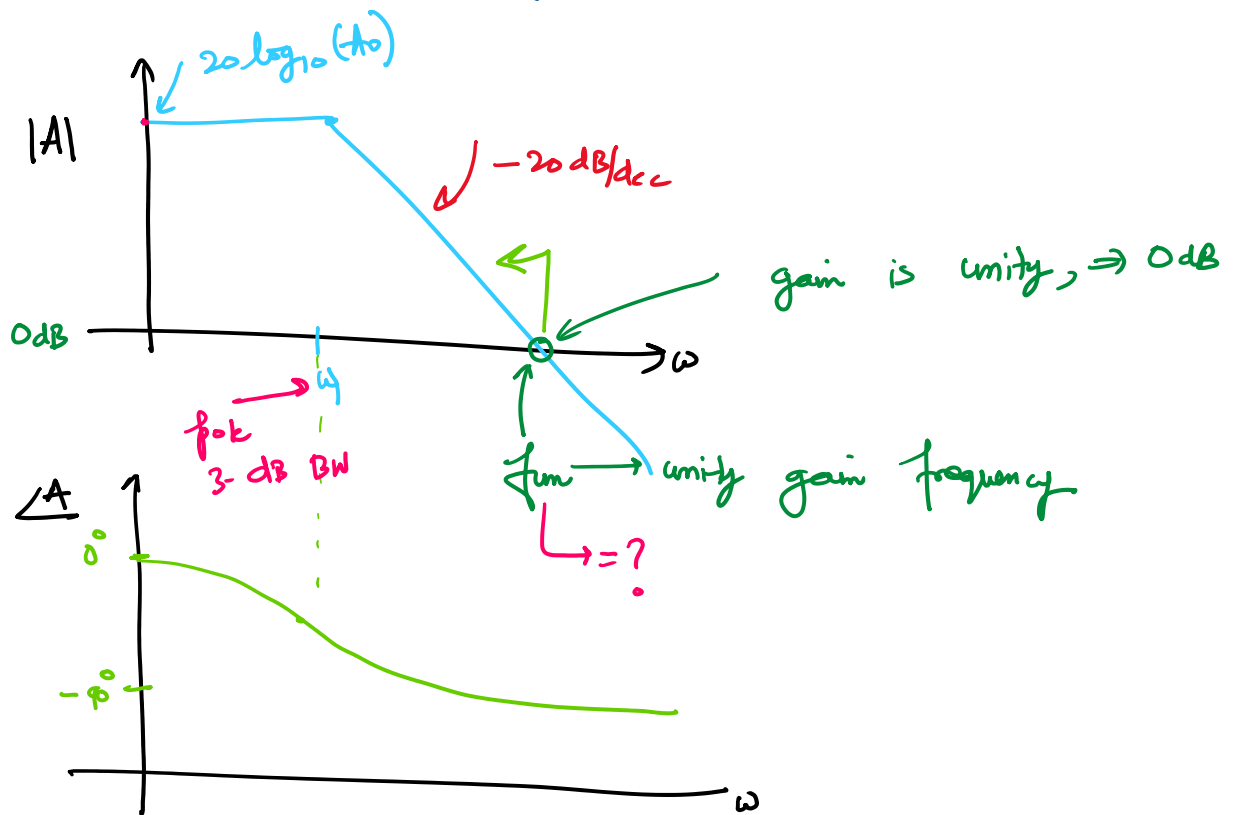* one pole at $\omega = \omega_p$ dominates the opamp frequency response




$$\frac{s}{\omega_1} = \left| \frac{j\omega}{\omega_1} \right|$$

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_1}}$$

At high frequencies $\left| \frac{s}{\omega_1} \right| \gg 1$
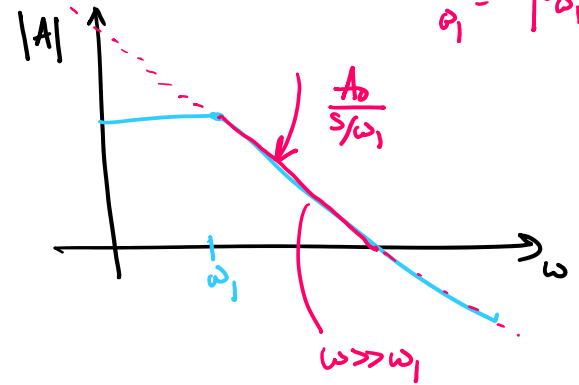
$$\approx \frac{A_0}{s/\omega_1} = \frac{A_0 \omega_1}{s}$$



at $\omega = \omega_{un} \Rightarrow |A(s)| = 1$

$$\Rightarrow \left| \frac{A_0 \omega_1}{j\omega_{un}} \right| = 1$$

$\Rightarrow$

$$\frac{\omega_{un}}{2\pi} = \frac{A_0 \omega_1}{2\pi}$$

$$\omega_{un} = A_0 \omega_1$$


$$f_{un} = A_0 f_1$$

unity-gain frequency

DC gain


3-dB frequency (BW)
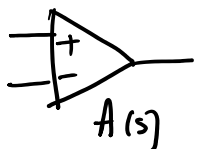
$$f_{un} = \underbrace{\text{Gain} \times \text{BW}}_{\text{Gain BW product}}$$



open loop

Now consider the non-inverting amplifier

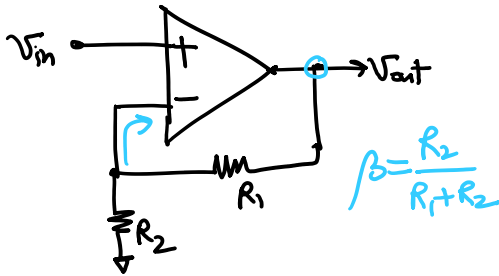

$$A(s) = \frac{A_0}{1 + s/\omega_1}$$

Closed-loop Transfer Function

$$\frac{V_{out}}{V_{in}}(s) = \frac{A(s)}{1 + \beta A(s)}$$

$$= \frac{\frac{A_0}{1 + s/\omega_1}}{1 + \frac{\beta A_0}{1 + s/\omega_1}}$$

$$= \frac{A_0}{1 + \frac{s}{\omega_1} + \beta A_0}$$

$$= \frac{A_0}{(1 + \beta A_0) + s/\omega_1}$$

$$= \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_1(1 + \beta A_0)}} \quad \text{single-pole form}$$

$$= \frac{A_{CL}}{1 + \beta A_0} \cdot \frac{1}{1 + \frac{s}{\omega_1(1 + \beta A_0)}}$$

closed loop gain without BW-limitations

single-pole transfer function

closed loop gain without BW-limitations $1 + \frac{A_o}{1+s/\omega_{p,cl}}$ ← single-pole transfer function

$$A_{cl} = \frac{A_o}{1 + \beta A_o} \approx \frac{1}{\beta} \cdot \underbrace{\left(1 - \frac{1}{A_o \beta}\right)}_{\text{precision error due to finite opamp gain}}$$

$$\frac{V_{out}}{V_{in}} = A_{cl} \cdot \frac{1}{1 + s/\omega_{p,cl}}$$

$$A_o \beta \gg 1$$

$$\omega_{p,cl} = \omega_1 (1 + \beta A_o) \approx \omega_1 A_o \beta$$

$$A_{cl} \approx \frac{1}{\beta}$$


$$A_{cl} \times \omega_{p,cl} = \omega_1 A_o \cancel{\beta} \cdot \frac{1}{\cancel{\beta}} = \omega_1 A_o = \omega_{un}$$


$A_{cl} \times \omega_{p,cl} = \omega_{un}$

← Unity-gain frequency

↙ Closed loop gain ↘ closed loop 3dB Bandwidth

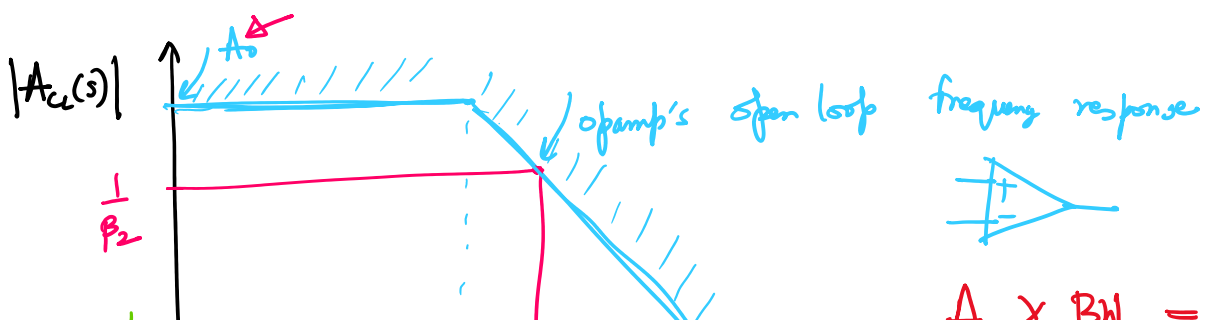This relation holds for all $0 \leq \beta \leq 1$




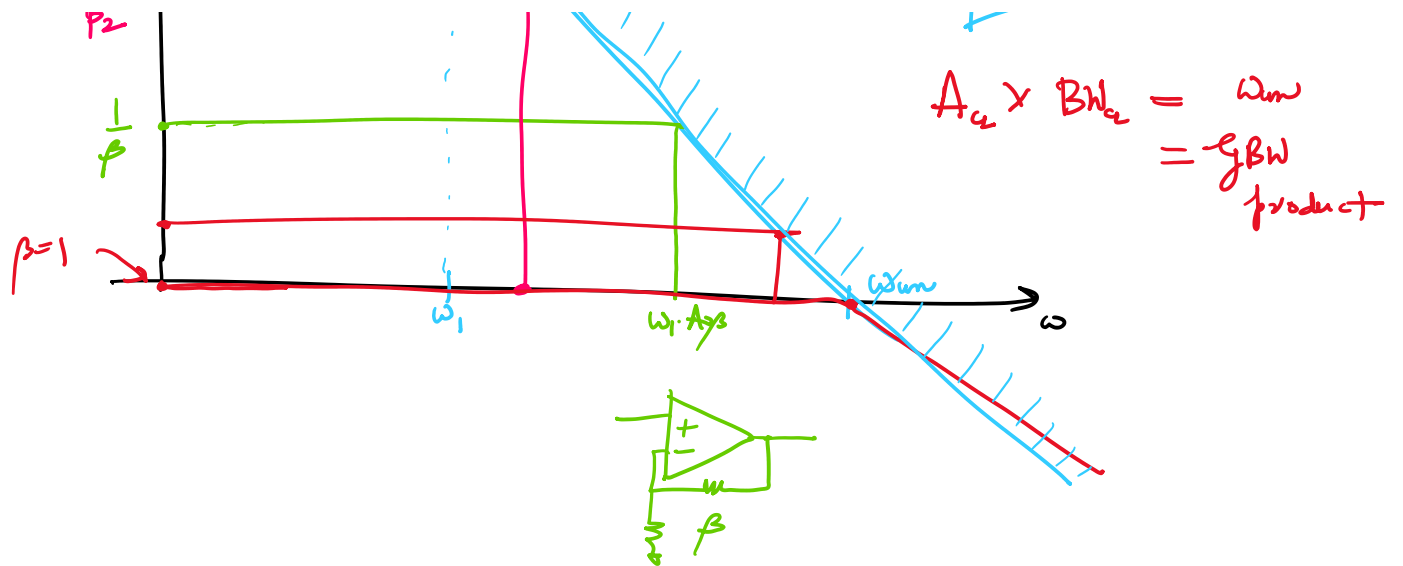

$G_{BW} = 10^6 \rightarrow 10^7$

$\begin{cases} A_u = 10 \\ BW_u = 100 \text{ kHz} \end{cases} \rightarrow 1 \text{ MHz}$

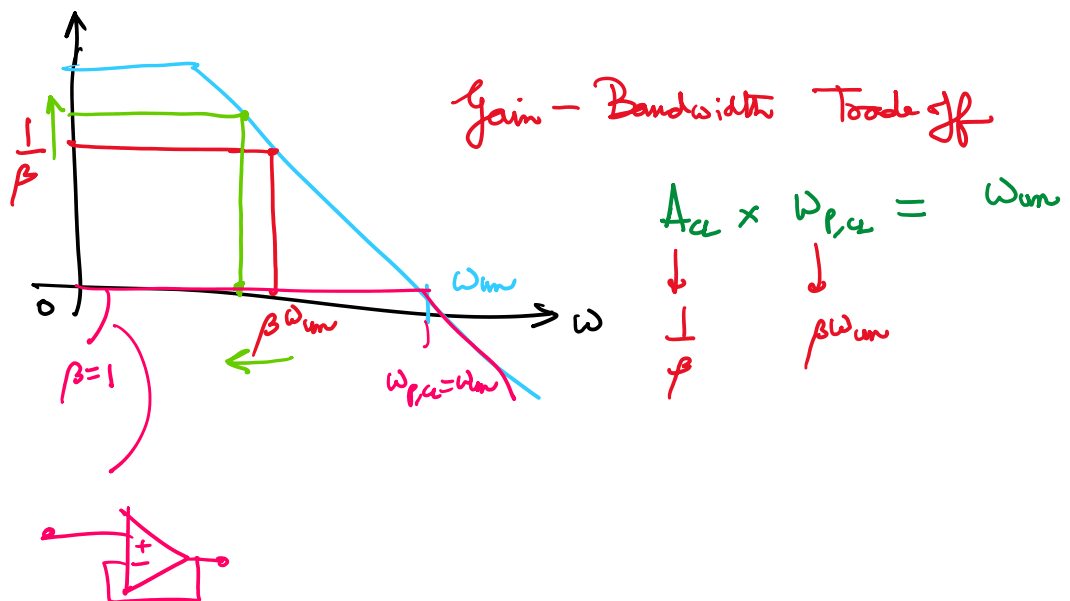If need higher gain $\times$ BW
 $\Rightarrow$ go for higher
 G_{BW} product stamp.



* Stability of stamp circuit is an
 important concern. (chapter 12)
 Read After the
 semester is over.

