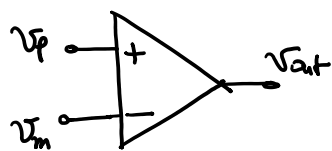



EECE 310 - Lecture 38

Wednesday, May 2, 2018 10:32 AM




$$A(s) = \frac{v_{out}}{v_p - v_m}(s) = \frac{A_o}{1 + s/\omega_1}$$

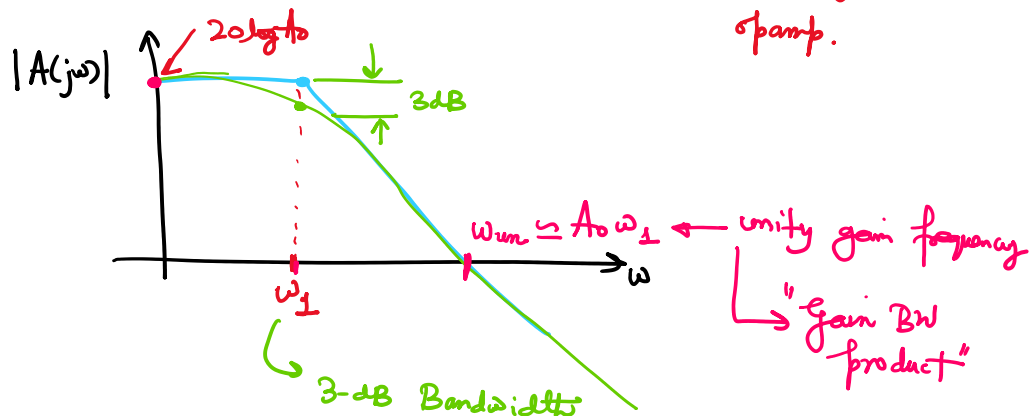A_o DC gain
 ω_1 3-dB pole modeling bandwidth limitation of the opamp.



Non-inverting amplifier

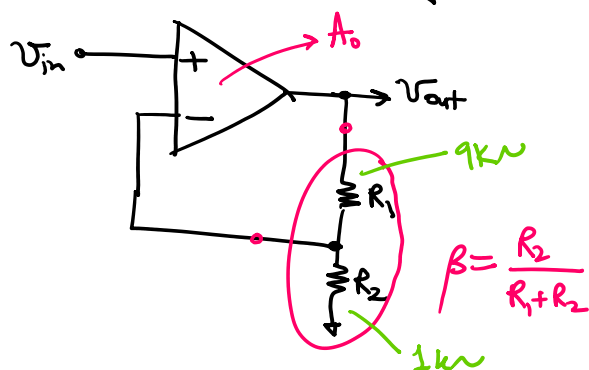

Design an amplifier with gain=10

$$\text{Ideal closed-loop gain} = \frac{1}{\beta} = \frac{R_1 + R_2}{R_2} = 1 + \frac{R_1}{R_2}$$

R_1 9k
 R_2 1k

* Gain (precision) error $< 1\%$

$$\text{closed-loop gain} \Rightarrow A_{cl} = \underbrace{\left(\frac{1}{\beta} \right)}_{\text{Ideal}} \underbrace{\left(1 - \frac{1}{A_o \beta} \right)}_{\text{error term}}$$

ϵ

$$\epsilon < 0.01$$

$$\frac{1}{A_0 \beta} < 10^{-2}$$

$$\Rightarrow A_0 > \frac{1}{10^{-2} \cdot \beta} = 10^3$$

We need opamp's DC gain, $A_0 > 10^3$

$$20 \log_{10}(10^3) = 60 \text{ dB}$$

* How about for 0.01% Error?

$$\epsilon = 10^{-4}$$

$$A_0 > \frac{1}{10^{-4} \cdot \beta} = 10^5 \Rightarrow 100 \text{ dB}$$

$$A(s) = \frac{A_0}{1 + s/\omega_1}$$


Amplifier with gain=10 and 10% error

Closed-loop bandwidth = 100 kHz

$$\frac{V_{out}(s)}{V_{in}} = A_{cl} \cdot \frac{1}{1 + \frac{s}{\omega_1(1+A_0\beta)}}$$

$$\downarrow$$
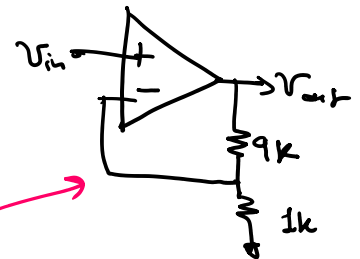
$$\frac{1}{\beta} \left(1 - \frac{1}{A_0\beta}\right)$$



3-dB BW for the amplifier
'NOT for the opamp'

Closed-loop BW of the amplifier = $\omega_1(1+A_0\beta) \approx \omega_1 A_0 \beta$

$$\omega_{p,cl} = \omega_1 A_0 \beta \leftarrow \frac{1}{10}$$

$$\leftarrow \frac{1}{10^3}$$

$2\pi \times 100 \text{ kHz}$

$$\swarrow$$

$$2\pi \times 100 \text{ kHz}$$

$$\rightarrow 10^5$$

$$\Rightarrow 2\pi \times 100 \text{ kHz} = \omega_1 \cdot 10^2$$


$$\Rightarrow \omega_1 = 2\pi \cdot \frac{10^5}{10^2} = 2\pi \cdot 10^3$$

$$\rightarrow f_1 = \underline{1 \text{ kHz}}$$

$$\omega_{un} = \omega_1 \times A_0 = 2\pi \cdot 10^3 \cdot 10^2$$

$$= 2\pi \times 1 \text{ MHz}$$
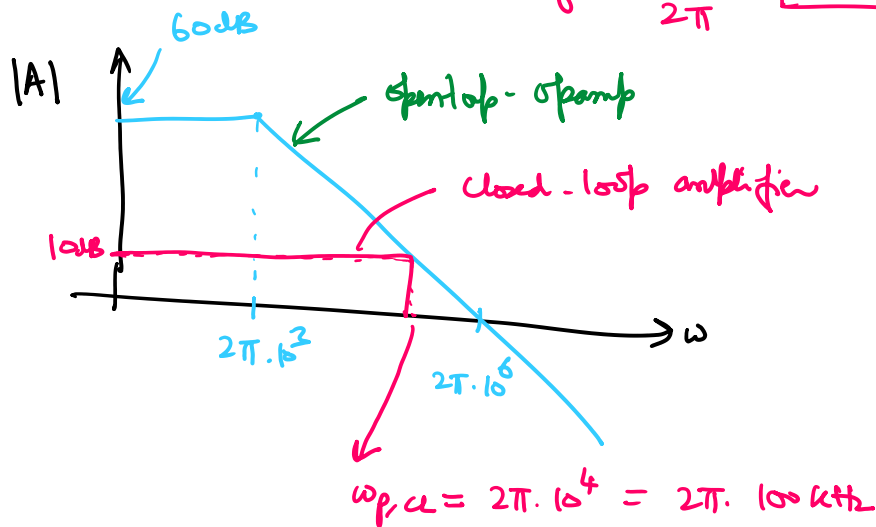
$$f_{un} = \frac{\omega_{un}}{2\pi} = \boxed{1 \text{ MHz}}$$






Recap

$$\text{Finite DC gain} \Rightarrow \frac{1}{\beta} \cdot \left(1 - \frac{1}{A_0 \beta}\right)$$

$$\text{Closed-loop BW} \Rightarrow \beta \omega_{un} = \beta \cdot (A_0 \omega_1)$$

DC offset

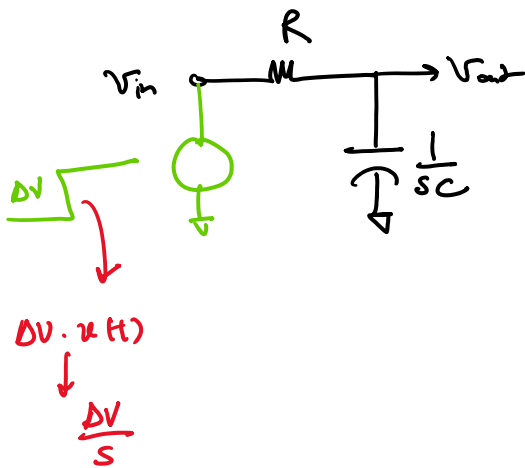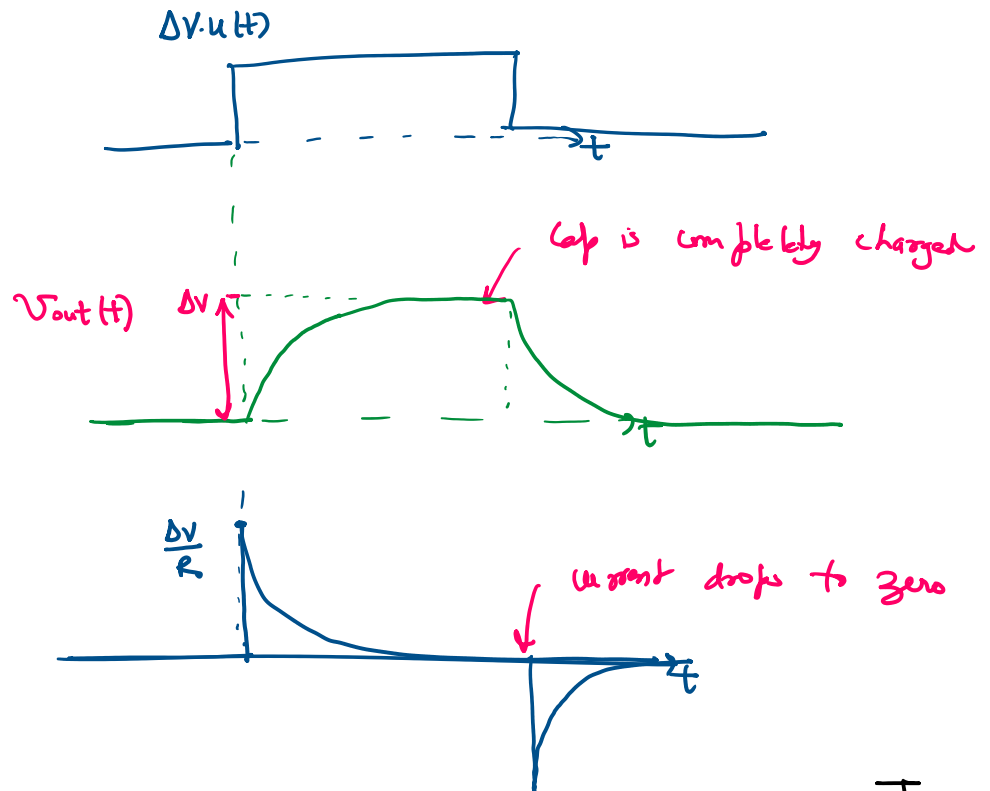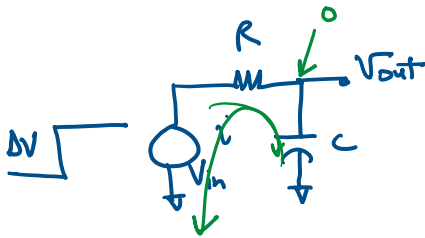

$$\frac{V_{out}(s)}{V_{in}} = \frac{1/sC}{R + 1/sC} = \frac{1}{1 + sRC} = \frac{1}{1 + s/\omega_p}$$

Time constant $\tau = RC$
 $\omega_p = \frac{1}{\tau}$

$$V_{out}(s) = \frac{1}{(1 + s/\omega_p)} \cdot \frac{\Delta V}{s} = \frac{\Delta V}{s(1 + s/\omega_p)} = \Delta V \left[\frac{A}{s} + \frac{B}{1 + s/\omega_p} \right]$$

$$= \Delta V \left[\frac{A + \frac{As}{\omega_p} + Bs}{s(1 + s/\omega_p)} \right]$$

$\downarrow$
 $V_{out}(t)$

$$\Rightarrow A + \left(\frac{A}{\omega_p} + B \right) s = 1$$

$$\Rightarrow A=1$$

$$\leftarrow B = -\frac{A}{\omega_p} = -\frac{1}{\omega_p}$$


$$V_{out}(s) = \Delta V \cdot \left[\frac{1}{s} - \frac{1}{s + \omega_p} \right]$$


$$V_{out}(t) = \Delta V \cdot \left[u(t) - e^{-\omega_p t} u(t) \right]$$

$$= \boxed{\Delta V [1 - e^{-\omega_p t}] u(t)}$$

$$= \Delta V [1 - e^{-t/\tau}] u(t)$$


RC charging/discharge waveform.

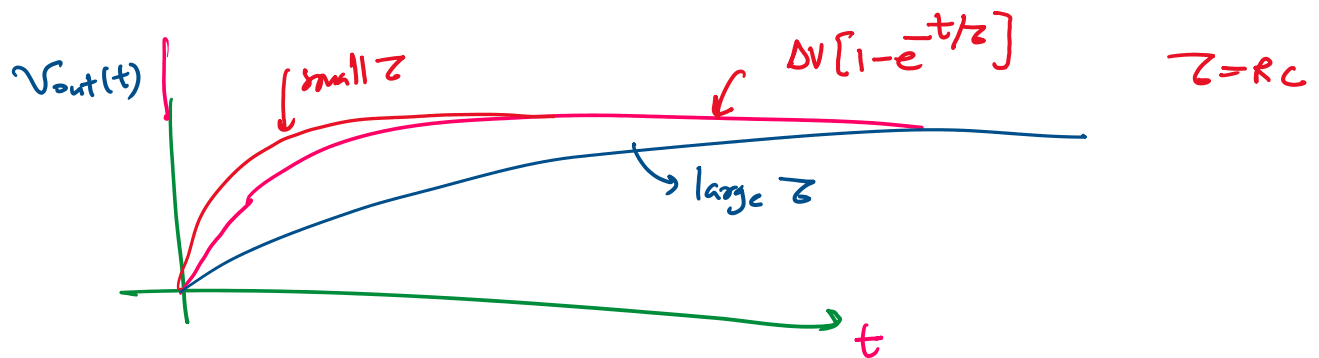

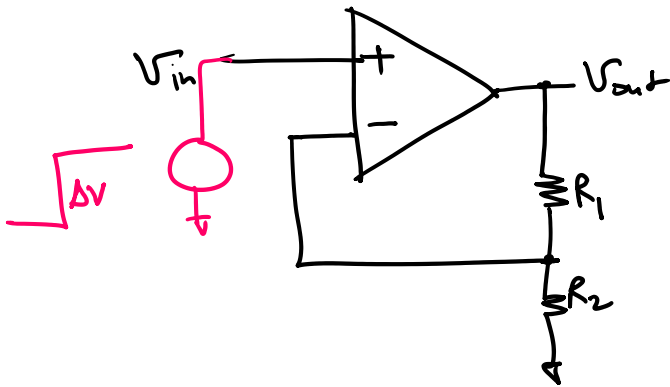

$$\frac{V_{out}}{V_{in}}(s) = \frac{1}{\beta} \cdot \frac{1}{\left(1 + \frac{s}{\beta \omega_{un}}\right)}$$

3-dB BW

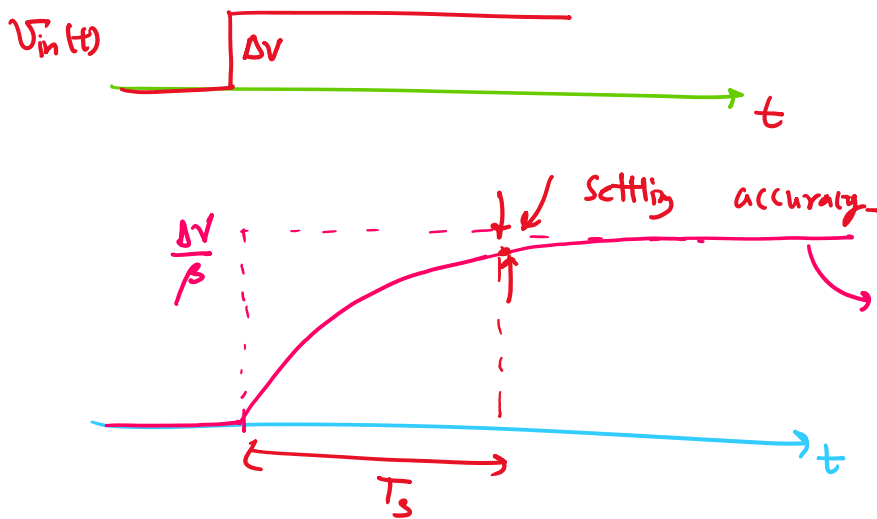

$$\frac{\Delta V}{\beta} \cdot [1 - e^{-t/\tau}] u(t)$$

$$\tau = \frac{1}{\omega_{p,c}} = \frac{1}{\beta \omega_{un}}$$

Small $\tau \Rightarrow$ large $\omega_{p,c}$
 $\Rightarrow$ large $\beta \omega_{un}$

$$V_{out}(t) = \frac{\Delta V}{\beta} \left[1 - e^{-2T/\beta f_{unt}} \right] u(t)$$

$$V_{out}(t) = \frac{A_V}{\beta} \left[1 - e^{-t/\tau_{funt}} \right] u(t)$$

large ω_p, u for faster settling.