



See [Sample Final Exam Classwork](#)

PDF posted on BBLearn for today's notes on the Sample Final Exam.

$$V_{cc} \cdot \frac{R_2}{R_1 + R_2} = \frac{I_E \cdot (R_1 || R_2)}{\beta} + 0.7V + I_E \cdot R_E$$

Solve for I_E