
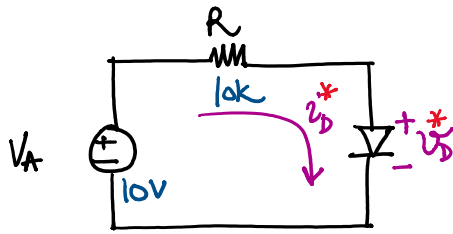


ECE 310 - Lecture 9

Wednesday, January 31, 2018 10:33 AM

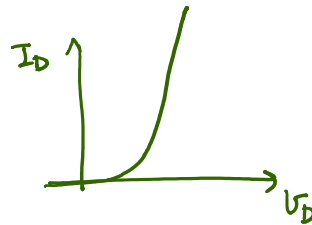

find i_D & v_D




Emission Coefficient
 $n=1$

$$i_D = I_S \left(e^{\frac{v_D}{nV_T}} - 1 \right) \rightarrow \textcircled{1}$$

KVL: $V_A = i_D R + v_D \rightarrow \textcircled{2}$


Load-line Analysis:

$$i_D = \frac{V_A - v_D}{R} = f(v_D)$$

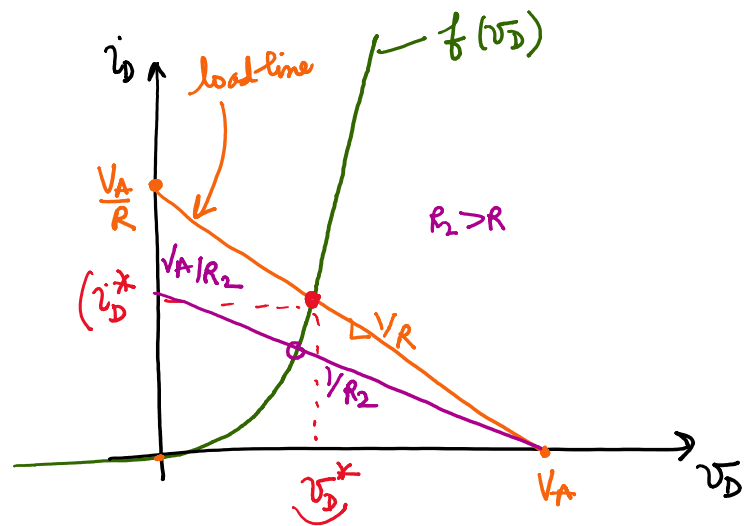

Constant Voltage Model

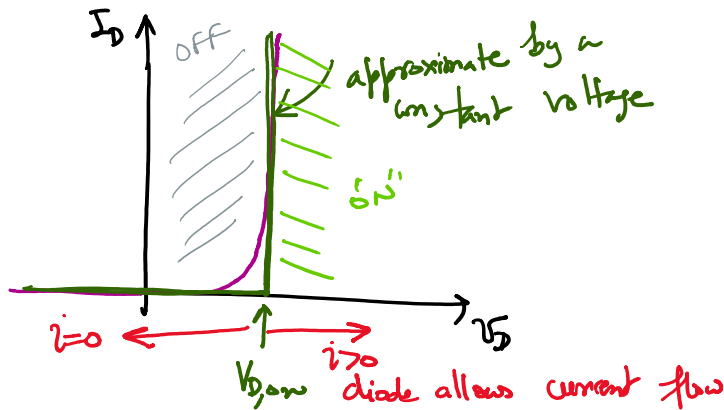
nonlinear I-V curve analysis is not straightforward.




Can approximate the fwd bias region by a constant $V_{D,on}$

→ Book uses 800mV or 0.8V


Reverse Bias

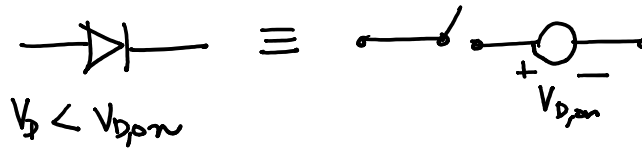


forward Bias

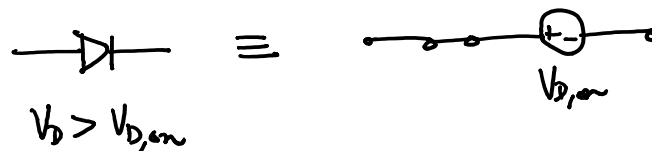

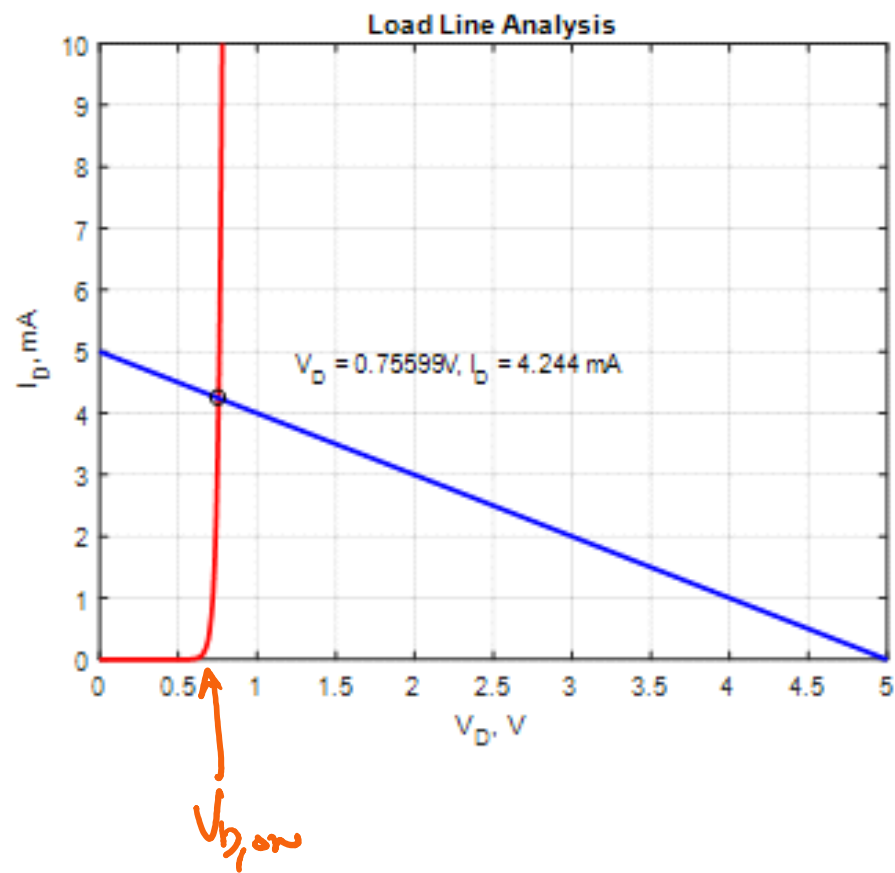The diode is turned on when the fwd bias voltage is $V_D > V_{D,on}$
 → 0.8V



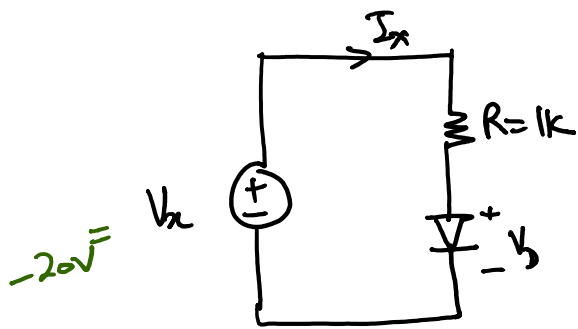

$$\because i_x = 0$$

$$V_x = V_D + I_x R$$

$$V_x = 3V \text{ \& } V_x = 0.5V$$

"ON"

a) $V_x = 3V$

$$V_D = V_{D,on} = 0.8V$$

$$\Rightarrow I_x = \frac{V_x - V_{D,on}}{R} = 2.2mA$$

'OFF'

b)

$$V_x = 0.5V$$

$$I_x \approx 0$$

$$V_D = 0.5V$$



Reverse Recovery of a Diode:

