



CMOS Inverter

Vishal Saxena
ECE, Boise State University


Oct 21, 2010



Inverter Operation Regions



Region	NMOS	PMOS
A	Cutoff	Triode
B	Saturation	Triode
C	Saturation	Saturation
D	Triode	Saturation
E	Triode	Cutoff

 




Noise Margin



 - How much noise can a gate input see before it does not recognise the output?
 - Noise margins of a digital gate indicate how well it will perform with noisy conditions





Noise Margin



- $NM_H = V_{IH} - V_{OH}$
 - **HIGH** noise margin

- $NM_L = V_{IL} - V_{OL}$

- **LOW** noise margin

- V_{IH} = minimum **HIGH** input voltage

- V_{IL} = maximum **LOW** input voltage

- V_{OH} = minimum **HIGH** output voltage

- V_{OL} = maximum **LOW** output voltage



Noise Margin



- $NM_H = V_{IH} - V_{OH}$
 - **HIGH** noise margin
- $NM_L = V_{IL} - V_{OL}$
 - **LOW** noise margin
 - V_{IH} = minimum **HIGH** input voltage
 - V_{IL} = maximum **LOW** input voltage
 - V_{OH} = minimum **HIGH** output voltage
 - V_{OL} = maximum **LOW** output voltage



Noise Margin



- $NM_H = V_{IH} - V_{OH}$
 - **HIGH** noise margin
- $NM_L = V_{IL} - V_{OL}$
 - **LOW** noise margin
 - V_{IH} = minimum **HIGH** input voltage
 - V_{IL} = maximum **LOW** input voltage
 - V_{OH} = minimum **HIGH** output voltage
 - V_{OL} = maximum **LOW** output voltage



Noise Margin



- $NM_H = V_{IH} - V_{OH}$
 - HIGH noise margin
- $NM_L = V_{IL} - V_{OL}$
 - LOW noise margin
 - V_{IH} = minimum HIGH input voltage
 - V_{IL} = maximum LOW input voltage
 - V_{OH} = minimum HIGH output voltage
 - V_{OL} = maximum LOW output voltage



Noise Margin



- $NM_H = V_{IH} - V_{OH}$
 - HIGH noise margin
- $NM_L = V_{IL} - V_{OL}$
 - LOW noise margin
 - V_{IH} = minimum HIGH input voltage
 - V_{IL} = maximum LOW input voltage
 - V_{OH} = minimum HIGH output voltage
 - V_{OL} = maximum LOW output voltage



Noise Margin




- $NM_H = V_{IH} - V_{OH}$
 - **HIGH** noise margin
- $NM_L = V_{IL} - V_{OL}$
 - **LOW** noise margin
 - V_{IH} = minimum **HIGH** input voltage
 - V_{IL} = maximum **LOW** input voltage
 - V_{OH} = minimum **HIGH** output voltage
 - V_{OL} = maximum **LOW** output voltage



Logic Levels



 - To maximize noise margins, select logic levels at
 - unity gain point of DC transfer characteristics






Logic Levels



 - To maximize noise margins, select logic levels at
 - unity gain point of DC transfer characteristics






Logic Levels



 - To maximize noise margins, select logic levels at
 - unity gain point of DC transfer characteristics
 - gate should be able to regenerate the levels






Logic Levels



 - To maximize noise margins, select logic levels at
 - unity gain point of DC transfer characteristics
 - gate should be able to **regenerate** the levels






Logic Levels



 - To maximize noise margins, select logic levels at
 - unity gain point of DC transfer characteristics
 - gate should be able to **regenerate** the levels





- If $\frac{\beta_n}{\beta_p} \neq 1$, inverter's switching point (V_{SP}) will move from the ideal value of $\frac{V_{DD}}{2}$
 - called **skewed** gate

