



# CMOS Inverter

## Additional Slides


Vishal Saxena  
ECE, Boise State University

Oct 21, 2010

# Inverter Operation Regions




Region	NMOS	PMOS
A	Cutoff	Triode
B	Saturation	Triode
C	Saturation	Saturation
D	Triode	Saturation
E	Triode	Cutoff

 
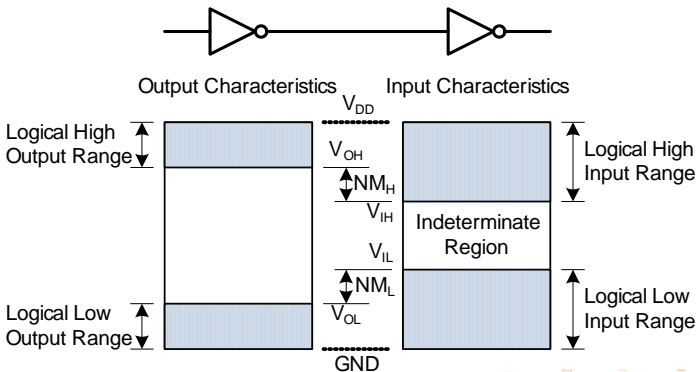
# Noise Margin




- How much noise can a gate input see before it does not recognize the output?
  - Noise margins of a digital gate indicate how well it will perform with noisy input


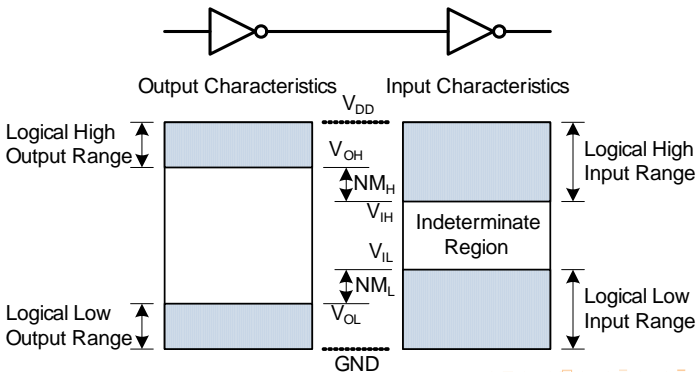
# Noise Margin



- How much noise can a gate input see before it does not recognize the output?
  - Noise margins of a digital gate indicate how well it will perform with noisy input





- $NM_H = V_{IH} - V_{OH}$ 
  - **HIGH** noise margin
- $NM_L = V_{IL} - V_{OL}$ 
  - **LOW** noise margin
- $V_{IH}$  = minimum **HIGH** input voltage
- $V_{IL}$  = maximum **LOW** input voltage
- $V_{OH}$  = minimum **HIGH** output voltage
- $V_{OL}$  = maximum **LOW** output voltage

# Noise Margin



- $NM_H = V_{IH} - V_{OH}$ 
  - HIGH noise margin
- $NM_L = V_{IL} - V_{OL}$ 
  - LOW noise margin
- $V_{IH}$  = minimum HIGH input voltage
- $V_{IL}$  = maximum LOW input voltage
- $V_{OH}$  = minimum HIGH output voltage
- $V_{OL}$  = maximum LOW output voltage

# Noise Margin



- $NM_H = V_{IH} - V_{OH}$ 
  - HIGH noise margin
- $NM_L = V_{IL} - V_{OL}$ 
  - LOW noise margin
- $V_{IH}$  = minimum HIGH input voltage
- $V_{IL}$  = maximum LOW input voltage
- $V_{OH}$  = minimum HIGH output voltage
- $V_{OL}$  = maximum LOW output voltage

# Noise Margin



- $NM_H = V_{IH} - V_{OH}$ 
  - HIGH noise margin
- $NM_L = V_{IL} - V_{OL}$ 
  - LOW noise margin
- $V_{IH}$  = minimum HIGH input voltage
- $V_{IL}$  = maximum LOW input voltage
- $V_{OH}$  = minimum HIGH output voltage
- $V_{OL}$  = maximum LOW output voltage



# Noise Margin



- $NM_H = V_{IH} - V_{OH}$ 
  - HIGH noise margin
- $NM_L = V_{IL} - V_{OL}$ 
  - LOW noise margin
- $V_{IH}$  = minimum HIGH input voltage
- $V_{IL}$  = maximum LOW input voltage
- $V_{OH}$  = minimum HIGH output voltage
- $V_{OL}$  = maximum LOW output voltage

 
# Noise Margin



- $NM_H = V_{IH} - V_{OH}$ 
  - HIGH noise margin
- $NM_L = V_{IL} - V_{OL}$ 
  - LOW noise margin
- $V_{IH}$  = minimum HIGH input voltage
- $V_{IL}$  = maximum LOW input voltage
- $V_{OH}$  = minimum HIGH output voltage
- $V_{OL}$  = maximum LOW output voltage




- To maximize noise margins, select logic levels at
  - unity gain point of DC transfer characteristics





 
- To maximize noise margins, select logic levels at
  - unity gain point of DC transfer characteristics


 
# Logic Levels




- To maximize noise margins, select logic levels at
  - unity gain point of DC transfer characteristics
  - regenerate the logic levels (gain > 1)


 
# Logic Levels




- To maximize noise margins, select logic levels at
  - unity gain point of DC transfer characteristics
  - regenerate the logic levels (gain > 1)


 
# Logic Levels




- To maximize noise margins, select logic levels at
  - unity gain point of DC transfer characteristics
  - regenerate the logic levels (gain > 1)


 
# Beta-Ratio



- If  $\frac{\beta_n}{\beta_p} \neq 1$ , inverter's switching point ( $V_{SP}$ ) will move from the ideal value of  $\frac{V_{DD}}{2}$ 
  - called **skewed** gate






  
# Inverter Layout





- Two styles for laying out an inverter
- Power and ground routed on metal-1 using standard frame


  
# Inverter Layout




- Two styles for laying out an inverter
- Power and ground routed on metal-1 using standard frame



 
# Latch-up



- Fast voltage pulses can feed-through the C1 or C2 and turn on the parasitic BJT
- If any of the BJT is turned on, it creates a positive feedback loop
  - eventually both the BJTs are turned fully on and the circuit is stuck in that state (undesired)



 Cross-sectional view of an inverter showing parasitic bipolar transistors and resistors




Schematic for understanding latch-up

 
# Latch-up



- Fast voltage pulses can feed-through the C1 or C2 and turn on the parasitic BJT
- If any of the BJT is turned on, it creates a positive feedback loop
  - eventually both the BJTs are turned fully on and the circuit is stuck in that state (undesired)



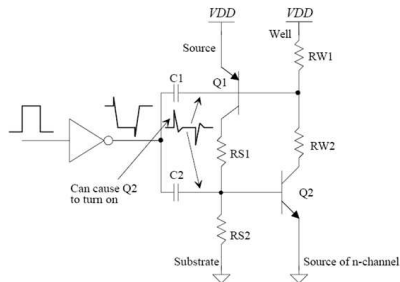Cross-sectional view of an inverter showing parasitic bipolar transistors and resistors




Schematic for understanding latch-up

 
# Latch-up



- Fast voltage pulses can feed-through the C1 or C2 and turn on the parasitic BJT
- If any of the BJT is turned on, it creates a positive feedback loop
  - eventually both the BJTs are turned fully on and the circuit is stuck in that state (undesired)



 Cross-sectional view of an inverter showing parasitic bipolar transistors and resistors




Schematic for understanding latch-up

 
# Latch-up prevention



- Reduce the well series resistances ( $R_{W1}$  and  $R_{W2}$ ) by using as many contacts as possible and closer to the inverter
  - can also use guard ring structures
- Use slow rise and fall times in the logic
- Reduce drain areas to reduce  $C1$  and  $C2$



 Cross-sectional view of an inverter showing parasitic bipolar transistors and resistors




Schematic for understanding latch-up

 
# Latch-up prevention



- Reduce the well series resistances ( $RW1$  and  $RW2$ ) by using as many contacts as possible and closer to the inverter
  - can also use guard ring structures
- Use slow rise and fall times in the logic
- Reduce drain areas to reduce  $C1$  and  $C2$



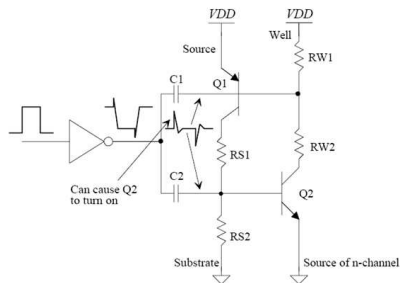Cross-sectional view of an inverter showing parasitic bipolar transistors and resistors




Schematic for understanding latch-up

 
# Latch-up prevention



- Reduce the well series resistances ( $RW1$  and  $RW2$ ) by using as many contacts as possible and closer to the inverter
  - can also use guard ring structures
- Use slow rise and fall times in the logic
- Reduce drain areas to reduce  $C1$  and  $C2$



 Cross-sectional view of an inverter showing parasitic bipolar transistors and resistors




Schematic for understanding latch-up



 
# Latch-up prevention



- Reduce the well series resistances ( $RW1$  and  $RW2$ ) by using as many contacts as possible and closer to the inverter
  - can also use guard ring structures
- Use slow rise and fall times in the logic
- Reduce drain areas to reduce  $C1$  and  $C2$



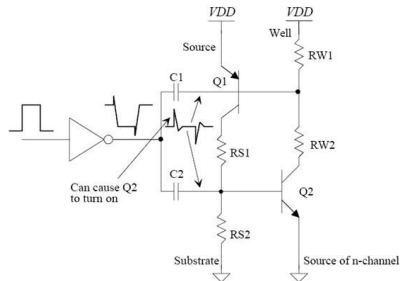Cross-sectional view of an inverter showing parasitic bipolar transistors and resistors



Schematic for understanding latch-up

# Normalized Inverter Delay



- In nm-CMOS, assuming that for equal drive strengths  $W_p = 2W_n$ 
  - effective switching resistance of PMOS & NMOS =  $R$
  - in MOSFETs switching model assume that  $C_{in} = C_{out} = C$
- Propagation delay ( $d$ ) =  
 $t_{pLH} = t_{pHL} = 0.7 \times R(C_{outp} + C_{outn}) \triangleq 0.7 \times 3RC$ 
  - $\Rightarrow \tau = 3RC$
- Can express delay in a process-independent unit
  - $d = d_{abs}/0.7\tau$
  - $d = 1$  for an inverter with no load

# Normalized Inverter Delay



- In nm-CMOS, assuming that for equal drive strengths  $W_p = 2W_n$ 
  - effective switching resistance of PMOS & NMOS =  $R$
  - in MOSFETs swicthing model assume that  $C_{in} = C_{out} = C$
- Propgataion delay ( $d$ ) =
 
$$t_{pLH} = t_{pHL} = 0.7 \times R(C_{outp} + C_{outn}) \triangleq 0.7 \times 3RC$$
  - $\Rightarrow \tau = 3RC$
- Can express delay in a process-independent unit
  - $d = d_{abs}/0.7\tau$
  - $d = 1$  for an inverter with no load

# Normalized Inverter Delay



- In nm-CMOS, assuming that for equal drive strengths  $W_p = 2W_n$ 
  - effective switching resistance of PMOS & NMOS =  $R$
  - in MOSFETs switching model assume that  $C_{in} = C_{out} = C$
- Propagation delay ( $d$ ) =
 
$$t_{pLH} = t_{pHL} = 0.7 \times R(C_{outp} + C_{outn}) \triangleq 0.7 \times 3RC$$
  - $\Rightarrow \tau = 3RC$
- Can express delay in a process-independent unit
  - $d = d_{abs}/0.7\tau$
  - $d = 1$  for an inverter with no load

# Normalized Inverter Delay



- In nm-CMOS, assuming that for equal drive strengths  $W_p = 2W_n$ 
  - effective switching resistance of PMOS & NMOS =  $R$
  - in MOSFETs switching model assume that  $C_{in} = C_{out} = C$
- Propagation delay ( $d$ ) =
 
$$t_{pLH} = t_{pHL} = 0.7 \times R(C_{outp} + C_{outn}) \triangleq 0.7 \times 3RC$$
  - $\Rightarrow \tau = 3RC$
- Can express delay in a process-independent unit
  - $d = d_{abs}/0.7\tau$
  - $d = 1$  for an inverter with no load

# Normalized Inverter Delay



- In nm-CMOS, assuming that for equal drive strengths  $W_p = 2W_n$ 
  - effective switching resistance of PMOS & NMOS =  $R$
  - in MOSFETs switching model assume that  $C_{in} = C_{out} = C$
- Propagation delay ( $d$ ) =
 
$$t_{pLH} = t_{pHL} = 0.7 \times R(C_{outp} + C_{outn}) \triangleq 0.7 \times 3RC$$
  - $\Rightarrow \tau = 3RC$
- Can express delay in a process-independent unit
  - $d = d_{abs}/0.7\tau$
  - $d = 1$  for an inverter with no load

# Delay in a Logic Gate



- Can express delay in a process-independent unit
  - $d = d_{abs}/\tau$        $\tau = 0.7 \times R(C_{outp} + C_{outn}) \triangleq 0.7 \times 3RC$
- Delay has two components:  $d = f + p$ 
  - $f$ : effort delay  $= g \cdot h$  (a.k.a. stage effort)
  - $g$ : logical effort
  - $h$ : electrical effort  $= C_{out}/C_{in}$
  - $p$ : parasitic delay

# Delay in a Logic Gate



- Can express delay in a process-independent unit
  - $d = d_{abs}/\tau$        $\tau = 0.7 \times R(C_{outp} + C_{outn}) \triangleq 0.7 \times 3RC$
- Delay has two components:  $d = f + p$ 
  - f: effort delay =  $g \cdot h$  (a.k.a. stage effort)
    - again has two components:
  - g: logical effort
    - measures relative ability of gate to deliver current
    - $g=1$  for inverter (baseline circuit)
  - h: electrical effort =  $C_{out}/C_{in}$ 
    - ratio of output to input capacitance
    - sometimes called fanout
  - p: parasitic delay
    - represents delay of gate driving no load
    - set by internal parasitic capacitance



# Delay in a Logic Gate



- Can express delay in a process-independent unit

- $d = d_{abs}/\tau$        $\tau = 0.7 \times R(C_{outp} + C_{outn}) \triangleq 0.7 \times 3RC$

- Delay has two components:  $d = f + p$

- $f$ : effort delay  $= g \cdot h$  (a.k.a. stage effort)

- again has two components:

- $g$ : logical effort

- measures relative ability of gate to deliver current

- $g=1$  for inverter (baseline circuit)

- $h$ : electrical effort  $= C_{out}/C_{in}$

- ratio of output to input capacitance

- sometimes called fanout

- $p$ : parasitic delay

- represents delay of gate driving no load

- set by internal parasitic capacitance

# Delay in a Logic Gate



- Can express delay in a process-independent unit
  - $d = d_{abs}/\tau$        $\tau = 0.7 \times R(C_{outp} + C_{outn}) \triangleq 0.7 \times 3RC$
- Delay has two components:  $d = f + p$ 
  - $f$ : effort delay  $= g \cdot h$  (a.k.a. stage effort)
    - again has two components:
      - $g$ : logical effort
        - measures relative ability of gate to deliver current
        - $g=1$  for inverter (baseline circuit)
      - $h$ : electrical effort  $= C_{out}/C_{in}$ 
        - ratio of output to input capacitance
        - sometimes called fanout
    - $p$ : parasitic delay
      - represents delay of gate driving no load
      - set by internal parasitic capacitance

# Delay in a Logic Gate



- Can express delay in a process-independent unit
  - $d = d_{abs}/\tau$        $\tau = 0.7 \times R(C_{outp} + C_{outn}) \triangleq 0.7 \times 3RC$
- Delay has two components:  $d = f + p$ 
  - $f$ : effort delay  $= g \cdot h$  (a.k.a. stage effort)
    - again has two components:
  - $g$ : logical effort
    - measures relative ability of gate to deliver current
    - $g=1$  for inverter (baseline circuit)
  - $h$ : electrical effort  $= C_{out}/C_{in}$ 
    - ratio of output to input capacitance
    - sometimes called fanout
  - $p$ : parasitic delay
    - represents delay of gate driving no load
    - set by internal parasitic capacitance

# Delay in a Logic Gate



- Can express delay in a process-independent unit
  - $d = d_{abs}/\tau$        $\tau = 0.7 \times R(C_{outp} + C_{outn}) \triangleq 0.7 \times 3RC$
- Delay has two components:  $d = f + p$ 
  - $f$ : effort delay  $= g \cdot h$  (a.k.a. stage effort)
    - again has two components:
  - $g$ : logical effort
    - measures relative ability of gate to deliver current
    - $g=1$  for inverter (baseline circuit)
  - $h$ : electrical effort  $= C_{out}/C_{in}$ 
    - ratio of output to input capacitance
    - sometimes called fanout
  - $p$ : parasitic delay
    - represents delay of gate driving no load
    - set by internal parasitic capacitance

# Delay in a Logic Gate



- Can express delay in a process-independent unit
  - $d = d_{abs}/\tau$        $\tau = 0.7 \times R(C_{outp} + C_{outn}) \triangleq 0.7 \times 3RC$
- Delay has two components:  $d = f + p$ 
  - $f$ : effort delay  $= g \cdot h$  (a.k.a. stage effort)
    - again has two components:
  - $g$ : logical effort
    - measures relative ability of gate to deliver current
    - $g=1$  for inverter (baseline circuit)
  - $h$ : electrical effort  $= C_{out}/C_{in}$ 
    - ratio of output to input capacitance
    - sometimes called fanout
  - $p$ : parasitic delay
    - represents delay of gate driving no load
    - set by internal parasitic capacitance



# Delay in a Logic Gate




- Can express delay in a process-independent unit
  - $d = d_{abs}/\tau$        $\tau = 0.7 \times R(C_{outp} + C_{outn}) \triangleq 0.7 \times 3RC$
- Delay has two components:  $d = f + p$ 
  - $f$ : effort delay  $= g \cdot h$  (a.k.a. stage effort)
    - again has two components:
  - $g$ : logical effort
    - measures relative ability of gate to deliver current
    - $g=1$  for inverter (baseline circuit)
  - $h$ : electrical effort  $= C_{out}/C_{in}$ 
    - ratio of output to input capacitance
    - sometimes called fanout
  - $p$ : parasitic delay
    - represents delay of gate driving no load
    - set by internal parasitic capacitance

# Delay Plots



■ Delay:  $d = f + p$

■  $= gh + p$

 


Note: In these slides it is assumed that the MOSFET capacitance model is  $C_{in} = C_{out} = C$ , and that  $W_p = 2W_n$  for equal drive strengths for the PMOS and NMOS in the inverter.

# Delay Plots



- Delay:  $d = f + p$
- $= gh + p$

 


Note: In these slides it is assumed that the MOSFET capacitance model is  $C_{in} = C_{out} = C$ , and that  $W_p = 2W_n$  for equal drive strengths for the PMOS and NMOS in the inverter.


 
# Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter




- Logical Effort:  $g = 1$
- Electrical Effort:  $h = 4$
- Parasitic Delay:  $p = 1$
- Stage Delay:  $d = 5$
- The FO4 delay is about 300 ps in 0.5  $\mu\text{m}$  process 15 ps in a 65 nm process
 
# Example: FO4 Inverter



- Estimate the delay of a fanout-of-4 (FO4) inverter




- Logical Effort:  $g = 1$
- Electrical Effort:  $h = 4$
- Parasitic Delay:  $p = 1$
- Stage Delay:  $d = 5$
- The FO4 delay is about 300 ps in 0.5  $\mu\text{m}$  process 15 ps in a 65 nm process


 
# Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter




- Logical Effort:  $g = 1$
- Electrical Effort:  $h = 4$
- Parasitic Delay:  $p = 1$
- Stage Delay:  $d = 5$
- The FO4 delay is about 300 ps in 0.5  $\mu\text{m}$  process 15 ps in a 65 nm process
 
# Example: FO4 Inverter



- Estimate the delay of a fanout-of-4 (FO4) inverter




- Logical Effort:  $g = 1$
- Electrical Effort:  $h = 4$
- Parasitic Delay:  $p = 1$
- Stage Delay:  $d = 5$
- The FO4 delay is about 300 ps in 0.5  $\mu\text{m}$  process 15 ps in a 65 nm process
 
# Example: FO4 Inverter



- Estimate the delay of a fanout-of-4 (FO4) inverter




- Logical Effort:  $g = 1$
- Electrical Effort:  $h = 4$
- Parasitic Delay:  $p = 1$
- Stage Delay:  $d = 5$
- The FO4 delay is about 300 ps in 0.5  $\mu\text{m}$  process 15 ps in a 65 nm process


 
# Example: FO4 Inverter



- Estimate the delay of a fanout-of-4 (FO4) inverter




- Logical Effort:  $g = 1$
- Electrical Effort:  $h = 4$
- Parasitic Delay:  $p = 1$
- Stage Delay:  $d = 5$
- The FO4 delay is about 300 ps in 0.5  $\mu\text{m}$  process 15 ps in a 65 nm process
 
## Multistage Logic Circuits




- Logical effort generalizes to multistage networks
- Path Logical Effort  $G = \prod g_i$
- Path Electrical Effort  $H = \frac{C_{out-path}}{C_{in-path}}$
- Path Effort  $F = \prod f_i = \prod g_i h_i$
- For a single path (no branching):  $F = G \cdot H$


 
# Multistage Logic Circuits




- Logical effort generalizes to multistage networks
- Path Logical Effort  $G = \prod g_i$
- Path Electrical Effort  $H = \frac{C_{out-path}}{C_{in-path}}$
- Path Effort  $F = \prod f_i = \prod g_i h_i$
- For a single path (no branching):  $F = G \cdot H$


 
# Multistage Logic Circuits




- Logical effort generalizes to multistage networks
- Path Logical Effort  $G = \prod g_i$
- Path Electrical Effort  $H = \frac{C_{out-path}}{C_{in-path}}$
- Path Effort  $F = \prod f_i = \prod g_i h_i$
- For a single path (no branching):  $F = G \cdot H$


 
# Multistage Logic Circuits




- Logical effort generalizes to multistage networks
- Path Logical Effort  $G = \prod g_i$
- Path Electrical Effort  $H = \frac{C_{out-path}}{C_{in-path}}$
- Path Effort  $F = \prod f_i = \prod g_i h_i$
- For a single path (no branching):  $F = G \cdot H$


 
# Multistage Logic Circuits



- Logical effort generalizes to multistage networks
- Path Logical Effort  $G = \prod g_i$
- Path Electrical Effort  $H = \frac{C_{out-path}}{C_{in-path}}$
- Path Effort  $F = \prod f_i = \prod g_i h_i$
- For a single path (no branching):  $F = G \cdot H$



# Multistage Delays



- Path Effort Delay  $D_F = \sum f_i$
- Path Parasitic Delay  $P = \sum p_i$
- Path Delay  $D = \sum d_i = D_F + P$

# Multistage Delays



- Path Effort Delay  $D_F = \sum f_i$
- Path Parasitic Delay  $P = \sum p_i$
- Path Delay  $D = \sum d_i = D_F + P$



# Multistage Delays



- Path Effort Delay  $D_F = \sum f_i$
- Path Parasitic Delay  $P = \sum p_i$
- Path Delay  $D = \sum d_i = D_F + P$

# Designing Fast Circuits



- $D = \sum d_i = D_F + P$
- Delay is smallest when each stage bears same effort
  - $\hat{f} = g_i h_i = F^{\frac{1}{N}}$
- Thus minimum delay of N stage path is
  - $D = NF^{\frac{1}{N}} + P$
- This is a key result of logical effort
  - find fastest possible delay
  - doesn't require calculating gate sizes

# Designing Fast Circuits



- $D = \sum d_i = D_F + P$
- Delay is smallest when each stage bears same effort
  - $\hat{f} = g_i h_i = F^{\frac{1}{N}}$
- Thus minimum delay of N stage path is
  - $D = NF^{\frac{1}{N}} + P$
- This is a key result of logical effort
  - find fastest possible delay
  - doesn't require calculating gate sizes

# Designing Fast Circuits



- $D = \sum d_i = D_F + P$
- Delay is smallest when each stage bears same effort
  - $\hat{f} = g_i h_i = F^{\frac{1}{N}}$
- Thus minimum delay of N stage path is
  - $D = NF^{\frac{1}{N}} + P$
- This is a key result of logical effort
  - find fastest possible delay
  - doesn't require calculating gate sizes

# Designing Fast Circuits



- $D = \sum d_i = D_F + P$
- Delay is smallest when each stage bears same effort
  - $\hat{f} = g_i h_i = F^{\frac{1}{N}}$
- Thus minimum delay of N stage path is
  - $D = NF^{\frac{1}{N}} + P$
- This is a key result of logical effort
  - find fastest possible delay
  - doesn't require calculating gate sizes

# Designing Fast Circuits



- $D = \sum d_i = D_F + P$
- Delay is smallest when each stage bears same effort
  - $\hat{f} = g_i h_i = F^{\frac{1}{N}}$
- Thus minimum delay of N stage path is
  - $D = NF^{\frac{1}{N}} + P$
- This is a key result of logical effort
  - find fastest possible delay
  - doesn't require calculating gate sizes



- How wide should the gates be for least delay?

- $\hat{f} = gh = g \frac{C_{out}}{C_{in}}$

- $C_{in_i} = \frac{g_i C_{out}}{\hat{f}}$

- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.



- How wide should the gates be for least delay?

- $\hat{f} = gh = g \frac{C_{out}}{C_{in}}$

- $C_{in_i} = \frac{g_i C_{out}}{\hat{f}}$

- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.





- How wide should the gates be for least delay?

- $\hat{f} = gh = g \frac{C_{out}}{C_{in}}$

- $C_{in_i} = \frac{g_i C_{out}}{\hat{f}}$

- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.



- How wide should the gates be for least delay?
  - $\hat{f} = gh = g \frac{C_{out}}{C_{in}}$
  - $C_{in_i} = \frac{g_i C_{out}}{\hat{f}}$
- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.



- How wide should the gates be for least delay?
  - $\hat{f} = gh = g \frac{C_{out}}{C_{in}}$
  - $C_{in_i} = \frac{g_i C_{out}}{\hat{f}}$
- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.

# Buffer Design: Best Number of Stages




- How many stages should a buffer use?

- Minimizing number of stages is not always fastest

- Example: drive  $64 \times C$  load with unit inverter

$$D = NF^{\frac{1}{N}} + P$$

$$= N(64)^{\frac{1}{N}} + N$$

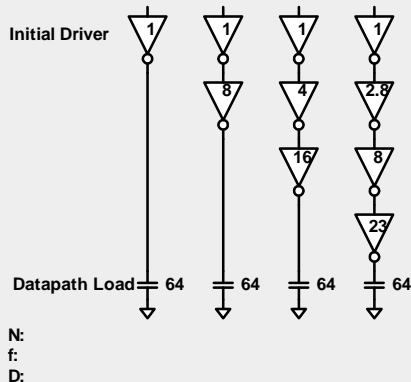


# Buffer Design: Best Number of Stages



- How many stages should a buffer use?
  - Minimizing number of stages is not always fastest
- Example: drive  $64 \times C$  load with unit inverter

$$t_D = N f t_{inv} + P$$

$$t_D = N(54)^{\frac{1}{N}} + N$$

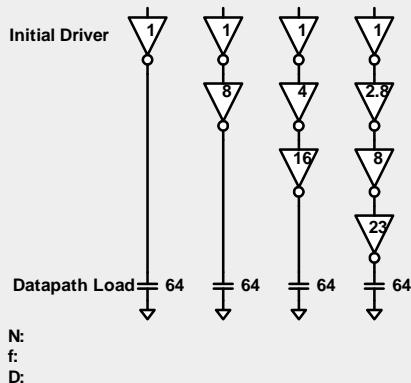


# Buffer Design: Best Number of Stages



- How many stages should a buffer use?
  - Minimizing number of stages is not always fastest
- Example: drive  $64 \times C$  load with unit inverter

$$D = NF^{\frac{1}{N}} + P$$


$$= N(64)^{\frac{1}{N}} + N$$

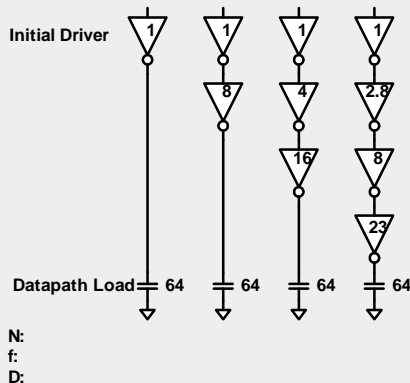
 
## Buffer Design: Best Number of Stages




- How many stages should a buffer use?
  - Minimizing number of stages is not always fastest
- Example: drive  $64 \times C$  load with unit inverter
  - $D = NF^{\frac{1}{N}} + P$
  - $= N(64)^{\frac{1}{N}} + N$


 
# Buffer Design: Best Number of Stages



- How many stages should a buffer use?
  - Minimizing number of stages is not always fastest
- Example: drive  $64 \times C$  load with unit inverter
  - $D = NF^{\frac{1}{N}} + P$
  - $= N(64)^{\frac{1}{N}} + N$





 
# Buffer Design: Best Number of Stages




- How many stages should a buffer use?
  - Minimizing number of stages is not always fastest
- Example: drive  $64 \times C$  load with unit inverter
  - $D = NF^{\frac{1}{N}} + P$
  - $= N(64)^{\frac{1}{N}} + N$


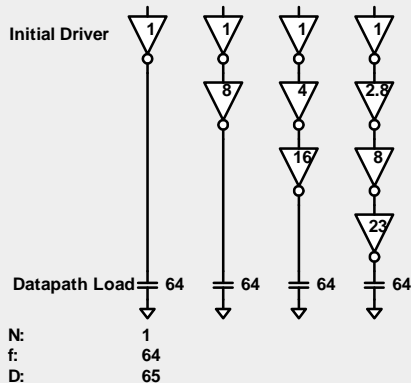
# Buffer Design: Best Number of Stages




- How many stages should a buffer use?
  - Minimizing number of stages is not always fastest
- Example: drive  $64 \times C$  load with unit inverter
  - $D = NF^{\frac{1}{N}} + P$
  - $= N(64)^{\frac{1}{N}} + N$


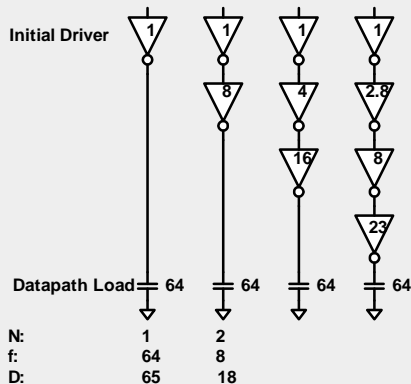
# Buffer Design: Best Number of Stages




- How many stages should a buffer use?
  - Minimizing number of stages is not always fastest
- Example: drive  $64 \times C$  load with unit inverter
  - $D = NF^{\frac{1}{N}} + P$
  - $= N(64)^{\frac{1}{N}} + N$


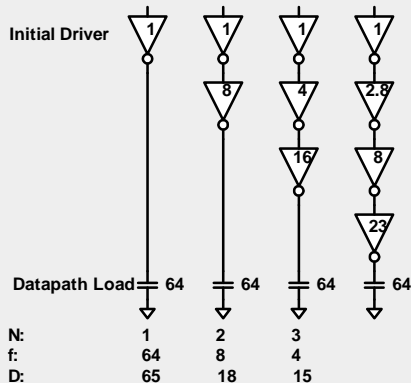
# Buffer Design: Best Number of Stages




- How many stages should a buffer use?
  - Minimizing number of stages is not always fastest
- Example: drive  $64 \times C$  load with unit inverter
  - $D = NF^{\frac{1}{N}} + P$
  - $= N(64)^{\frac{1}{N}} + N$


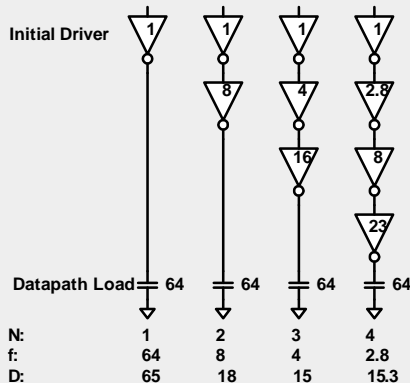
# Buffer Design: Best Number of Stages




- How many stages should a buffer use?
  - Minimizing number of stages is not always fastest
- Example: drive  $64 \times C$  load with unit inverter
  - $D = NF^{\frac{1}{N}} + P$
  - $= N(64)^{\frac{1}{N}} + N$


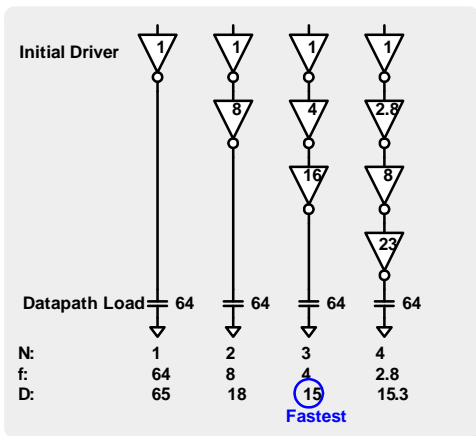
# Buffer Design: Best Number of Stages



- How many stages should a buffer use?
  - Minimizing number of stages is not always fastest
- Example: drive  $64 \times C$  load with unit inverter
  - $D = NF^{\frac{1}{N}} + P$
  - $= N(64)^{\frac{1}{N}} + N$



# Derivation



- How many inverters in a buffer give the least delay?
- For  $N$  inverters:  $D = NF^{\frac{1}{N}} + N \cdot p_{inv}$ 
  - $p_{inv}$  is the parasitic delay of the inverter,  $F$  is the path effort
  - Path Effort:  $F = G \cdot H = \frac{C_{out}}{C_{in}}$
- Minimize delay:  $\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \cdot \ln \left( F^{\frac{1}{N}} \right) + F^{\frac{1}{N}} + p_{inv} = 0$
- Define best stage effort  $\rho = F^{\frac{1}{N}}$ 
  - $p_{inv} + \rho(1 - \ln \rho) = 0$

# Derivation



- How many inverters in a buffer give the least delay?
- For  $N$  inverters:  $D = NF^{\frac{1}{N}} + N \cdot p_{inv}$ 
  - $p_{inv}$  is the parasitic delay of the inverter,  $F$  is the path effort
  - Path Effort:  $F = G \cdot H = \frac{C_{out}}{C_{in1}}$
- Minimize delay:  $\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \cdot \ln \left( F^{\frac{1}{N}} \right) + F^{\frac{1}{N}} + p_{inv} = 0$
- Define best stage effort  $\rho = F^{\frac{1}{N}}$ 
  - $p_{inv} + \rho(1 - \ln \rho) = 0$



# Derivation



- How many inverters in a buffer give the least delay?
- For  $N$  inverters:  $D = NF^{\frac{1}{N}} + N \cdot p_{inv}$ 
  - $p_{inv}$  is the parasitic delay of the inverter,  $F$  is the path effort
  - Path Effort:  $F = G \cdot H = \frac{C_{out}}{C_{in1}}$
- Minimize delay:  $\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \cdot \ln \left( F^{\frac{1}{N}} \right) + F^{\frac{1}{N}} + p_{inv} = 0$
- Define best stage effort  $\rho = F^{\frac{1}{N}}$ 
  - $p_{inv} + \rho(1 - \ln \rho) = 0$

# Derivation



- How many inverters in a buffer give the least delay?
- For  $N$  inverters:  $D = NF^{\frac{1}{N}} + N \cdot p_{inv}$ 
  - $p_{inv}$  is the parasitic delay of the inverter,  $F$  is the path effort
  - Path Effort:  $F = G \cdot H = \frac{C_{out}}{C_{in1}}$
- Minimize delay:  $\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \cdot \ln \left( F^{\frac{1}{N}} \right) + F^{\frac{1}{N}} + p_{inv} = 0$
- Define best stage effort  $\rho = F^{\frac{1}{N}}$ 
  - $p_{inv} + \rho(1 - \ln \rho) = 0$

# Derivation



- How many inverters in a buffer give the least delay?
- For  $N$  inverters:  $D = NF^{\frac{1}{N}} + N \cdot p_{inv}$ 
  - $p_{inv}$  is the parasitic delay of the inverter,  $F$  is the path effort
  - Path Effort:  $F = G \cdot H = \frac{C_{out}}{C_{in1}}$
- Minimize delay:  $\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \cdot \ln \left( F^{\frac{1}{N}} \right) + F^{\frac{1}{N}} + p_{inv} = 0$
- Define best stage effort  $\rho = F^{\frac{1}{N}}$
- $p_{inv} + \rho(1 - \ln \rho) = 0$

# Derivation



- How many inverters in a buffer give the least delay?
- For  $N$  inverters:  $D = NF^{\frac{1}{N}} + N \cdot p_{inv}$ 
  - $p_{inv}$  is the parasitic delay of the inverter,  $F$  is the path effort
  - Path Effort:  $F = G \cdot H = \frac{C_{out}}{C_{in1}}$
- Minimize delay:  $\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \cdot \ln\left(F^{\frac{1}{N}}\right) + F^{\frac{1}{N}} + p_{inv} = 0$
- Define best stage effort  $\rho = F^{\frac{1}{N}}$ 
  - $p_{inv} + \rho(1 - \ln \rho) = 0$

# Derivation



- How many inverters in a buffer give the least delay?
- For  $N$  inverters:  $D = NF^{\frac{1}{N}} + N \cdot p_{inv}$ 
  - $p_{inv}$  is the parasitic delay of the inverter,  $F$  is the path effort
  - Path Effort:  $F = G \cdot H = \frac{C_{out}}{C_{in1}}$
- Minimize delay:  $\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \cdot \ln \left( F^{\frac{1}{N}} \right) + F^{\frac{1}{N}} + p_{inv} = 0$
- Define best stage effort  $\rho = F^{\frac{1}{N}}$ 
  - $p_{inv} + \rho(1 - \ln \rho) = 0$

# Best Stage Effort



- $p_{inv} + \rho(1 - \ln \rho) = 0$  has no closed form solution
- Neglecting parasitics ( $p_{inv} = 0$ ) we find  $\rho = e = 2.718$
- For  $p_{inv} = 1$ , numerical solution yields  $\rho = 3.59$
- Least delay for:
  - stage effort (or fan-out) equal to  $\rho = F^{\frac{1}{N}} = 4$
  - and when using  $N = \log_{\rho} F$
  - $$= \log_4 F = \log_4 \left( \frac{C_{out}}{C_{in}} \right)$$
- Rule of thumb: Fan-out of 4 (FO4) stage effort results in fastest path

# Best Stage Effort



- $p_{inv} + \rho(1 - \ln \rho) = 0$  has no closed form solution
- Neglecting parasitics ( $p_{inv} = 0$ ) we find  $\rho = e = 2.718$
- For  $p_{inv} = 1$ , numerical solution yields  $\rho = 3.59$
- Least delay for:
  - stage effort (or fan-out) equal to  $\rho = F^{\frac{1}{N}} = 4$
  - and when using  $N = \log_{\rho} F$
  - $$= \log_4 F = \log_4 \left( \frac{C_{out}}{C_{in}} \right)$$
- Rule of thumb: Fan-out of 4 (FO4) stage effort results in fastest path

# Best Stage Effort



- $p_{inv} + \rho(1 - \ln \rho) = 0$  has no closed form solution
- Neglecting parasitics ( $p_{inv} = 0$ ) we find  $\rho = e = 2.718$
- For  $p_{inv} = 1$ , numerical solution yields  $\rho = 3.59$
- Least delay for:
  - stage effort (or fan-out) equal to  $\rho = F^{\frac{1}{N}} = 4$
  - and when using  $N = \log_{\rho} F$
  - $$= \log_4 F = \log_4 \left( \frac{C_{out}}{C_{in}} \right)$$
- Rule of thumb: Fan-out of 4 (FO4) stage effort results in fastest path



# Best Stage Effort



- $p_{inv} + \rho(1 - \ln \rho) = 0$  has no closed form solution
- Neglecting parasitics ( $p_{inv} = 0$ ) we find  $\rho = e = 2.718$
- For  $p_{inv} = 1$ , numerical solution yields  $\rho = 3.59$
- Least delay for:
  - stage effort (or fan-out) equal to  $\rho = F^{\frac{1}{N}} = 4$
  - and when using  $\hat{N} = \log_{\rho} F$
  - $$= \log_4 F = \log_4 \left( \frac{C_{out}}{C_{in1}} \right)$$
- Rule of thumb: Fan-out of 4 (FO4) stage effort results in fastest path

# Best Stage Effort



- $p_{inv} + \rho(1 - \ln \rho) = 0$  has no closed form solution
- Neglecting parasitics ( $p_{inv} = 0$ ) we find  $\rho = e = 2.718$
- For  $p_{inv} = 1$ , numerical solution yields  $\rho = 3.59$
- Least delay for:
  - stage effort (or fan-out) equal to  $\rho = F^{\frac{1}{N}} = 4$
  - and when using  $\hat{N} = \log_{\rho} F$
  - $$= \log_4 F = \log_4 \left( \frac{C_{out}}{C_{in1}} \right)$$
- Rule of thumb: Fan-out of 4 (FO4) stage effort results in fastest path

# Best Stage Effort



- $p_{inv} + \rho(1 - \ln \rho) = 0$  has no closed form solution
- Neglecting parasitics ( $p_{inv} = 0$ ) we find  $\rho = e = 2.718$
- For  $p_{inv} = 1$ , numerical solution yields  $\rho = 3.59$
- Least delay for:
  - stage effort (or fan-out) equal to  $\rho = F^{\frac{1}{N}} = 4$
  - and when using  $\hat{N} = \log_{\rho} F$
  - $$= \log_4 F = \log_4 \left( \frac{C_{out}}{C_{in1}} \right)$$
- Rule of thumb: Fan-out of 4 (FO4) stage effort results in fastest path

# Best Stage Effort



- $p_{inv} + \rho(1 - \ln \rho) = 0$  has no closed form solution
- Neglecting parasitics ( $p_{inv} = 0$ ) we find  $\rho = e = 2.718$
- For  $p_{inv} = 1$ , numerical solution yields  $\rho = 3.59$
- Least delay for:
  - stage effort (or fan-out) equal to  $\rho = F^{\frac{1}{N}} = 4$
  - and when using  $\hat{N} = \log_{\rho} F$
  - $$= \log_4 F = \log_4 \left( \frac{C_{out}}{C_{in1}} \right)$$
- Rule of thumb: Fan-out of 4 (FO4) stage effort results in fastest path

# Best Stage Effort




- $p_{inv} + \rho(1 - \ln \rho) = 0$  has no closed form solution
- Neglecting parasitics ( $p_{inv} = 0$ ) we find  $\rho = e = 2.718$
- For  $p_{inv} = 1$ , numerical solution yields  $\rho = 3.59$
- Least delay for:
  - stage effort (or fan-out) equal to  $\rho = F^{\frac{1}{N}} = 4$
  - and when using  $\hat{N} = \log_{\rho} F$
  - $$= \log_4 F = \log_4 \left( \frac{C_{out}}{C_{in1}} \right)$$
- Rule of thumb: Fan-out of 4 (FO4) stage effort results in fastest path
 
# Sensitivity Analysis




- How sensitive is delay to using exactly the best number of stages?
- $2.4 < \rho < 6$  gives delay within 15% of optimal
  - we can be sloppy!
  - Common standard is  $\rho = 4$


 
## Sensitivity Analysis




- How sensitive is delay to using exactly the best number of stages?
- $2.4 < \rho < 6$  gives delay within 15% of optimal
  - we can be sloppy!
  - Common standard is  $\rho = 4$


 
## Sensitivity Analysis



- How sensitive is delay to using exactly the best number of stages?
- $2.4 < \rho < 6$  gives delay within 15% of optimal
  - we can be sloppy!
  - Common standard is  $\rho = 4$





 
# Sensitivity Analysis



- How sensitive is delay to using exactly the best number of stages?
- $2.4 < \rho < 6$  gives delay within 15% of optimal
  - we can be sloppy!
  - Common standard is  $\rho = 4$



# Method of Logical Effort



- Note that for the buffer design problem:  $G = B = 1$ ,  $g_i = 1$ , and  $F = H = \frac{C_{out}}{C_{in1}}$

# Minimizing Layout Area?



- Total transistor area can be roughly estimated as  $A = A_1 \sum_{i=0}^{N-1} (\hat{f})^N$ , where  $A_1$  is the area of the first inverter.
- The area can be minimized for a specified delay ( $D_0$ ) by optimizing the following set of constraints



$$\text{minimize } \frac{(\hat{f})^N - 1}{\hat{f} - 1}$$

$$\text{for } D = P + N\hat{f} \leq D_0$$

- A fan-out of 8 can be used as a good trade-off to reduce layout area when designing large buffers.

# Minimizing Layout Area?



- Total transistor area can be roughly estimated as  $A = A_1 \sum_{i=0}^{N-1} (\hat{f})^N$ , where  $A_1$  is the area of the first inverter.
- The area can be minimized for a specified delay ( $D_0$ ) by optimizing the following set of constraints

■

$$\text{minimize } \frac{(\hat{f})^N - 1}{\hat{f} - 1}$$

$$\text{for } D = P + N\hat{f} \leq D_0$$

- A fan-out of 8 can be used as a good trade-off to reduce layout area when designing large buffers.

# Minimizing Layout Area?



- Total transistor area can be roughly estimated as  $A = A_1 \sum_{i=0}^{N-1} (\hat{f})^N$ , where  $A_1$  is the area of the first inverter.
- The area can be minimized for a specified delay ( $D_0$ ) by optimizing the following set of constraints

■

$$\text{minimize } \frac{(\hat{f})^N - 1}{\hat{f} - 1}$$

$$\text{for } D = P + N\hat{f} \leq D_0$$

- A fan-out of 8 can be used as a good trade-off to reduce layout area when designing large buffers.

# References I



N. Weste and D. Harris, CMOS VLSI Design: A circuits and systems perspective, 4th Ed., Addison-Wesley, 2010.



R. J. Baker, CMOS Circuit Design, Layout and Simulation, revised 2nd Edition, Wiley-IEEE, 2008.