



Clocked Circuits Additional Slides

Vishal Saxena ECE, Boise State University

Nov 30, 2010


Vishal Saxena | CMOS Inverter



• When CLK = 1, latch is transparent

- D flows through to Q like a buffer
- When CLK = 0, the latch is opaque


Q holds its old value independent of D

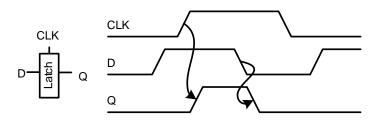



- When CLK = 1, latch is transparent
 - D flows through to Q like a buffer
 - When CLK = 0, the latch is opaque


Q holds its old value independent of D

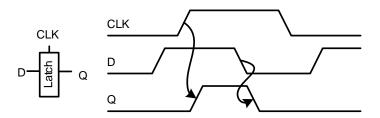




- When CLK = 1, latch is transparent
 - D flows through to Q like a buffer
- When CLK = 0, the latch is opaque

Q holds its old value independent of D

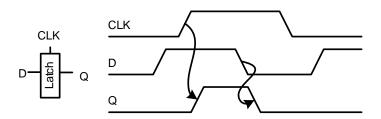



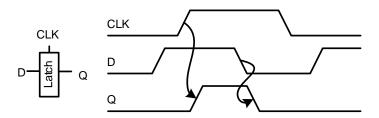
- When CLK = 1, latch is transparent
 - D flows through to Q like a buffer
- When CLK = 0, the latch is opaque
 - Q holds its old value independent of D









Multiplexer chooses D or old Q

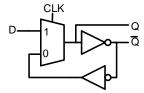


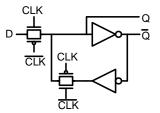






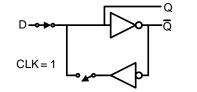

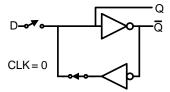

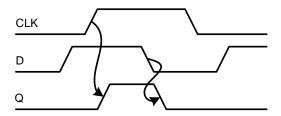






■ When CLK rises, D is copied to Q

• At all other times, Q holds its value

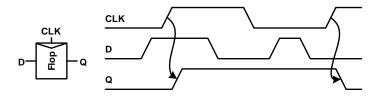a.k.a. positive edge-triggered flip-flop, master-slave flip-flop








■ When CLK rises, D is copied to Q

• At all other times, Q holds its value

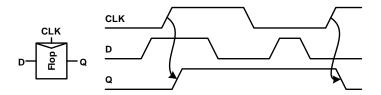a.k.a. positive edge-triggered flip-flop, master-slave flip-flop










■ When CLK rises, D is copied to Q

• At all other times, Q holds its value

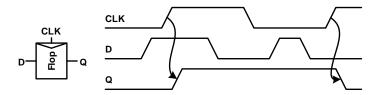
a.k.a. positive edge-triggered flip-flop, master-slave flip-flop









Built from master and slave D latches

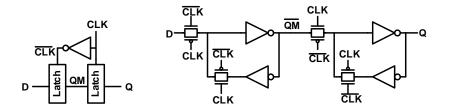


D Flip-flop Operation




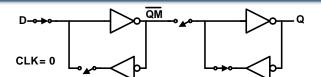

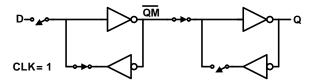

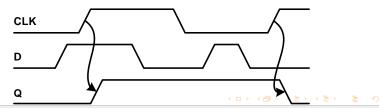



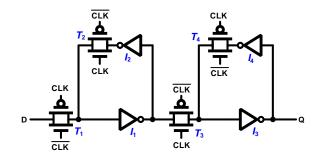


$$\bullet t_{setup} = t_{T_1} + t_{I_1}$$

$$\bullet t_{hold} = -(t_{T_1} + t_{I_1})$$

$$\bullet t_{pcq} = t_{T_3} + t_{I_3}$$

Vishal Saxena | CMOS Inverter



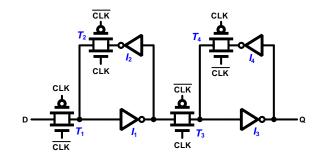


$$\bullet t_{setup} = t_{T_1} + t_{I_1}$$

$$\bullet t_{hold} = -(t_{T_1} + t_{l_1})$$

$$\bullet t_{pcq} = t_{T_3} + t_{I_3}$$




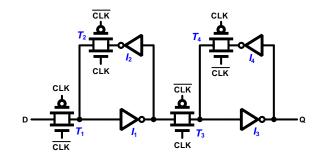

•
$$t_{setup} = t_{T_1} + t_{I_1}$$

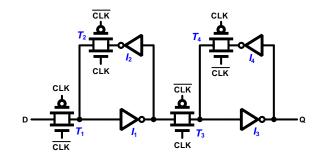• $t_{hold} = -(t_{T_1} + t_{I_1})$
• $t_{nca} = t_{T_2} + t_{I_2}$






•
$$t_{setup} = t_{T_1} + t_{I_1}$$

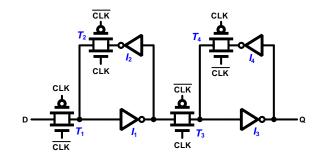• $t_{hold} = -(t_{T_1} + t_{I_1})$
• $t_{nca} = t_{T_2} + t_{I_2}$






•
$$t_{setup} = t_{T_1} + t_{l_1}$$

• $t_{hold} = -(t_{T_1} + t_{l_1})$
• $t_{pcq} = t_{T_3} + t_{l_3}$

Vishal Saxena | CMOS Inverter

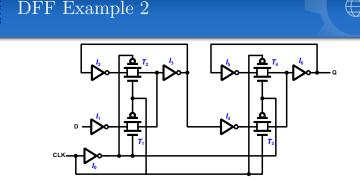


$$t_{setup} = t_{I_1} + t_{T_1} + t_{I_3} + t_{I_4}$$

• $t_{hold} = t_{I_0} - (t_{I_1} + t_{T_1} + t_{I_3})$ (Note that the \overline{CLK} and CLK have an overlap equal to an inverter delay (t_{I_0}))

 Need to hold input (D), otherwise the master will latch new D value.

$$\bullet t_{pcq} = t_{T_3} + t_{I_6}$$

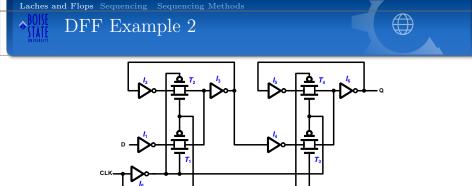


$$t_{setup} = t_{I_1} + t_{T_1} + t_{I_3} + t_{I_4}$$

• $t_{hold} = t_{I_0} - (t_{I_1} + t_{T_1} + t_{I_3})$ (Note that the \overline{CLK} and CLK have an overlap equal to an inverter delay (t_{I_0}))


 Need to hold input (D), otherwise the master will latch new D value.

$$\bullet t_{pcq} = t_{T_3} + t_{I_6}$$

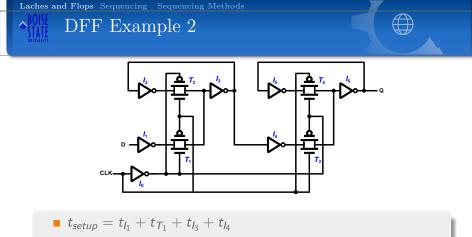

- $t_{hold} = t_{l_0} (t_{l_1} + t_{T_1} + t_{l_3})$ (Note that the \overline{CLK} and CLK have an overlap equal to an inverter delay (t_{l_0}))
 - Need to hold input (D), otherwise the master will latch new D value.


$$\bullet t_{pcq} = t_{T_3} + t_{l_6}$$

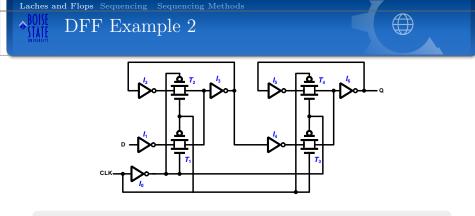

$$t_{setup} = t_{I_1} + t_{T_1} + t_{I_3} + t_{I_4}$$

- $t_{hold} = t_{l_0} (t_{l_1} + t_{T_1} + t_{l_3})$ (Note that the \overline{CLK} and CLK have an overlap equal to an inverter delay (t_{l_0}))
 - Need to hold input (D), otherwise the master will latch new D value.

$$\bullet t_{pcq} = t_{T_3} + t_{I_6}$$

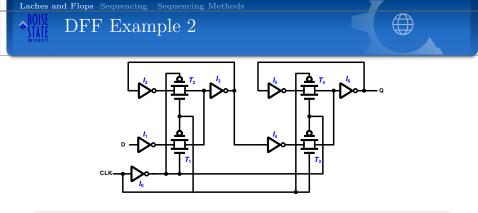

$$t_{setup} = t_{I_1} + t_{T_1} + t_{I_3} + t_{I_4}$$


- $t_{hold} = t_{l_0} (t_{l_1} + t_{T_1} + t_{l_3})$ (Note that the \overline{CLK} and CLK have an overlap equal to an inverter delay (t_{l_0}))
 - Need to hold input (D), otherwise the master will latch new D value.

$$\bullet t_{pcq} = t_{T_3} + t_{I_6}$$




■ Set forces output high when enabled

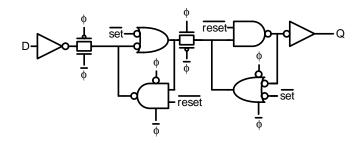Flip-flop with asynchronous set and reset





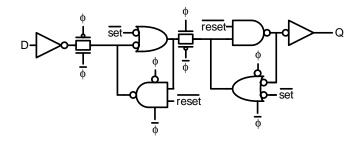- Set forces output high when enabled
- Flip-flop with asynchronous set and reset








A dynamic latch

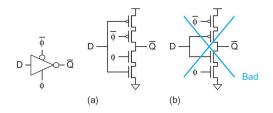sometimes called clocked CMOS (C²MOS) latch
 second design is inferior as the input noise passed into the output when the latch is opaque








A dynamic latch

• sometimes called clocked CMOS (C^2MOS) latch

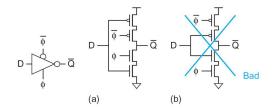second design is inferior as the input noise passed into the output when the latch is opaque










A dynamic latch

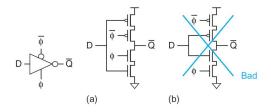- sometimes called clocked CMOS (C^2MOS) latch
- second design is inferior as the input noise passed into the output when the latch is opaque






Sequencing



Combinational logic

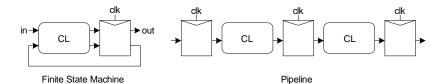- output depends on current inputs
- Sequential logic
 - output depends on current and previous inputs
 - Requires separating previous, current, future
 - Called state or tokens
 - Ex: FSM, pipeline





Sequencing




Combinational logic

output depends on current inputs

Sequential logic

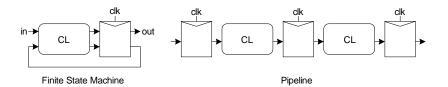- output depends on current and previous inputs
- Requires separating previous, current, future
- Called state or tokens
- Ex: FSM, pipeline








Combinational logic

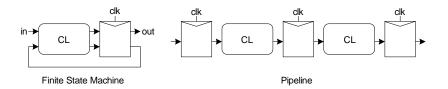
- output depends on current inputs
- Sequential logic
 - output depends on current and previous inputs
 - Requires separating previous, current, future
 - Called state or tokens
 - Ex: FSM, pipeline







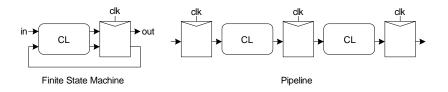
- Combinational logic
 - output depends on current inputs
- Sequential logic
 - output depends on current and previous inputs
 - Requires separating previous, current, future
 - Called state or tokens
 - Ex: FSM, pipeline







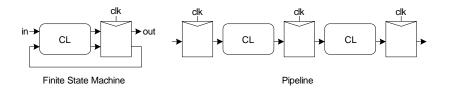
- Combinational logic
 - output depends on current inputs
- Sequential logic
 - output depends on current and previous inputs
 - Requires separating previous, current, future
 - Called state or tokens
 - Ex: FSM, pipeline







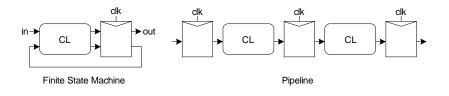
- Combinational logic
 - output depends on current inputs
- Sequential logic
 - output depends on current and previous inputs
 - Requires separating previous, current, future
 - Called state or tokens
 - Ex: FSM, pipeline







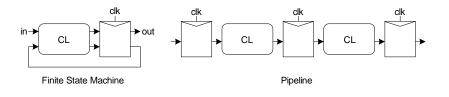- Combinational logic
 - output depends on current inputs
- Sequential logic
 - output depends on current and previous inputs
 - Requires separating previous, current, future
 - Called state or tokens
 - Ex: FSM, pipeline







- If tokens moved through pipeline at constant speed, no sequencing elements would be necessary
- Ex: fiber-optic cable
 - Light pulses (tokens) are sent down cable
 - Next pulse sent before first reaches end of cable
 - No need for hardware to separate pulses
 - But dispersion sets min time between pulses
- This is called wave pipelining in circuits
- In most circuits, dispersion is high
 - Delay fast tokens so they don't catch slow ones.





- If tokens moved through pipeline at constant speed, no sequencing elements would be necessary
- Ex: fiber-optic cable
 - Light pulses (tokens) are sent down cable
 - Next pulse sent before first reaches end of cable
 - No need for hardware to separate pulses
 - But dispersion sets min time between pulses
- This is called wave pipelining in circuits
- In most circuits, dispersion is high
 - Delay fast tokens so they don't catch slow ones.





- If tokens moved through pipeline at constant speed, no sequencing elements would be necessary
- Ex: fiber-optic cable
 - Light pulses (tokens) are sent down cable
 - Next pulse sent before first reaches end of cable
 - No need for hardware to separate pulses
 - But dispersion sets min time between pulses
- This is called wave pipelining in circuits
- In most circuits, dispersion is high
 - Delay fast tokens so they don't catch slow ones.





- If tokens moved through pipeline at constant speed, no sequencing elements would be necessary
- Ex: fiber-optic cable
 - Light pulses (tokens) are sent down cable
 - Next pulse sent before first reaches end of cable
 - No need for hardware to separate pulses
 - But dispersion sets min time between pulses
- This is called wave pipelining in circuits
- In most circuits, dispersion is high
 - Delay fast tokens so they don't catch slow ones.





- If tokens moved through pipeline at constant speed, no sequencing elements would be necessary
- Ex: fiber-optic cable
 - Light pulses (tokens) are sent down cable
 - Next pulse sent before first reaches end of cable
 - No need for hardware to separate pulses
 - But dispersion sets min time between pulses
- This is called wave pipelining in circuits
 - In most circuits, dispersion is high
 - Delay fast tokens so they don't catch slow ones.





- If tokens moved through pipeline at constant speed, no sequencing elements would be necessary
- Ex: fiber-optic cable
 - Light pulses (tokens) are sent down cable
 - Next pulse sent before first reaches end of cable
 - No need for hardware to separate pulses
 - But dispersion sets min time between pulses
- This is called wave pipelining in circuits
- In most circuits, dispersion is high

Delay fast tokens so they don't catch slow ones.





- If tokens moved through pipeline at constant speed, no sequencing elements would be necessary
- Ex: fiber-optic cable
 - Light pulses (tokens) are sent down cable
 - Next pulse sent before first reaches end of cable
 - No need for hardware to separate pulses
 - But dispersion sets min time between pulses
- This is called wave pipelining in circuits
- In most circuits, dispersion is high
 - Delay fast tokens so they don't catch slow ones.





- Use flip-flops to delay fast tokens so they move through exactly one stage each cycle.
- Inevitably adds some delay to the slow tokens
- Makes circuit slower than just the logic delay
 - Called sequencing overhead
- Some people call this clocking overhead
 - But it applies to asynchronous circuits too
 - Inevitable side effect of maintaining sequence





- Use flip-flops to delay fast tokens so they move through exactly one stage each cycle.
- Inevitably adds some delay to the slow tokens
- Makes circuit slower than just the logic delay
 - Called sequencing overhead
- Some people call this clocking overhead
 - But it applies to asynchronous circuits too
 - Inevitable side effect of maintaining sequence



- Use flip-flops to delay fast tokens so they move through exactly one stage each cycle.
- Inevitably adds some delay to the slow tokens
- Makes circuit slower than just the logic delay
 - Called sequencing overhead
- Some people call this clocking overhead
 - But it applies to asynchronous circuits too
 - Inevitable side effect of maintaining sequence





- Use flip-flops to delay fast tokens so they move through exactly one stage each cycle.
- Inevitably adds some delay to the slow tokens
- Makes circuit slower than just the logic delay
 - Called sequencing overhead
- Some people call this clocking overhead
 - But it applies to asynchronous circuits too
 - Inevitable side effect of maintaining sequence.





- Use flip-flops to delay fast tokens so they move through exactly one stage each cycle.
- Inevitably adds some delay to the slow tokens
- Makes circuit slower than just the logic delay
 - Called sequencing overhead
- Some people call this clocking overhead
 - But it applies to asynchronous circuits too
 - Inevitable side effect of maintaining sequence





- Use flip-flops to delay fast tokens so they move through exactly one stage each cycle.
- Inevitably adds some delay to the slow tokens
- Makes circuit slower than just the logic delay
 - Called sequencing overhead
- Some people call this clocking overhead
 - But it applies to asynchronous circuits too
 - Inevitable side effect of maintaining sequence





- Use flip-flops to delay fast tokens so they move through exactly one stage each cycle.
- Inevitably adds some delay to the slow tokens
- Makes circuit slower than just the logic delay
 - Called sequencing overhead
- Some people call this clocking overhead
 - But it applies to asynchronous circuits too
 - Inevitable side effect of maintaining sequence



Latch: Level sensitive

- a.k.a. transparent latch, D latch
- Flip-flop: edge triggered
 - a.k.a. master-slave flip-flop, D flip-flop, D register



Latch: Level sensitive

- a.k.a. transparent latch, D latch
- Flip-flop: edge triggered
 - a.k.a. master-slave flip-flop, D flip-flop, D register





Latch: Level sensitive

• a.k.a. transparent latch, D latch

■ Flip-flop: edge triggered

a.k.a. master-slave flip-flop, D flip-flop, D register





Latch: Level sensitive


• a.k.a. transparent latch, D latch

■ Flip-flop: edge triggered

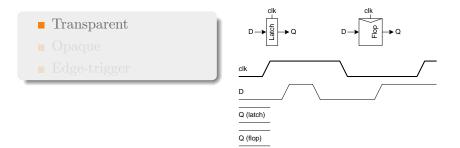a.k.a. master-slave flip-flop, D flip-flop, D register








▲ □ ▶ ▲ 圖 ▶ ▲ 圖 ▶ ▲ 圖 ■ ● ● ● ●

Vishal Saxena | CMOS Inverter






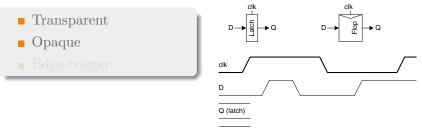

Q (flop)






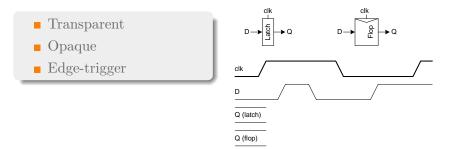






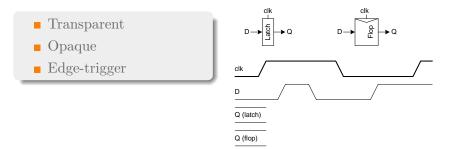





- Transparent
- Opaque
- Edge-trigger

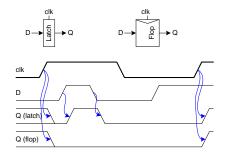







- * ロ * * 御 * * 国 * * 国 * ・ 国 * の & @

Vishal Saxena | CMOS Inverter




Sequencing Methods





2-Phase Transparent Latches

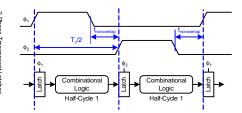


- イロト イヨト イヨト イヨト ヨー わへぐ








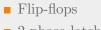

- 2-phase latches
- Pulsed Latches

Pulsed Latches

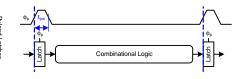






Sequencing Methods



Flip-flops2-phase latchesPulsed Latches

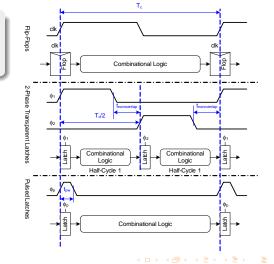








| Logic Prop. Delay | A- |
|-------------------------------|--|
| Logic Cont. Delay | |
| Latch/Flop Clk->Q Prop. Delay | 1 |
| Latch/Flop Clk->Q Cont. Delay | 1 |
| Latch D->Q Prop. Delay | 1 |
| Latch D->Q Cont. Delay | 1 |
| Latch/Flop Setup Time | 1 |
| Latch/Flop Hold Time | 1 |
| | Logic Cont. Delay Latch/Flop Clk->Q Prop. Delay Latch/Flop Clk->Q Cont. Delay Latch D->Q Prop. Delay Latch D->Q Cont. Delay Latch/Flop Setup Time |


Table: Contamination and Propagation Delays

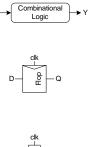



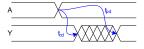

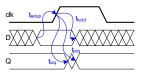


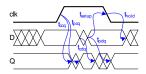



Max-Delay:Flip-Flops



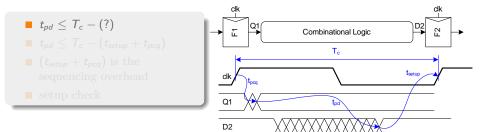


Vishal Saxena | CMOS Inverter

19/21



Max-Delay:Flip-Flops




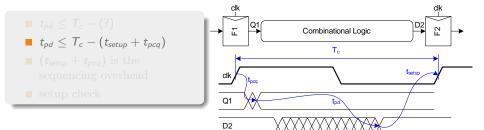



Max-Delay:Flip-Flops



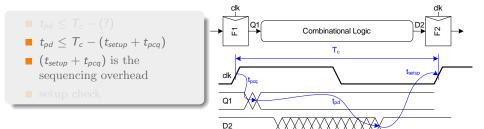


Vishal Saxena | CMOS Inverter

19/21



Max-Delay:Flip-Flops




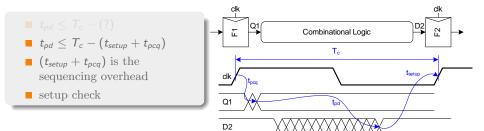



Min-Delay:Flip-Flops




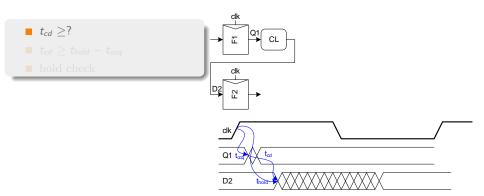

Vishal Saxena | CMOS Inverter




 $t_{cd} \geq t_{hold} - t_{ccq}$

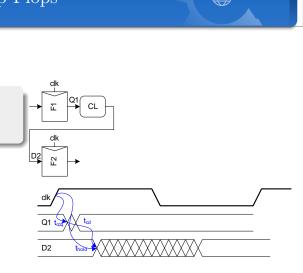

Vishal Saxena | CMOS Inverter





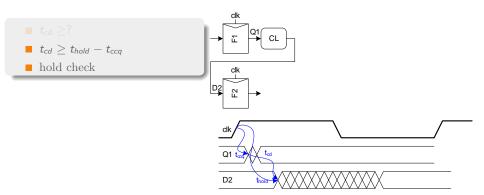

Vishal Saxena | CMOS Inverter

20/21







N. Weste and D. Harris, CMOS VLSI Design: A circuits and systems perspective, 4th Ed., Addison-Wesley, 2010.

R. J. Baker, CMOS Circuit Design, Layout and Simulation, revised 2nd Edition, Wiley-IEEE, 2008.

▲日 ▶ ▲ 聞 ▶ ▲ 国 ▶ ▲ 国 ▶ ● の Q ()~