

ECE 445 INTRO TO VLSI DESIGN

DIGITAL DESIGN USING LOGICAL EFFORT

VISHAL SAXENA

VSAXENA@UIDAHO.EDU



© Vishal Saxena

University of Idaho
College of Engineering


OUTLINE

- Logical Effort
- Delay in a Logic Gate
- Multistage Logic Networks
- Choosing the Best Number of Stages
- Example
- Summary



INTRODUCTION

- Chip designers face a bewildering array of choices
 - What is the best circuit topology for a function?
 - How many stages of logic give least delay?
 - How wide should the transistors be?
- Logical effort is a method to make these decisions
 - Uses a simple model of delay
 - Allows back-of-the-envelope calculations
 - Helps make rapid comparisons between alternatives
 - Emphasizes remarkable symmetries

 

DELAY IN A LOGIC GATE

Express delays in process-independent unit

Delay has two components: $d = f + p$

f : effort delay = gh (a.k.a. stage effort)

- Again has two components

g : logical effort

- Measures relative ability of gate to deliver current
- $g \equiv 1$ for inverter

h : electrical effort = C_{out} / C_{in}

- Ratio of output to input capacitance
- Sometimes called fanout

p : parasitic delay

- Represents delay of gate driving no load
- Set by internal parasitic capacitance

$$d = \frac{d_{abs}}{\tau}$$

$$\tau = 3RC$$


\approx 3 ps in 65 nm process

60 ps in 0.6 μ m process




DELAY PLOTS

 - $d = f + p$
 - $= gh + p$
- What about
- NOR2?




DELAY PLOTS

 - $d = f + p$
 - $= gh + p$
- What about
- NOR2?




COMPUTING LOGICAL EFFORT

 
- DEF: *Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current.*
- Measure from delay vs. fanout plots
- Or estimate by counting transistor widths



$$C_{in} = 3$$
$$g = 3/3$$

 

$$C_{in} = 4$$
$$g = 4/3$$

 

$$C_{in} = 5$$
$$g = 5/3$$



CATALOG OF GATES

- Logical effort of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		4/3	5/3	6/3	$(n+2)/3$
NOR		5/3	7/3	9/3	$(2n+1)/3$
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	



CATALOG OF GATES


- Parasitic delay of common gates
 - In multiples of p_{inv} (≈ 1)

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	



 EXAMPLE: RING OSCILLATOR

- Estimate the frequency of an N-stage ring oscillator




- Logical Effort: $g = 1$
- Electrical Effort: $h = 1$
- Parasitic Delay: $p = 1$
- Stage Delay: $d = 2$
- Frequency: $f_{\text{osc}} = 1/(2 \cdot N \cdot d) = 1/4N$

31 stage ring oscillator in
0.6 μm process has
frequency of ~ 200 MHz



 EXAMPLE: FO4 INVERTER

- Estimate the delay of a fanout-of-4 (FO4) inverter



- Logical Effort: $g = 1$
- Electrical Effort: $h = 4$
- Parasitic Delay: $p = 1$
- Stage Delay: $d = 5$

The FO4 delay is about
300 ps in 0.6 μm process
15 ps in a 65 nm process




MULTISTAGE LOGIC NETWORKS

- Logical effort generalizes to multistage networks
- *Path Logical Effort*
- *Path Electrical Effort*
- *Path Effort*

$$G = \prod g_i$$

$$H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$$

$$F = \prod f_i = \prod g_i h_i$$

 

MULTISTAGE LOGIC NETWORKS

- Logical effort generalizes to multistage networks

- *Path Logical Effort* $G = \prod g_i$

- *Path Electrical Effort* $H = \frac{C_{out-path}}{C_{in-path}}$

- *Path Effort* $F = \prod f_i = \prod g_i h_i$


- Can we write $F = GH$?



PATHS THAT BRANCH

- No! Consider paths that branch:

 - $G = 1$
- $H = 90 / 5 = 18$
- $GH = 18$
- $h_1 = (15 + 15) / 5 = 6$
- $h_2 = 90 / 15 = 6$
- $F = g_1 g_2 h_1 h_2 = 36 = 2GH$



BRANCHING EFFORT

- Introduce *branching effort*
 - Accounts for branching between stages in path

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

- Now we compute the path effort
 - $F = GBH$



MULTISTAGE DELAYS

- Path Effort Delay

$$D_F = \sum f_i$$

- Path Parasitic Delay

$$P = \sum p_i$$

- Path Delay

$$D = \sum d_i = D_F + P$$



DESIGNING FAST CIRCUITS

- Delay is smallest when each stage bears same effort

$$D = \sum d_i = D_F + P$$

- Thus minimum delay of N stage path is

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

- This is a **key** result of logical effort
 - Find fastest possible delay
 - Doesn't require calculating gate sizes



GATE SIZES

- How wide should the gates be for least delay?


$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$
$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.



 EXAMPLE: 3-STAGE PATH

- Select gate sizes x and y for least delay from A to B



EXAMPLE: 3-STAGE PATH

Logical Effort

$$G = (4/3) * (5/3) * (5/3) = 100/27$$

Electrical Effort

$$H = 45/8$$

Branching Effort

$$B = 3 * 2 = 6$$

Path Effort

$$F = GBH = 125$$

Best Stage Effort


$$\hat{f} = \sqrt[3]{F} = 5$$

Parasitic Delay

$$P = 2 + 3 + 2 = 7$$

Delay

$$D = 3 * 5 + 7 = 22 = 4.4 \text{ FO4}$$

 


EXAMPLE: 3-STAGE PATH

- Work backward for sizes
- $y = 45 * (5/3) / 5 = 15$
- $x = (15 * 2) * (5/3) / 5 = 10$


$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$
 
$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$



 EXAMPLE: 3-STAGE PATH


- Work backward for sizes
- $y = 45 * (5/3) / 5 = 15$
- $x = (15 * 2) * (5/3) / 5 = 10$



BEST NUMBER OF STAGES

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

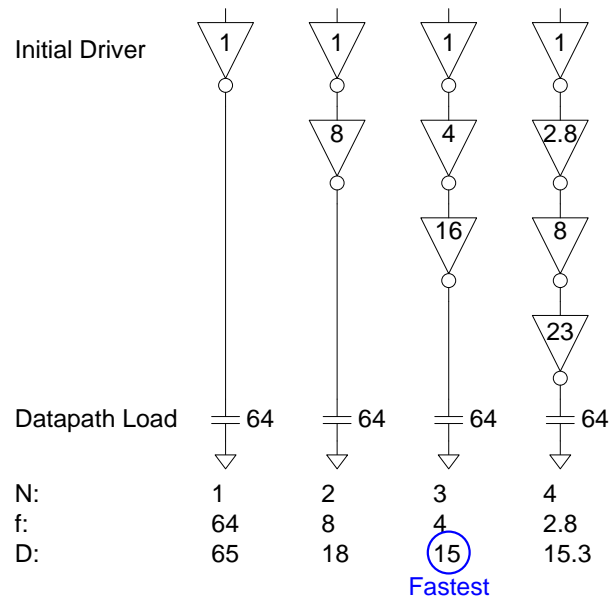- $D = NF^{1/N} + P$
- $= N(64)^{1/N} + N$



DERIVATION

- Consider adding inverters to end of path
 - How many give least delay?


$$D = NF^{\frac{1}{N}} + \sum_{i=1}^{n_1} p_i + (N - n_1) p_{inv}$$

$$\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \ln F^{\frac{1}{N}} + F^{\frac{1}{N}} + p_{inv} = 0$$

- Define best stage effort

$$\rho = F^{\frac{1}{N}}$$

$$p_{inv} + \rho(1 - \ln \rho) = 0$$

 


BEST STAGE EFFORT

- $p_{inv} + \rho(1 - \ln \rho) = 0$ has no closed-form solution
- Neglecting parasitics ($p_{inv} = 0$), we find $\rho = 2.718$ (e)
- For $p_{inv} = 1$, solve numerically for $\rho = 3.59$



SENSITIVITY ANALYSIS

 - How sensitive is delay to using exactly the best number of stages?



- $2.4 < \rho < 6$ gives delay within 15% of optimal
 - We can be sloppy!
 - I like $\rho = 4$



REVIEW OF DEFINITIONS

Term	Stage	Path
number of stages	1	N
logical effort	g	$G = \prod g_i$
electrical effort	$h = \frac{C_{\text{out}}}{C_{\text{in}}}$	$H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$
branching effort	$b = \frac{C_{\text{on-path}} + C_{\text{off-path}}}{C_{\text{on-path}}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
effort delay	f	$D_F = \sum f_i$
parasitic delay	p	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_F + P$



METHOD OF LOGICAL EFFORT

- 1) Compute path effort
- 2) Estimate best number of stages
- 3) Sketch path with N stages
- 4) Estimate least delay
- 5) Determine best stage effort
- 6) Find gate sizes

$$F = GBH$$

$$N = \log_4 F$$

$$D = NF^{\frac{1}{N}} + P$$

$$\hat{f} = F^{\frac{1}{N}}$$

$$C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$



LIMITS OF LOGICAL EFFORT

- Chicken and egg problem
 - Need path to compute G
 - But don't know number of stages without G
- Simplistic delay model
 - Neglects input rise time effects
- Interconnect
 - Iteration required in designs with wire
- Maximum speed only
 - Not minimum area/power for constrained delay



SUMMARY

- Logical effort is useful for thinking of delay in circuits
 - Numeric logical effort characterizes gates
 - NANDs are faster than NORs in CMOS
 - Paths are fastest when effort delays are ~ 4
 - Path delay is weakly sensitive to stages, sizes
 - But using fewer stages doesn't mean faster paths
 - Delay of path is about $\log_4 F$ FO4 inverter delays
 - Inverters and NAND2 best for driving large caps
- Provides language for discussing fast circuits
 - But requires practice to master

