



Static Logic

Additional Slides



Vishal Saxena
ECE, Boise State University

Nov 10, 2010



- Tristate buffer produces Z when not enabled


EN	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

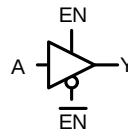 

Nonrestoring Tristate



 
- Transmission gate acts as a tristate buffer
 - only 2 transistors
 - but non-restoring
 - noise on A is passed on to Y



Nonrestoring Tristate



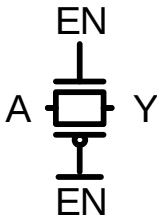
- Transmission gate acts as a tristate buffer
 - only 2 transistors
 - but non-restoring
 - noise on A is passed on to Y



Nonrestoring Tristate



 
- Transmission gate acts as a tristate buffer
 - only 2 transistors
 - but non-restoring
 - noise on A is passed on to Y



Nonrestoring Tristate







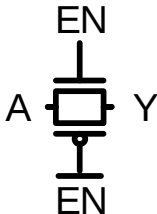- Transmission gate acts as a tristate buffer
 - only 2 transistors
 - but non-restoring
 - noise on A is passed on to Y







Tristate Inverter

    - Tristate inverter produces restored output
 - violates conduction complement rule
 - because we want a Z output







Tristate Inverter

    - Tristate inverter produces restored output
 - violates conduction complement rule
 - because we want a Z output



Tristate Inverter

    
- Tristate inverter produces restored output
 - violates conduction complement rule
 - because we want a Z output





- 2X1 multiplexer chooses between two inputs

S	D1	D0	Y
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1

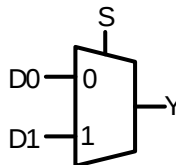

Gate-Level Mux Design





- $Y = SD_1 + \overline{S}D_0$
- How many transistors are needed?

Gate-Level Mux Design



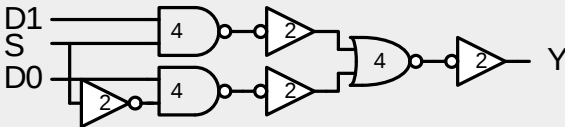 
- $Y = SD_1 + \bar{S}D_0$
- How many transistors are needed?



Transmission Gate (TG) Mux



 
- Nonrestoring mux uses two transmission gates
 - only 4 transistors



Transmission Gate (TG) Mux






 - Nonrestoring mux uses two transmission gates
 - only 4 transistors






Inverting Mux

   - Inverting multiplexer
 - use compound AOI22
 - or pair of tristate inverters
 - essentially the same thing
- Noninverting multiplexer adds an inverter






Inverting Mux

   - Inverting multiplexer
 - use compound AOI22
 - or pair of tristate inverters
 - essentially the same thing
- Noninverting multiplexer adds an inverter






Inverting Mux

 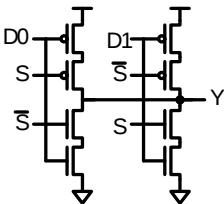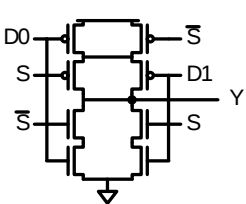- Inverting multiplexer
 - use compound AOI22
 - or pair of tristate inverters
 - essentially the same thing
- Noninverting multiplexer adds an inverter






Inverting Mux

   - Inverting multiplexer
 - use compound AOI22
 - or pair of tristate inverters
 - essentially the same thing
- Noninverting multiplexer adds an inverter





Inverting Mux

   - Inverting multiplexer
 - use compound AOI22
 - or pair of tristate inverters
 - essentially the same thing
- Noninverting multiplexer adds an inverter





4X1 Multiplexer

  - 4X1 Mux chooses one of 4 inputs using two selects
 - two levels of 2X1 Muxes
 - or four tri-states





4X1 Multiplexer

  - 4X1 Mux chooses one of 4 inputs using two selects
 - two levels of 2X1 Muxes
 - or four tri-states



4X1 Multiplexer

  
- 4X1 Mux chooses one of 4 inputs using two selects
 - two levels of 2X1 Muxes
 - or four tri-states



Bubble Pushing: Example 1



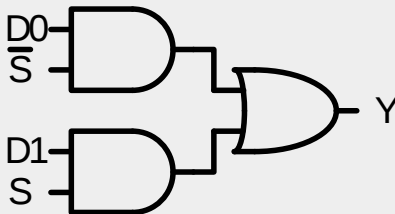
- MUX: $Y = \overline{S}D_0 + SD_1$
- 1) Sketch a design using AND, OR, and NOT gates



Bubble Pushing: Example 1




- MUX: $Y = \overline{S}D_0 + SD_1$
- 1) Sketch a design using AND, OR, and NOT gates

 

Example 2







 - 2) Sketch a design using NAND, NOR, and NOT gates
 - assume $\bar{S}$ is available







Bubble Pushing

    - Start with network of AND / OR gates
- Convert to NAND / NOR + inverters
- Push bubbles around to simplify logic
 - Remember DeMorgan's Law







Bubble Pushing

    - Start with network of AND / OR gates
- Convert to NAND / NOR + inverters
- Push bubbles around to simplify logic
 - Remember DeMorgan's Law



Bubble Pushing

    - Start with network of AND / OR gates
- Convert to NAND / NOR + inverters
- Push bubbles around to simplify logic
 - Remember DeMorgan's Law



Compound Gates




■ Sizing of compound gates

**unit
inverter**
 $Y = \overline{A}$




AOI21

$$Y = \overline{A \cdot B + C}$$

 



AOI22

$$Y = \overline{A \cdot B + C \cdot D}$$

 


Complex AOI
  
$$Y = \overline{A \cdot (B + C) + D \cdot E}$$




Input Order

 - Calculate parasitic delay for Y falling
 - If A arrives latest?
 - $6RC = 2\tau$
 - If B arrives latest?
 - 2.33τ




Input Order

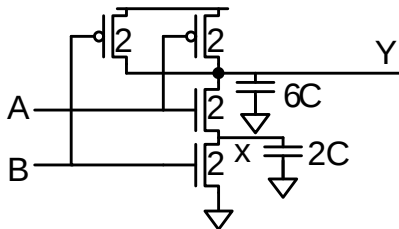- Calculate parasitic delay for Y falling
 - If A arrives latest?
 - $6RC = 2\tau$
 - If B arrives latest?
 - 2.33τ




Input Order

 - Calculate parasitic delay for Y falling
 - If A arrives latest?
 - $6RC = 2\tau$
 - If B arrives latest?
 - 2.33τ




Input Order

 - Calculate parasitic delay for Y falling
 - If A arrives latest?
 - $6RC = 2\tau$
 - If B arrives latest?
 - 2.33τ




Input Order

 - Calculate parasitic delay for Y falling
 - If A arrives latest?
 - $6RC = 2\tau$
 - If B arrives latest?
 - 2.33τ




Inner and Outer Inputs

 - Inner input is closest to output (A)
- Outer input is closest to rail (B)
- If input arrival time is known
 - Connect latest input to inner terminal



Inner and Outer Inputs

 
- Inner input is closest to output (A)
- Outer input is closest to rail (B)
- If input arrival time is known
 - Connect latest input to inner terminal



Inner and Outer Inputs



 
- Inner input is closest to output (A)
- Outer input is closest to rail (B)
- If input arrival time is known
 - Connect latest input to inner terminal



Inner and Outer Inputs



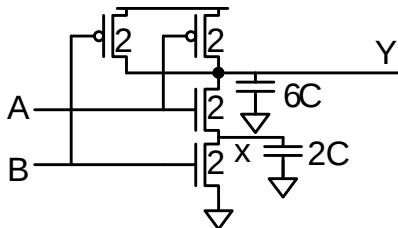- Inner input is closest to output (A)
- Outer input is closest to rail (B)
- If input arrival time is known
 - Connect latest input to inner terminal





- For speed:
 - NAND vs NOR
 - Many simple stages vs. fewer high fan-in stages
 - Latest-arriving input
- For area and power:
 - Many simple stages vs. fewer high fan-in stages



- For speed:
 - NAND vs NOR
 - Many simple stages vs. fewer high fan-in stages
 - Latest-arriving input
- For area and power:
 - Many simple stages vs. fewer high fan-in stages



- For speed:
 - NAND vs NOR
 - Many simple stages vs. fewer high fan-in stages
 - Latest-arriving input
- For area and power:
 - Many simple stages vs. fewer high fan-in stages



- For speed:
 - NAND vs NOR
 - Many simple stages vs. fewer high fan-in stages
 - Latest-arriving input
- For area and power:
 - Many simple stages vs. fewer high fan-in stages



- For speed:
 - NAND vs NOR
 - Many simple stages vs. fewer high fan-in stages
 - Latest-arriving input
- For area and power:
 - Many simple stages vs. fewer high fan-in stages



- For speed:
 - NAND vs NOR
 - Many simple stages vs. fewer high fan-in stages
 - Latest-arriving input
- For area and power:
 - Many simple stages vs. fewer high fan-in stages

References I



N. Weste and D. Harris, CMOS VLSI Design: A circuits and systems perspective, 4th Ed., Addison-Wesley, 2010.



R. J. Baker, CMOS Circuit Design, Layout and Simulation, revised 2nd Edition, Wiley-IEEE, 2008.