## ECE 445 Intro to VLSI Design Sample Midterm 2 Apr 8, 2019

Name:

Closed Book, Closed Notes, Closed Computer. Show your steps clearly to get credit. State clearly any assumptions made. This exam has 6 questions, for a total of 100 points.

Unless otherwise indicated use the following device parameters for the C5 process for hand calculations:

Value
$0.3\mu m$
5 V
$2.8 \frac{fF}{\mu m^2}$
0.8 V
0.9 V
$115 \frac{\mu A}{V^2}$
$60 \frac{\mu A}{V^2}$

(5) 0-5

## Long Channel MOSFET equations:

$$V_{THN} = V_{THN0} + \gamma(\sqrt{|2V_{fp}| + V_{SB}} - \sqrt{|2V_{fp}|})$$

$$I_{D} = \begin{cases} KP_{n}\frac{W}{L} \left( (V_{GS} - V_{THN}) V_{DS} - \frac{V_{DS}^{2}}{2} \right), & V_{DS} < V_{GS} - V_{THN} \\ \frac{1}{2}KP_{n}\frac{W}{L} \left( V_{GS} - V_{THN} \right)^{2}, & V_{DS} \ge V_{GS} - V_{THN} \end{cases}, & V_{GS} > V_{THN} \end{cases}$$
Digital MOSFET Model:

Model ugit

$$R'_{n,p} = \frac{V_{DD}}{\frac{1}{2}KP_{n,p}(V_{DD} - V_{THN})^2} \\ R_{n,p} = R'_{n,p}\frac{L}{W}$$

## Logical Effort equations:

$$\begin{cases} F = GBH \triangleq H \text{ for an inverter chain} \\ \hat{f} = F^{\frac{1}{N}} \text{ for the least delay} \\ D = P + N \cdot \hat{f} \end{cases}$$

1. (10 points) For the circuits seen below, plot the current  $I_x$  as the voltage  $V_x$  is swept from 0 to  $V_{DD}$ .



 $V_{SD}$ 

VSD, Sat = VSG-VAHP

2. (a) (5 points) Based on the data provided on the first page, estimate  $C'_{ox}$ ,  $R'_n$ , and  $R'_p$ . Show your work.



(b) (5 points) Fill the following table using the data provided on the first page.

Device	Drawn	Actual size	$R_{n,p}$	$C_{oxn,p}$
NMOS	10/2 🗸	$3\mu m$ by $0.6\mu m$		fF
PMOS	20/2 r	$45 \mu m$ by 0.6 $\mu m$		fF

 $R_{m} = k_{m}' \cdot \frac{L}{w} = 5kn \cdot \frac{2}{10} = 1kn$   $R_{p} = k_{p}' \cdot \frac{L}{w} = 10kn \cdot \frac{2}{20} = 1kn$   $Com = Car' (WL)_{n} = .50 \text{ ff}$   $Coup = Con'(WL)_{p} = 100 \text{ ff}$ 

3. (a) (10 points) Estimate the oscillation frequency  $(f_{osc})$  of a 21-stage ring oscillatory designed using 10/2 NMOS and 20/2 PMOS devices.

$$f_{osc} = \frac{1}{n \times (t_{p+h,t} + t_{p+h,t})} = \frac{1}{n \times o.7 (R_{p} + R_{m})C_{tot}}$$

$$= 91.74 \text{ MHz} = 375 \text{ ff}$$

(b) (5 points) Calculate the total dynamic power dissipated in the oscillator?

$$f_{k} = n \times CV^{2} f$$

$$= n \times \frac{5}{2} (c_{nn} + c_{onp}) \cdot V_{DD}^{2} \cdot \frac{1}{5} sc$$

$$= 21 \times 375 ff \times 5^{2} \times 91.74 \text{ MHz}$$

$$= 18.1 \text{ mW}$$

(c) (5 points) How does  $f_{osc}$  change when the supply voltage  $V_{DD}$  is varied from 0 to 5V? *Explain.* 

$$f_{DSC} = \frac{1}{n_{X} \circ 7} (R_{P} + R_{n}) C_{+} t$$

$$R_{n_{P}} = \frac{V_{DD}}{\frac{1}{2} K_{n_{P}} (V_{12} - V_{21} W_{1})^{2}} \propto \frac{1}{V_{DD} - V_{21} W_{1}}$$

$$V_{DD} = \frac{V_{DD}}{V_{DD} - V_{21} W_{1}} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{21} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{21} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{21} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{21} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{21} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{21} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{21} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{21} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{21} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{21} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{21} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{21} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{21} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{12} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{12} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{12} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{12} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{12} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{12} W_{1})^{2} \qquad f_{OSC}$$

$$V_{DD} = \frac{1}{2} K_{n_{P}} (V_{12} - V_{12} W_{1})^{2} \qquad f_{OSC}$$



- 4. This problem involves the design a buffer to drive 10 pF load with the least delay. Use the C5 process data from the first page, and the approximated switching model of MOSFETs with  $C_{in} = C_{out} = C_{ox}$ .
  - (a) (5 points) Calculate the input capacitance  $(C_{in1})$  and the time-constant  $(\tau)$  of a unit inverter (size 20/10).

$$C_{inj} = Count Conp = 3 Conm = 150 ff$$

$$C_{inv} = 3RC \Rightarrow 3Rn Conn = 3x1lm \times 50 ff$$

$$= 150 fs$$

$$C_{inv} = 150 fs$$

$$C_{inv} = 20/2 priors$$

$$C_{inv} = 20/2 priors$$

$$C_{inv} = 20/2 priors$$

(b) (10 points) Calculate the path effort (F) for a load of 10 pF, and find the number of stages in the buffer for least delay.

Path effort  

$$F = \int_{1}^{C} \cdot \beta \cdot H = H = \frac{C_{L}}{C_{m_{1}}} = \frac{10 pF}{150 gF} = \frac{66.67}{150 gF}$$

$$\int_{N}^{N} = \log_{1}(F) = \frac{\log_{1}(F)}{\log_{1}(F)} = \frac{3.03}{3.03} \xrightarrow{\text{cound s}} 3 \text{ stopes}$$

$$\int_{N}^{N} = \log_{1}(F) = \frac{\log_{1}(F)}{\log_{1}(F)} = \frac{4.055}{4} \text{ slightly off from } f=4.$$
Revise  $f = F^{V_{N}} = (L6.67)^{V_{3}} = \frac{4.055}{4} \text{ slightly off from } f=4.$ 

(c) (5 points) What is the normalized buffer delay (D)? What is the absolute buffer delay  $(t_d)$ ?







5. (15 points) Find the voltages at each of the nodes, A, B, C, D, E and F below. Use the circuit parameters for the 300nm model given on the first page.







6. Consider the NMOS-only inverter shown below. Use the square-law equations and C5 process data from page 1. Show steps for partial credit.





(b) (5 points) Find the voltage levels for output logic high  $(V_{high})$  and low  $(V_{low})$ .



(c) (5 points) Plot the voltage transfer curve (VTC) for the inverter and **clearly** label  $V_{sp}$ ,  $V_{high}$  and  $V_{low}$  values on the curve.



(d) (5 points) Estimate the delays  $t_{pLH}$  and  $t_{pHL}$  for the inverter driving a 100 fF load.

