

ECF 445 - Lecture 13.


Wednesday, February 27, 2019 8:06 AM

①

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{j\omega C}}{1 + \frac{j\omega}{\omega_c}}$$

$$\omega_c = \frac{1}{2\pi RC}$$
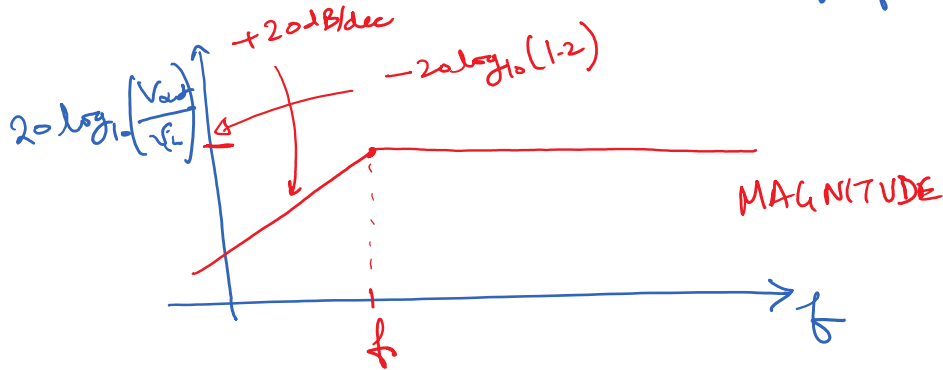
$$\Rightarrow \frac{V_{out}}{V_{in}} = \left(\frac{1}{1.2}\right) \cdot \frac{j\omega/\omega_c}{1 + j\omega/\omega_c}$$



HPF

