 


ECF 445 - Lecture 22

Wednesday, April 17, 2019 8:04 AM


Latches :

SR Latches (NAND)



S	R	Q	$\bar{Q}$	
0	0	1	1	reset
0	1	0	1	} set
1	0	1	0	
1	1	Q	$\bar{Q}$	} previous state



SR Latch (NOR)

 

S	R	Q	$\bar{Q}$	
0	0	Q	$\bar{Q}$	← previous state
0	1	0	1	} set
1	0	1	0	
1	1	0	0	← reset




- * Can design these using CMOS static logic
- * Asynchronous latch (no clock input)



Synchronous Latch $\rightarrow$ CMOS

  

* metastable state $\Rightarrow$ switching point of the inverters

* Crosscoupled inverters

   

  


$$\therefore V_A > V_B$$

$$V_{GS2} > V_{GS1}$$

as time progresses


$$V_{GS2} \gg V_{GS1}$$

* positive feedback


 


$$V_{SG3} > V_{SG4}$$

M3 is stronger

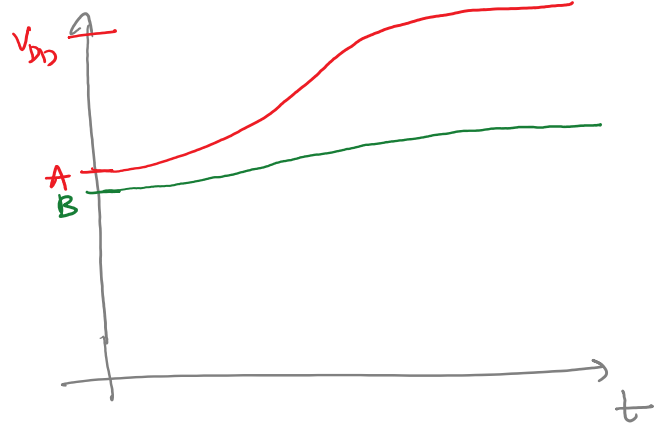


  * Combining the cross coupled NMOS & PMOS together



known as Sense amplifiers in the context of memory ICs

* Core component of analog comparators

 

* Regenerative Latch

↳ regenerate the levels back

↳ positive feedback

↳ very fast circuit


↳ a key component of comparators

* minimum value of ΔV which can be resolved
 ↳ resolution of the latch



Too small a value of $\Delta V \rightarrow$ metastability
 ↳ takes long time of resolve

* To avoid meta stability.

 
- ① Use clean logic levels
- ② increase gain of the inverters $\Rightarrow$ use longer lengths $\Rightarrow$ more stages




- ③ Add a switch

  

 
ϕ & $\bar{\phi}$ are non-overlapping clocks.



apply the input



 


regeneration

 

* The feedback inverter is not fighting the input driver
 $\hookrightarrow$ avoids metastability

Level-sensitive Latch

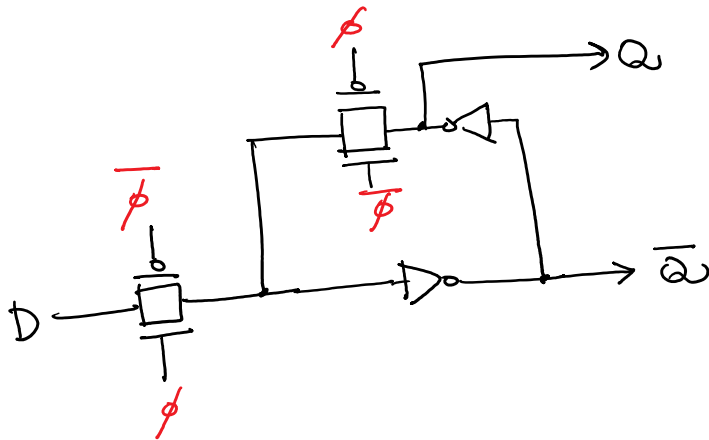  


When $\phi = 1 \Rightarrow D$ is stored on $\bar{Q}$
 When $\phi \Rightarrow \bar{\phi} = 1 \Rightarrow$ input D is "latched"
 $\hookrightarrow$ regenerated in the cross-coupled latch

* Clock Edge-triggered digital circuits are more robust to glitches.

Edge-triggered Flip Flop

 ↳ registers input on rising (or falling) edges of the clock as opposed to the level of the clock.



When $\phi = 0 \Rightarrow$ first stage tracks the input (D) $\rightarrow$ Master is transparent & Slave is opaque



Second stage holds the previous output (Q)

When ϕ goes from 0 to 1 $\Rightarrow$ first stage captures the input and transfers to the second stage


* The value of D at the instance when ϕ has a rising edge is captured. In other instances in

↳ value of D at any time when $\phi=1$ is immaterial

⇒ Positive Edge-triggered flip-flop

  

← Master Latch → ← Slave Latch →

 

determines the triggering edge

