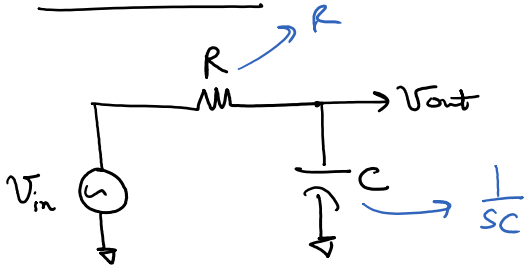


ECE 445- Lecture 2

Monday, January 14, 2019 8:01 AM

RC Circuits:



$$\frac{V_{out}}{V_{in}}(s) = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{1 + sRC}$$

$$= \frac{1}{1 + sRC}$$

1st-order Transfer function

$$\tau = RC$$

$$\omega_{3dB} = \frac{1}{\tau} \quad \text{Bandwidth}$$

frequency Response:

$$H(s) = \frac{1}{1 + sRC} = \frac{1}{1 + \frac{s}{\omega_{3dB}}}$$

Single-pole

$$s \leftarrow j\omega$$


$$H(j\omega) = \frac{1}{1 + j\frac{\omega}{\omega_{3dB}}}$$


$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_{3dB}}\right)^2}}$$

$$\angle H(j\omega) = -\tan^{-1}\left(\frac{\omega}{\omega_{3dB}}\right)$$

Bode Plots

$$\begin{aligned} H(j\omega) &= \frac{1}{(1 + j\frac{\omega}{\omega_{3dB}})} \cdot \frac{(1 - j\frac{\omega}{\omega_{3dB}})}{(1 - j\frac{\omega}{\omega_{3dB}})} \\ &= \frac{(1 - j\frac{\omega}{\omega_{3dB}})}{1 + \left(\frac{\omega}{\omega_{3dB}}\right)^2} \\ \angle &= \tan^{-1}\left(\frac{y}{x}\right) = \tan^{-1}\left(\frac{-\frac{\omega}{\omega_{3dB}}}{1}\right) \\ &= \tan^{-1}\left(-\frac{\omega}{\omega_{3dB}}\right) = -\tan^{-1}\left(\frac{\omega}{\omega_{3dB}}\right) \end{aligned}$$

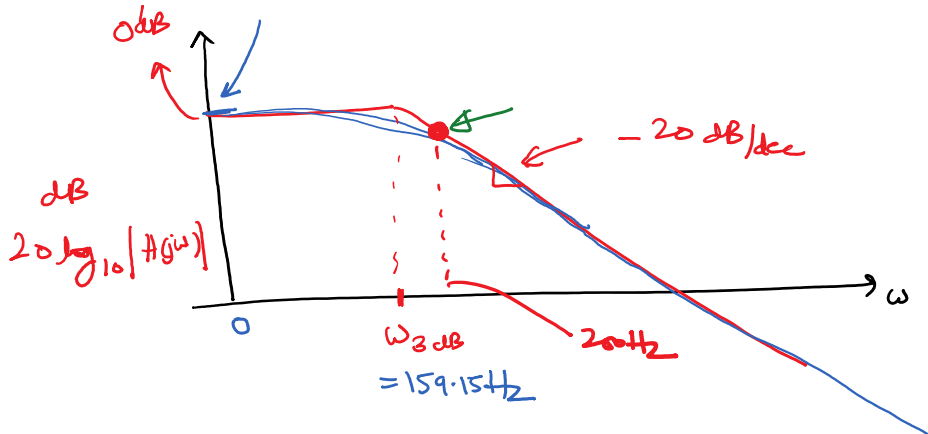

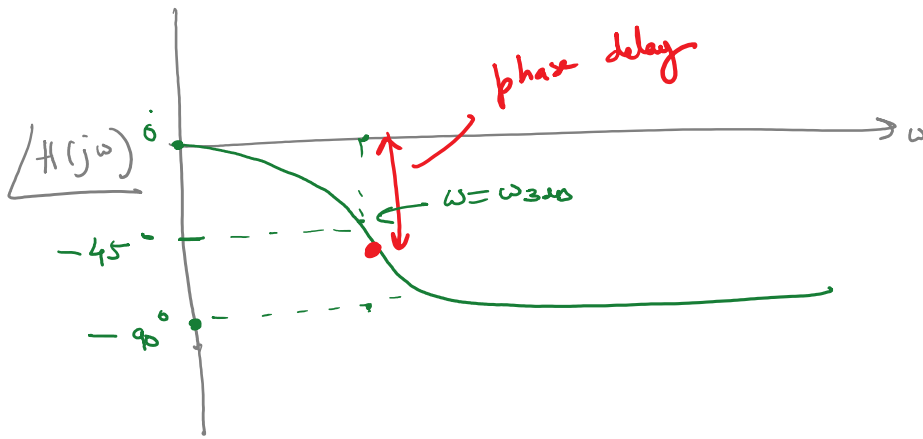

$$-\tan^{-1}\left(\frac{\omega}{\omega_{3dB}}\right)$$

Let $R = 1k\Omega$, $C = 1\mu F$

$$\omega_{3dB} = \frac{1}{RC} \quad \leftarrow \text{rad/s}$$


$$f_{3dB} = \frac{\omega_{3dB}}{2\pi} = \frac{1}{2\pi RC} \quad \leftarrow \text{Hz}$$

$$= 159.155 \text{ Hz}$$

$$f_{in} = 200 \text{ Hz}$$

$$\text{Amplitude} = 1V$$

$$V_{in} = 1 \cdot \sin(2\pi f_{in} t)$$

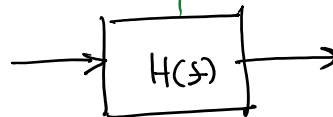

$$H(j\omega) = \frac{1}{1 + j\frac{\omega}{\omega_{3dB}}}$$

$$H(f) = \frac{1}{1 + j\frac{f}{f_{3dB}}}$$

$$\omega \rightarrow 2\pi f$$

$$= |H(f_{in})| \cdot \sin\left(2\pi f_{in} t + \angle H(f_{in})\right)$$

$$|H(f_{in})| = \frac{1}{\sqrt{1 + \left(\frac{f_{in}}{f_{3dB}}\right)^2}} = \frac{1}{\sqrt{1 + \left(\frac{200}{159.15}\right)^2}} = \underline{0.623}$$

-ve sign shows lag


$$\angle H(f_{in}) = -\tan^{-1}\left(\frac{200}{159.15}\right) = \underline{-0.898 \text{ rad}}$$

$$\angle H(f_{in}) = -\tan^{-1}\left(\frac{200}{159.15}\right) = \underline{-0.898 \text{ rad}}$$

⇒ output is lagging the input
by 0.898 rad

$$\rightarrow \left(\frac{0.898}{\pi}\right) 180^\circ = \underline{\underline{51.5^\circ \text{ lag}}}$$
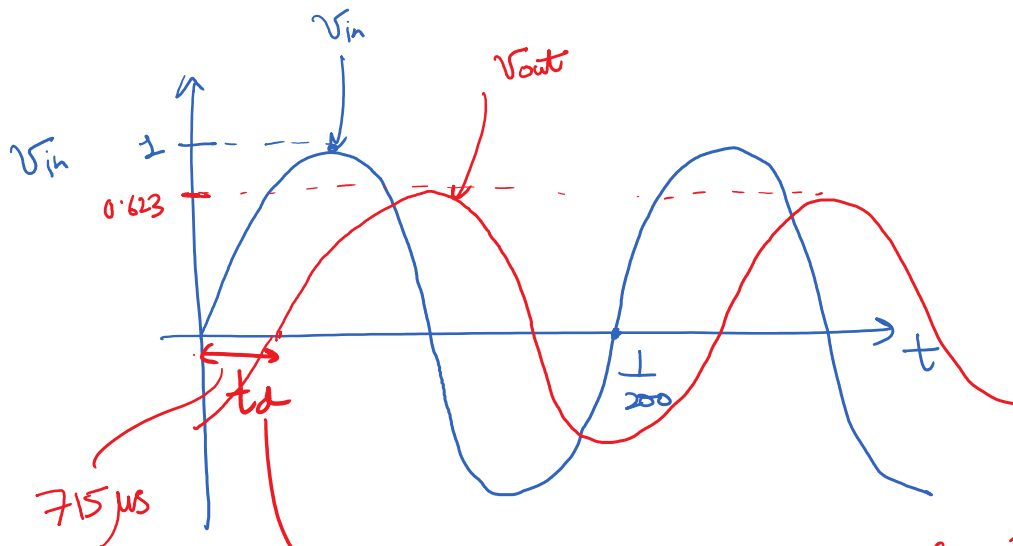
$$\left(\frac{\text{radians}}{\pi}\right) \times 180^\circ = \text{degrees}$$






output lags the input

715 μs

$$\text{time delay, } t_d = \left(\frac{\Delta\theta}{360^\circ}\right) T$$

$$= \frac{-51.5^\circ}{360^\circ} \times \left(\frac{1}{200 \text{ Hz}}\right)$$


$$= -715 \mu\text{s}$$

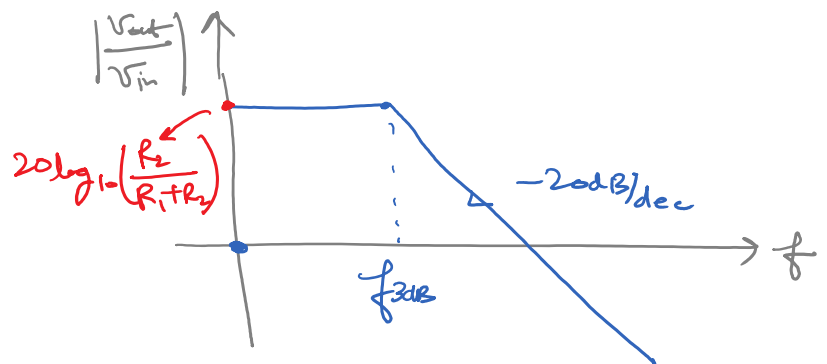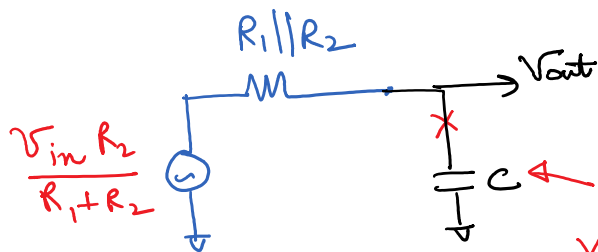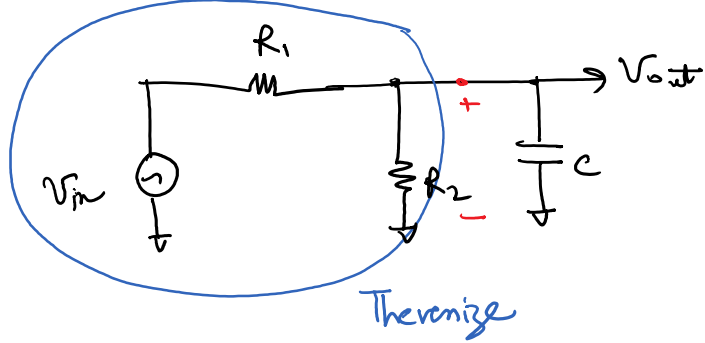

$$X_c = \frac{1}{j\omega C} \rightarrow \infty \text{ at DC}$$


Capacitor is open at DC

$$f_{3dB} = \frac{1}{2\pi(R_1 || R_2)C}$$

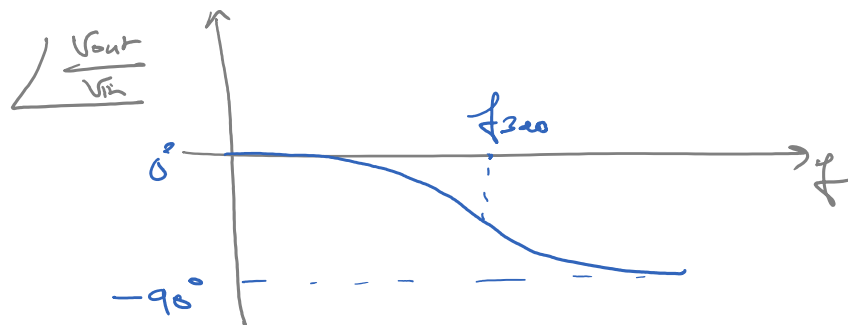


Transient Response of an RC Circuit :

plot V_{out}

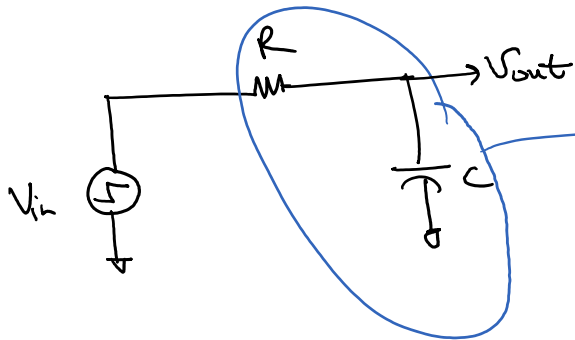
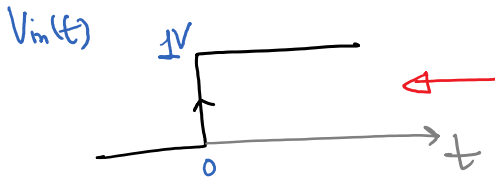
$$H(s) = \frac{1}{1 + \frac{s}{\omega_{3dB}}} = \frac{1}{1 + s\tau}$$



$V_{in}(t) = 1 \cdot u(t)$ $\longleftrightarrow \frac{1}{s}$

Step function

$$V_{out}(s) = H(s) \cdot V_{in}(s)$$

$$= \frac{1}{(1 + \frac{s}{\omega_{3dB}})} \cdot \frac{1}{s}$$

partial fraction

$$= \frac{1}{s} - \frac{\frac{1}{\omega_{3dB}}}{(1 + s/\omega_{3dB})}$$

$$= \frac{1}{s} - \frac{1}{s + \omega_{3dB}}$$


go back to the time domain

$$v_{out}(t) = u(t) - e^{-\omega_{3dB} t} \cdot u(t)$$

+L1

$$\begin{aligned}
 V_{out}(t) &= u(t) - e^{-\omega_{3dB} t} \cdot u(t) \\
 &= (1 - e^{-\omega_{3dB} t}) \cdot u(t) \triangleq (1 - e^{-t/\tau}) \cdot u(t)
 \end{aligned}$$
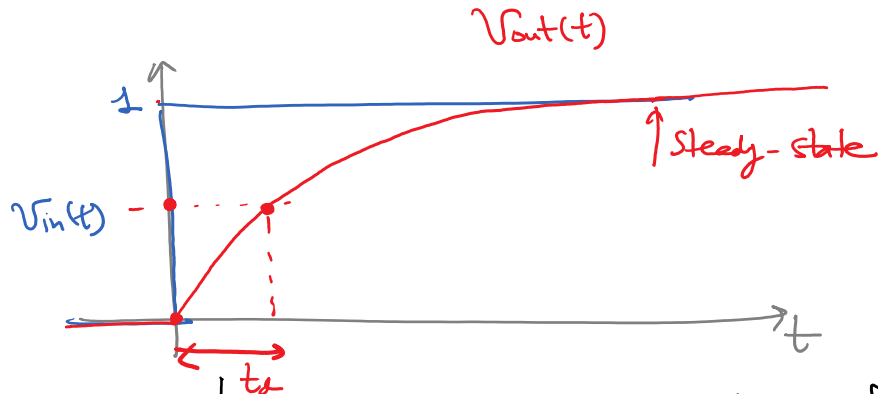
$$V_{out}(t) = 1 \cdot (1 - e^{-t/\tau}) u(t) \leftarrow$$



\hookrightarrow 50% delay \rightarrow time taken for the output to reach 50% of its final value.

\hookrightarrow propagation delay, t_d

$$V_{out}(t) = V_0 (1 - e^{-t/\tau}) u(t)$$

$$\text{@ } t = t_d \Rightarrow V_{out}(t_d) = \frac{V_0}{2}$$

$$\frac{V_0}{2} = V_0 (1 - e^{-t_d/\tau})$$

$$\Rightarrow e^{-t_d/\tau} = \frac{1}{2}$$

$$\Rightarrow -\frac{t_d}{\tau} = \ln\left(\frac{1}{2}\right) = -\ln(2)$$


$\tau = \frac{t_d}{\ln(2)}$

$\tau = 1.44 \cdot t_d$

$$\Rightarrow \boxed{t_d = \tau \ln(2)}$$

$$\ln(2) = 0.7$$



$$t_d = 0.7 \tau = \boxed{0.7 RC}$$

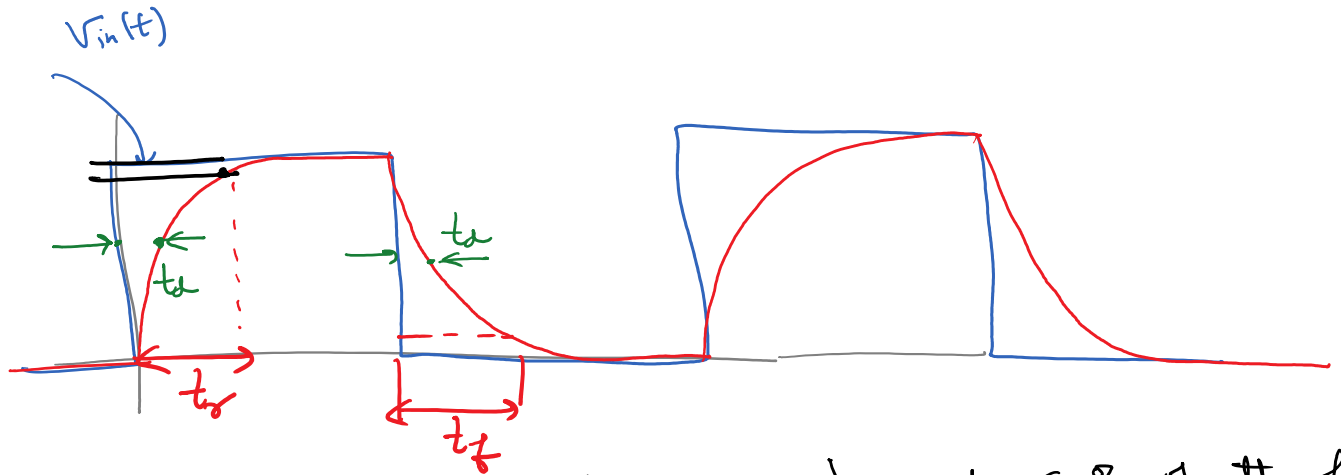

90% rise time \Rightarrow time taken to reach 90% of the final output

$$t_r = \underline{\underline{2.2 \tau}} = 2.2 RC$$

Chapter 2 : N-well :

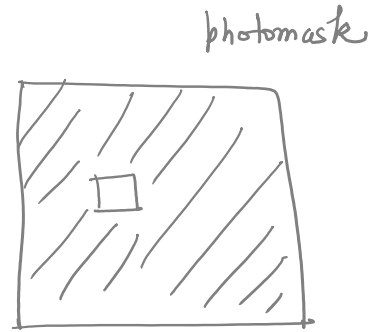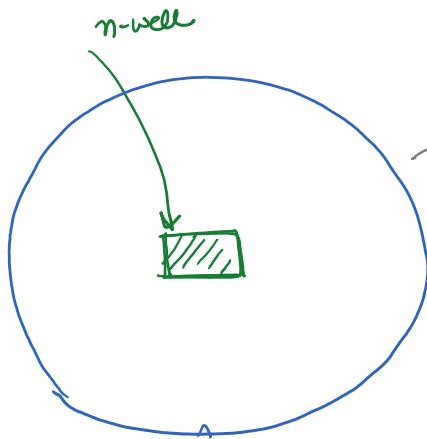


dark field

Photolithography

p-doped Silicon (p-si)

photoresist

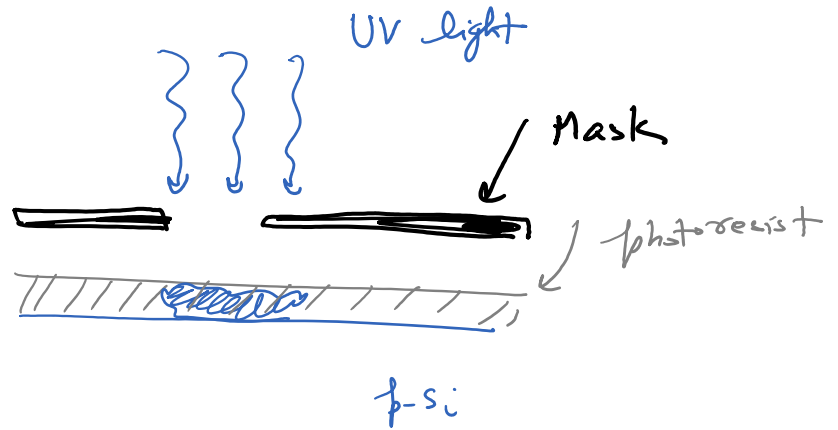


developed the photoresist

Ion Implant

Implant with n-type dopants

⇒ P, As

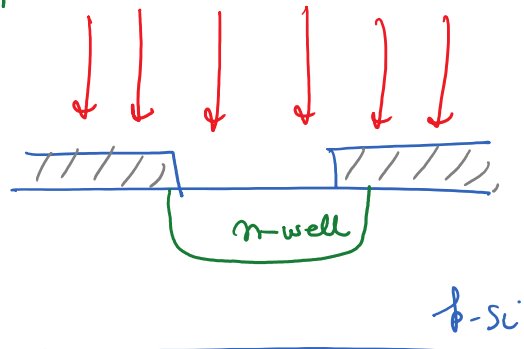


PMOS



/ h.h.

NMOS

/ h.h.


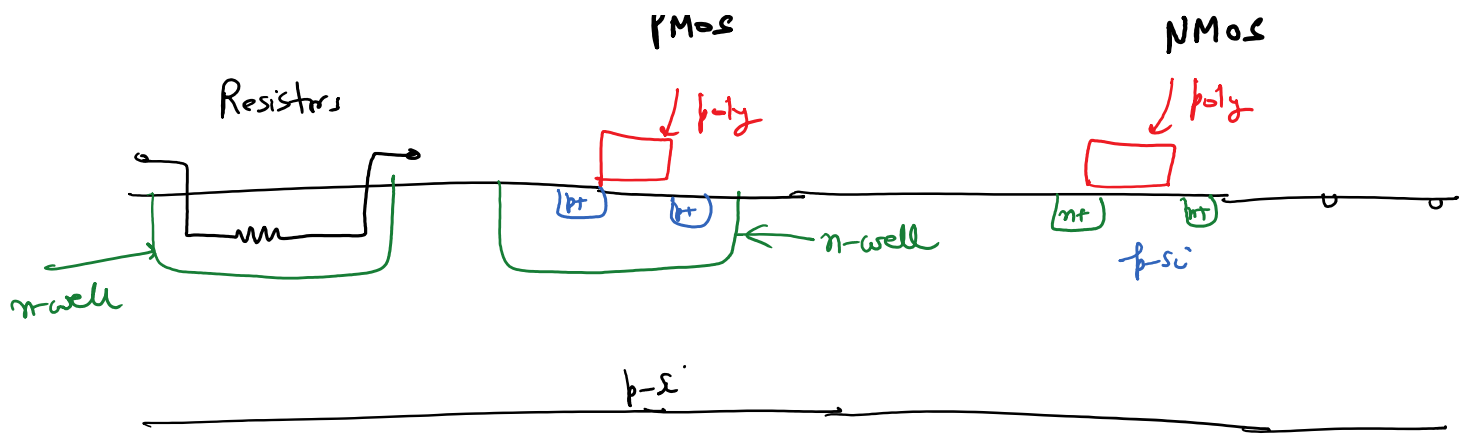


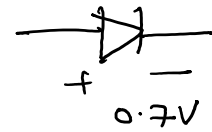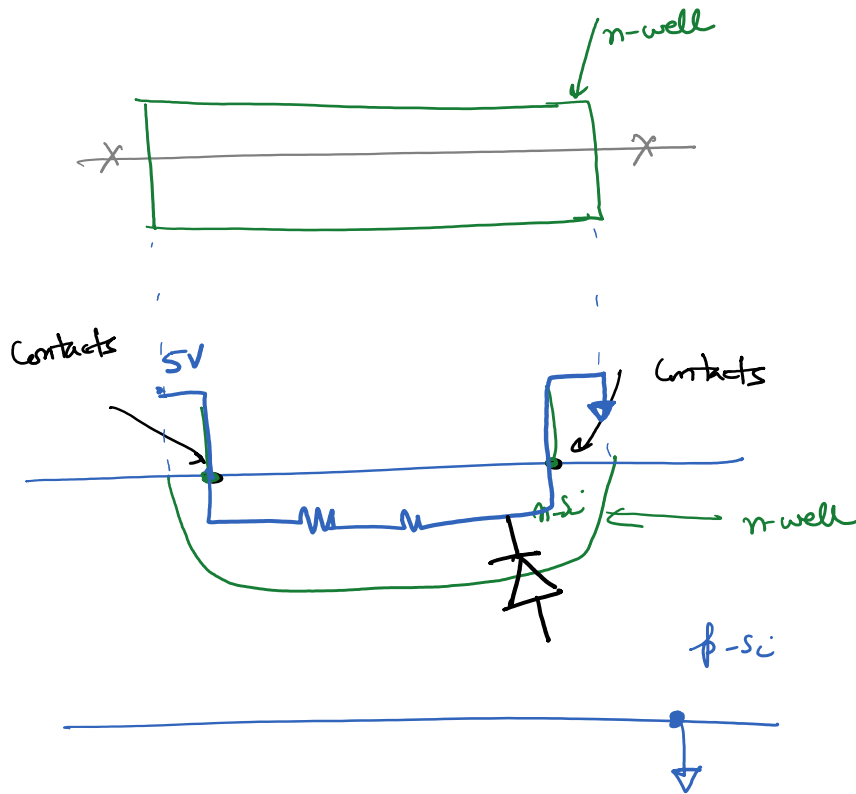N-well \rightarrow fabrication of p-channel MOSFETs (PMOS)
n-well resistors



n-well diode turns on only for $V_A < -0.7V$

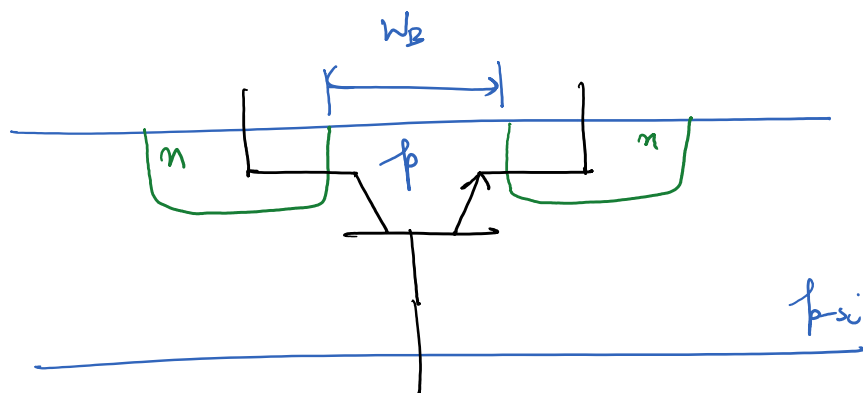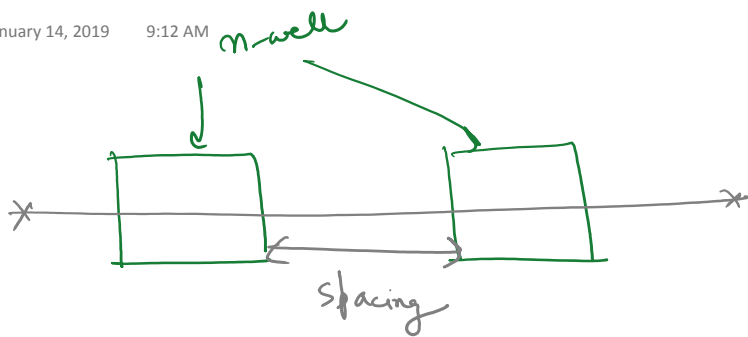in CMOS technology \Rightarrow "typically" positive voltages are employed and the p-substrate is connected to the lowest potential on the chip i.e. ground.



x parasitic npn BJT
is formed