



$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{1 + sRC} = \frac{1}{1 + \frac{s}{10^5}} = \frac{10^5}{s + 10^5}$$

$$V_o(s) = H(s)V_i(s) = \left(\frac{10^5}{s + 10^5} \right) \left(\frac{10^5}{s^2 + (10^5)^2} \right)$$

with partial fraction expansion

$$V_o(s) = \frac{\frac{1}{2}}{s + 10^5} - \frac{\frac{1}{2}s}{s^2 + (10^5)^2} + \frac{\frac{1}{2}(10^5)}{s^2 + (10^5)^2}$$

with inverse Laplace Transform

$$v_o(t) = \frac{1}{2}e^{-10^5 t} - \frac{1}{2}\cos(10^5 t) + \frac{1}{2}\sin(10^5 t) = \frac{1}{2}e^{-10^5 t} + \frac{1}{\sqrt{2}}\sin(10^5 t - 45^\circ)$$

We can decompose the output into it's transient and steady - state response

$$v_o(t) = \frac{1}{2}e^{-10^5 t} + \frac{1}{\sqrt{2}}\sin(10^5 t - 45^\circ) = v_{tr}(t) + v_{ss}(t)$$

$$v_{tr}(t) = \frac{1}{2}e^{-10^5 t}$$

$$v_{ss}(t) = \frac{1}{\sqrt{2}}\sin(10^5 t - 45^\circ)$$

