

Homework 4

ECE 5/404 – PLL and High-Speed Link Design

Note: Use Cadence schematic capture and Spectre simulation tools, available on the AMS servers for the homework problems. Use TSMC 180nm models with $V_{DD} = 1.8\text{ V}$.

Problem 1- Type-II PLL Design

A Type-II charge-pump PLL needs to be designed to generate $f_{out} = 500\text{ MHz}$ clock frequency from a $f_{ref} = 50\text{ MHz}$ reference. Assume that the VCO has a free running frequency of $f_{c0} = 400\text{ MHz}$ and a linearized gain $K_{VCO} = 300 \frac{\text{MHz}}{\text{V}}$ around the input bias point of $V_c = 0.9\text{ V}$.

1. Select a loop bandwidth ($\omega_{u,loop} < \frac{\omega_{ref}}{10}$). Give at least two reasons for this design constraint.
2. Design the loop for a 60° phase margin. What are the closed-loop natural frequency (ω_n) and damping factor (ζ) for this design?
3. Sketch incremental phase domain model of the PLL. Plot open- and closed-loop frequency responses as well as the transient step response and properly label them.
4. Choose appropriate values for the charge-pump current (I_0) and the loop-filter components? Sketch circuit-level schematic for the PLL.
5. Using a behavioral model¹, perform transient simulation of the PLL and demonstrate locking (plot the VCO control voltage, v_c , and the VCO frequency, f_{VCO}). Does the transient settling behavior of the PLL correspond to the results in part 3? Explain.
6. In part 5, apply a frequency step of $\delta f = 1\text{ MHz}$ and show PLL locking. Comment on the settling response.

Bonus points: Plot spectrum (using FFT) of the VCO output in the steady-state. Study the PLL settling response for different phase margin values (45° and 72°).

¹Add the following line entry to your cds.lib and look at the example schematic PLL1. Make a local copy of the library before starting your work.

DEFINE PLL_Design /home/vsaxena/ece504/PLL_Design