

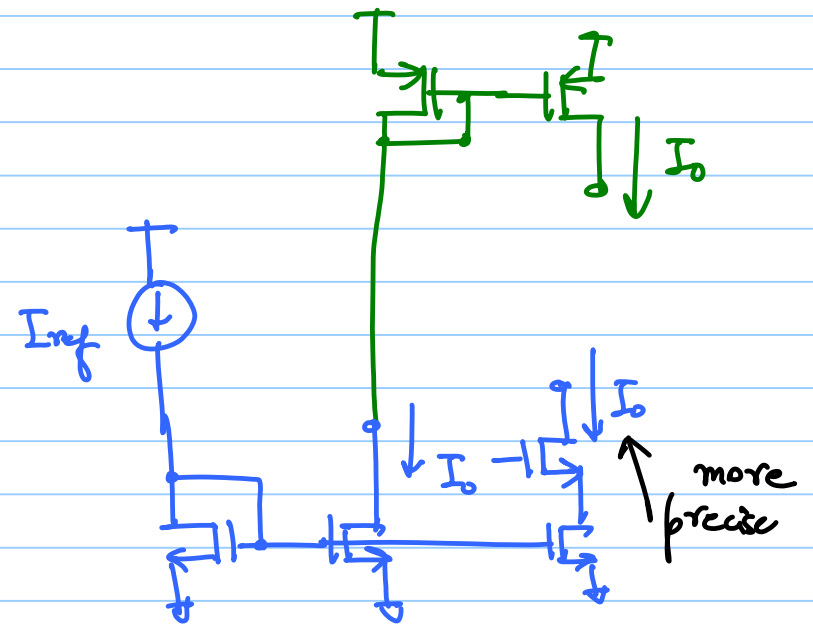
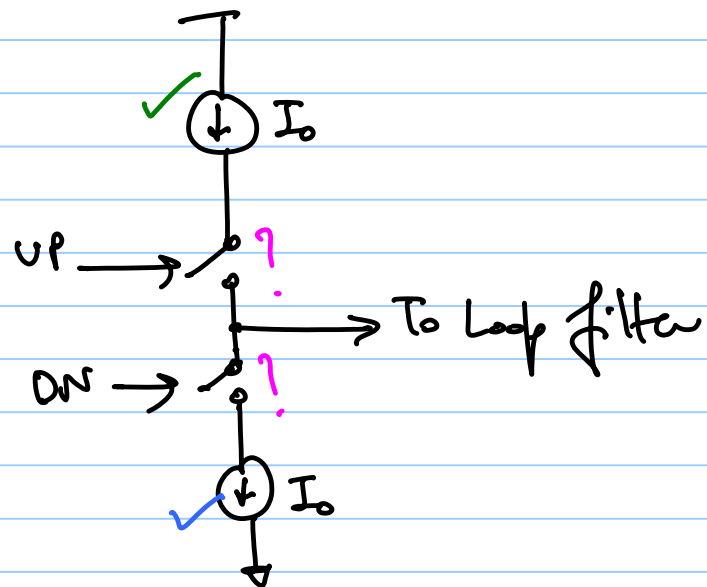
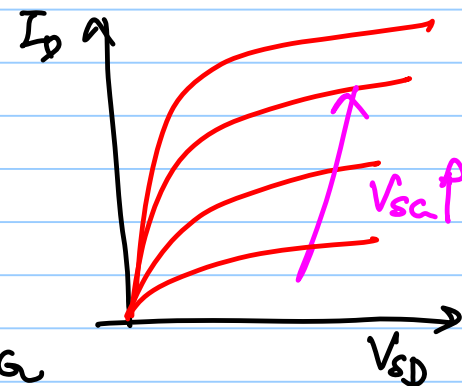
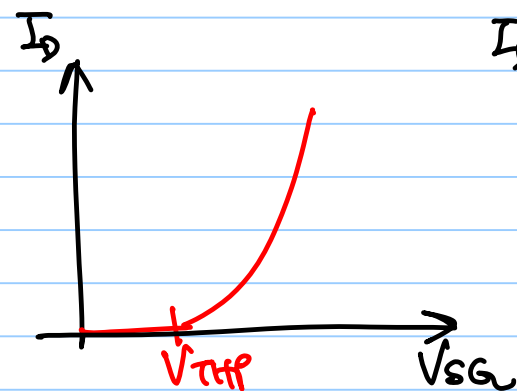
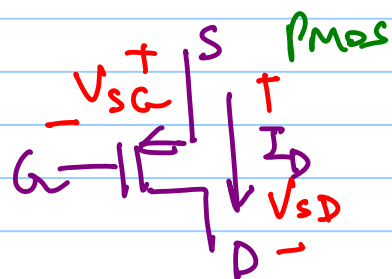
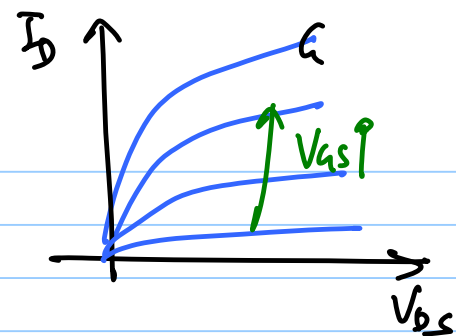
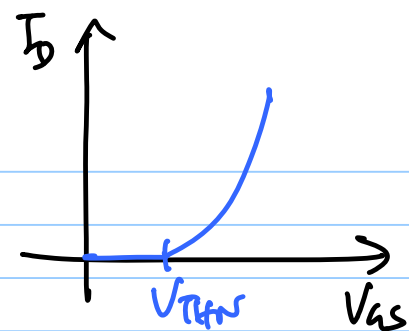



ECE 504- Lecture 11


Note Title

9/28/2016

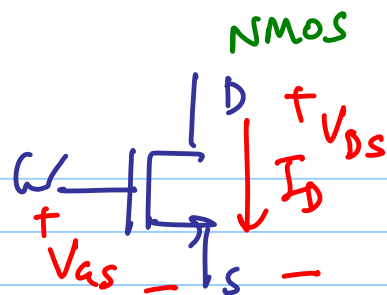


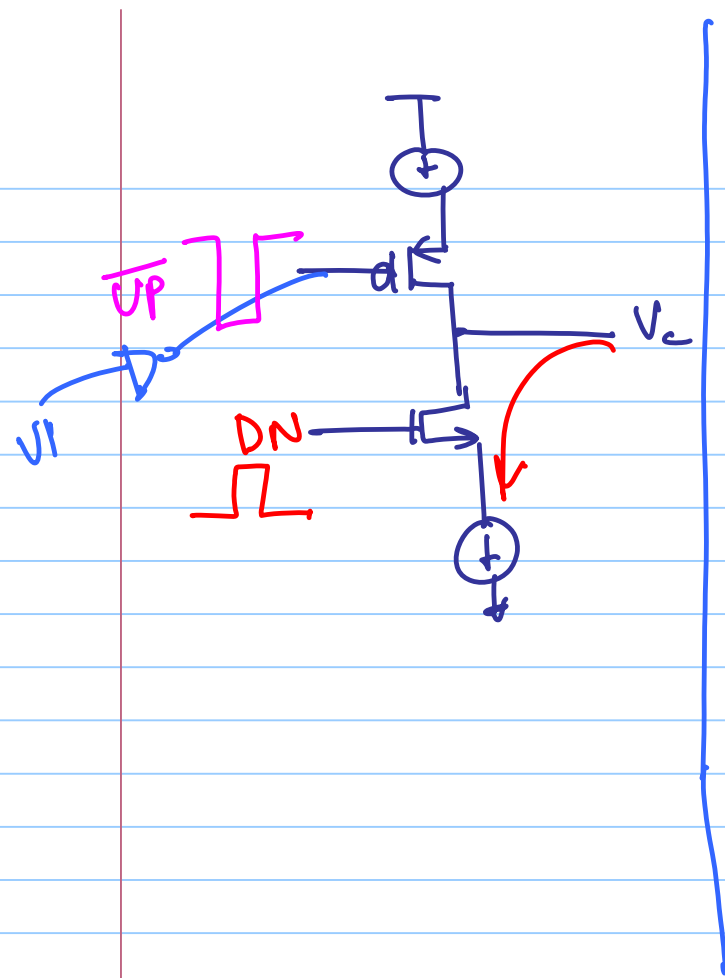

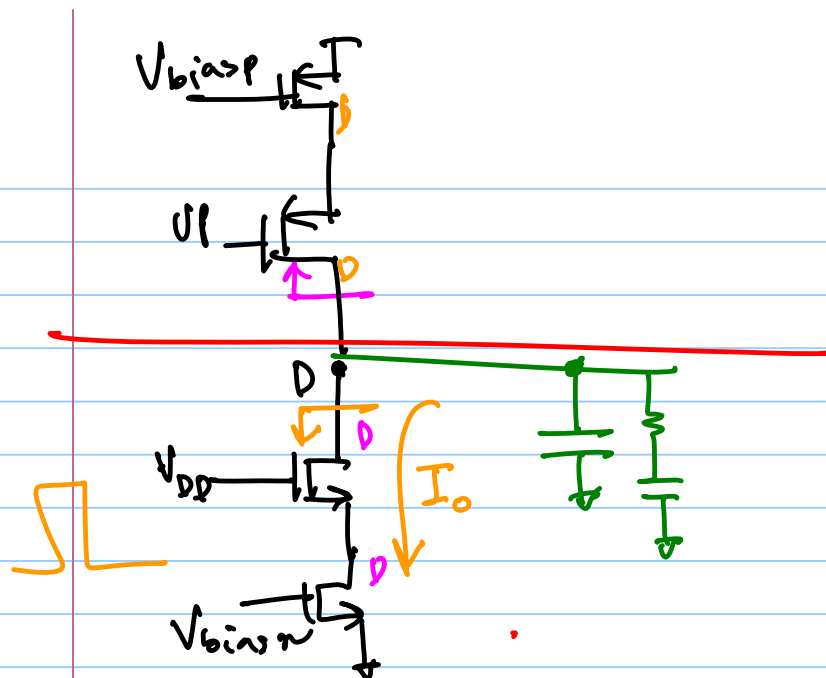




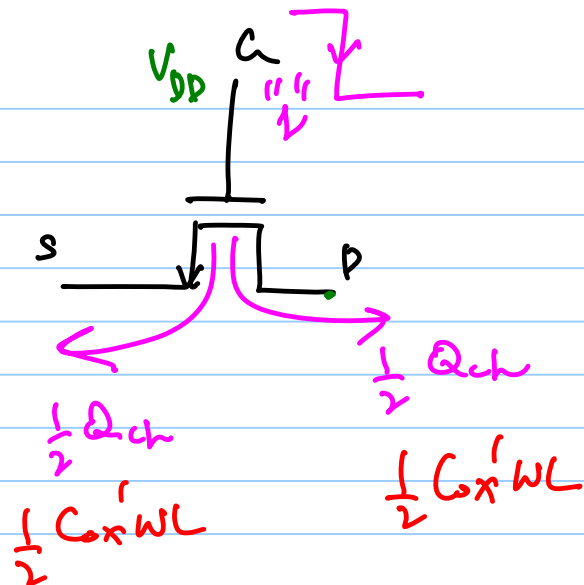


"Charge injection"

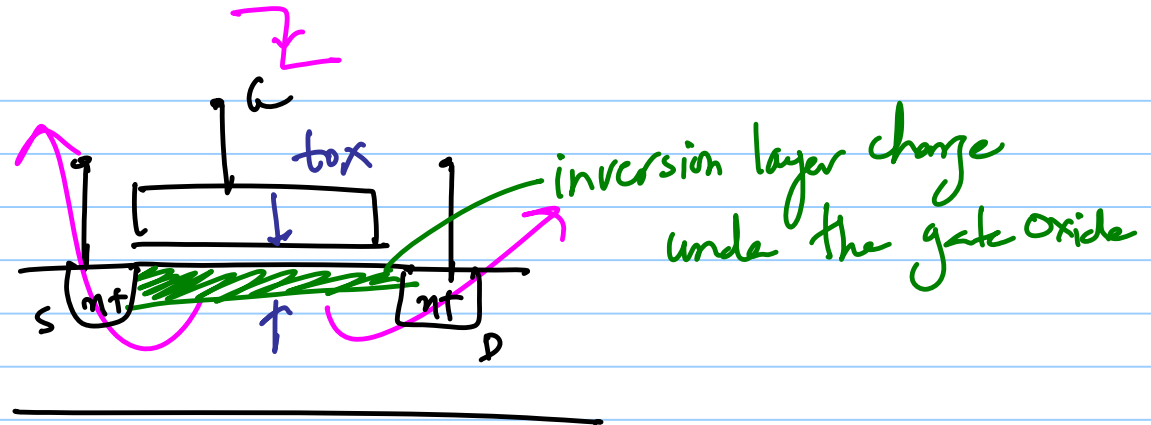

$$Q_{ch} = C_{ox}'WL$$

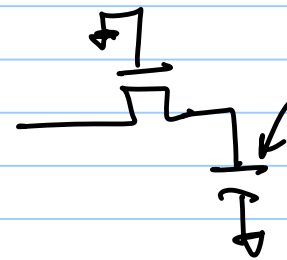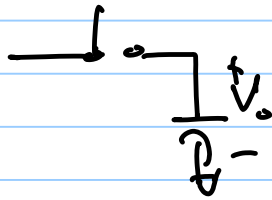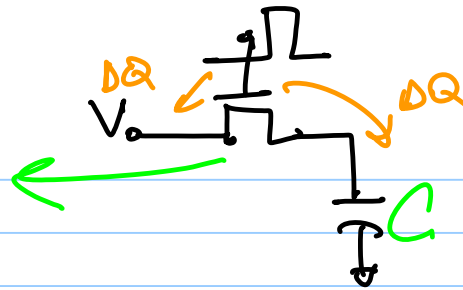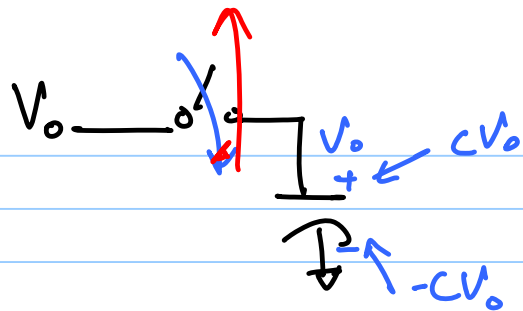
$\downarrow$ $\frac{\epsilon_0 \epsilon_{oxide}}{t_{ox}}$



$$Q = CV_o - \frac{1}{2}C_{ox}'WL$$



$$V_{final} = \frac{Q}{C} = V_o - \frac{1}{2} \frac{C_{ox}'WL}{C}$$




switched-capacitor circuits

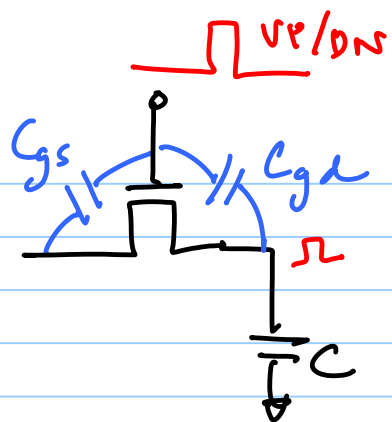

clock feedthrough



parasitic capacitances

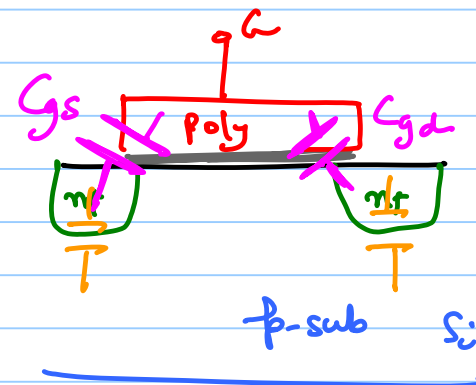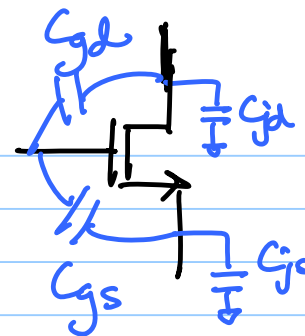

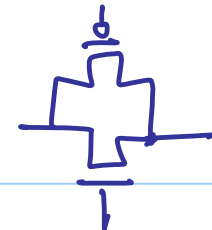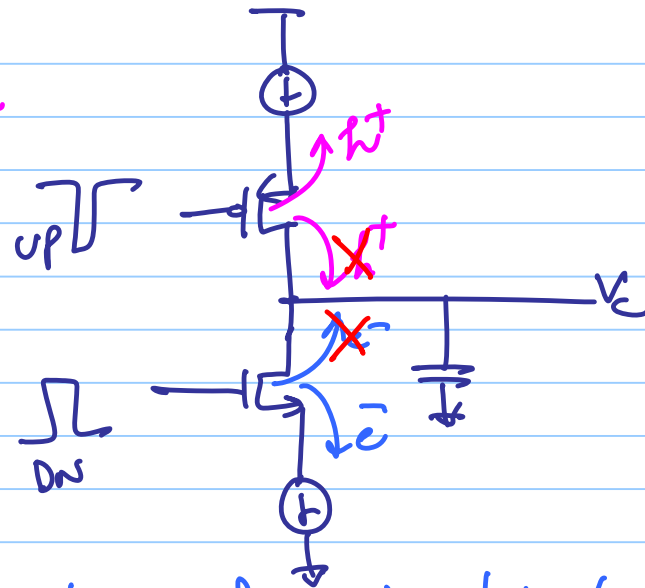
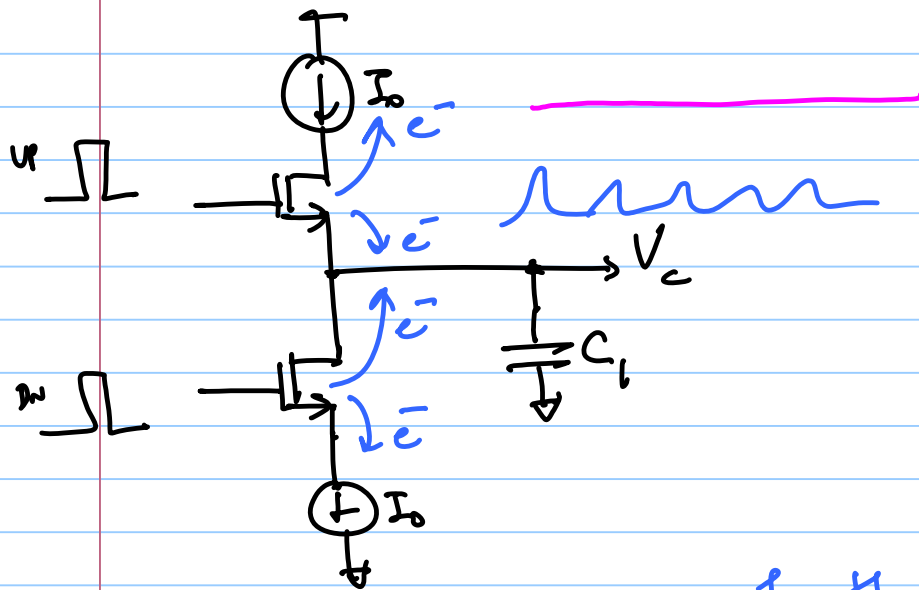


$\times$ if the # of holes injected $\neq$ # of e^- injected
 $\hookrightarrow V_c$ is disturbed

clock-feedthrough

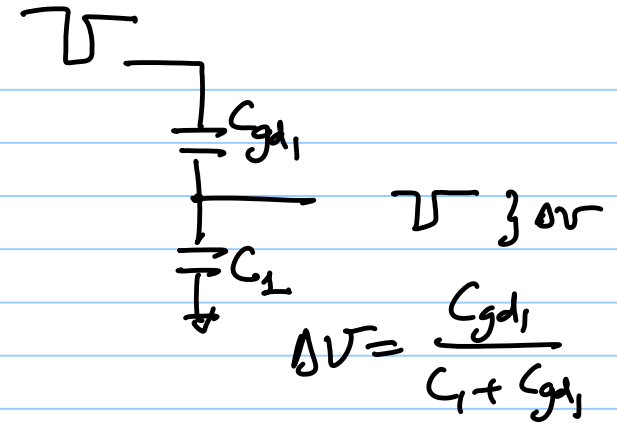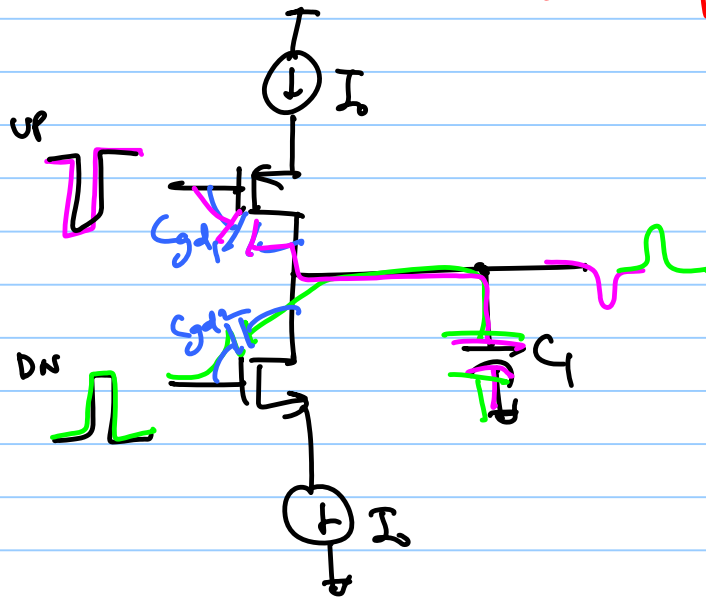


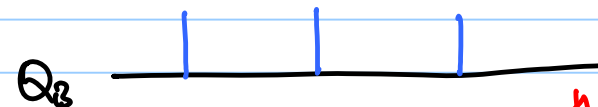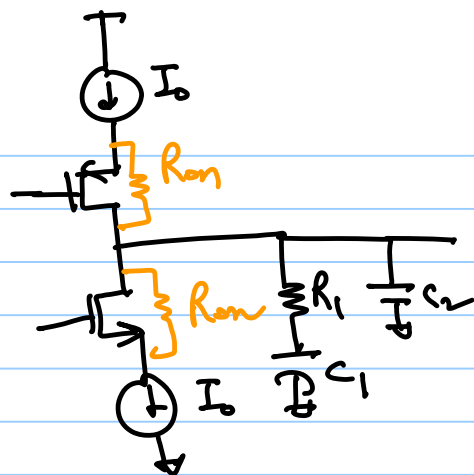* clock feedthrough: UP & DN pulses couple through C_{gd1} & C_{gd2} respectively and reach V_c



$\Delta\phi = 0$

Ideally when the PLL is locked



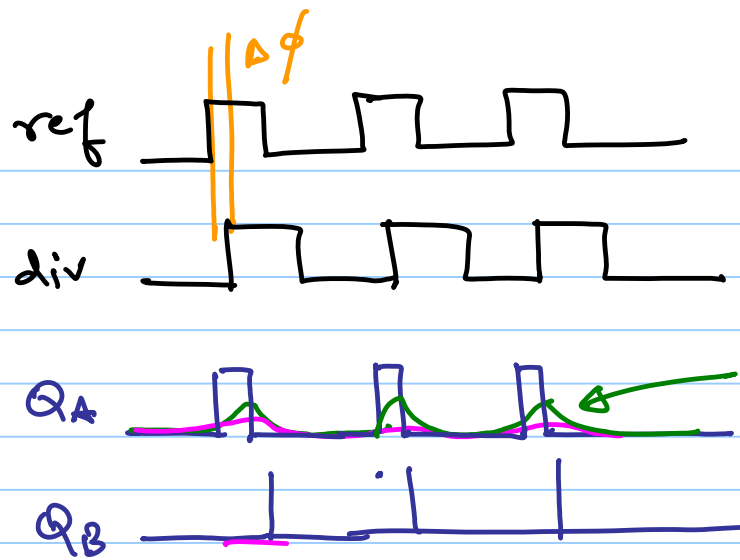



$\Delta\phi > 0$, small value

Limited RC time constants

for small $\Delta\phi \Rightarrow$ the charge pump switches fail to turn on

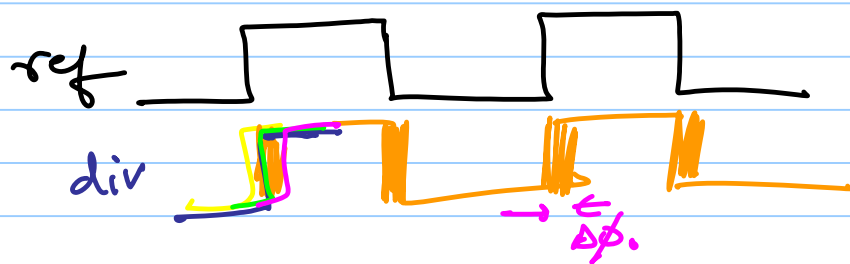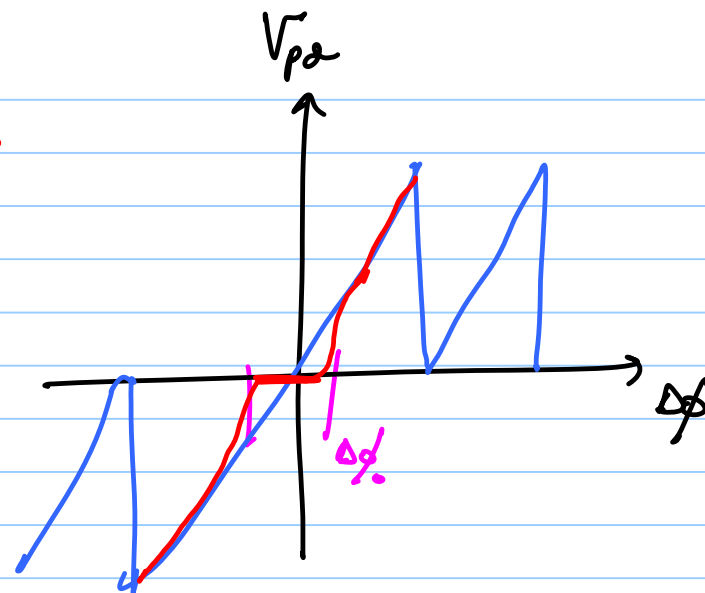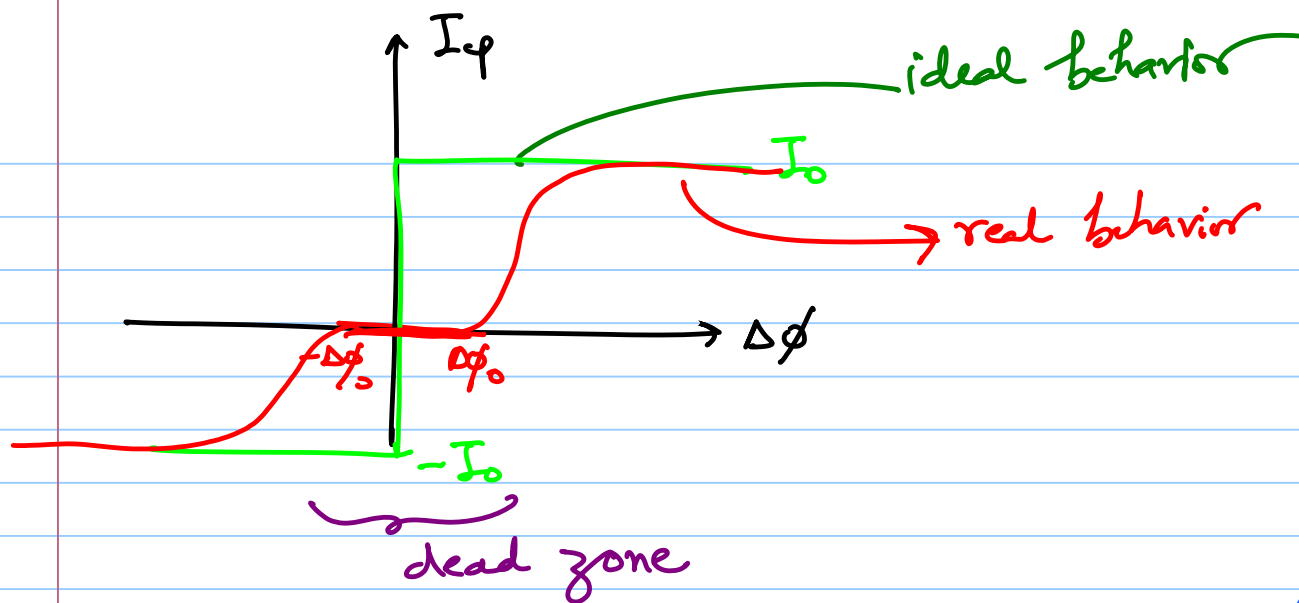$\Rightarrow I_{cp} = 0$ for some $\Delta\phi < \Delta\phi_0$



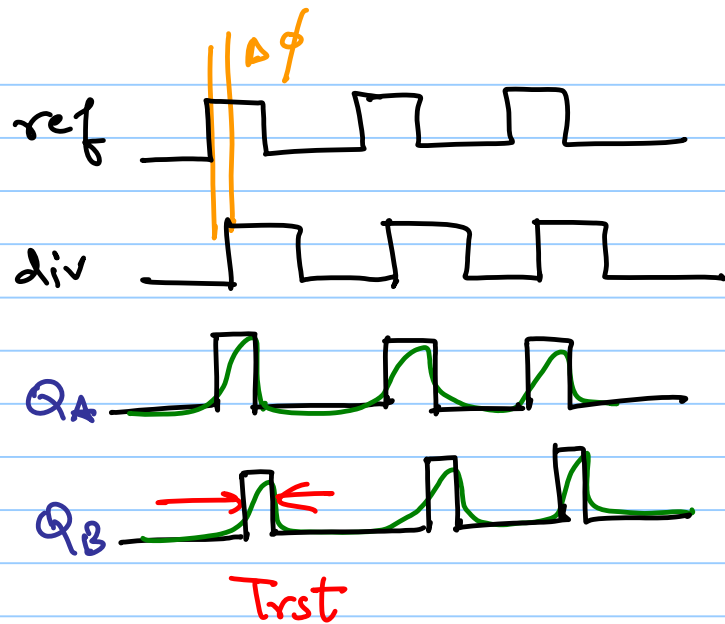

Enforce a finite reset
pulse width (T_{rst})

* PFD/cf suffers from a dead
zone around zero & equal to
 $\pm \Delta\phi_0$

↳ dead zone allows the V_{CO} to
accumulate as much phase
error as $\Delta\phi_0$, as there is no
corrective feedback. → **Jitter**

* But if we use coincident pulses on Q_A & Q_B , we can eliminate the dead zone

$$\Delta\phi = 0$$

