

ECE 504 - Lecture 14

Note Title

10/10/2016

Cadence

↳ Post poll on

Piazza

↳ Skype

Midterm Exam

Oct 31, Monday

in class

↳ closed Book/note/PC


* Cheat sheet A4 size
both sides

* Sample Exam Upload

Oscillators Basics!

LTI

NL + TV

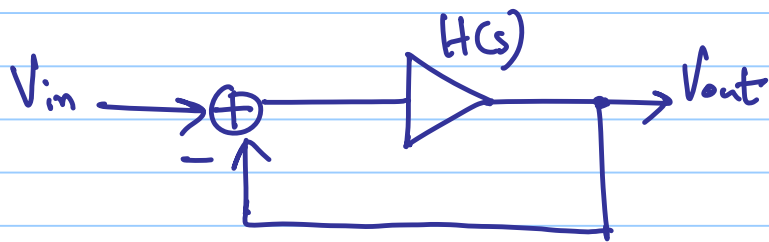

loop-gain

$$L(s) = H(s) \\ \therefore K=1$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{H(s)}{1 + L(s)}$$

" Small-signal understanding "




for oscillate at $s = j\omega_0$, we require
 $L(j\omega_0) = -1 \Rightarrow$

$$\Rightarrow |L(j\omega_0)| = 1 \quad \& \quad \angle L(j\omega_0) = -180^\circ$$

in this case

$$\Rightarrow \text{closed-loop gain} = \infty$$

noise at ω_0

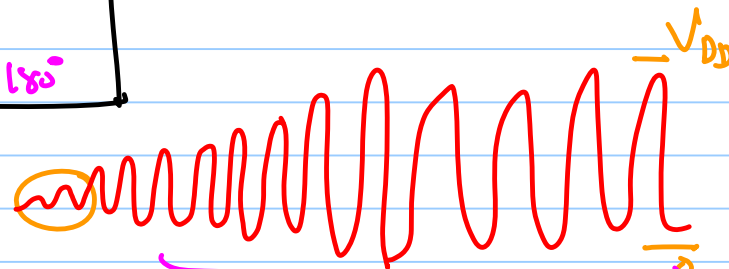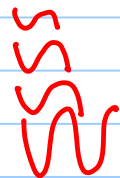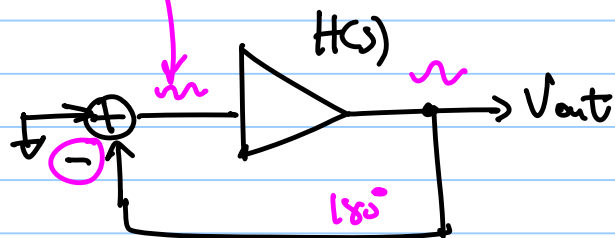


large signal behavior


$|L(j\omega_0)| = -1$ is necessary but not sufficient

↳ typically we choose the loop gain
 $|L(j\omega_0)|$ at least 2 or more

Common Source Amp.

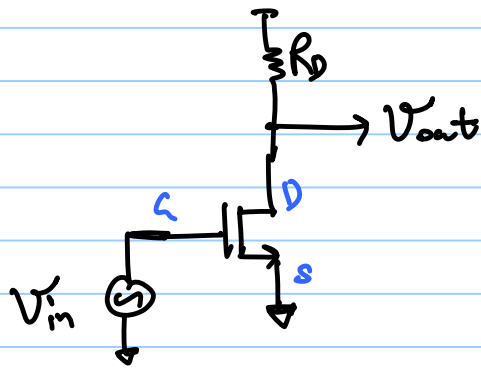

Small-signal
picture of the
amplifier

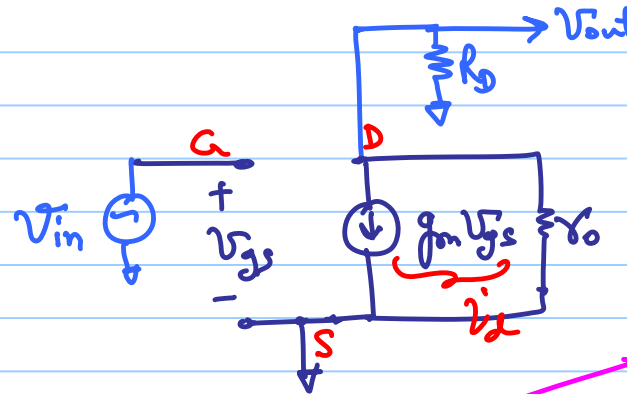

$$V_{out} = -i_x (r_o \parallel R_D)$$


$$= -g_m (r_o \parallel R_D) V_{in}$$



$$i_x + \frac{V_{out}}{R_D \parallel r_o} = 0$$

$$\Rightarrow V_{out} = -i_x (R_D \parallel r_o)$$

$$g_m V_{gs} = g_m V_{in}$$

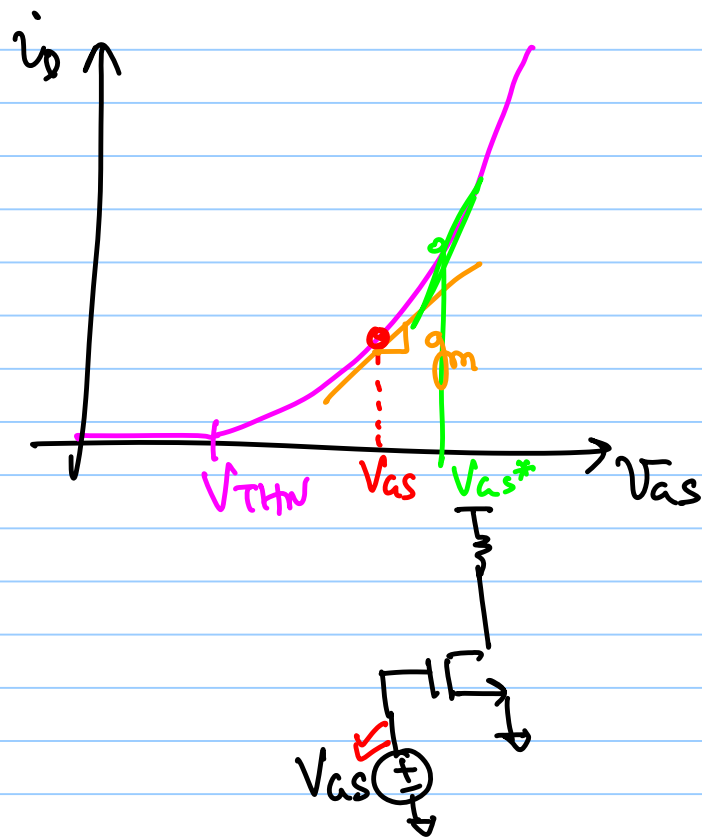

$$A_v = \frac{v_{out}}{v_{in}} = -g_m (R_D || r_o) \quad ??$$

$$\approx -g_m R_D$$

$$R_D \ll r_o$$

trans conductance

$$g_m = \left. \frac{\partial i_D}{\partial V_{GS}} \right|_{V_{GS} = V_{GS}^*}$$

Bias-point

$g_{m, sat}$

$$i_D = \frac{K_p}{2} \frac{W}{L} (V_{GS} - V_{THN})^2$$


, $\lambda = 0$

$$\frac{\partial i_D}{\partial V_{GS}} = K_p \frac{W}{L} (V_{GS} - V_{THN})$$


$$g_m = \left. \frac{\partial i_D}{\partial V_{GS}} \right|_{V_{GS} = V_{GS}}$$

$$\Rightarrow g_m = \underbrace{K_p \frac{W}{L}}_{\mu_n C_{ox}} (V_{GS} - V_{THN}) = \beta V_{ov}$$


overdrive voltage, V_{ov}

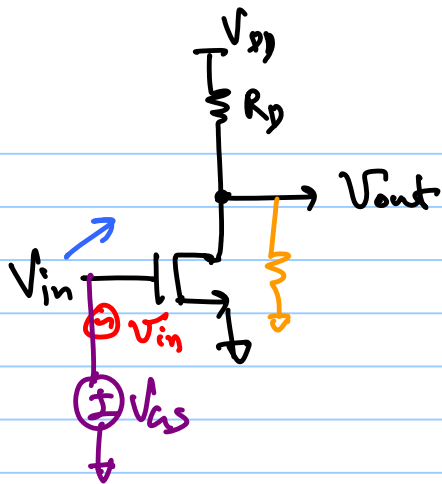

* Looks like an
inverter from large
signal point of view

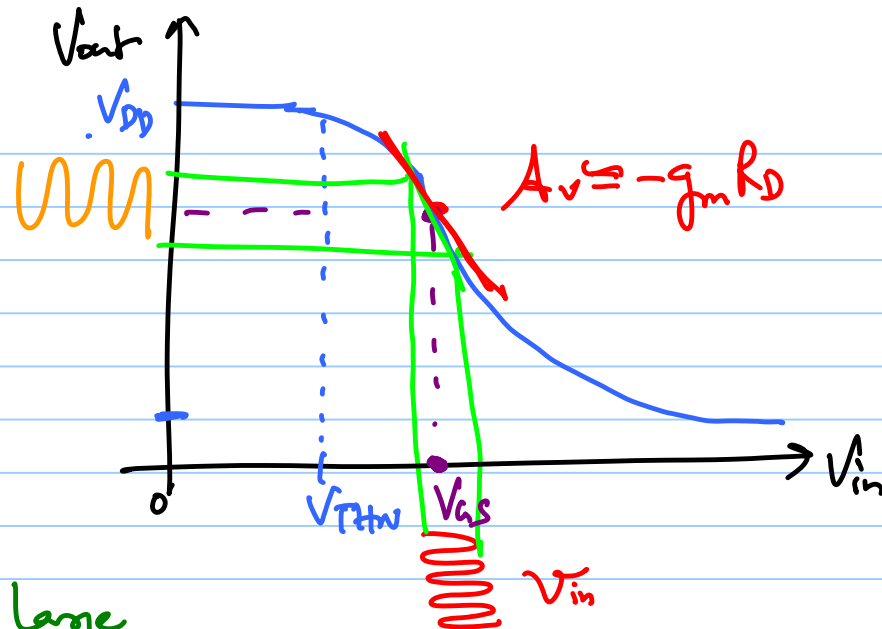


Ex. 1

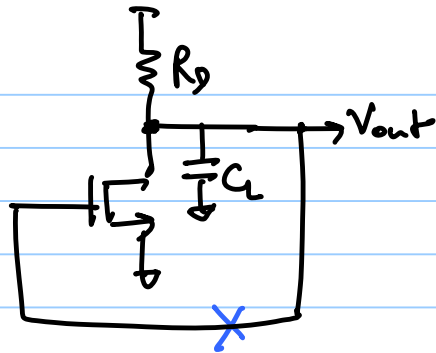


$$L(s) = \frac{-g_m R_D}{1 + s R_D C_L}$$

max phase shift = 90°
X


Ex. 2

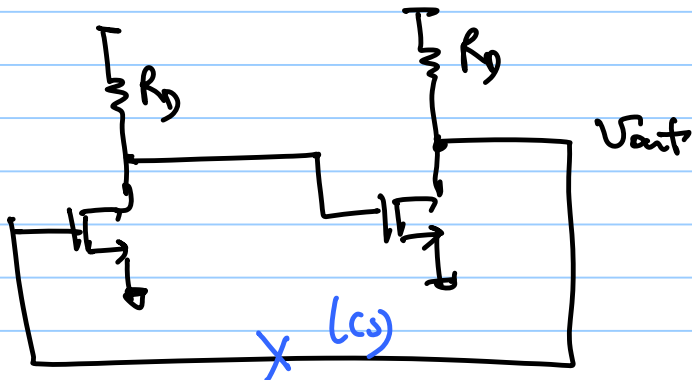
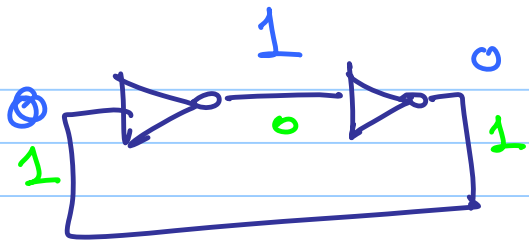
$$L(s) = \frac{(g_m R_D)^2}{(1 + s R_D C_L)^2}$$



"Latch"

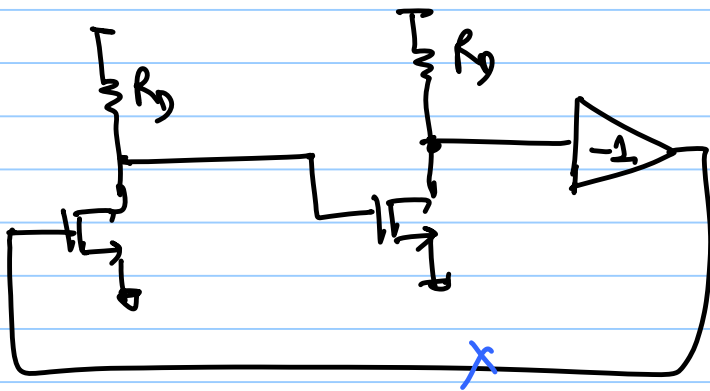




The excess phase shift
of 180° occurs at $\omega \rightarrow \infty$

$\hookrightarrow$ doesn't satisfy the
oscillation criterion

$$L(s) = \frac{-(g_m R_D)^2}{(1 + s R_D C)^2}$$


$\omega_p = \frac{1}{R_D C}$

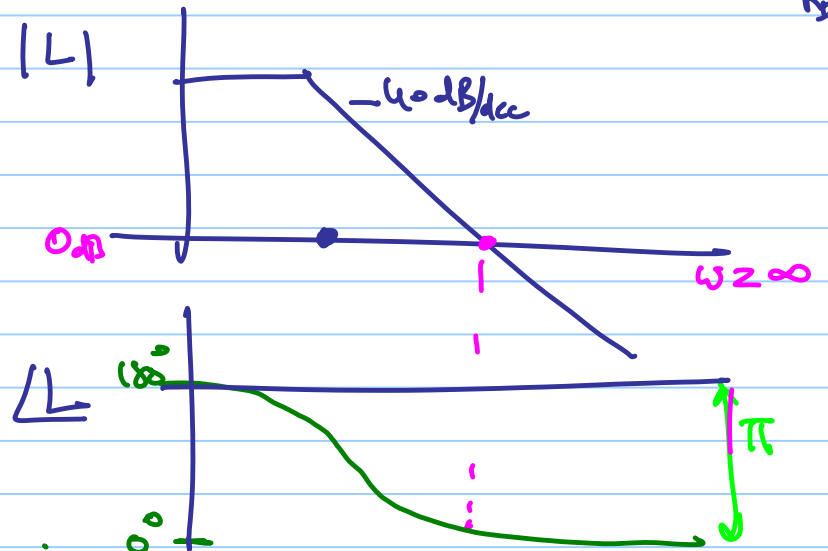

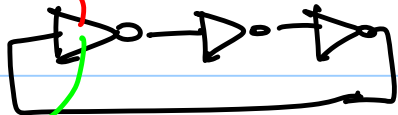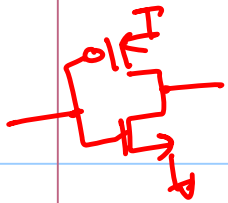



$n \geq 3$ & odd

(Ring Oscillator)

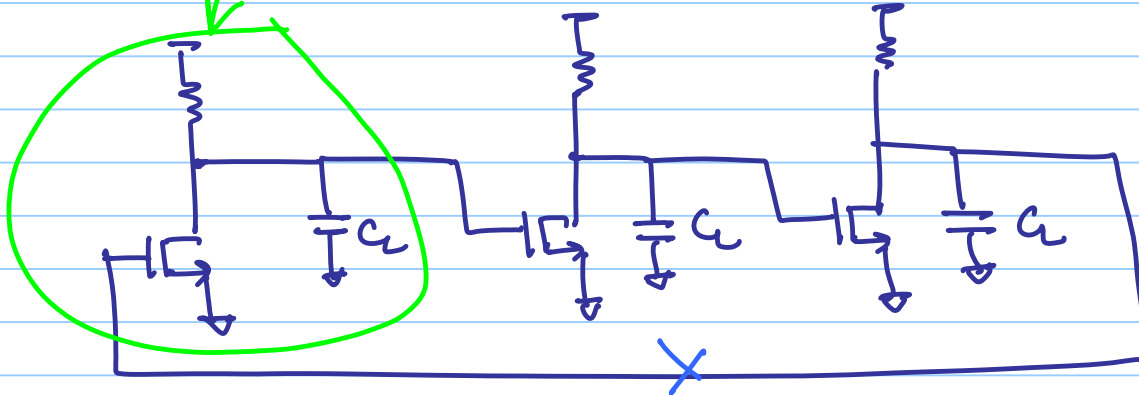

$$L(s) = - \frac{A_0^3}{(1 + s/\omega_0)^3}$$

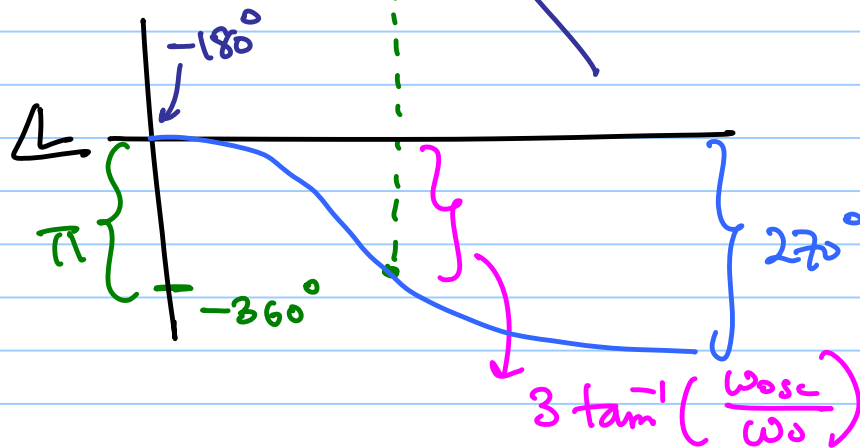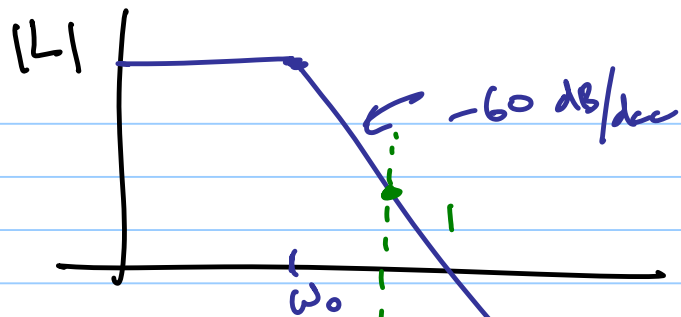where $A_0 = g_m R_D$
 $\omega_0 = \frac{1}{R_D C_L}$



The circuit oscillates if
excess phase

$$\angle L(j\omega_{osc}) = 180^\circ$$

$$3 \tan^{-1}\left(\frac{\omega_{osc}}{\omega_0}\right) = 180^\circ - 60^\circ$$

$$\frac{\omega_{osc}}{\omega_0} = \tan(60^\circ)$$

$$\Rightarrow \omega_{osc} = \omega_0 \tan(60^\circ)$$

$$\boxed{\omega_{osc} = \omega_0 \sqrt{3}}$$

Also, the minimum gain is estimated as:

$$|L(j\omega_{osc})| = 1$$

$$\Rightarrow \left(\frac{A_0}{\sqrt{1 + \left(\frac{\omega_{osc}}{\omega_0}\right)^2}} \right)^3 = 1$$

$\Rightarrow$


$$\frac{A_0}{\sqrt{1 + \left(\frac{\omega_0 \sqrt{3}}{\omega_0}\right)^2}} = 1$$

$\Rightarrow$

$$\boxed{A_0 = 2}$$

per stage DC gain = 2

$$\Rightarrow |L(\omega_{osc})| = 2^3 = 8$$

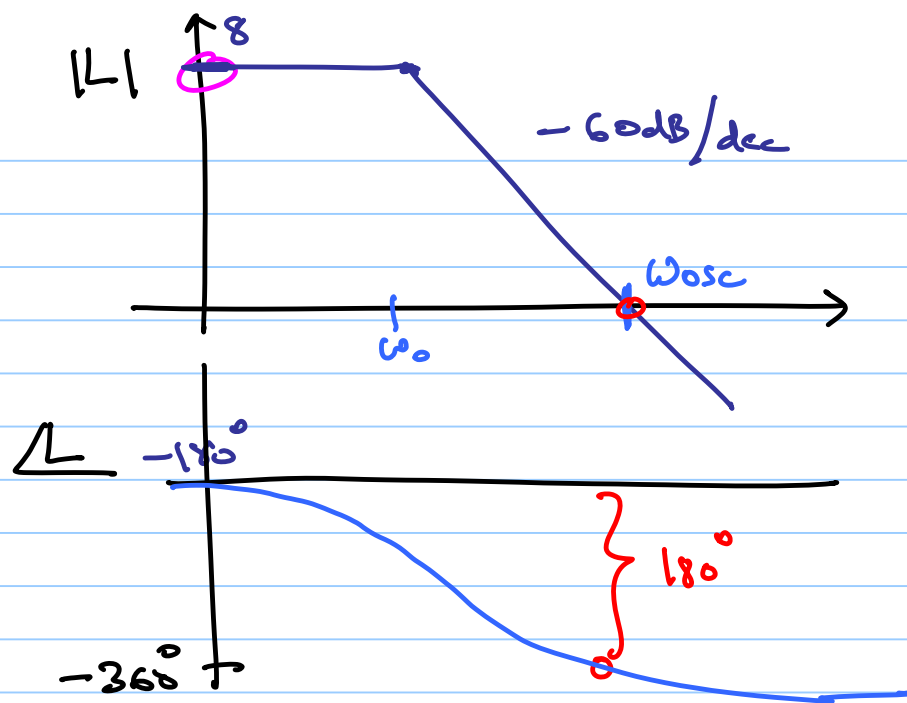

$\Rightarrow$ $\boxed{g_m R_D = 2}$

