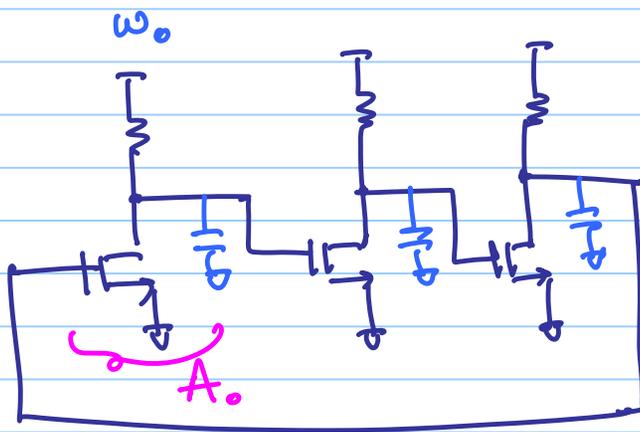


# ECE 504 - Lecture 15


Note Title

10/12/2016

## Oscillators:




3-stage oscillator

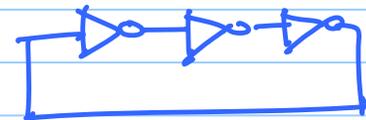

for oscillation  $A_o = 2$

$$\omega_{osc} = \omega_o \sqrt{3}$$

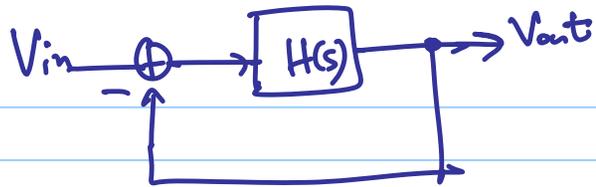

$$L(s) = H(s)$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{H(s)}{1 + L(s)}$$

$$= \frac{-A_0^3}{\left(1 + s/\omega_0\right)^3} \bigg/ \left(1 - \frac{A_0^3}{\left(1 + s/\omega_0\right)^3}\right)$$


$$= \frac{-A_0^3}{\left(1 + s/\omega_0\right)^3 - A_0^3}$$

closed loop poles:

$$D(s) = 0$$

$$\Rightarrow \left(1 + \frac{s}{\omega_0}\right)^3 - A_0^3 = 0$$
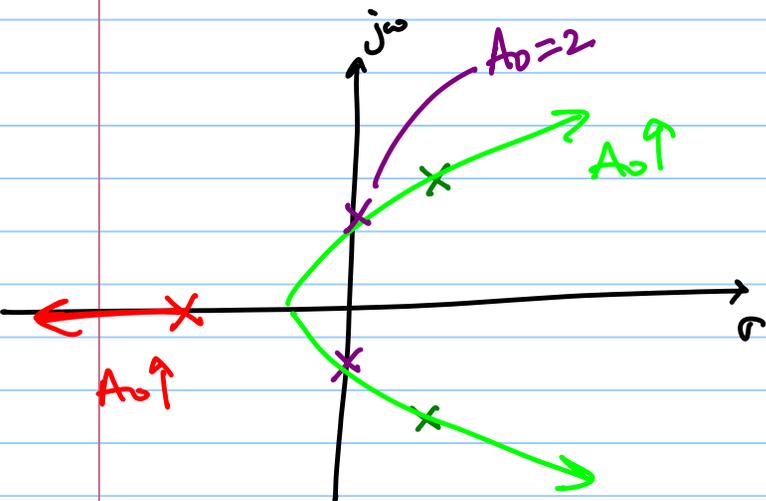
$$\Rightarrow \left(1 + \frac{s}{\omega_0}\right)^3 = A_0^3$$



$$s = \begin{cases} -(A_0 + 1)\omega_0 \checkmark \\ \left( \frac{A_0(1 \pm j\sqrt{3})}{2} - 1 \right) \omega_0 \end{cases}$$

$$\rightarrow \pm j\sqrt{3}\omega_0 \text{ for } A_0 = 2$$

\* first pole leads to decaying exponential term

$$e^{-(A_0+1)\omega_0 t}$$

\* the complex conjugate poles are on the  $j\omega$ -axis


⇒ for  $A_0 \geq 2$ .

for  $A_0 < 2$




→ No oscillation


for  $A_0 \geq 2$

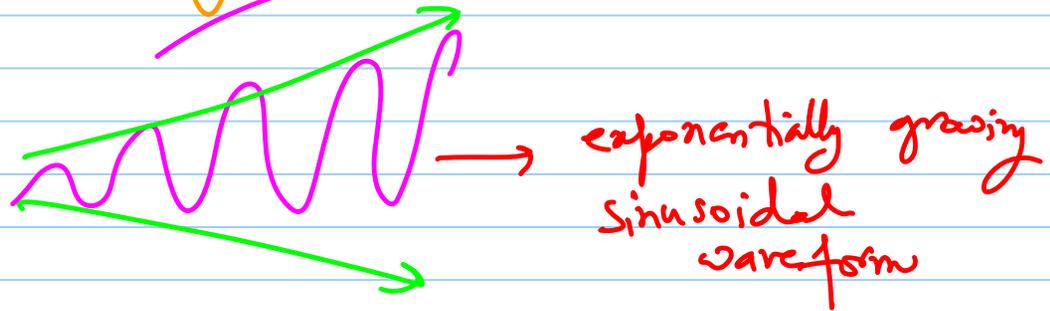

→ exponentially growing sinusoidal waveform
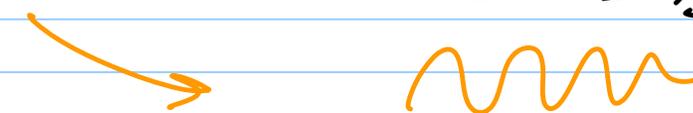
$$V_{out}(t) = a \left[ e^{-(A_0+1)\omega_0 t} + \cos\left(\frac{A_0\sqrt{3}\omega_0 t}{2}\right) \right]$$


In theory  
for  
 $A_0 > 2$

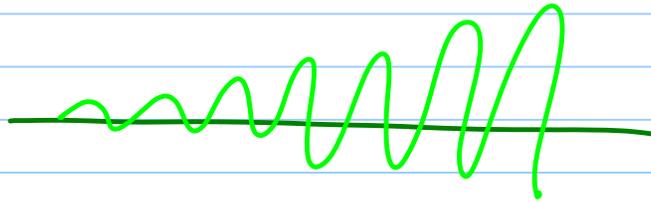



In practice



initial condition




$-A_0$


$A_0 > 2$

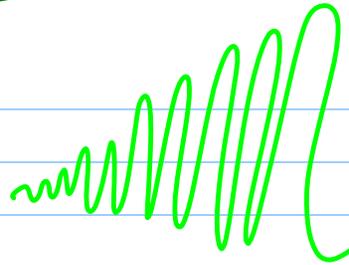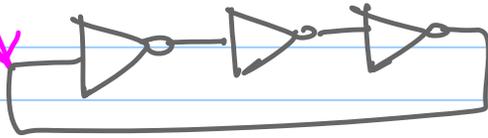

Average gain

$V_{out}$

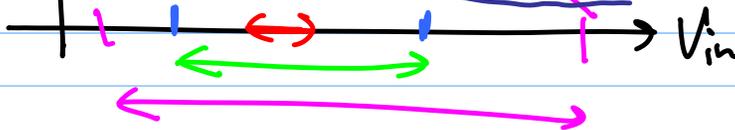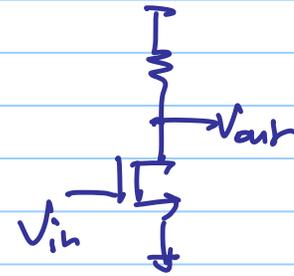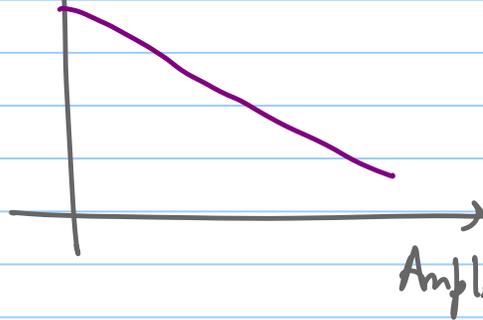

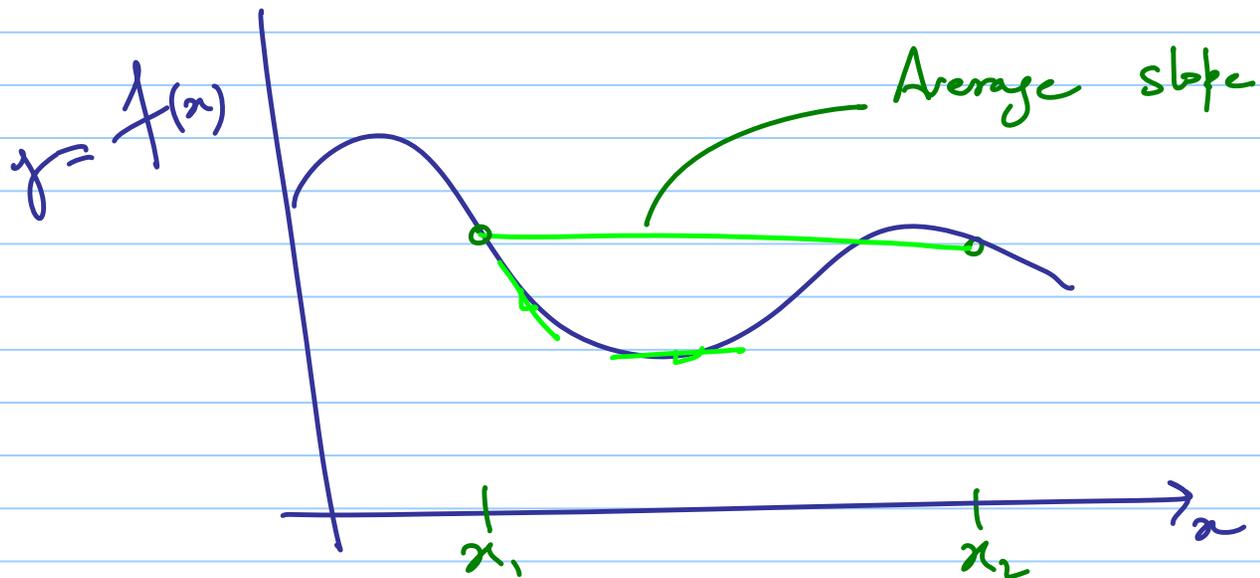




$$\frac{f(b) - f(a)}{b - a}$$



\* Oscillation amplitude increases

\* gain stage experiences non-linearity

↳ average gain drops

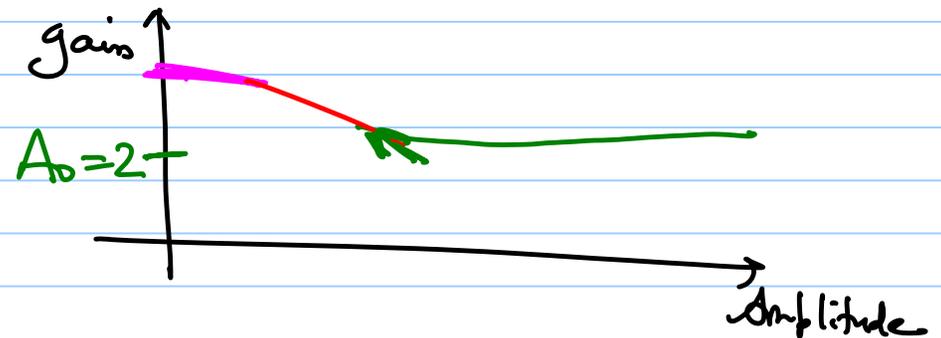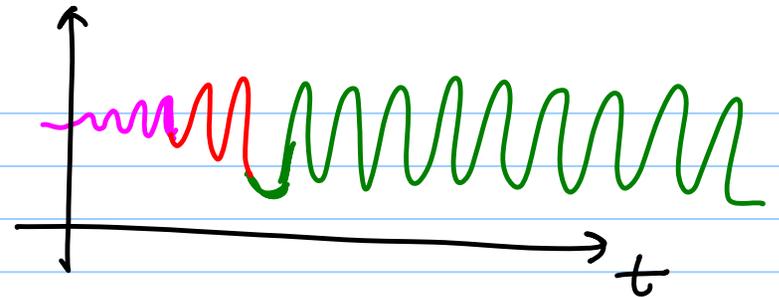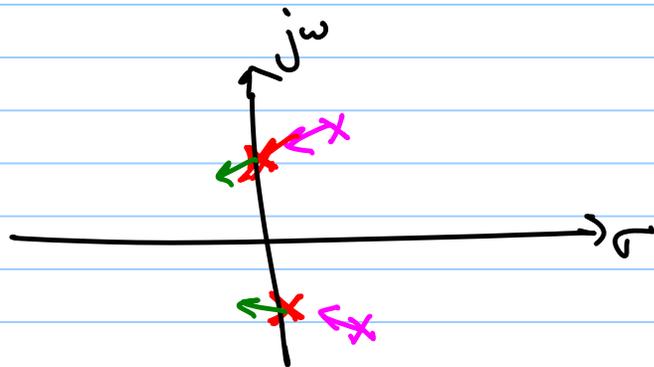
↳ conjugate poles move towards  $j\omega$ -axis



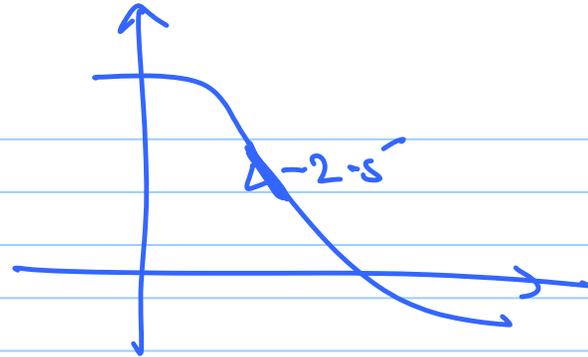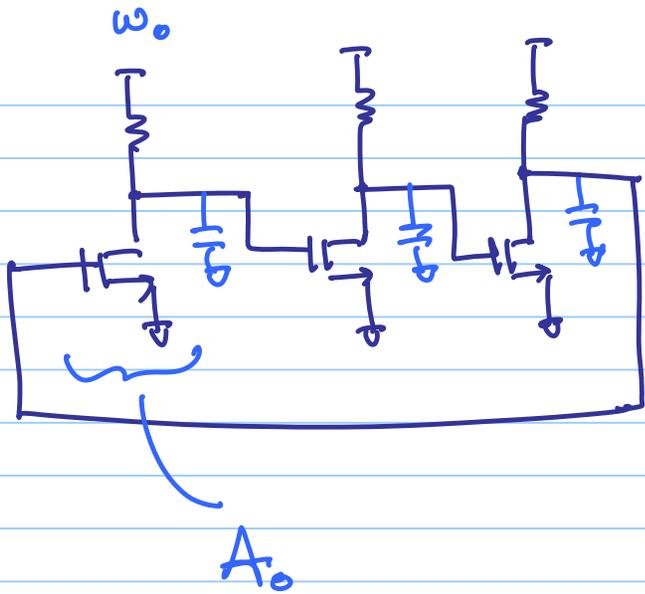



Aside

LC-Tank

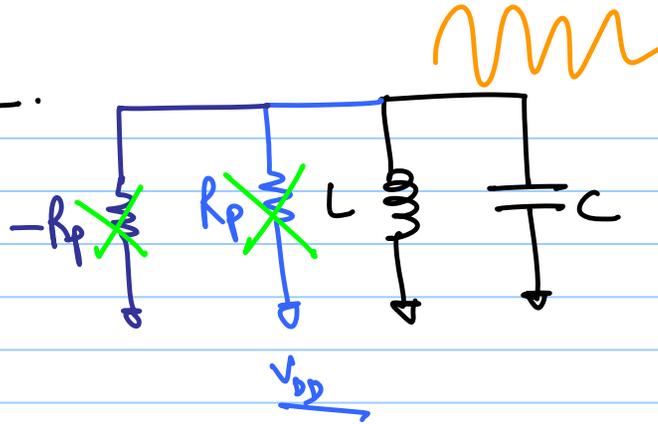

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


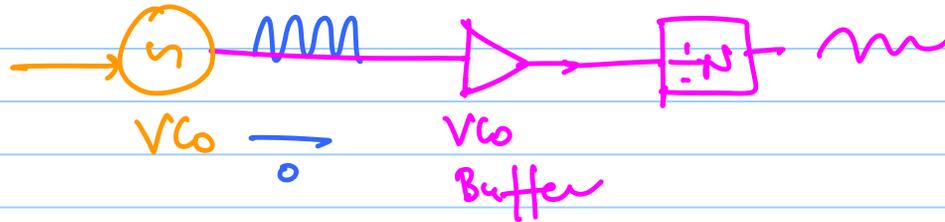


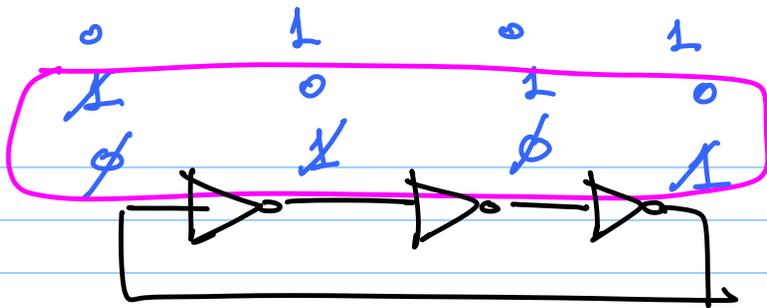

$$T_{ck} = 2nT_d = 6T_d$$

$$\omega_{osc} = \frac{2\pi}{6T_d} = \frac{\pi}{3T_d}$$

Large-signal

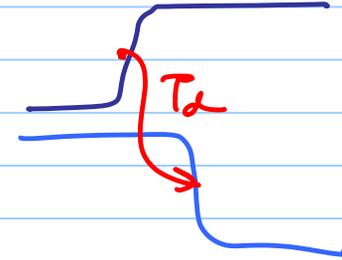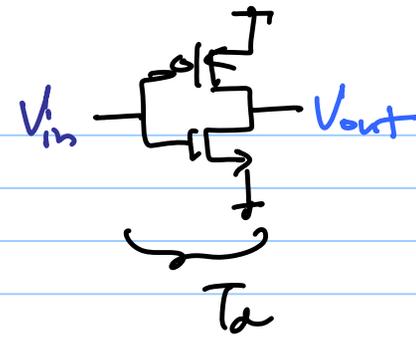


But from small signal analysis

$$\omega_{osc} = \omega_0 \sqrt{3}$$

small-signal

Reconciliation :



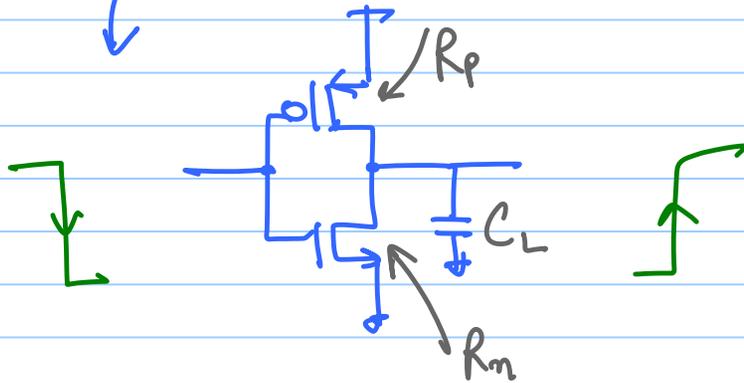
the small-signal oscillation starts with  $\omega_0 \sqrt{3}$  and as the amplitude builds up, the circuit gets more non-linear and the frequency of oscillation drops to  $\frac{2\pi}{6T_2}$



$$f_{osc} = \frac{1}{2nT_d}$$

$T_d = \text{inverter delay}$

$$t_w = 0.7R_pC_L$$

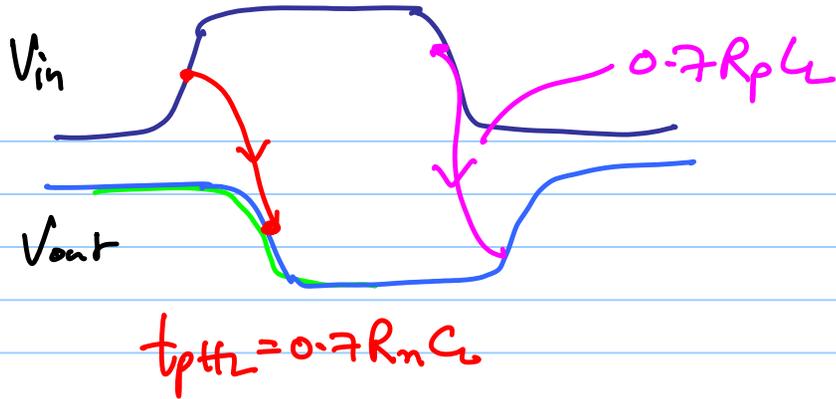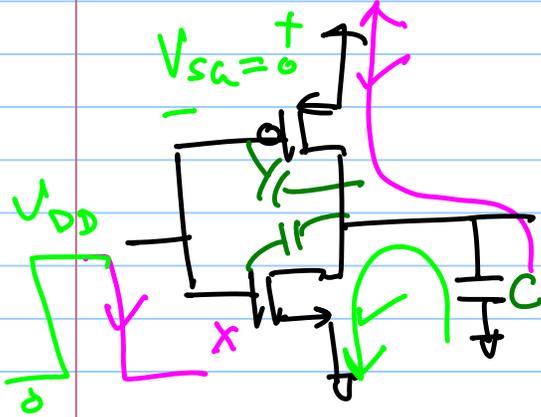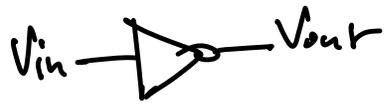

$$f_{osc} = \frac{1}{2n (0.7 R_n C)}$$

$$n=3;$$

$$R_n = \frac{1}{k P_n \left(\frac{W}{L}\right)_n (V_{DD} - V_{thn})}$$

$$R_p = \frac{1}{k P_p \left(\frac{W}{L}\right)_p (V_{DD} - V_{thp})}$$

$$C = \frac{5}{2} [C_{oxn} + C_{oxp}] \rightarrow C_{oxnp} = W L C_{ox}$$

Scribe lines  $\rightarrow$  Rij oscillator

$$R = \frac{1}{K_P \left(\frac{W}{L}\right) (V_{DD} - V_{THN})}$$

Need to make a  $V_{CO}$  from oscillator


Control variable

$$\rightarrow V_{DD} \uparrow \Rightarrow R \downarrow \Rightarrow f_o \uparrow$$

$\rightarrow$  vary  $R$


$\rightarrow$  vary  $C$

Vary charging /  
discharging current

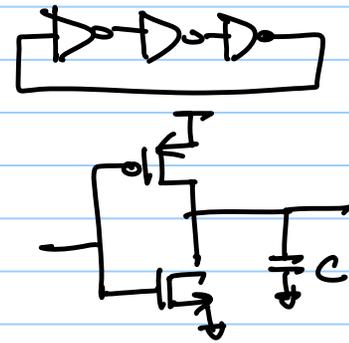


$$f_{osc} = \frac{1}{2n \times 0.7RC}$$
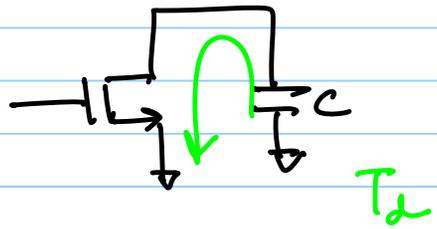
$$R = \frac{1}{K_P \left(\frac{W}{L}\right) (V_{DD} - V_{THN})}$$





$\Rightarrow$

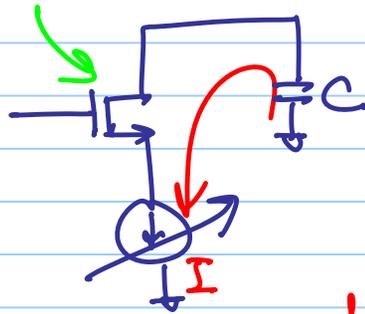

discharge rate  $\propto \frac{1}{RC}$

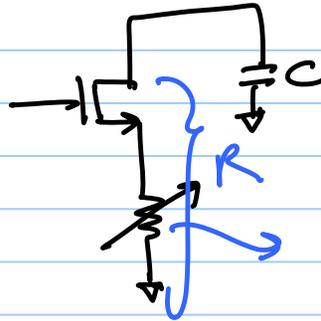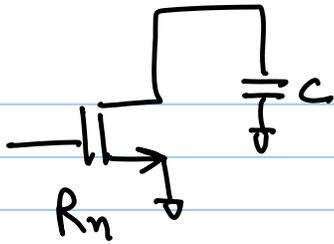discharge rate  $\propto \frac{I}{C}$   $f(V_c)$



Voltage controlled resistor

↳ trioded transistor

