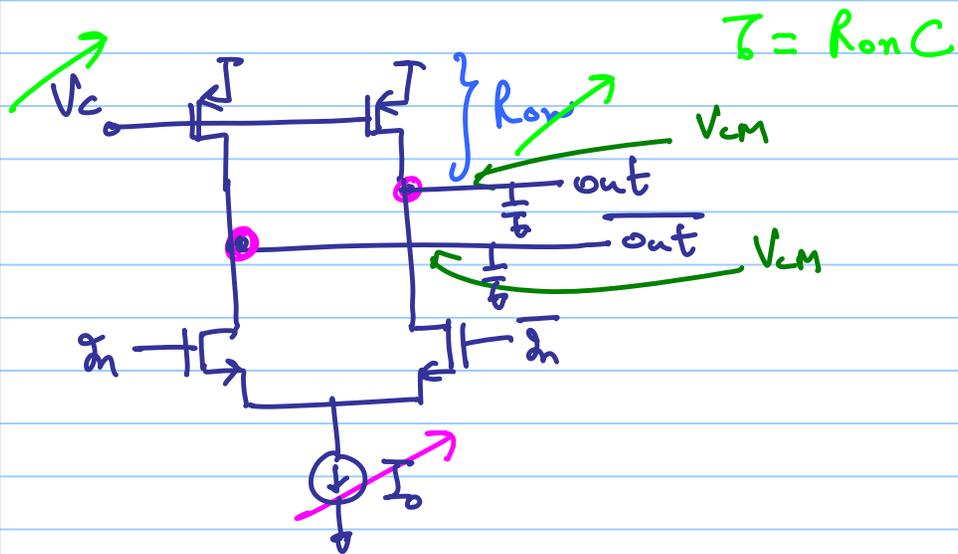



ECE 504 - Lecture 17

Note Title

10/19/2016



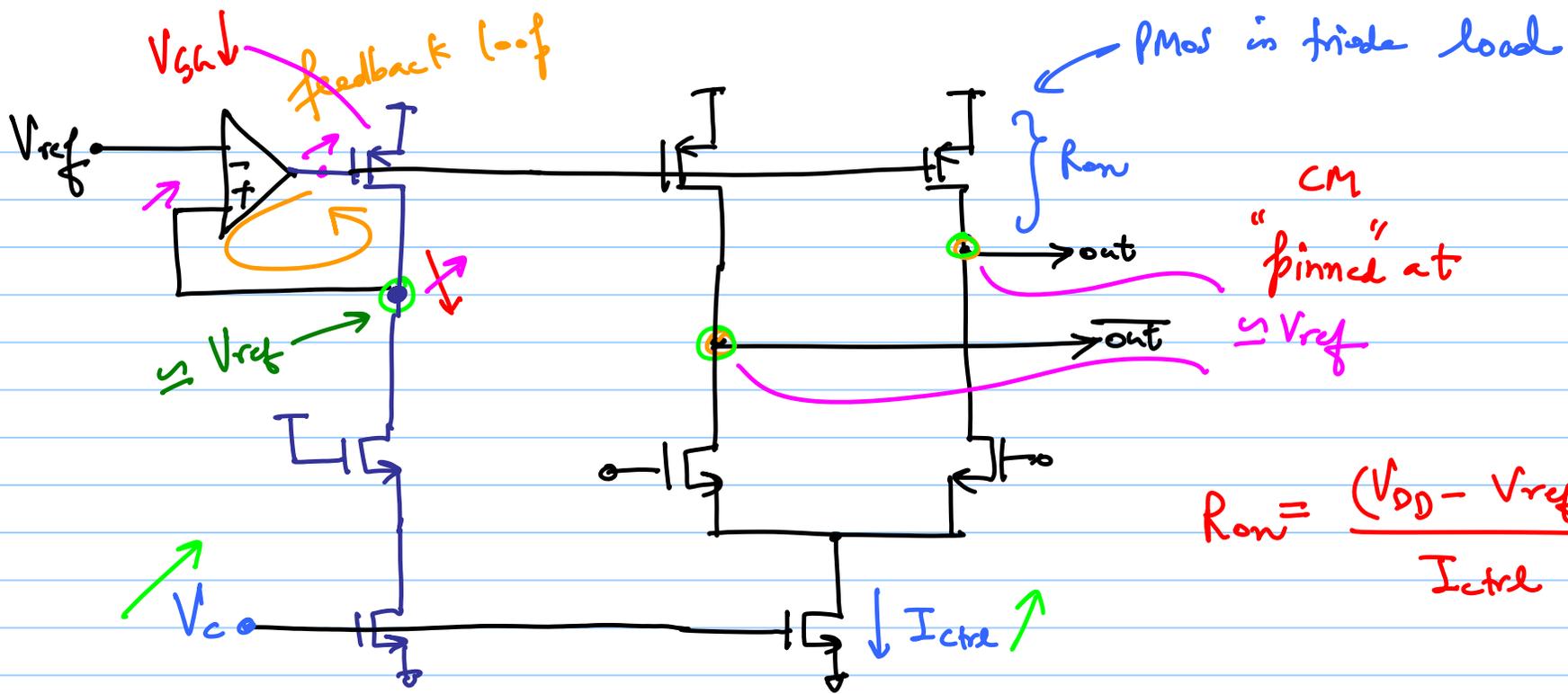$V_c \uparrow \Rightarrow R_{out} \uparrow$
 $\Rightarrow V_{cm}$ varies




Replica Bias forces

$$R_{on} = \frac{(V_{DD} - V_{ref})}{I_{ctrl}}$$

$$f_{out} \propto \frac{1}{\tau} = \frac{1}{R_{on} C} \propto \frac{I_{ctrl}}{(V_{DD} - V_{ref}) C}$$

$I_{ctrl} = f(V_c)$


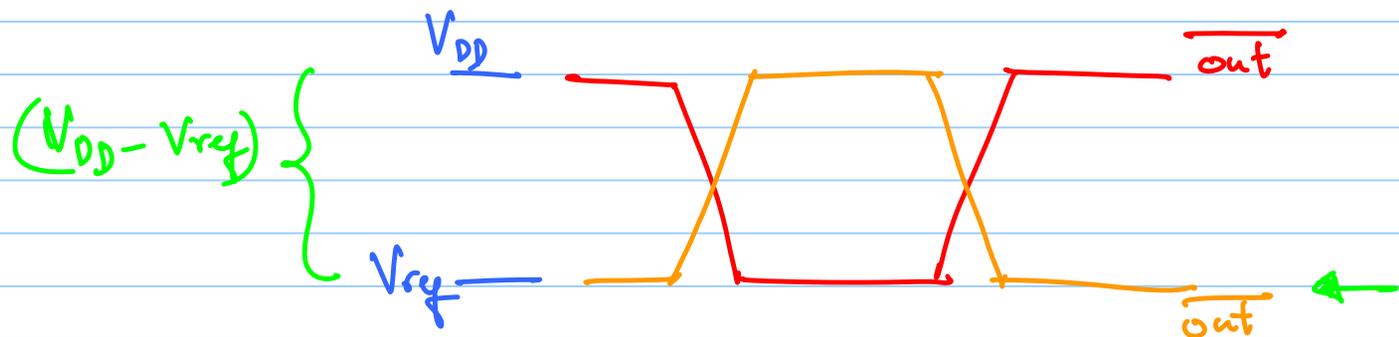



$$f_{out} \propto I_{drc} = f(V_{in})$$

Here,

$$\begin{aligned} I_{drc} &= f(V_{in}) \\ &= \frac{K_p n}{2} \frac{W}{L} (V_{in} - V_{thn})^2 \end{aligned}$$

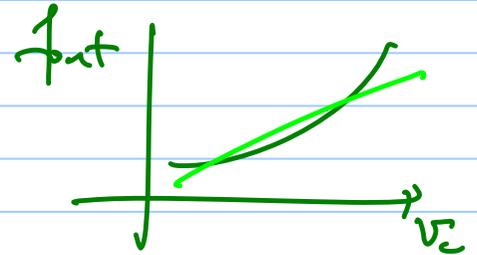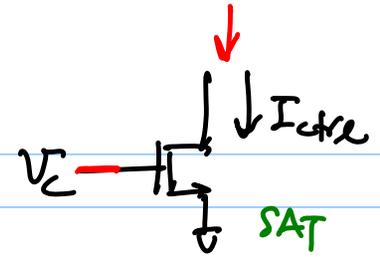
$\Rightarrow g_m V_{in}$ for small V_{in}



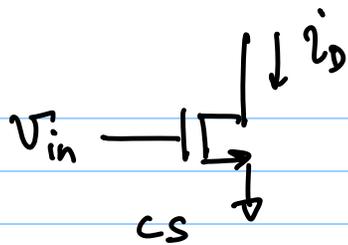

$$i_d = g_m V_{in} \text{ for small signal}$$
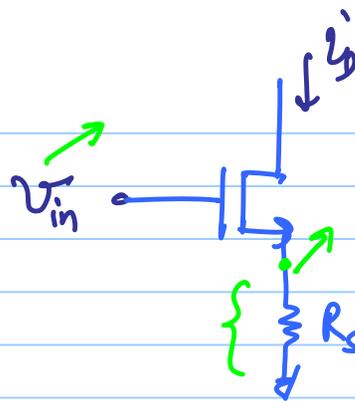
$$i_d \propto (V_{in} - V_{th})^2 \text{ for large signal}$$



CS with source degeneration



$$i_d = \frac{g_m V_{in}}{1 + g_m R_s}$$


$$= \frac{1}{\frac{1}{g_m} + R_s} V_{in}$$

$$\approx \frac{V_{in}}{R_s}$$

$$\text{if } \frac{1}{g_m} \ll R_s$$

$$\text{or } g_m \gg \frac{1}{R_s}$$

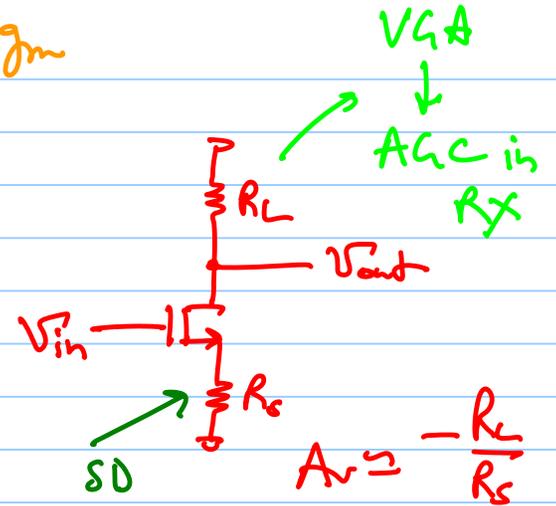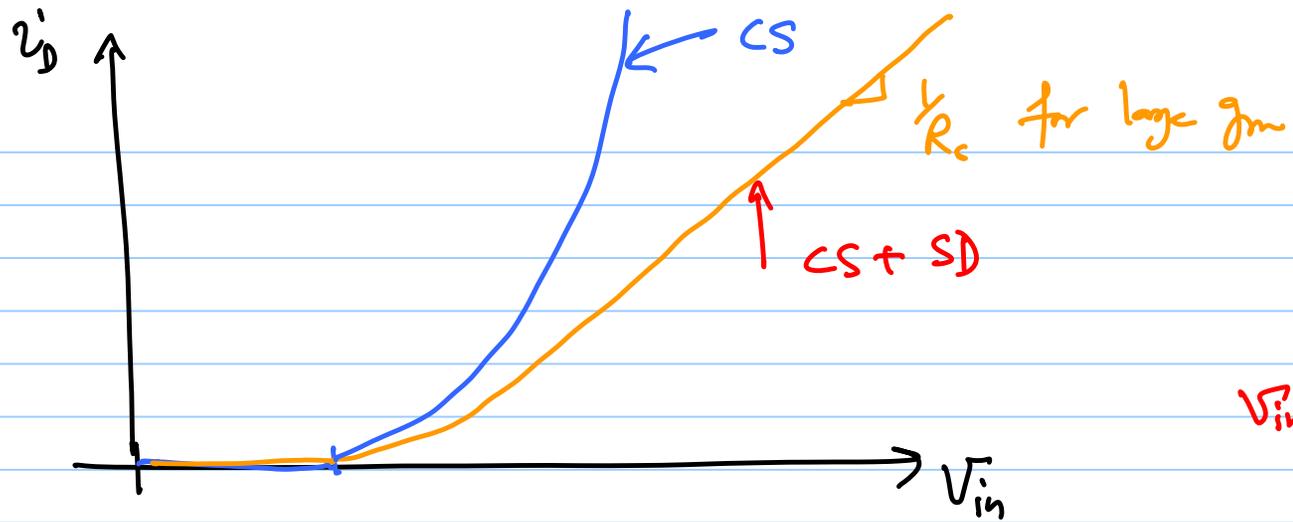


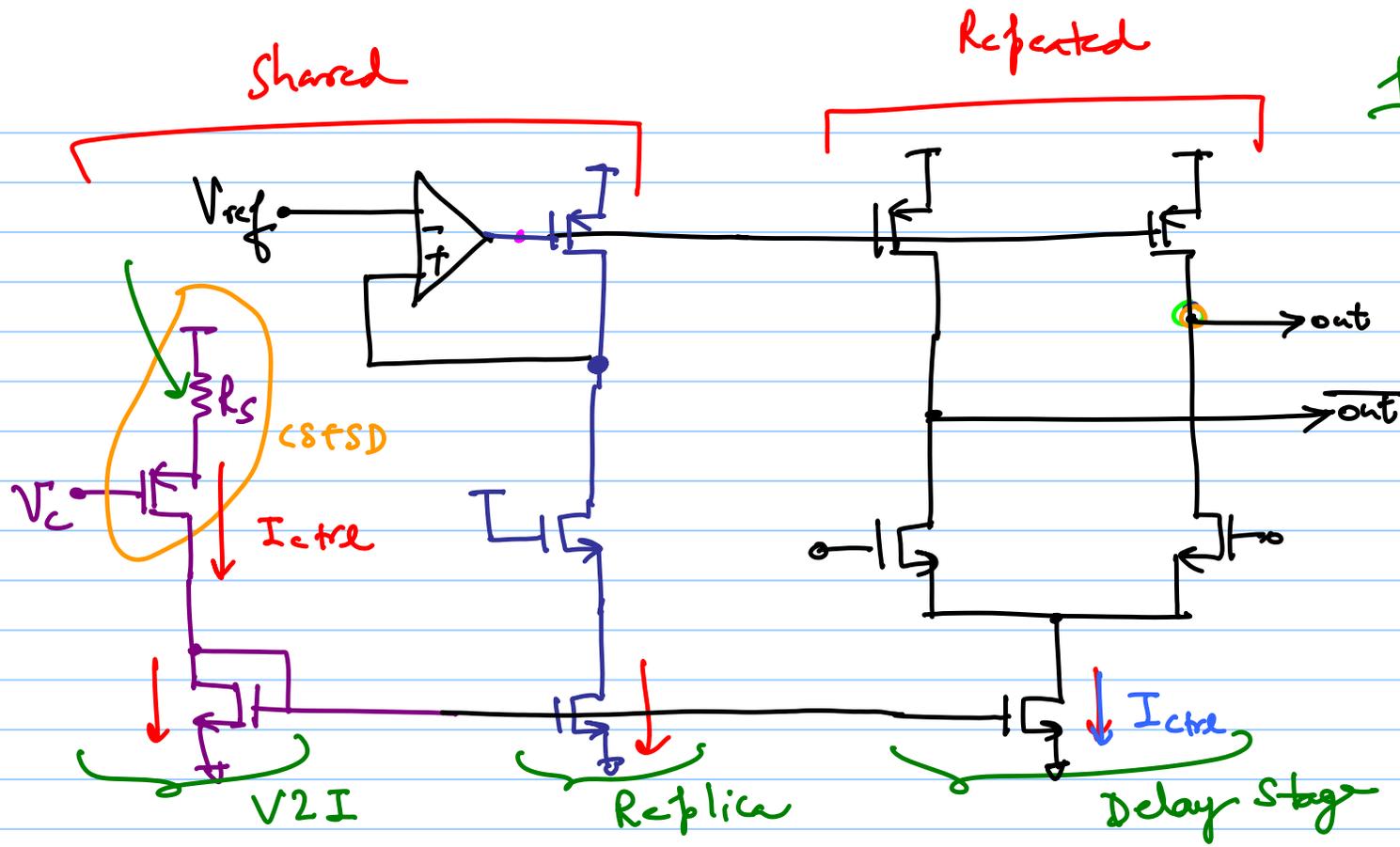

$$f_{out} \propto \frac{V_c}{R_s (V_{DD} - V_{th})C}$$

Linear V_{GS} characteristics


Power Supply Rejection

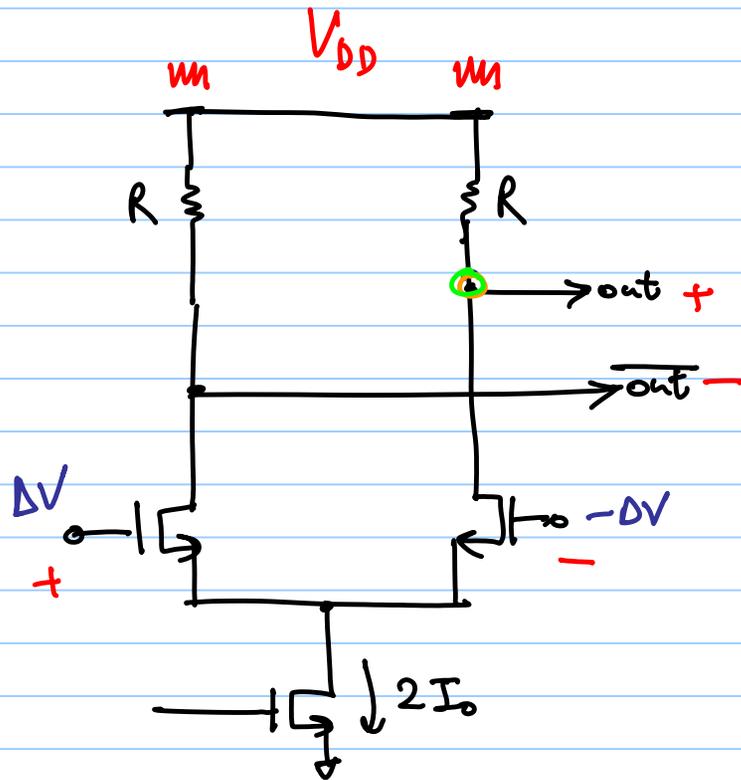

$$out = V_{DD} - (I_0 + \Delta I)R$$

$$\overline{out} = V_{DD} - (I_0 - \Delta I)R$$

$$= -2(\Delta I)R$$

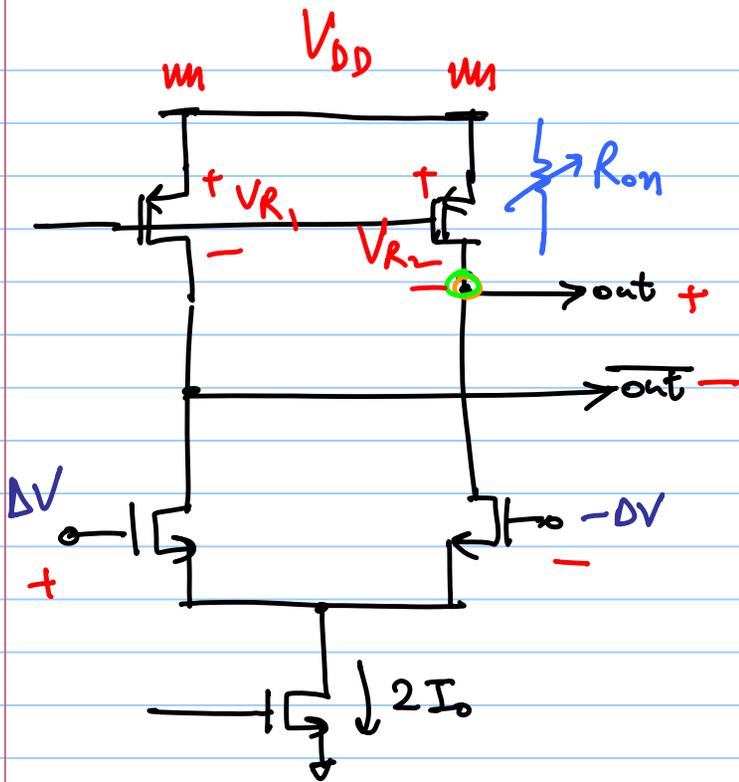

$$out = V_{DD} - (I_0 + \Delta I) R_{on}$$

$$\overline{out} = V_{DD} - (I_0 - \Delta I) R_{on}$$




$\nearrow f(V_{R1})$
 $\nwarrow f(V_{R2})$

$$R_{on} = R(V_R, I_R)$$

Non-linear

Non-linear resistor converts supply noise into differential output

↳ PSRR
power supply (noise) Rejection Ratio

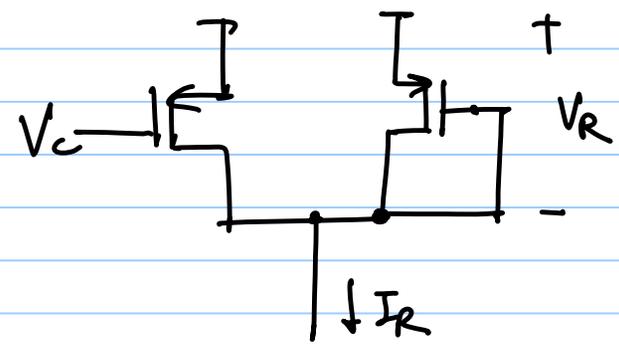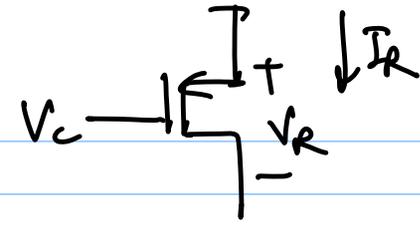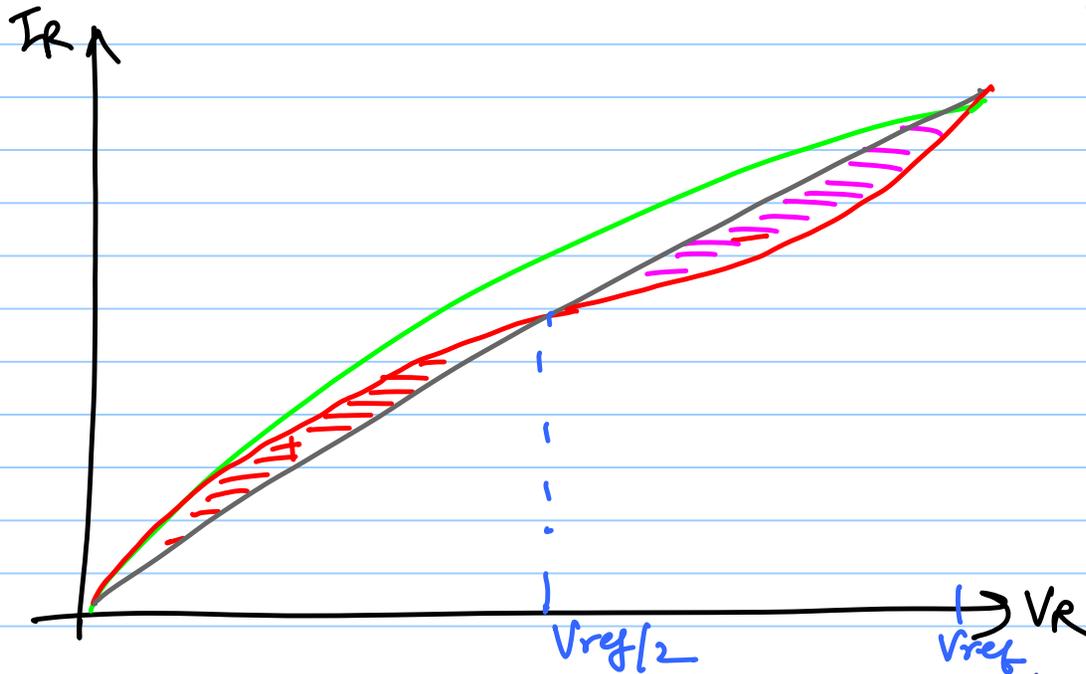

Symmetric I-V characteristics about the center of voltage swing
 ↳ nominally equal incremental resistance

Small-swing Differential V_o

PSRR ✓

Swing ⚡


Phase Noise ⚡

Need low-swing to rail-to-rail swing converters

Large-Swing VCOs


- + Simpler delay cells
- + Rail-to-rail output swings
- Poor PSRR
- + Better phase noise performance

↳ devices are mostly in Triode

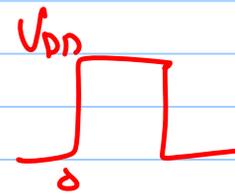

Variable Delay Inverter


① Vary the charging/discharging current

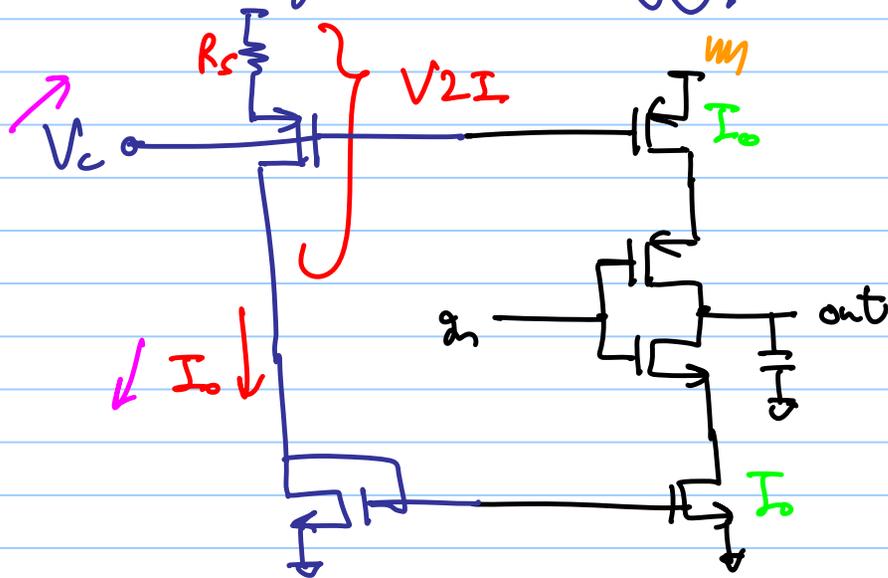

font ↓

Current-Controlled Oscillator (CCO)

↳ current started V_{CO}

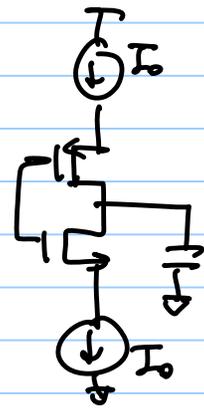

② Vary load Capacitance

