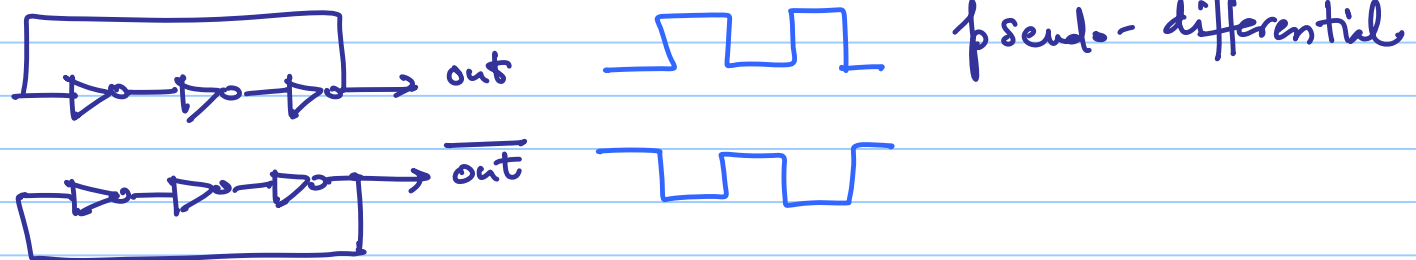


ECE 504 - Lecture 18

Note Title



10/24/2016

Rail-to-rail Differential



* No way we can match the phase of the two oscillators!



Couple the two oscillators

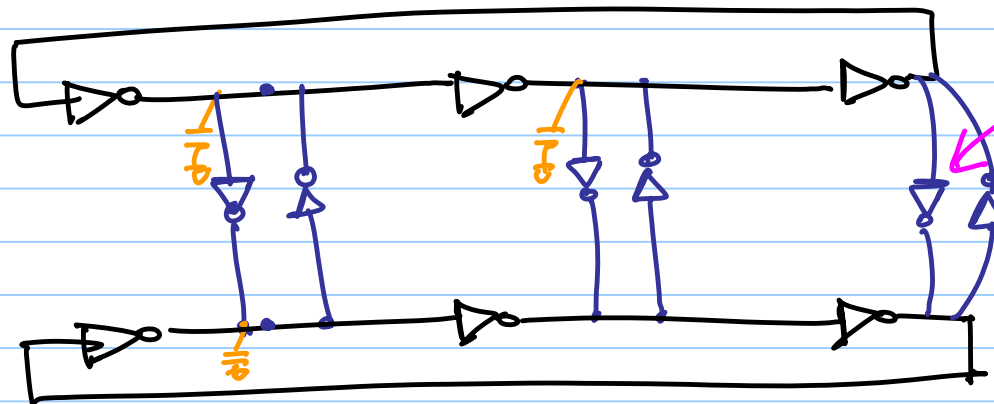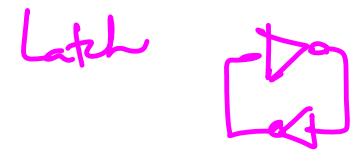



Small latches
force differential
operation


→ slower oscillation frequency

Even stages?

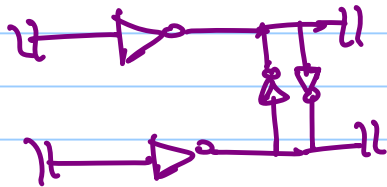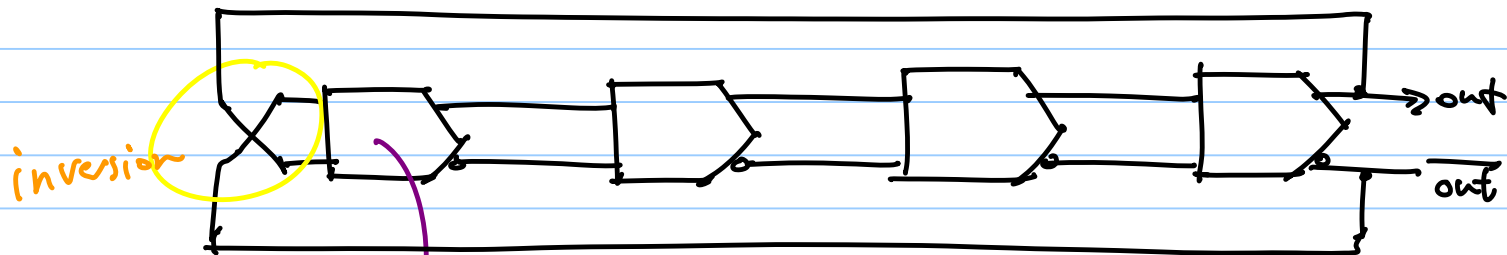


Reduce $\tau = R_{on}C$

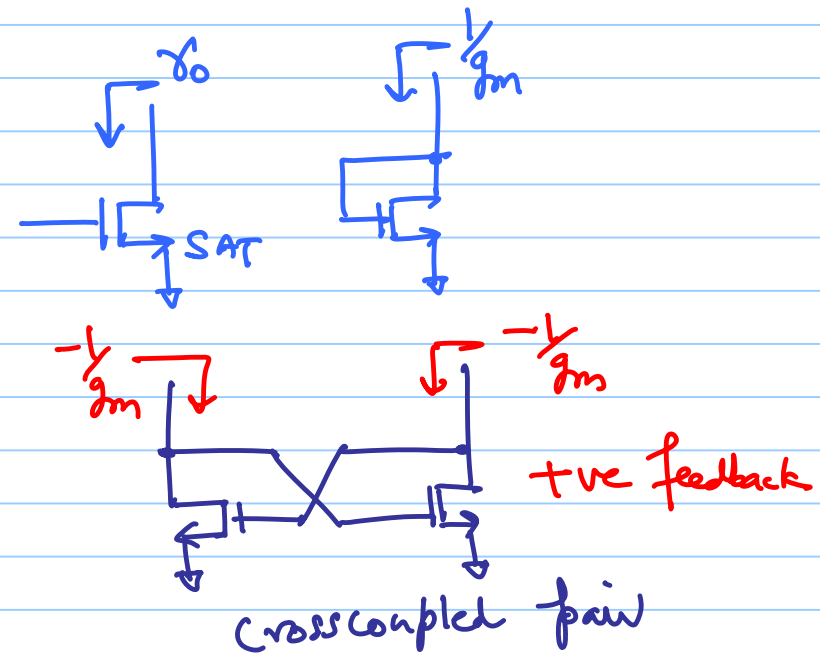
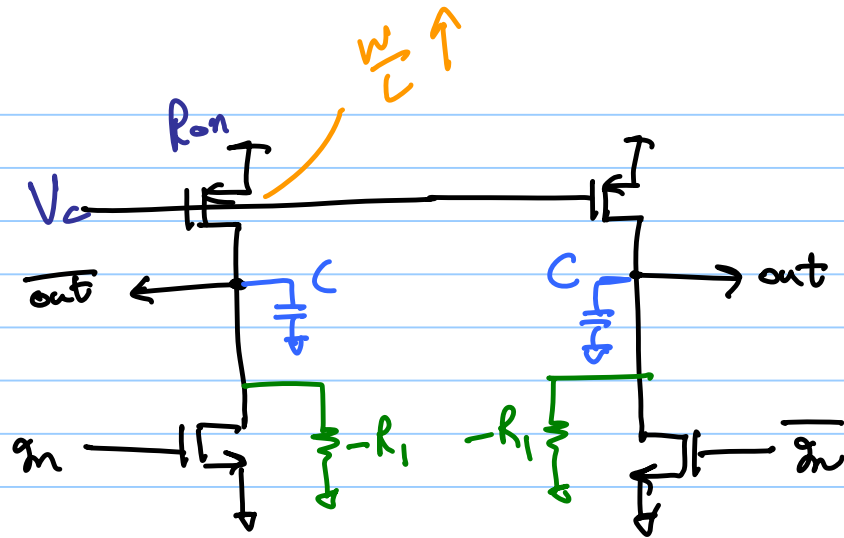


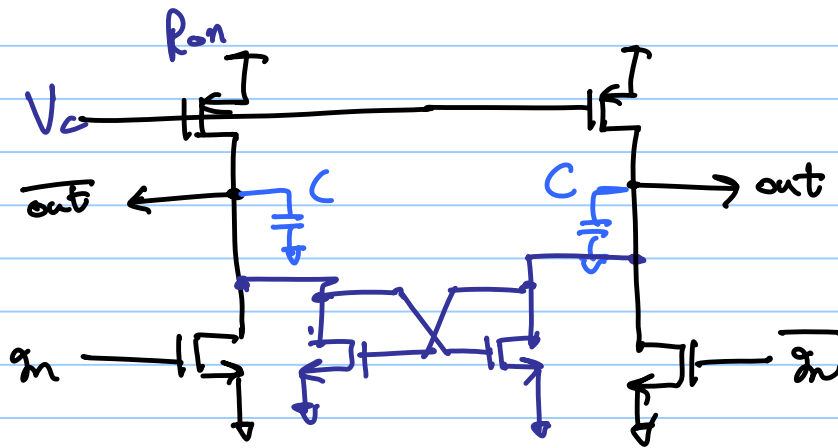

- + wide tuning range
- Asymmetric output waveforms

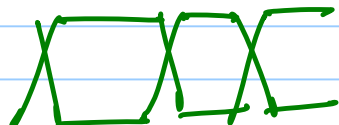

 ↳ duty cycle distortion
 ↳ degraded noise performance

Aside

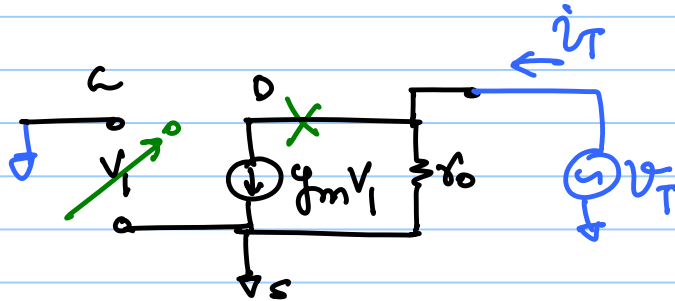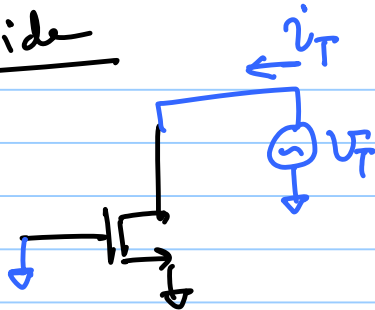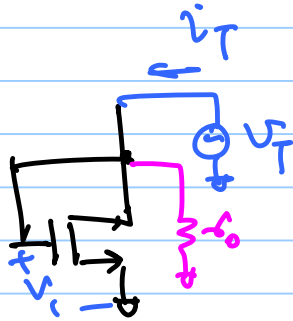


$$R_{out} \triangleq \frac{V_T}{i_T}$$

$$R_{out} = r_o$$



Diode Connected
MOSFET

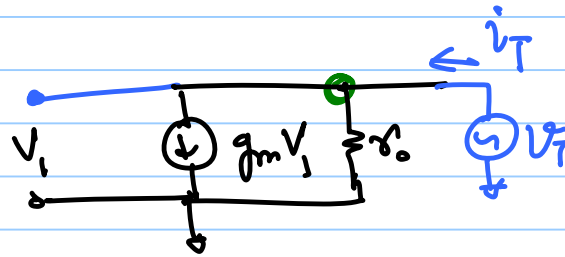


$$V_i = V_T$$

$$g_m V_1 + \frac{V_T}{r_o} - i_T = 0$$

$$V_T (g_m + \frac{1}{r_o}) = i_T$$

$$R_{out} = \frac{V_T}{i_T} = \frac{1}{g_m + \frac{1}{r_o}} = \frac{1}{g_m} \parallel r_o \approx \frac{1}{g_m}$$

Tuning by Supply Voltage.

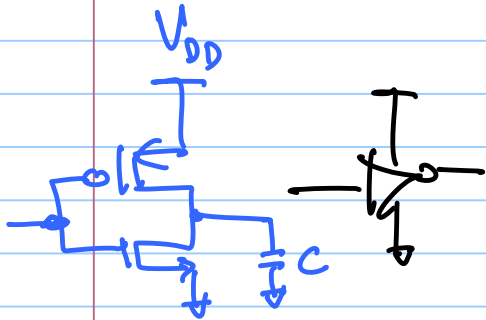

* Inverter delay is a strong function of V_{DD}

$$\tau = R_{on} C = \frac{1}{k_p (V_{DD} - V_{thn})} \cdot C$$

$$f_{osc} \propto \frac{1}{2N\tau} = \frac{k_p (V_{DD} - V_{thn})}{2NC}$$




$$V_{DD} \uparrow \Rightarrow R_{on} \downarrow \Rightarrow \tau \downarrow \Rightarrow f_{osc} \uparrow$$

* Wide tuning range!

$$* \quad P_d = CV^2f$$






$$= \alpha C V_{DD}^3 = \frac{C f_{osc}^3}{\alpha^2} \quad \text{if } f_{osc} = \alpha V_{DD}$$



* Automatic power scaling

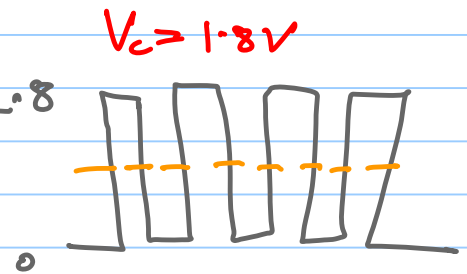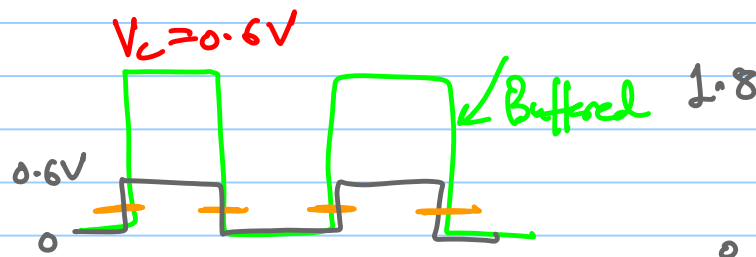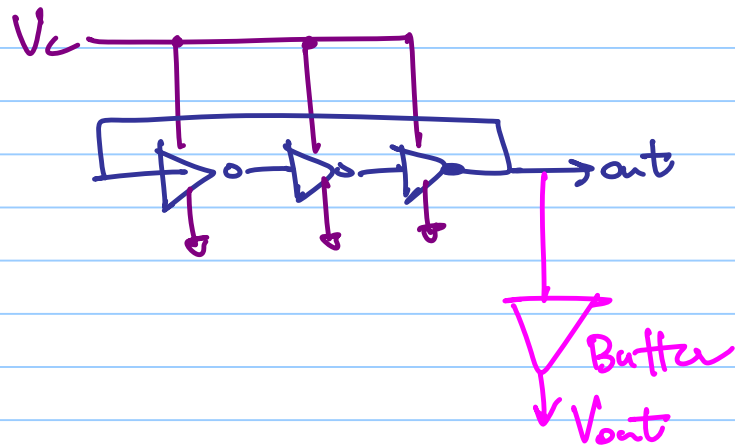



VCO Buffers:

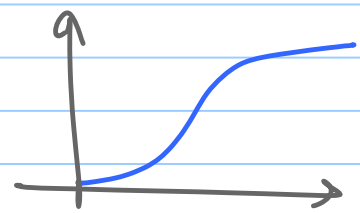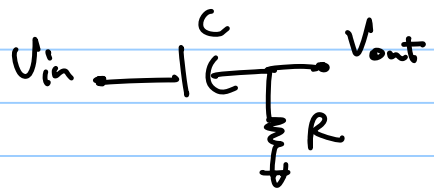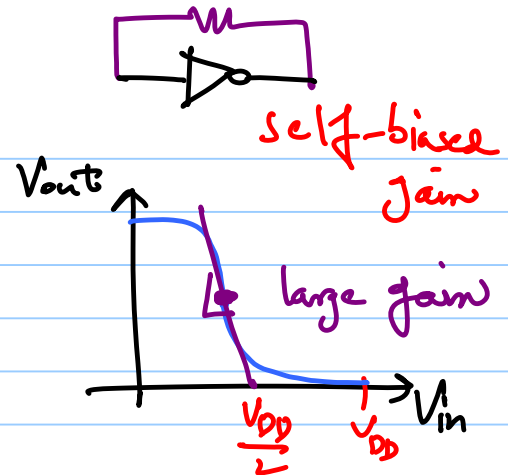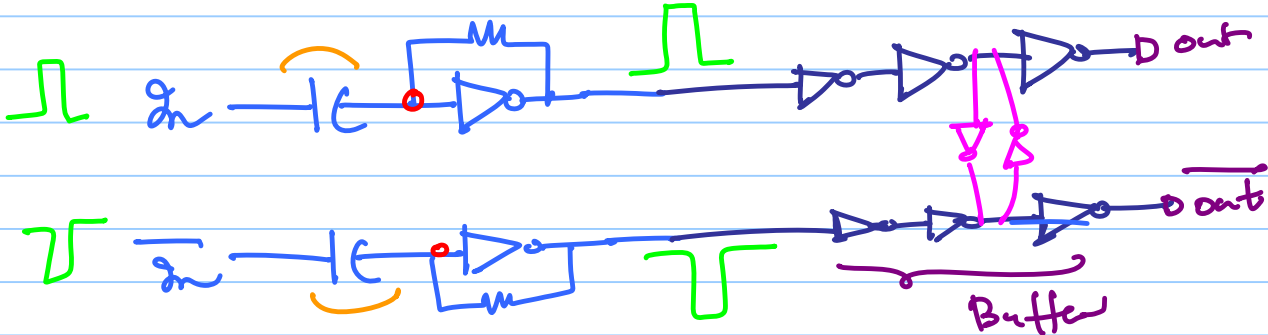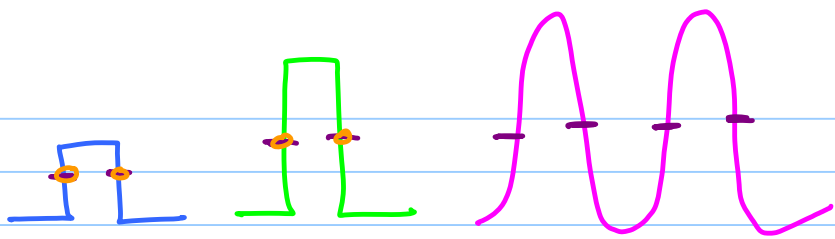- * Buffers convert low-swing VCO output to full-swing
 - ↳ 50% output duty cycle
 - ↳ fast rise/fall times
 - ↳ low power
 - ↳ PSRR
 - ↳ Add low capacitance to the VCO




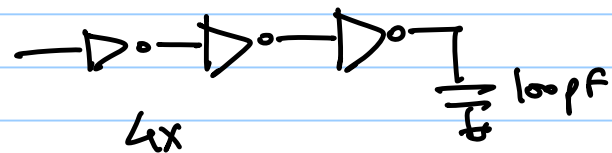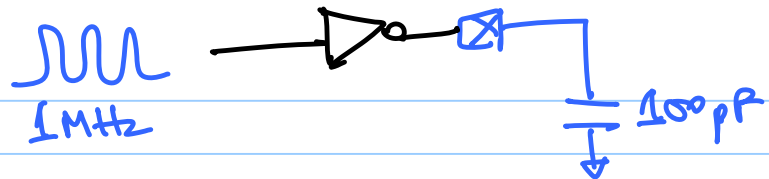

Butter Design

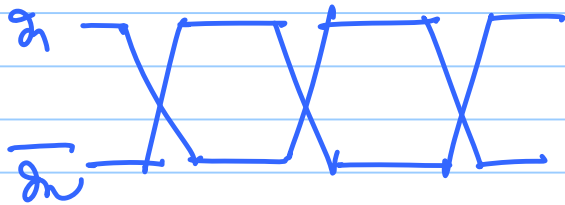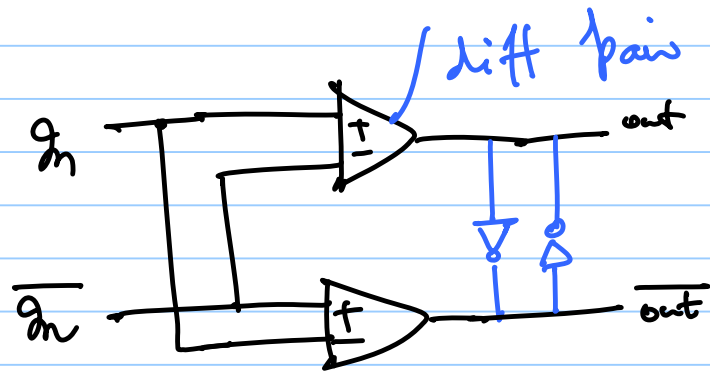


Supply Regulated VCO
opamp

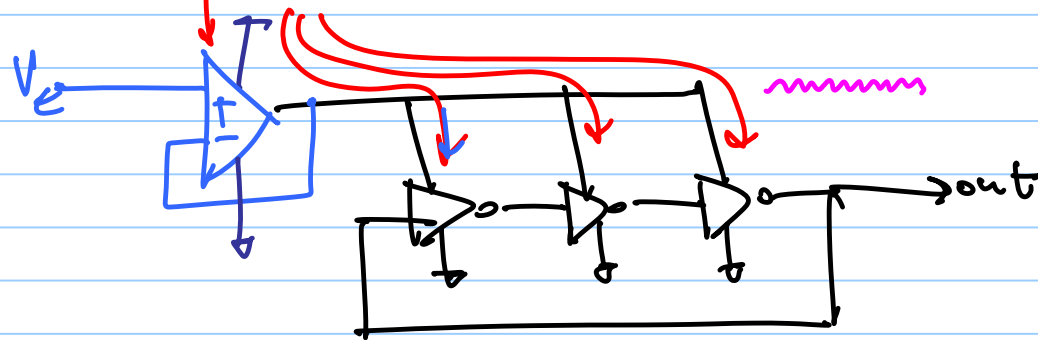

* PSRR is good, but limited by opamp's PSRR

↳ 5-10x power penalty
 ↳ large opamp bias

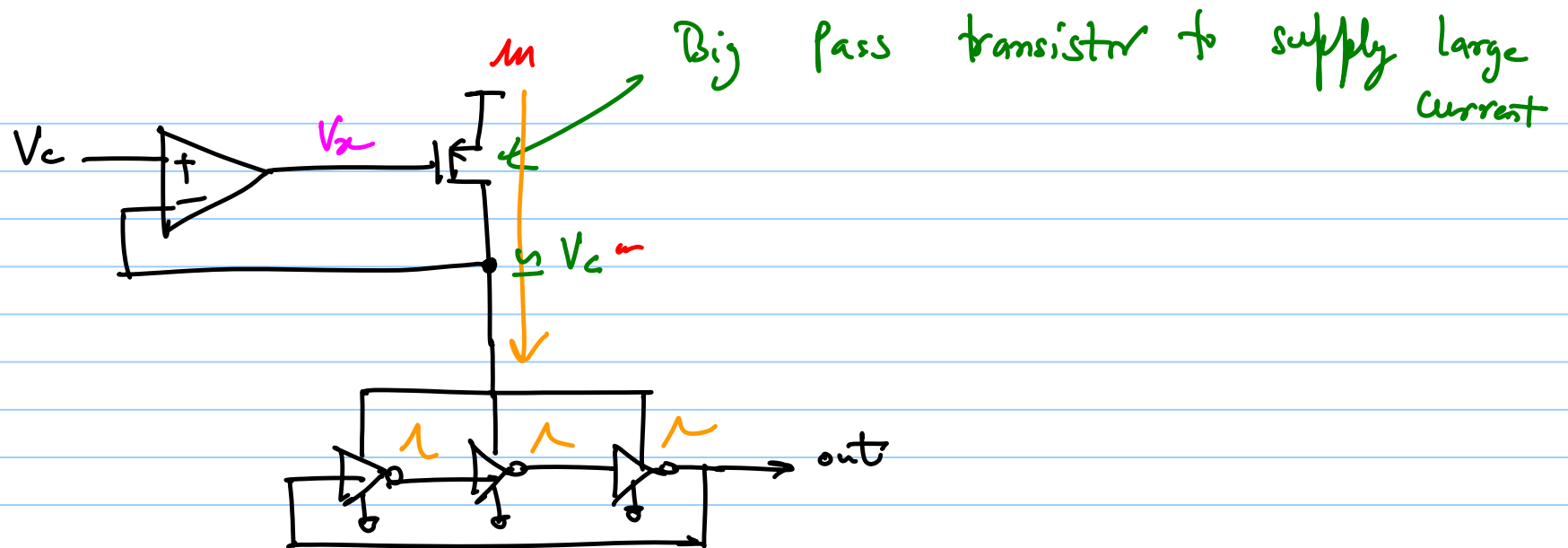* Opamp output swing limit limits the frequency tuning range



x Current is drawn from supply, not from OpAmp's output
 ↳ OpAmp is low-power


* Pass device alleviates opamp output swing requirements

* Trade off between pass device S_{je} & PSRR.

Oscillator Phase Noise


Ideal Oscillator

$$A \cos(\omega_c t)$$

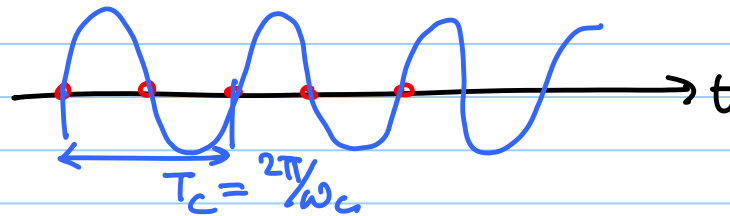


Noisy Oscillator

$$A \cos(\omega_c t + \phi_n(t))$$

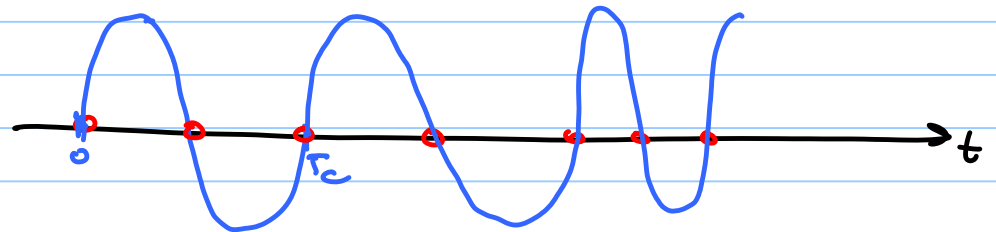


$\phi_n(t)$ is a random phase quantity that deviates zero crossings from multiples of T_c .

PSD:


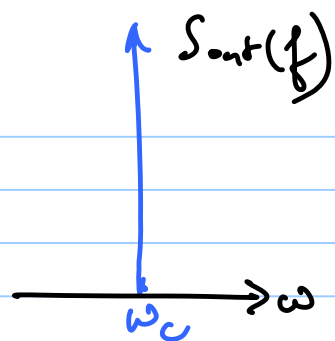


Ideal

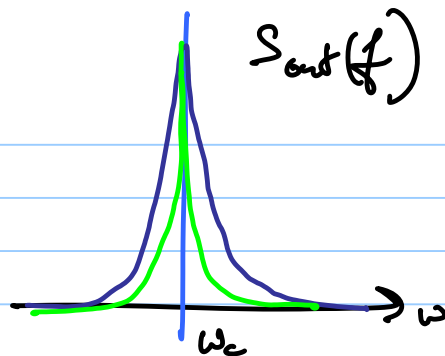

Real

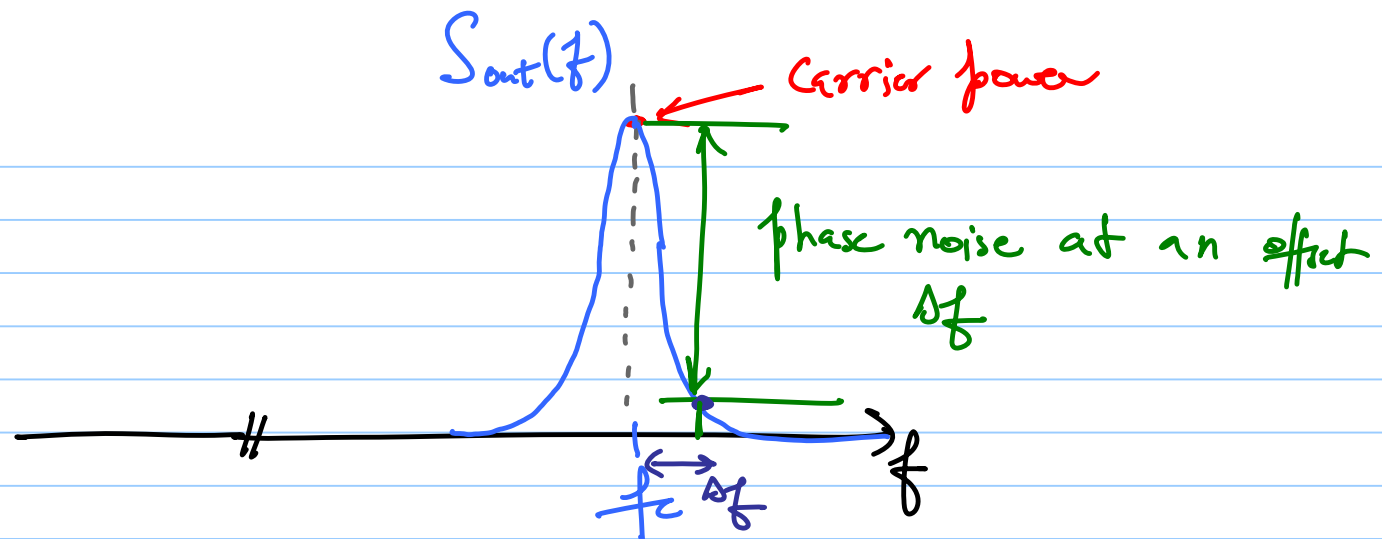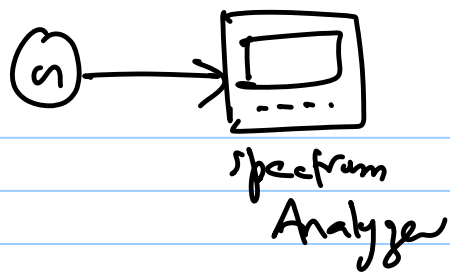$\Rightarrow$ Impulse is broadened by the phase noise



Ex GSM:

$< -115 \text{ dB}_c/\text{Hz}$ at 60 kHz offset