
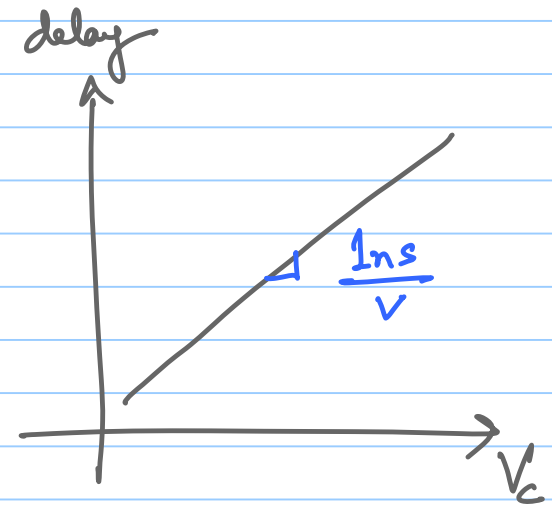


ECE 504 - Lecture 19


Note Title

10/26/2016

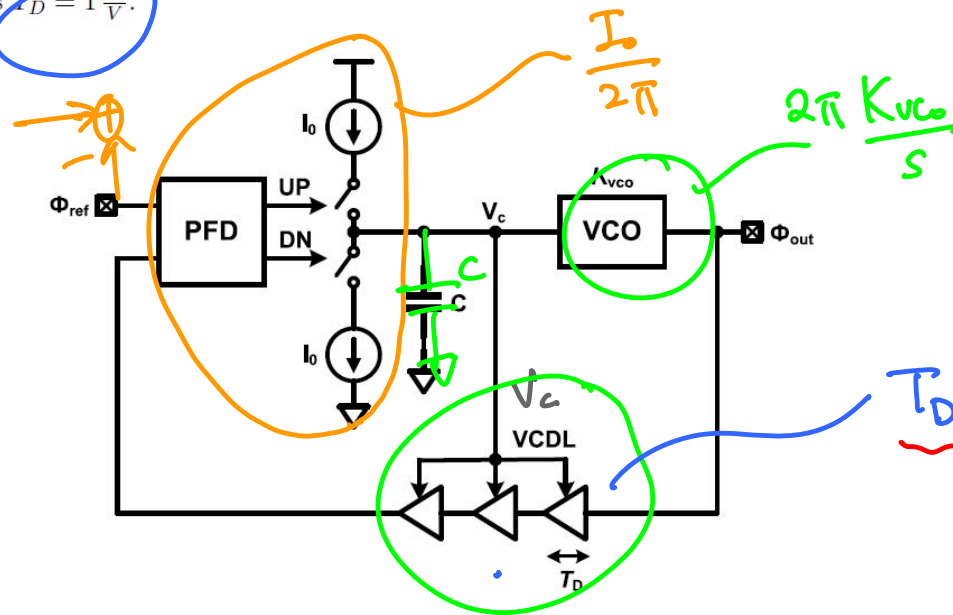- Consider an alternative PLL design shown below. Here, $K_{VCO} = 150 \frac{\text{MHz}}{\text{V}}$, $I_0 = 100 \mu\text{A}$, frequencies $f_{in} = f_{out} = 500 \text{ MHz}$, and the delay of each of the elements in the VCDL is given as $T_D = 1 \frac{\text{ns}}{\text{V}}$.


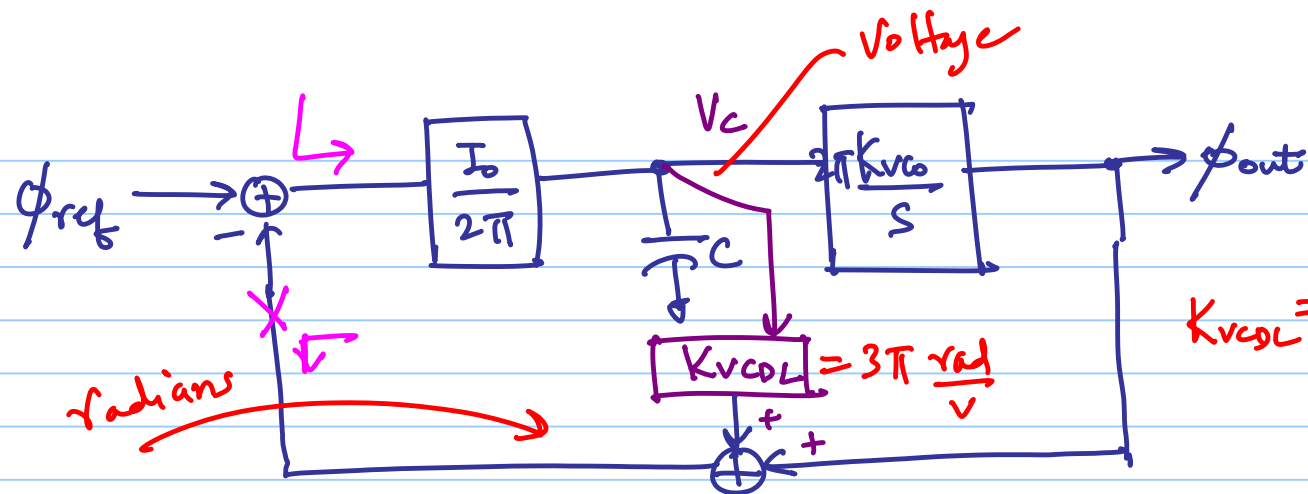
$$T_D \Rightarrow \frac{1 \text{ ns}}{\text{V}}$$




$$\begin{aligned}
 K_{vcdL} &= 3T_D \times \frac{2\pi}{T_{ck}} \text{ rad/V} \\
 &= 6\pi \cdot f_{ref} \cdot T_D \\
 &= 3\pi \frac{\text{rad}}{\text{V}}
 \end{aligned}$$

$$L(s) = \frac{I_0}{2\pi s C} \left(\overset{\text{integral}}{\frac{2\pi K_{vco}}{s}} + \overset{\text{prop paths}}{K_{vcdL}} \right)$$


$$= \frac{I_0}{2\pi \underline{s^2} C} [2\pi K_{vco} + s K_{vcdL}] \rightarrow \textcircled{1}$$
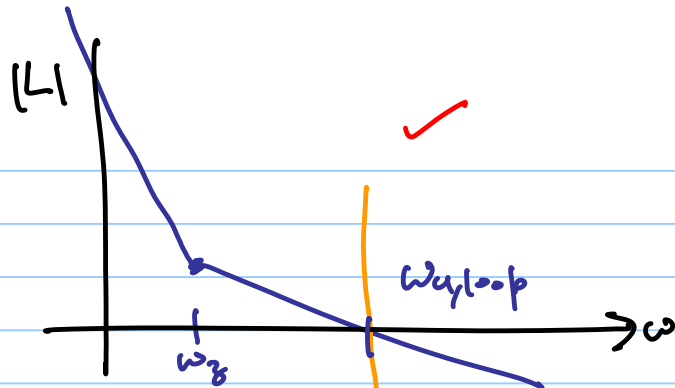
$$\omega_z = \frac{2\pi K_{vco}}{K_{vcdL}} \quad \omega_z = \frac{1}{RC}$$



Type-II, 2nd-order system
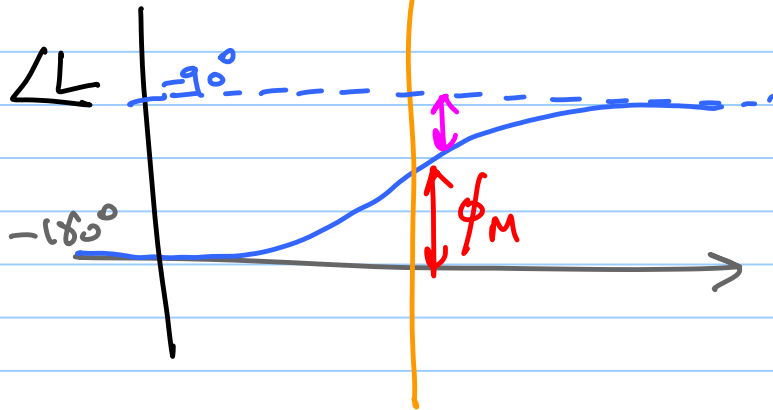
$$\phi_M = \tan^{-1} \left(\frac{\omega_{u(loop)}}{\omega_z} \right) = 45^\circ$$



$$\omega_{u(loop)} = \omega_z \cdot \tan(45^\circ)$$

$$L(s) = \frac{2\pi I_o}{2\pi C s^2} \left[1 + \frac{s K_{vcl}}{2\pi K_{vco}} \right]$$

$$|L(j\omega_{u(loop)})| = 1$$

~~$\omega_{u(loop)} \gg \omega_z$~~

$$\omega_n, \zeta = \omega_z$$


$$\hookrightarrow C = ?$$

(d) $H_{CL}(s) = \frac{\phi_{out}}{\phi_{ref}}(s) = \frac{G(s)}{1+L(s)} \quad \because N=1$


$$= \frac{L(s)}{1+L(s)}$$

(e) $\nearrow$ plug-in $L(s)$

14

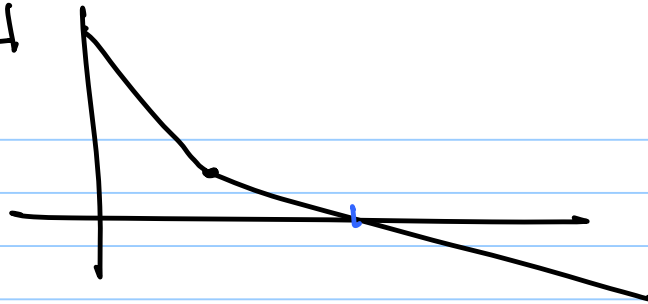


$$\left| \frac{L}{1+L} \right|$$

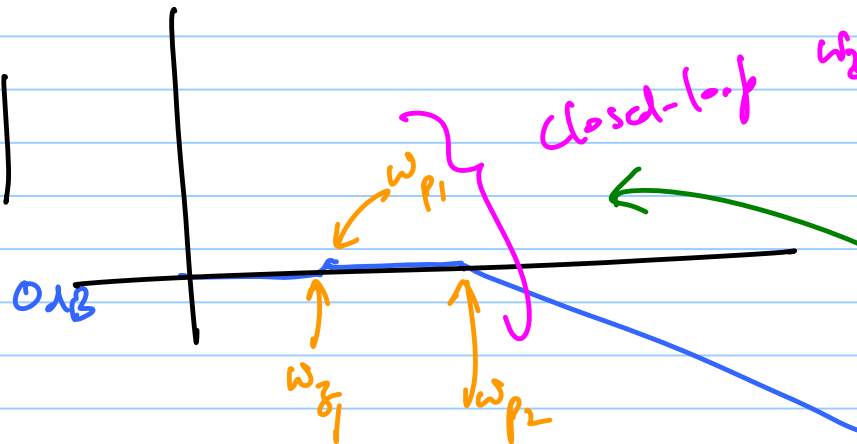

closed-loop ω_z & ω_p 's

closed loop Bode Mag

$\therefore N=1$

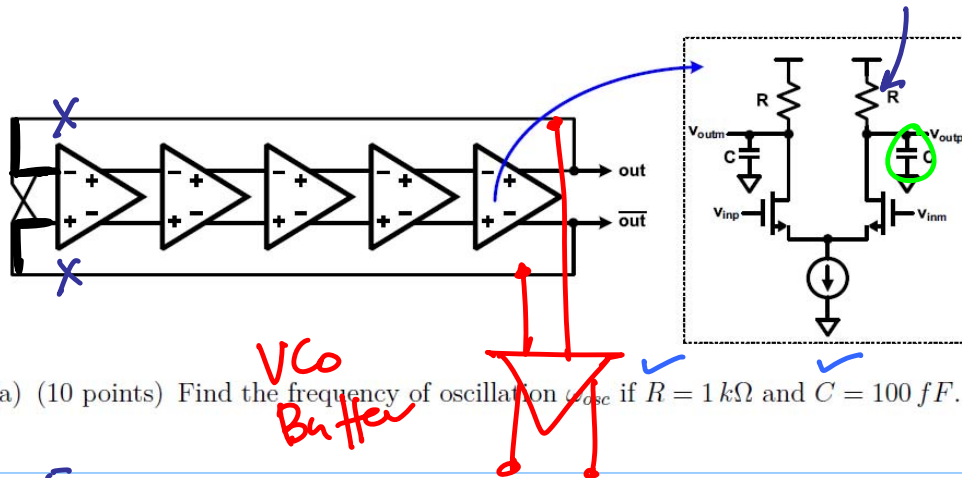

(a) (10 points) Find the frequency of oscillation ω_{osc} if $R = 1 \text{ k}\Omega$ and $C = 100 \text{ fF}$.

$$H(s) = \frac{A_0}{(1 + s/\omega_0)}$$

$$\omega_0 = \frac{1}{RC}$$

$$A_0 = g_m R$$

$$L(s) = \frac{A_0^5}{(1 + s/\omega_0)^5}$$

$$\angle L(j\omega) = -5 \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

$$|\angle L(j\omega)| = 180^\circ$$

$$\tan^{-1}\left(\frac{\omega_{osc}}{\omega_0}\right) = \frac{180^\circ}{5} \Rightarrow \omega_{osc} = \omega_0 \tan(36^\circ) = 7.265 \text{ Mrad/s}$$

By Barkhausen criterion

$$= 1.156 \text{ GHz}$$

$$(b) \quad |L(j\omega_{osc})| = 1$$



$$\left| \frac{g_m R}{\sqrt{1 + \left(\frac{\omega_{osc}}{\omega_0}\right)^2}} \right|^5 = 1 \quad \Rightarrow$$

$$\frac{g_m R}{\sqrt{1 + \tan^2 36^\circ}} = 1$$


$$g_m = ? = 1.236 \frac{\text{mA}}{\text{V}}$$

$$g_m \triangleq \frac{2\text{mA}}{\text{V}}$$

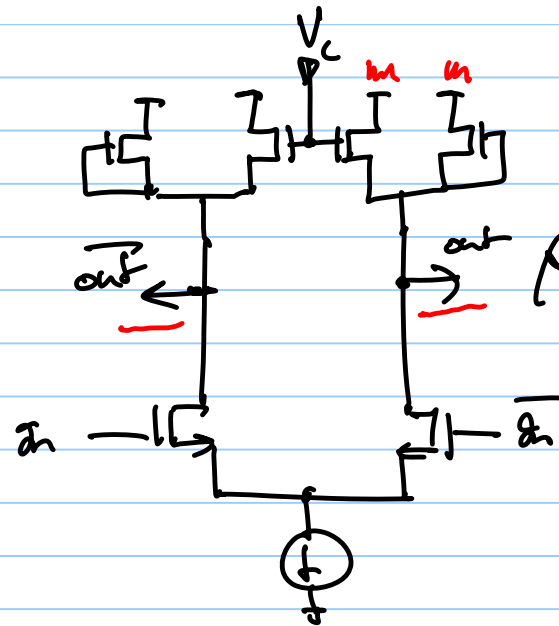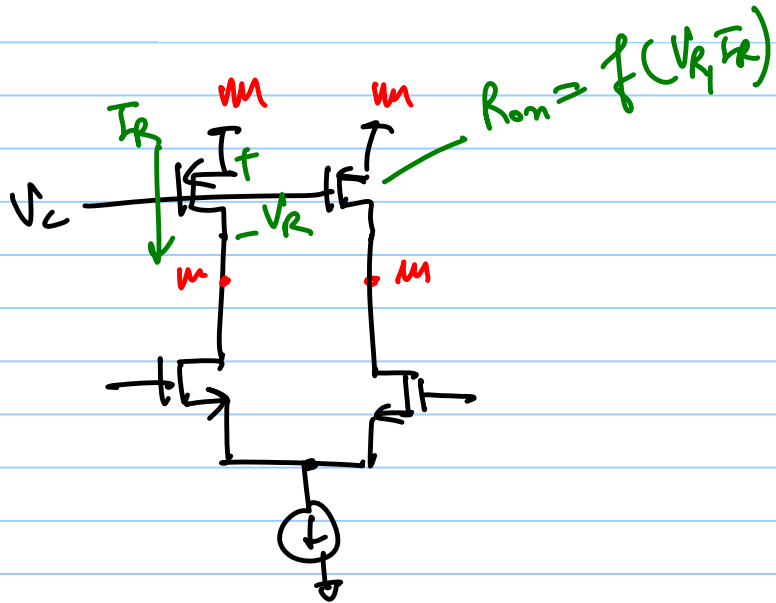- (c) (10 points) A 5-stage VCO needs to be designed based upon the above schematic. Draw schematic of a delay cell to achieve this with best possible PSRR.




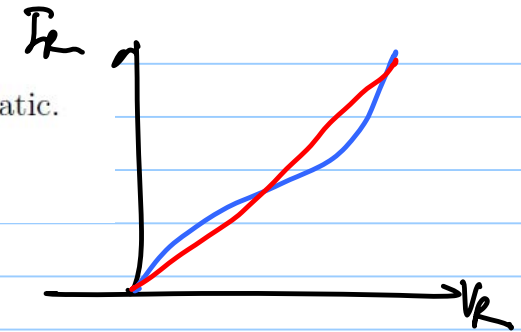Symmetric delay cell
to average out
variations in R_{out}





1.8V


out
out

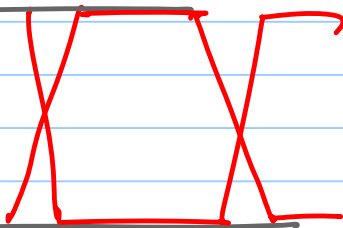


VCO Buffer
output

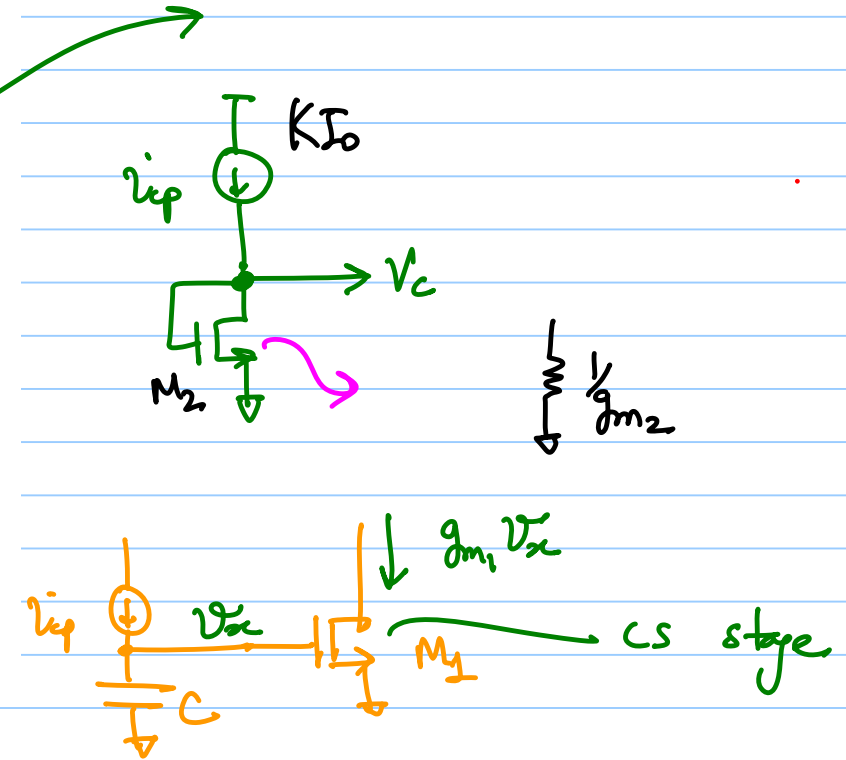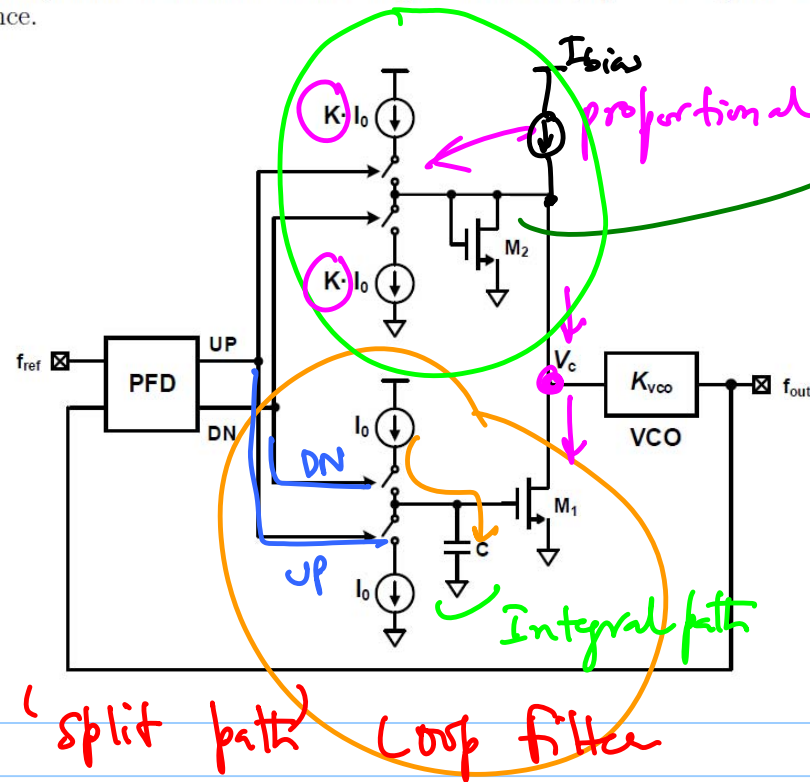3. In the resistor-less PLL shown below, assume that the VCO gain K_{VCO} is positive, all transistors operate in saturation with output resistance, $r_o = \infty$. Ignore the NMOS capacitance.



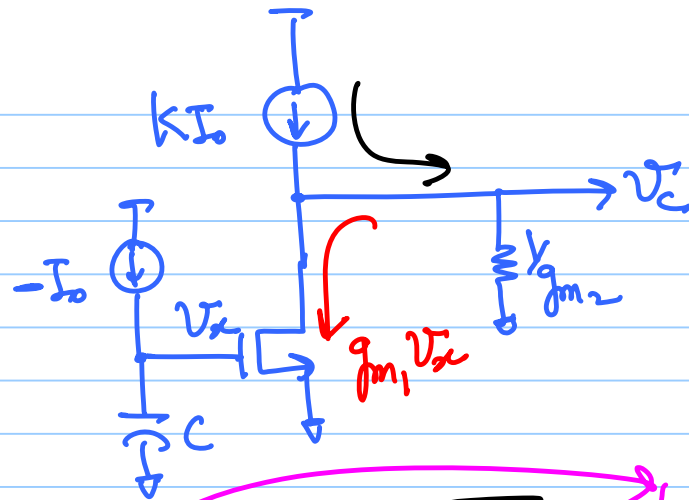
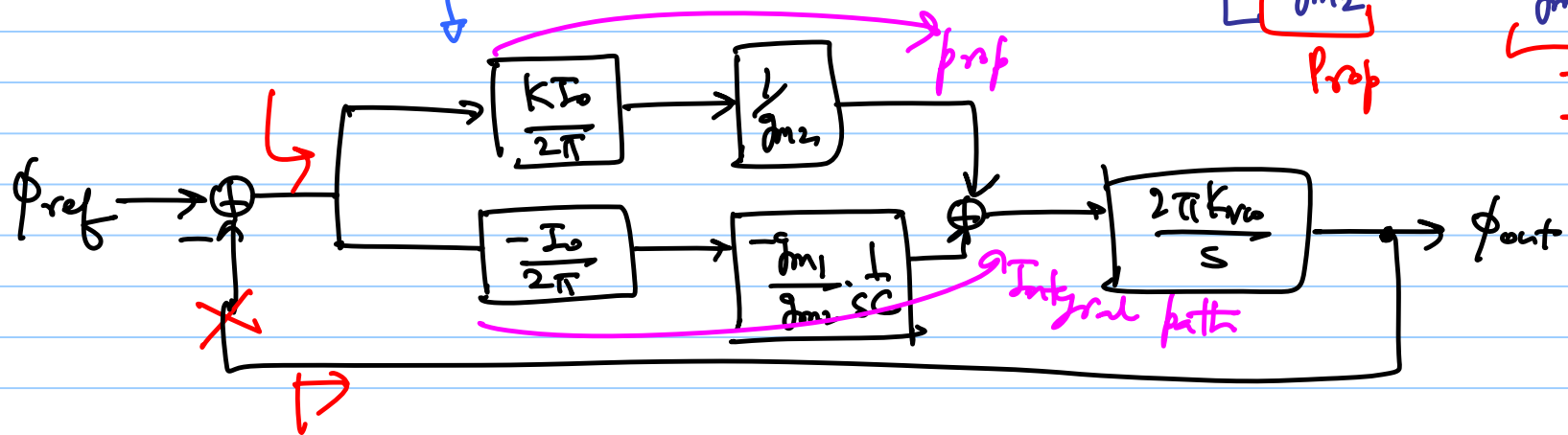
$$\begin{aligned}
 V_c &= \left(KI_0 - g_{m1} V_c \right) \frac{1}{g_{m2}} \\
 &= \left[KI_0 + g_{m1} \frac{I_0}{sC} \right] \cdot \frac{1}{g_{m2}} \\
 &= \underbrace{\left[\frac{KI_0}{g_{m2}} \right]}_{\text{Prop}} + \underbrace{\left[\frac{g_{m1}}{g_{m2}} \cdot \frac{I_0}{sC} \right]}_{\text{Integral}}
 \end{aligned}$$







$$b) \quad F(s) = \frac{V_c(s)}{I_0} = \frac{K}{g_{m2}} + \left(\frac{g_{m1}}{g_{m2}} \right) \cdot \frac{1}{sC}$$

$$c) \quad L(s) = \frac{I_0}{2\pi} F(s) \cdot \frac{K_{vco}}{s} \Rightarrow$$

$$\omega_z = \frac{g_{m1}}{K C} \sim \frac{1}{RC}$$

e) Maximizing K helps reduce Capacitor Area for the same zero location.

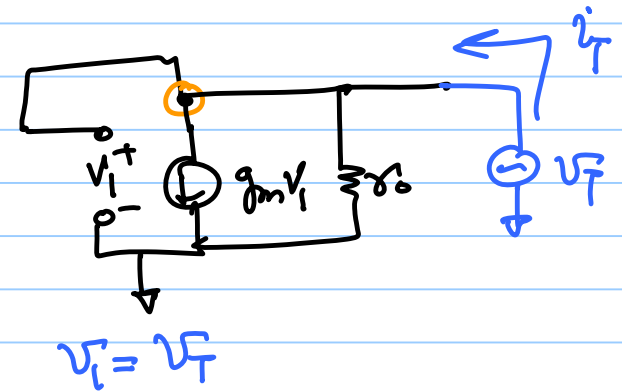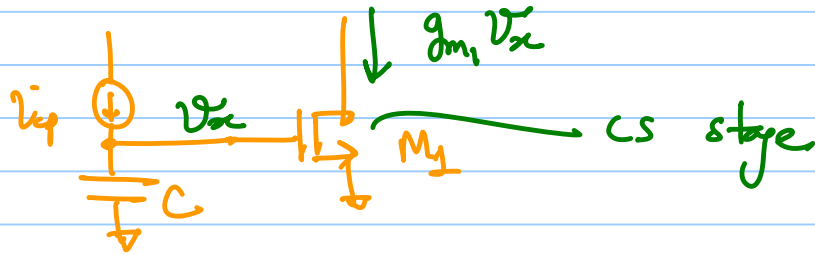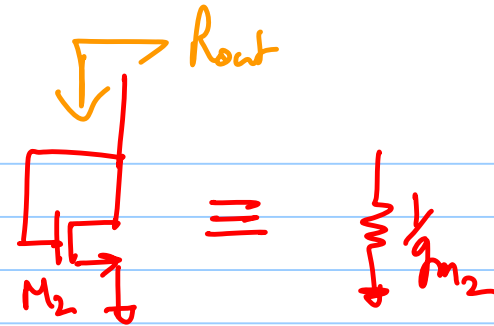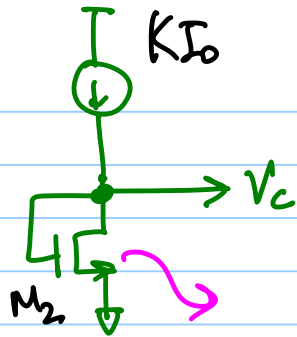d) $H_{cc}(s) \rightarrow$ same as problem 1



$$KCL \Rightarrow R_{out} = \frac{V_T}{i_T} = \frac{1}{g_m} \parallel r_o = \frac{1}{g_m}$$

$$\begin{array}{c} \downarrow i_d = g_m v_{gs} \\ v_{gs}^+ \text{---} \boxed{\text{---}} \downarrow \text{C.S.} \\ v_{gs}^- \end{array}$$