
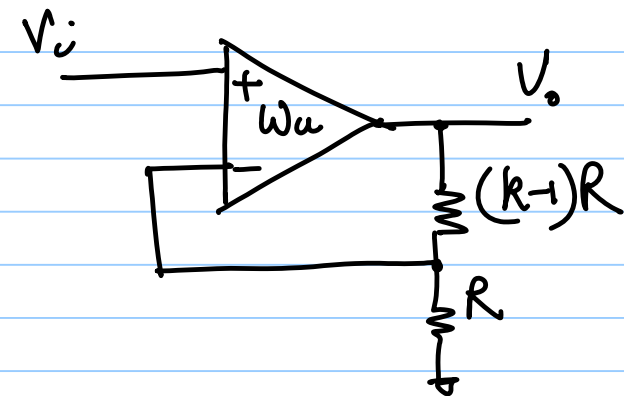


ECE 4/504 - Lecture 2

Note Title

8/24/2016




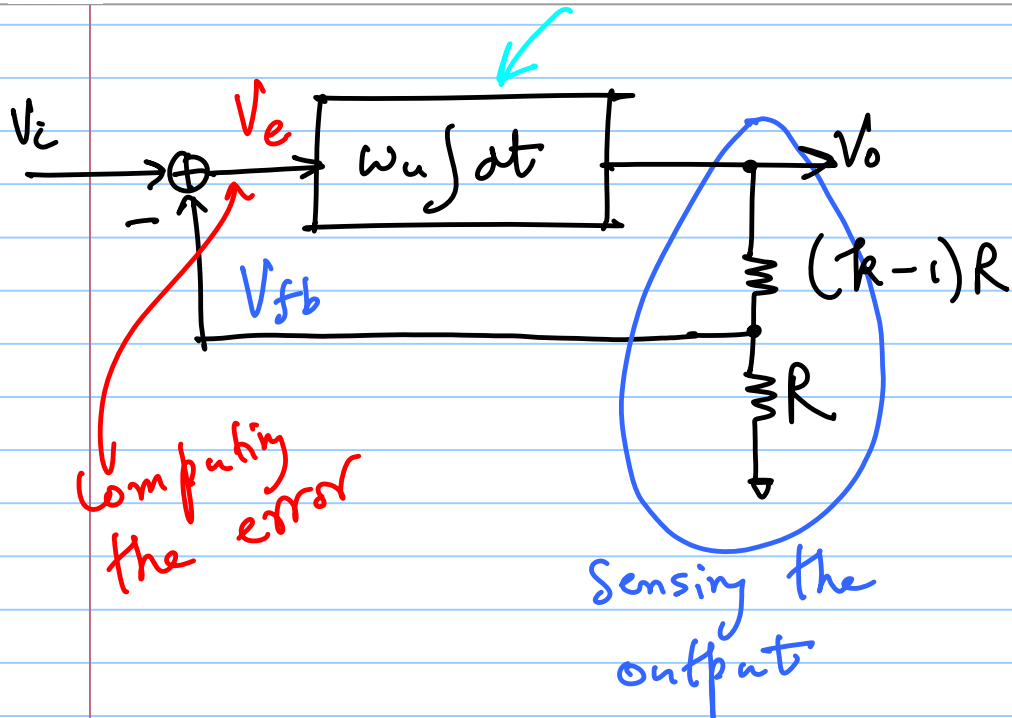


desired value $\rightarrow V_i$
sensed value $\rightarrow V_{fb} = \frac{V_o}{k}$

when $V_e = V_i - V_{fb} \rightarrow 0$
 $\Rightarrow V_i \rightarrow \frac{V_o}{k}$
 $\Rightarrow \boxed{V_o \rightarrow k V_i}$

In steady-state error $\rightarrow 0 \Rightarrow V_o = k V_i$

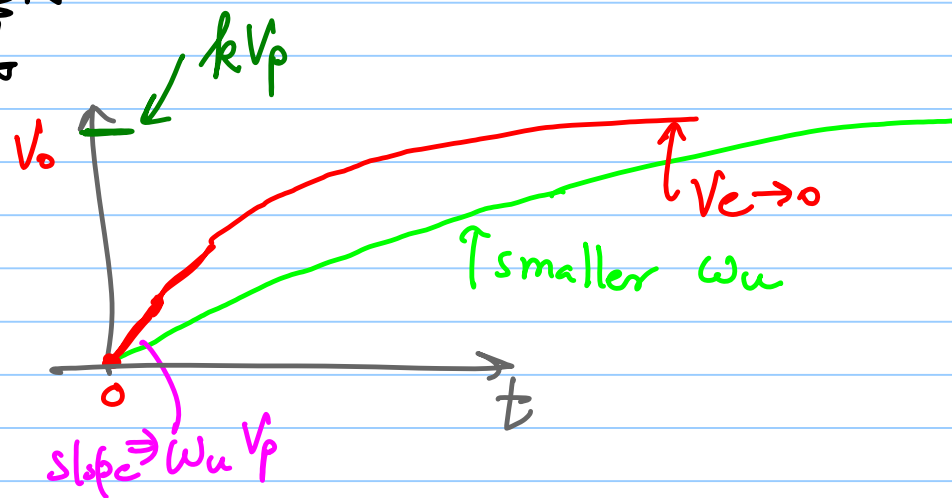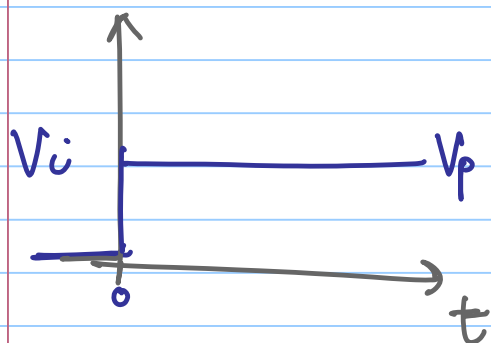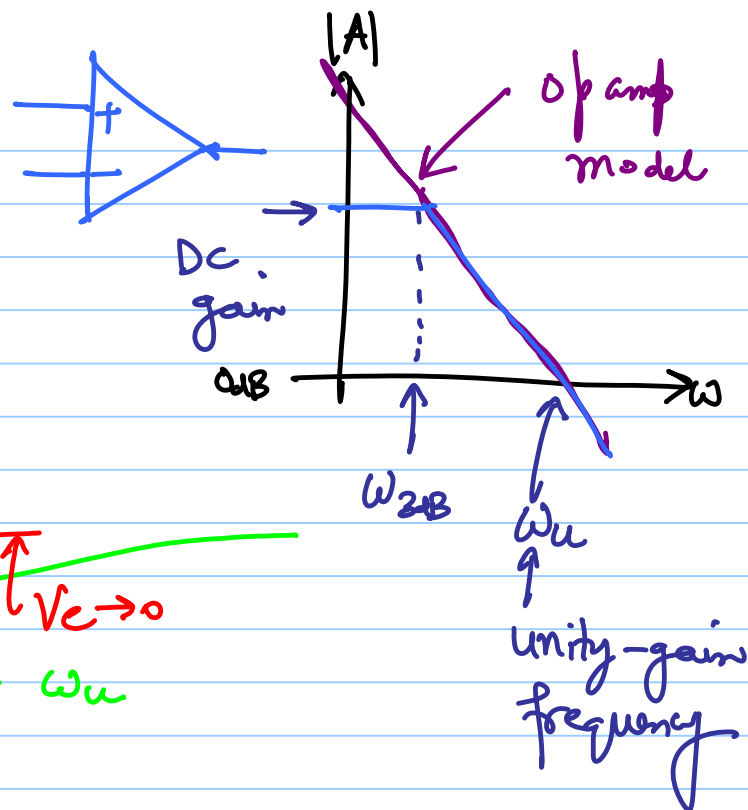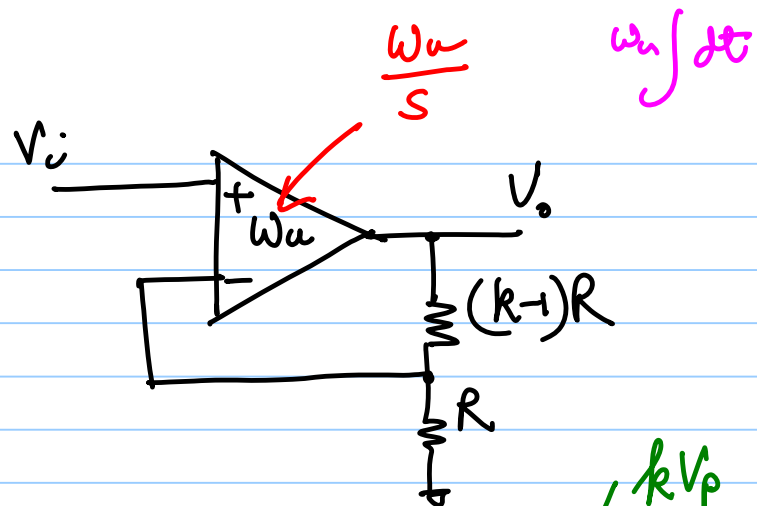for any other error $\neq 0$, the output will change continuously.



Diff Σ :

$$\frac{dV_o}{dt} = \omega_u V_e = \omega_u \left(V_i - \frac{V_o}{k} \right)$$

$$\Rightarrow \frac{1}{\omega_u} \cdot \frac{dV_o}{dt} = V_i - \frac{V_o}{k}$$

$$V_o(t) = kV_p \left(1 - e^{-\frac{\omega_u t}{k}} \right) \cdot u(t)$$

$$\frac{1}{\tau}$$

time constant $\tau = \frac{k}{\omega_u}$

Closed-loop Gain $\times$ BW =


$$\cancel{k} \times \frac{\omega_u}{\cancel{k}}$$

$$= \omega_u$$

$\Rightarrow$ Gain-BW product

Detailed information
on spams

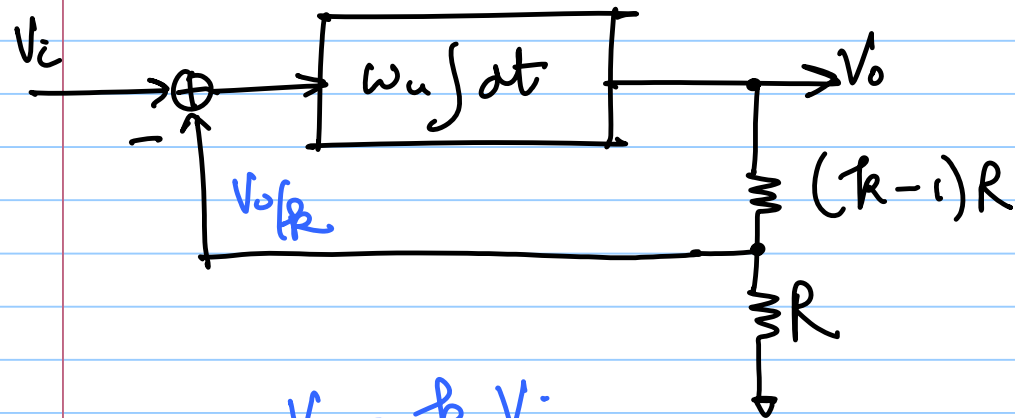
http://lumerink.com/pages/teaching_arxiv.html




$$V_o = k V_i$$


comparing $\frac{V_o}{k}$ & V_i
 integrating V_e till $V_e \rightarrow 0$

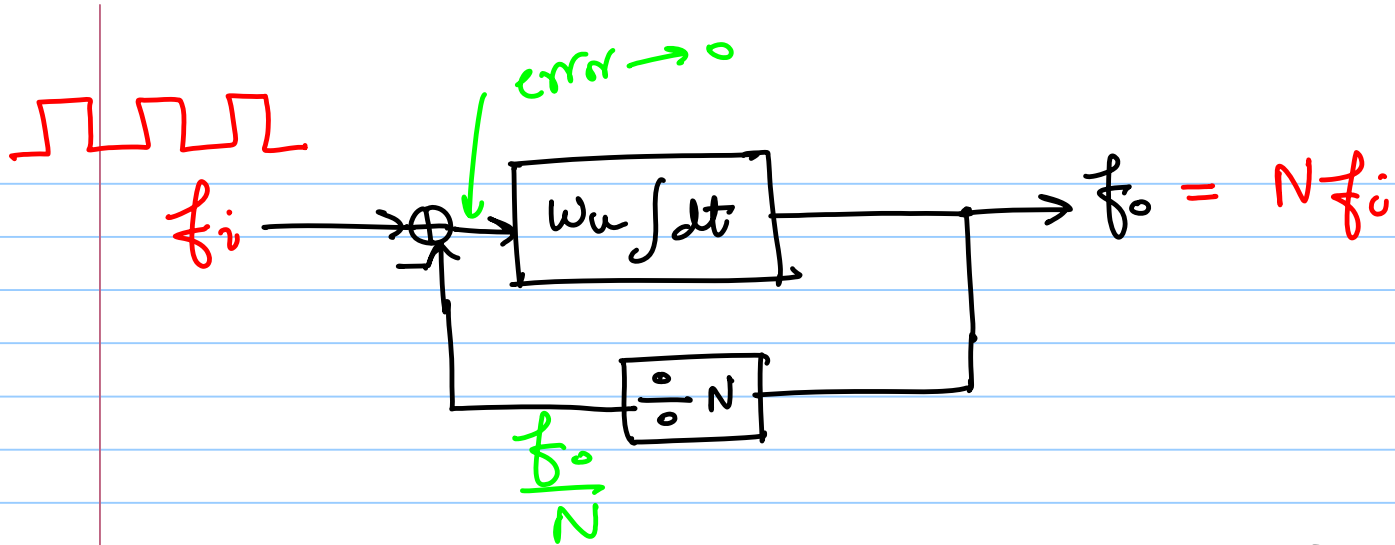
desired $f_o = k \times f_i$ ← input frequency




frequency Divider?

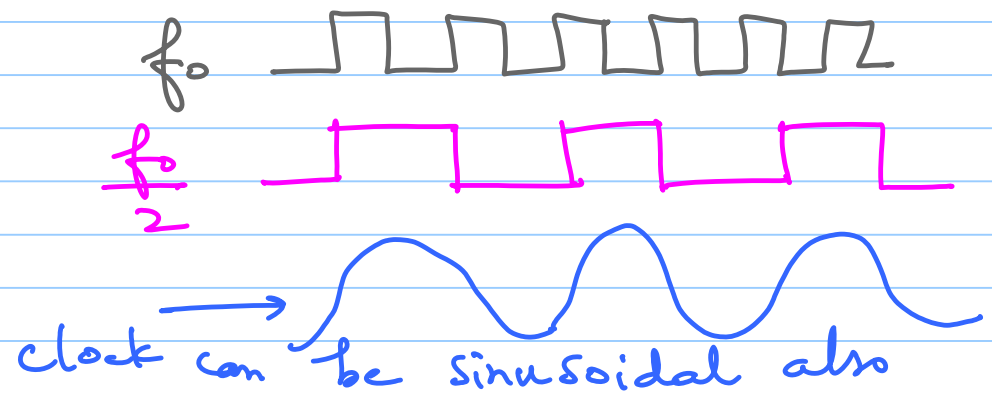

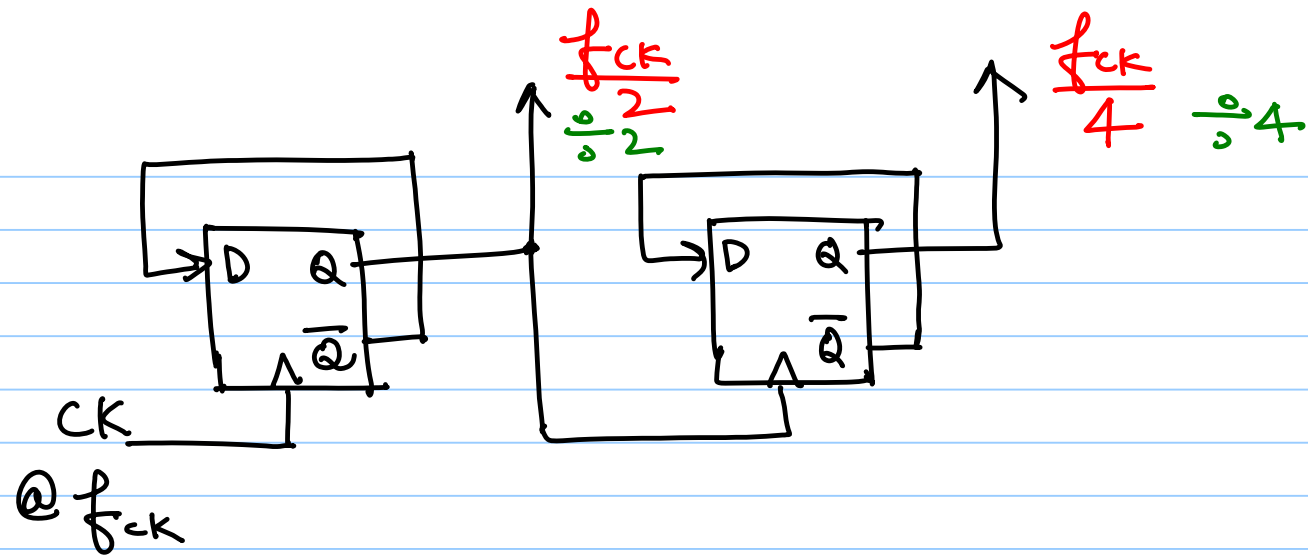

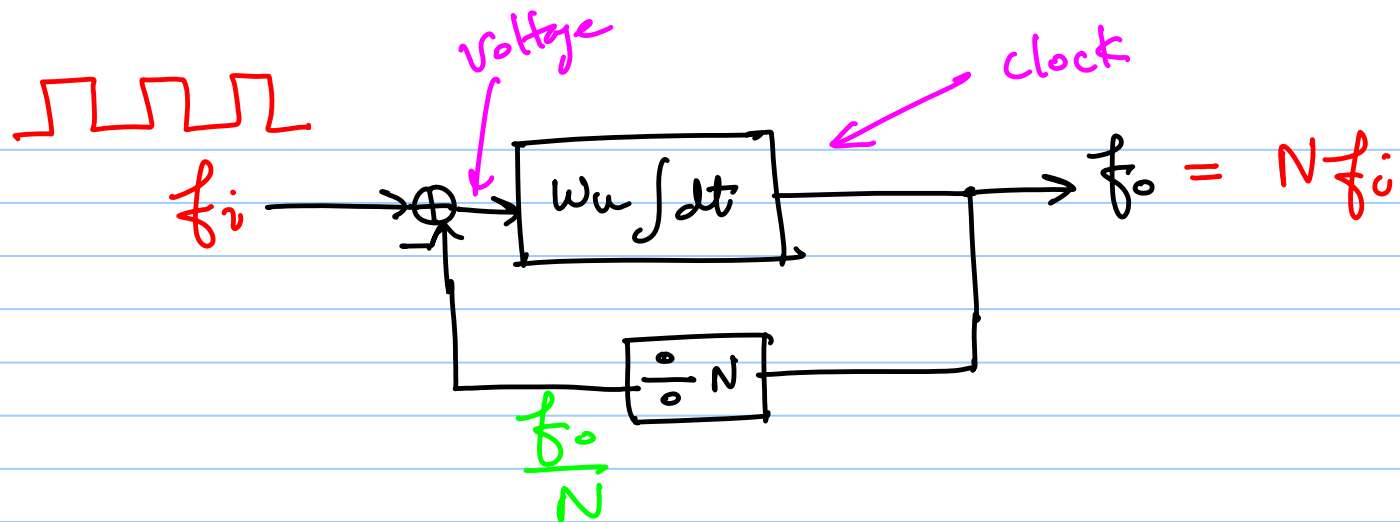


Voltage Controlled Oscillator (VCO)

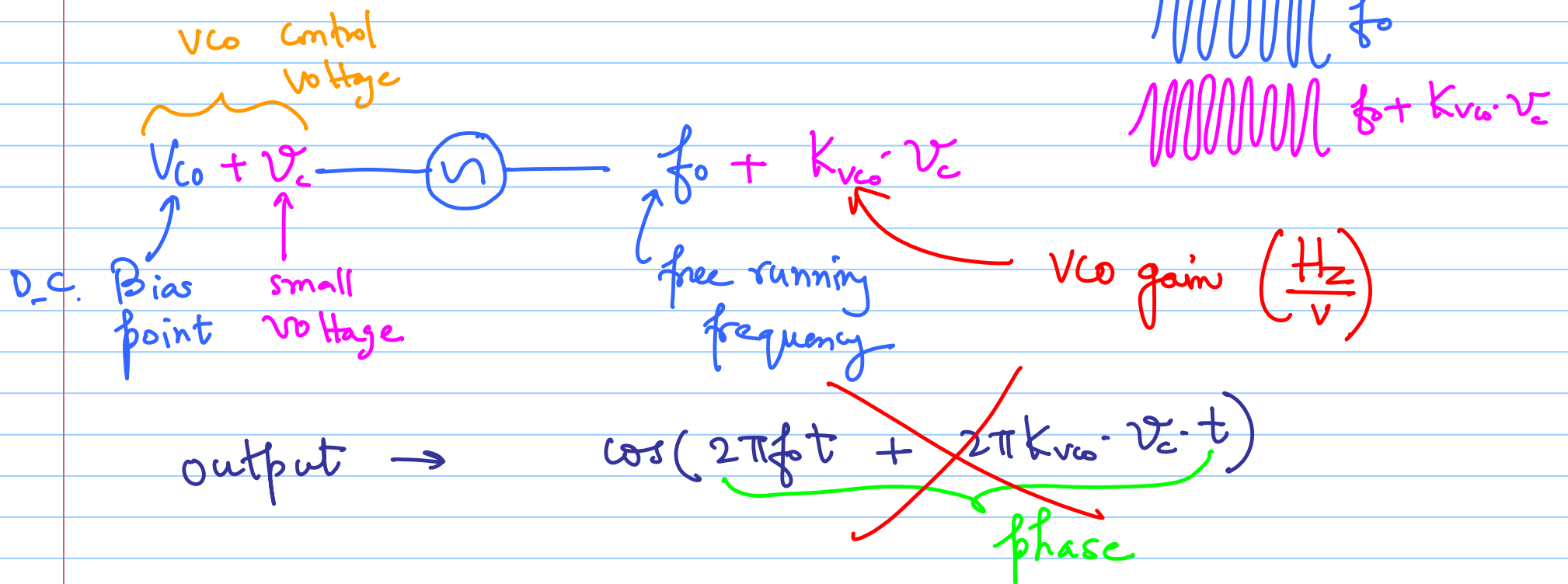

In reality, phase is always continuous

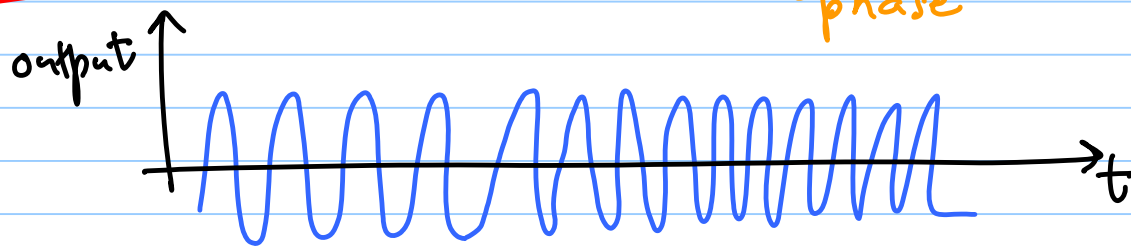output $\Rightarrow$ $\cos \left(\underbrace{2\pi f_0 t + 2\pi K_{VCO} \int_0^t V_c(t) dt}_{\text{phase}} \right)$



pulse shape
can be any periodic
pulse

V_{CO} $V_C + V_C$
The frequency change doesn't happen
instantaneously.

Vco output :


$$\text{phase: } \phi(t) = \underbrace{\cos(2\pi f_0 t)}_{\text{free running}} + \underbrace{2\pi K_{VCO} \int V_c(t) dt}_{\text{incremental part of the phase}}$$

D.C. $V_c > 0$


incremental part of the phase

$V_c \Rightarrow$ cosinusoidal 

D.C. $V_c < 0$

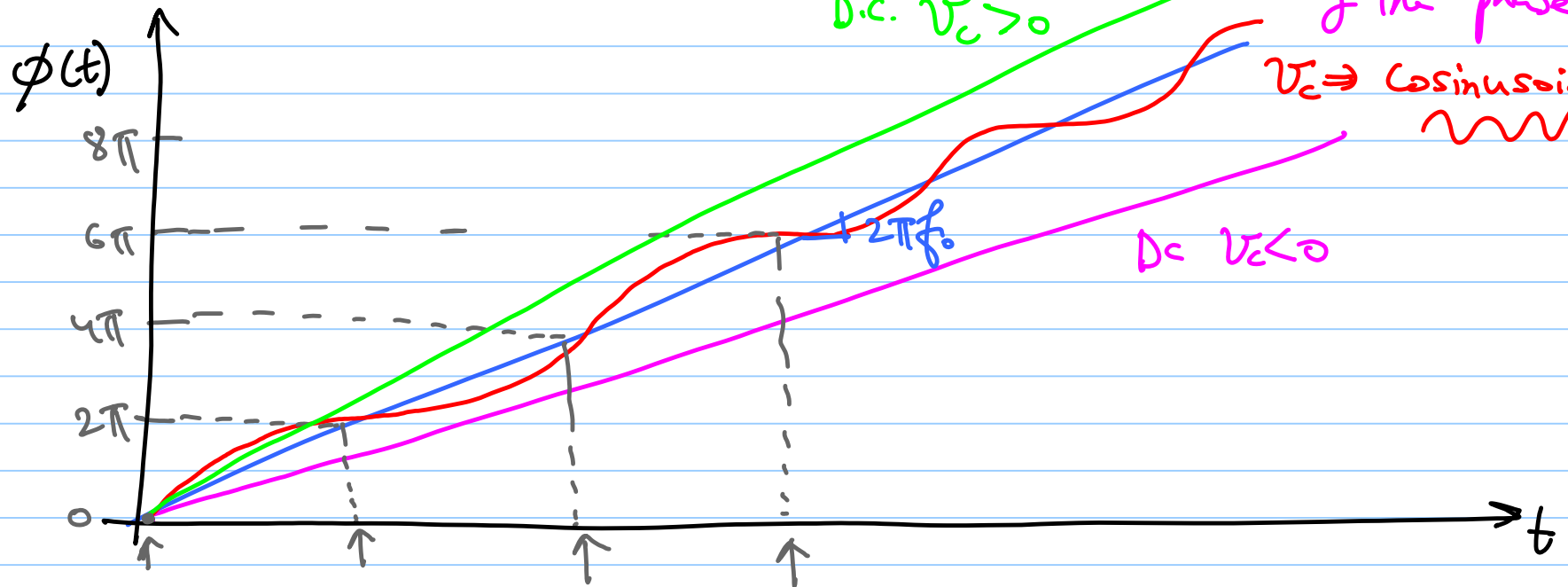

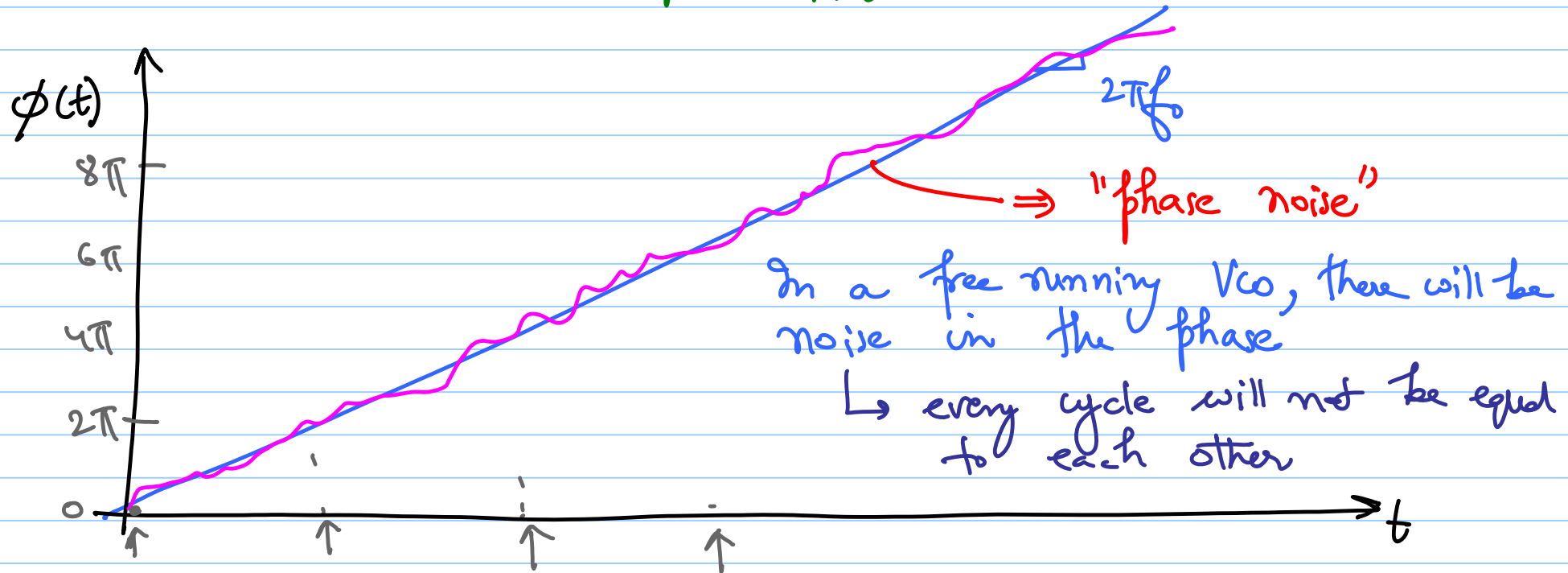In a real amplifier
output $\Rightarrow kV_i + \text{noise}$



* We choose phase $\phi(t)$ as the basic variable in PLL design


instantaneous frequency; $f_i(t) = \frac{1}{2\pi} \frac{d\phi(t)}{dt}$

$$\phi(t) = 2\pi f_0 t + 2\pi K_{vco} \int_0^t v_c(t) dt$$

$$\Rightarrow \frac{d\phi(t)}{dt} = 2\pi f_0 + 2\pi K_{vco} v_c(t)$$

instantaneous frequency $f_i(t) = f_0 + K_{vco} \cdot v_c(t)$

Frequency Divider

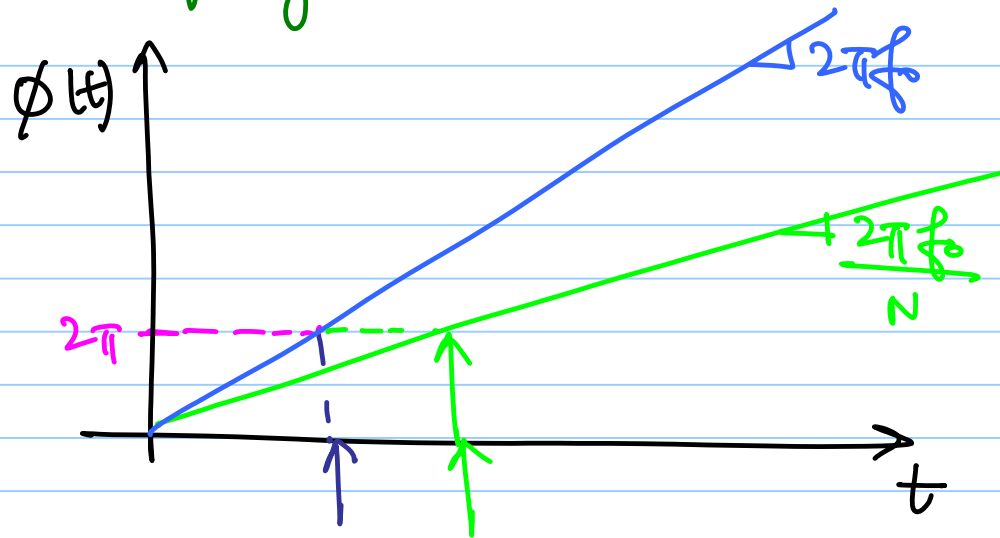

$$f_0 \rightarrow \boxed{\div N} \rightarrow \frac{f_0}{N}$$

↑
green arrow

The divided phase ($\div N$) takes ' N ' longer steps than the output of the VCO.

$$\phi_{out} \rightarrow \boxed{\div N} \rightarrow \phi_{Div}$$



$$\phi_{out} \rightarrow \boxed{\div N} \rightarrow \phi_{Div}$$

gain of $1/N$

