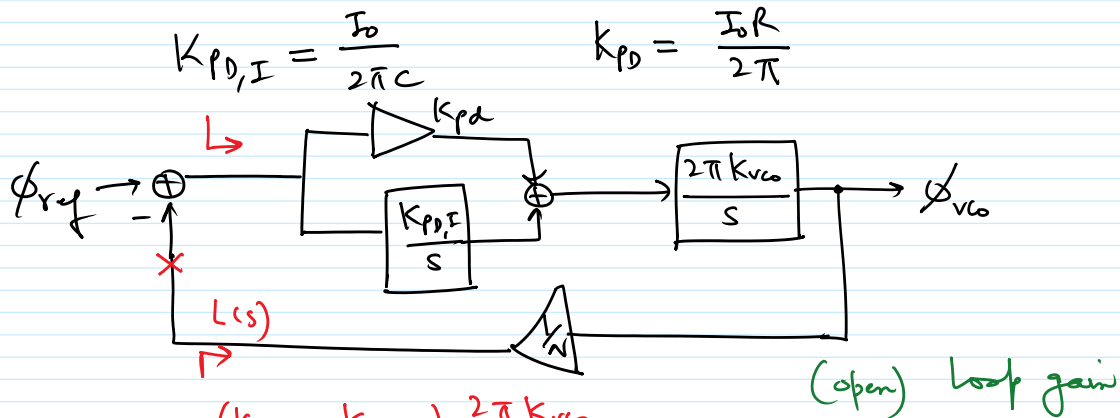


ECE 504 - Lecture 8



$$L(s) = \left(K_{pd} + \frac{K_{pd,I}}{s} \right) \frac{2\pi K_{vco}}{s \cdot N}$$

$$= \left(\frac{I_0 R}{2\pi} + \frac{I_0}{2\pi C \cdot s} \right) \frac{2\pi K_{vco}}{s \cdot N} = \frac{(1 + sRC) K_{vco} I_0 R}{N \cdot s^2 \cdot RC}$$


(open) loop gain

$$L(s) = \frac{(1 + sRC) K_{vco} I_0 R}{N s^2 RC}$$

$$= \frac{(1 + s/\omega_z)}{s^2} \cdot \frac{K_{vco} I_0}{NC}$$

@ $\omega = \omega_{u,loop}$, $|L(j\omega)| = 1$

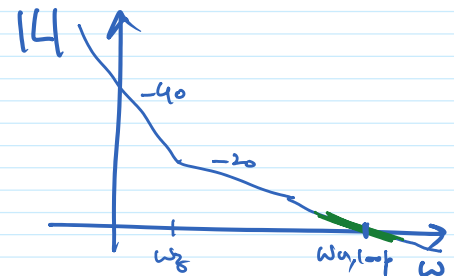around unity-gain crossing
 $1 + sRC \approx sRC$



$$\omega_z = \frac{1}{RC}$$

$$\frac{\omega}{\omega_z} \gg 1$$

$$L(s) \approx \frac{sRC \cdot K_{vco} I_0 R}{s^2 RC \cdot N} = \frac{K_{vco} I_0 R}{s \cdot N} = \frac{\alpha}{s}$$

where $\alpha = \frac{K_{vco} I_0 R}{N}$

$$|L(j\omega)| = 1, \omega = \omega_z$$

$$\omega_{u,loop} \gg \omega_z$$

$$\omega_{u,loop} \approx \frac{K_{vco} I_0 R}{N}$$


$$\omega_{u,loop} \gg \omega_z$$

$$\omega_{u,loop} = \alpha \sqrt{\frac{1}{2} \times (1 + \sqrt{1 + 4/z^2})}$$

$$z = RC = \frac{1}{\omega_z}$$

* Understanding $\omega_{u,loop} = \frac{I_0 R K_{vco}}{N}$

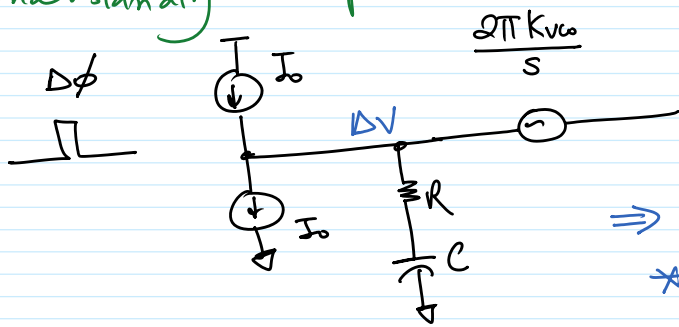* Understanding $\omega_{u,loop} = I_o R K_{vco} / N$



$$\Rightarrow \Delta\omega = \frac{I_o R}{2\pi} \times 2\pi K_{vco} \times \Delta\phi$$


$$= I_o R K_{vco} \cdot \Delta\phi$$

$\Rightarrow$

* current pulse I_o is applied for $\Delta\phi$ time

$$\Rightarrow \text{voltage increment in one cycle} = \frac{I_o R \cdot \Delta\phi}{2\pi}$$
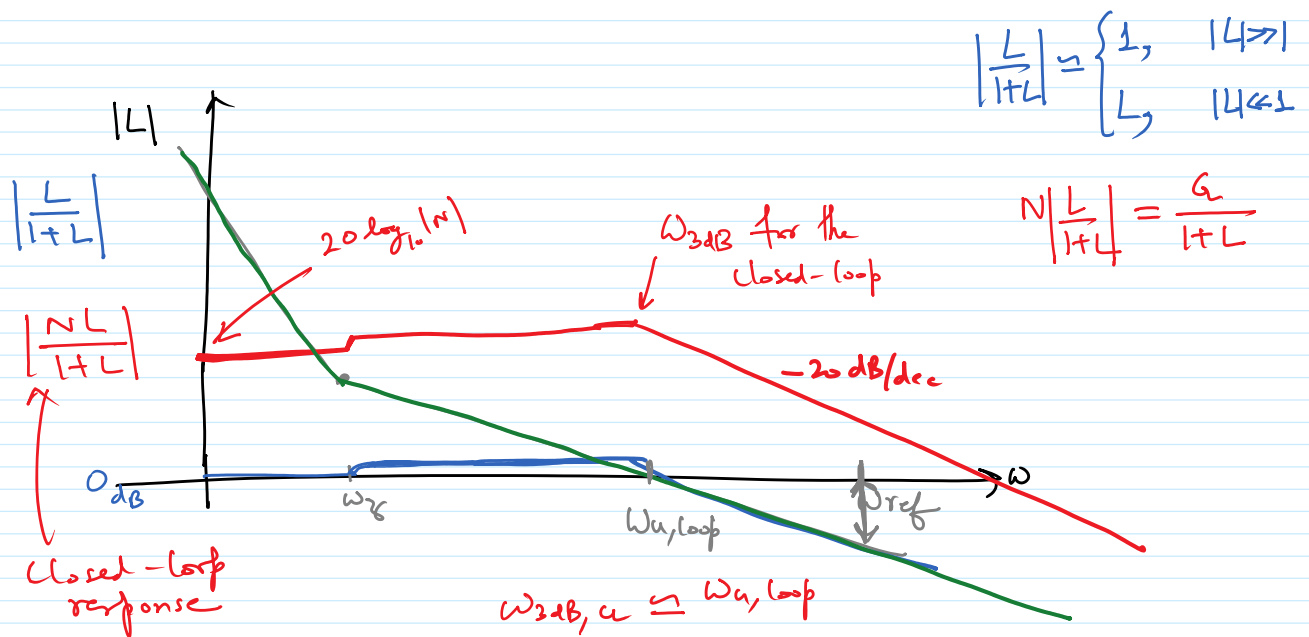
$$\Rightarrow \text{frequency increment} \Rightarrow I_o R K_{vco} \cdot \Delta\phi$$




$\omega_{ref} \gg \omega_{u,loop}$ to minimize "reference feedthrough" at ω_{ref}


$\omega_{ref} > 10 \omega_{u,loop}$

loop-bandwidth, $\omega_{3dB} \approx \omega_{u,loop} = \frac{K_{vco} I_o R}{N}$

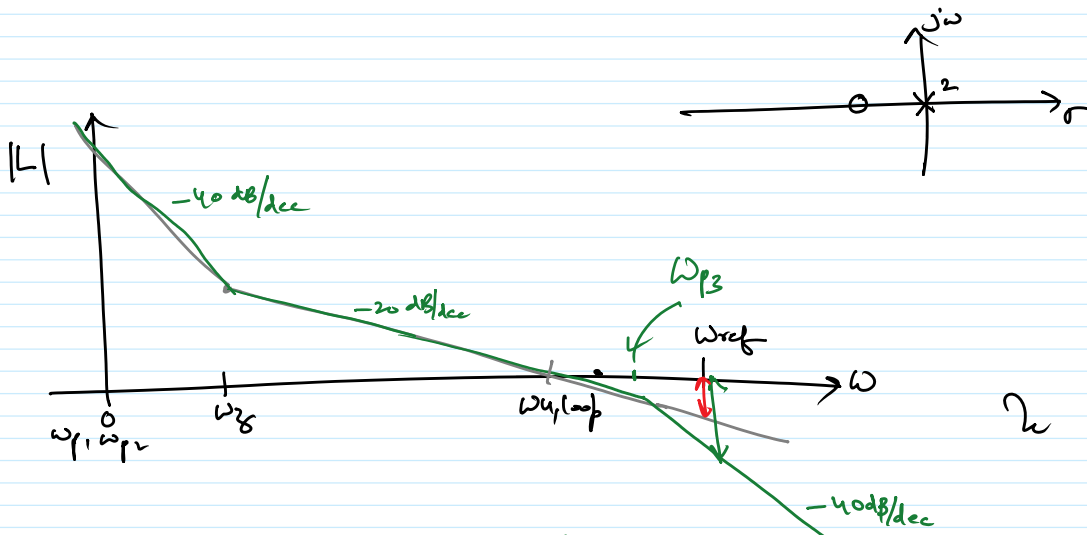* A higher $\omega_{u,loop} \Rightarrow$ PLL settles faster



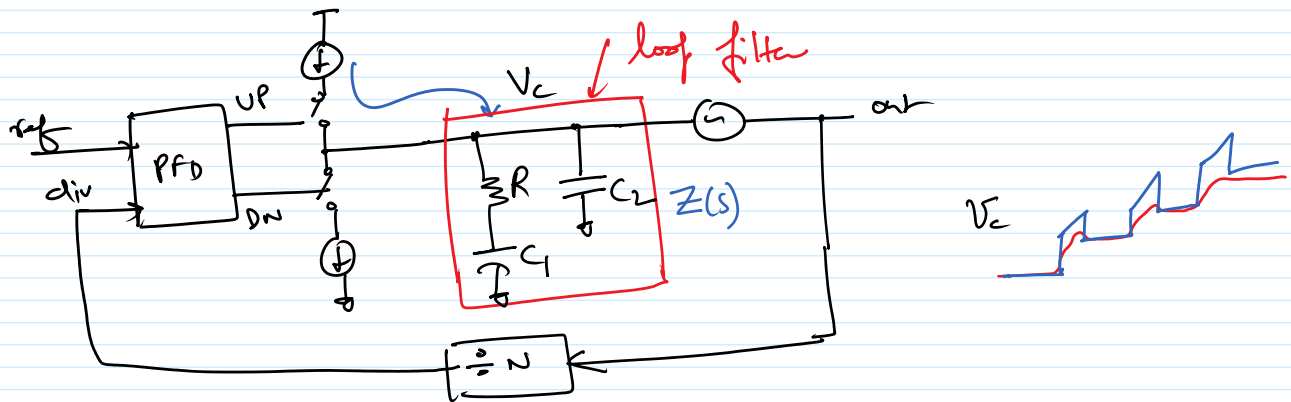Add a third pole $\Rightarrow$ higher reference feedthrough
 $\rightarrow$ can reduce phase margin and affect stability.




$$L(s) = \frac{I_o \cdot Z(s)}{2\pi} \cdot \frac{2\pi K_{vco}}{s \cdot N} = \frac{K_{vco} \cdot I_o}{s \cdot N} \cdot Z(s) \leftarrow \text{loop filter impedance}$$

Before $Z(s) = R + \frac{1}{sC_1}$

Now with the addition of C_2
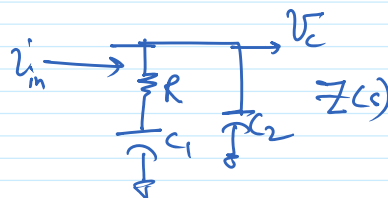
$$Z(s) = \left(R + \frac{1}{sC_1} \right) \parallel \frac{1}{sC_2}$$



$$= \frac{(R + \frac{1}{sC_1}) \cdot \frac{1}{sC_2}}{R + \frac{1}{sC_1} + \frac{1}{sC_2}} = \frac{(1 + sRC_1)}{s(C_1 + C_2)(1 + sR \frac{C_1 C_2}{C_1 + C_2})}$$

$$Z(s) = \frac{(1 + sRC_1)}{s(C_1 + C_2)(1 + sR \cdot C_{||}C_2)}$$

where $a \parallel b = \frac{ab}{a+b}$

$$\omega_p \Rightarrow \frac{1}{R(C_{||}C_2)}$$

$$L(s) = \frac{K_{v\omega} I_o}{s \cdot N} \cdot Z(s)$$

$$= \frac{K_{v\omega} I_o}{s^2 (C_1 + C_2) N} \cdot \frac{(1 + sRC_1)}{(1 + sR \cdot C_{||}C_2)} = \frac{K_{v\omega} I_o (1 + s/\omega_z)}{(C_1 + C_2) N \cdot s^2 (1 + s/\omega_p)}$$

