

Power Amplifier Design Methodology

Vishal Saxena

University of Idaho

12/03/2018

Typical Class-A PA Power Densities and R_{LOPT}

- ▶ 90/65nm CMOS

- ▶ $V_{MAX} = 1.5V$, $J_{sat,p} = 0.6 \frac{mA}{\mu m}$; $P_{sat} = 0.11 \frac{mW}{\mu m}$;
 $R_{LOPT} = 2.5k\Omega \cdot \times m$.

- ▶ 0.15 μm GaN FET

- ▶ $V_{MAX} = 40V$, $J_{sat,p} = 1 \frac{mA}{\mu m}$; $P_{sat} = 5 \frac{mW}{\mu m}$;
 $R_{LOPT} = 40k\Omega \cdot \times m$.

- ▶ 50GHz GaAs HBT

- ▶ $V_{MAX} = 6V$, $J_{sat,p} = 0.5 \frac{mA}{\mu m}$; $P_{sat} = 0.375 \frac{mW}{\mu m}$;
 $R_{LOPT} = 12k\Omega \cdot \times m$.

- ▶ 230GHz SiGe HBT

- ▶ $V_{MAX} = 3V$, $J_{sat,p} = 3.9 \frac{mA}{\mu m}$; $P_{sat} = 1.5 \frac{mW}{\mu m}$;
 $R_{LOPT} = 770\Omega \cdot \times m$.

Example of 1W PA Design (through 40GHz)


- ▶ 90/65nm CMOS: $W=0.09\text{mm}$; $R_{LOPT} = 0.27\Omega$ (impossible to match to 50Ω)
- ▶ 150nm GaN FET: $W=0.2\text{mm}$; $R_{LOPT} = 200\Omega$ (each to match from 50Ω)
- ▶ 50GHz GaAs HBT: $l_E=2.66\text{mm}$; $R_{LOPT} = 4.5\Omega$ (possible to match to 50Ω)
- ▶ 230GHz SiGe HBT: $l_E=0.67\text{mm}$; $R_{LOPT} = 1.16\Omega$ (possible but difficult to match from 50Ω)

Conclusion: Need a high voltage device for $> 1W$ or $> +30\text{dBm}$ power level.

PA Design Equations (1)

- ▶ Linear swing of a class-A PA depends on the flatness of the f_{MAX} vs J_D characteristics
- ▶ OP_{1dB} is maximized when the transistor is biased at the peak f_T current density, J_{pfT}
- ▶ SiGe HBT J_{pfT} increases as square of the technology scaling factor
 - ▶ Despite of reduction in breakdown voltage, large output power can be obtained in the newer technology nodes
 - ▶ Enables higher frequency designs
- ▶ In CMOS, linear voltage swing at the input/output decreases with each new node while J_{pfT} remains largely constant at $0.3 - 0.4 \frac{mA}{\mu m}$
 - ▶ In CMOS PAs, the OP_{1dB} current swing $J_{swing,pp}$ remains largely constant across nodes at $\approx 0.4 \frac{mA_{pp}}{\mu m}$, to avoid transistor cutoff

PA Design Equations (2)

 

- ▶ The OP_{1dB} can be directly linked to technology data and W

$$\begin{aligned}
 OP_{1dB} &= W \cdot J_{swing,pp} \frac{(V_{DD} - V_{DSsat})}{4} \\
 &= W \cdot J_{swing,pp} \frac{(V_{MAX} - V_{DSsat})}{8}
 \end{aligned}$$

only valid when the output is terminated on R_{LOPT}

PA Design Equations (3)

- ▶ To obtain saturated output power P_{SAT} , the corresponding current swing $J_{sat,pp}$ is $0.6 - 0.7 \frac{mA_{pp}}{\mu m}$ for nFETs and $2 \cdot J_{pFT}$ for HBTs
- ▶ The maximum current that can pass through a MOSFET is limited by I_{ON}
 - ▶ continues to increase with CMOS scaling
 - ▶ I_{ON} values as high as $1.3 \frac{mA}{\mu m}$ and $1 \frac{mA}{\mu m}$ have been reported in 45nm NMOS and PMOS respectively.
- ▶ For class A, B, and AB PAs, the maximum voltage swing $V_{sat,pp}$ of the fundamental at P_{SAT} is $\approx 2V_{DD}$, which is limited by V_{MAX}
 - ▶ The maximum peak-to-peak current swing at the fundamental frequency is limited by $J_{sat,pp}$
 - ▶ Thus, the saturated output power for these PA classes is limited by

$$P_{sat} = \frac{WJ_{sat,pp}V_{DD}}{4} = \frac{WJ_{sat,pp}V_{MAX}}{8}$$


mmWave Class-A PAs: Need for Multi-Stage Design

- ▶ Multistage PA topologies are essential to obtain adequate gain at mmWaves, esp. in CMOS
- ▶ $\approx 8 - 10\text{dB}$ MAG of a 90nm or 65nm CMOS is degraded by $3 - 4\text{dB}$
 - ▶ due to the limited load impedance that can be realized at the drain output at high frequencies, and
 - ▶ due to the losses of the matching networks
- ▶ The optimal distribution of power gain and bias current (and hence $P_{1\text{dB}}$) across the gain stages can be obtained by inspecting the expression

$$\frac{1}{OP_{1\text{dB}_{\text{cascade}}}} = \frac{1}{OP_{1\text{dB}_3}} + \frac{1}{OP_{1\text{dB}_2} \cdot G_3} + \frac{1}{OP_{1\text{dB}_1} \cdot G_2 \cdot G_3}$$

- ▶ In order to minimize the power consumption and to improve the efficiency of the overall PA for the given $OIP_{1\text{dB}}$, the gain and voltage swing of each stage must be maximized.

 Schematic of the Output Stage used for the Design Methodology



mmWave class-A PA Design Algorithm (1)

- ▶ **Step 1:** Starting at the output stage, determine the maximum allowed voltage swing for the given technology.
 - ▶ From the load line theory, the optimal linearity and output power are obtained when the transistor is biased such that the drain voltage swings equally between $V_{DS,sat}$ and V_{MAX} , centered at V_{DD} .
 - ▶ V_{MAX} is dictated by the breakdown or reliability limit.
 - ▶ Thus, the maximum voltage swing is $V_{swing} = V_{MAX} - V_{DS,sat}$, where $V_{MAX} = 2V_{DD} - V_{DS,sat}$
- ▶ **Step 2:** Set the bias current density to $J_{pFT} = 0.3 - 0.4 \frac{mA}{\mu m}$ to maximum linearity.

mmWave class-A PA Design Algorithm (2)

- ▶ **Step 3:** Determine the bias current that meets the P_{1dB} requirements and, from that find W .
 - ▶ An expression for P_{1dB} can be derived from the load line theory

$$P_{1dB} = I_{swing} \frac{(V_{DD} - V_{DS,sat})}{4}$$

where $I_{swing} = 0.4 \frac{mA}{\mu m} \cdot W$ is the maximum current swing before 1dB compression, instead of $2 \cdot I_{DC}$

- ▶ In most scaled CMOS technologies, the value of $V_{DS,sat}$ corresponding to the optimal linearity bias point of $0.3 \frac{mA}{\mu m}$ is about 0.3V.
 - ▶ We have $W = 4 \frac{P_{1dB}}{0.4 \frac{mA_{pp}}{\mu m} \cdot (V_{DD} - V_{DS,sat})}$ and $I_{DC} = W \cdot 0.3 \frac{mA}{\mu m}$.
- ▶ **Step 4:** Add a degeneration inductor L_S to improve stability.
 - ▶ Otherwise, the input resistance can become negative for an inductively loaded CS stage.
 - ▶ Iterations may be needed since L_S also changes MAG.
 - ▶ The degeneration inductor also improves linearity.

mmWave class-A PA Design Algorithm (3)

- ▶ **Step 5:** Add an output matching network (to transform from Z_0 to R_{LOPT}) for the last stage and (if necessary) inter-stage matching networks for intermediate stages to maximize power transfer.
- ▶ **Step 6:** Repeat steps 1-5 for each preceding stage with the V_{swing} determined by V_{input} for the subsequent stage to avoid gain compression.
- ▶ **Step 7:** Design the first stage to be input-matched to $Z_0 = 50\omega$. A cascode topology may be used in the first stage for higher gain.

In multistage PAs, the size and bias current of transistor increase towards the output.

Example: A 65nm CMOS Output Stage with P_{1dB} of 7dBm at 60GHz

- ▶ **Given:** $V_{DD} = 0.7V$, $V_{DS,sat} = V_{MIN} = 0.2V$ at $0.3 \frac{mA}{\mu m}$
- ▶ **Goal:** $OIP_{1dB} = 7dBm = 5mW$
- ▶ We determine $V_1 = V_{DD} - V_{DS,sat} = 0.5V$ or $1V_{pp}$ and $V_{MAX} = 1.5V$
- ▶ From $OIP_{1dB} = 5mW = \frac{V_1 \cdot I_{swing}}{4}$
 - ▶ $\implies I_{swing} = 40mA_{pp}$ and $W = \frac{I_{swing}}{0.4 \frac{mA_{pp}}{\mu m}} = 100\mu m$
- ▶ $R_{LOPT}(P_{1dB}) = \frac{2V_1}{I_{swing}} = \frac{1000}{40} = 25\Omega$
 - ▶ The corresponding DC bias current in the output transistor is $I_{DC} = W \cdot 0.3 \frac{mA}{\mu m} = 30mA$
 - ▶ $P_{DC} = I_{DC} \cdot V_{DD} = 30mA \cdot 0.7V = 21mW$
 - ▶ $\eta = 22.2\%$
- ▶ Note that we ignored the losses in the output matching network due to its finite Q .

Example: A SiGe HBT Output Stage at 60GHz

- ▶ **Given:** $V_{CC} = 1.5V$. The J_{pfT} is $2 \frac{mA}{\mu m}$, the linear current swing at J_{pfT} bias is $3 \frac{mA_{pp}}{\mu m}$, and $V_{CE,sat} = V_{MIN} = 0.5V$.
- ▶ **Goal:** $OIP_{1dB} = 10dBm = 10mW$
- ▶ We determine $V_1 = V_{CC} - V_{CE,sat} = 1V$ or $2V_{pp}$ and $V_{MAX} = 2.5V$
- ▶ From $OIP_{1dB} = 10mW = \frac{V_1 \cdot I_{swing}}{4}$
 - ▶ $\implies I_{swing} = 40mA_{pp}$ and $I_E = \frac{I_{swing}}{3 \frac{mA_{pp}}{\mu m}} = 13.3\mu m$
- ▶ $R_{LOPT}(P_{1dB}) = \frac{2V_1}{I_{swing}} = \frac{2000}{40} = 50\Omega$
 - ▶ The corresponding DC bias current in the output transistor is $I_{DC} = I_E 2 \frac{mA}{\mu m} = 26.7mA$
 - ▶ $P_{DC} = I_{DC} \cdot V_{DD} = 26.7mA \cdot 1.5V = 40mW$
 - ▶ $\eta = 25\%$
- ▶ The output matching network is simplified because it only needs to tune out the reactance of the output transistor.
- ▶ Note that we ignored the losses in the output matching network due to its finite Q .

Computer-based Algorithmic Class-A PA Design Methodology to Obtain a Target $OP_{1dB}(1)$

- ▶ **Step 1:** Start with a periodic S-parameter simulation at the desired frequency of operation.
 - ▶ Bias the transistor at the maximum linearity bias current density.
 - ▶ Use the transistor size calculated by hand analysis and 50Ω input and output ports.
 - ▶ Plot MAG as a function of P_{in} and find IP_{1dB} . This corresponds to $OP_{1dB} = IP_{1dB} + MAG$.
 - ▶ Set this OP_{1dB} power level to be at least 1-2dBm larger than the target. Otherwise will need to increase the transistor size.
- ▶ **Step 2:** Plot the real and imaginary parts of Z_{in} and Z_{out} . Examine their values at the IP_{1dB} input power level and conjugate match the input and output at this input/output power level.

Computer-based Algorithmic Class-A PA Design Methodology to Obtain a Target $OP_{1dB}(2)$

- ▶ **Step 3:** Re-run the periodic S-parameter simulation on the matched amplifier and plot P_{out} versus P_{in} , Gain versus P_{in} and PAE versus P_{in} .
 - ▶ A load-pull simulation should be conducted to further tweak the output impedance and to obtain the maximum possible output power.
 - ▶ If you still cannot achieve the desired output power, repeat Steps 1-2 after further increasing transistor sizes.



PA Output Power Control

- ▶ The TX power level is usually specified by the various IEEE standards.
- ▶ Most of these standards mandate at least some capability to dynamically control the output power level.
- ▶ Its also desirable that the efficiency of the PA doesn't degrade as the output power is reduced (or **back-off**).
- ▶ Several techniques have been developed for improving back-off energy efficiency.



PA Linearity

- ▶ Methods to improve PA linearity remain very attractive area of research.
- ▶ Two transmitter specification parameters address the PA linearity performance.
 - ▶ The spectral mask
 - ▶ The error vector magnitude (EVM) of the output signal
- ▶ Depending upon the modulation format, the PA design is either limited by the spectral mask or by the EVM specification.
- ▶ In general, in higher data-rate standards, which require more complex modulations and higher BW efficiency, the EVM specification is more difficult to satisfy.

 
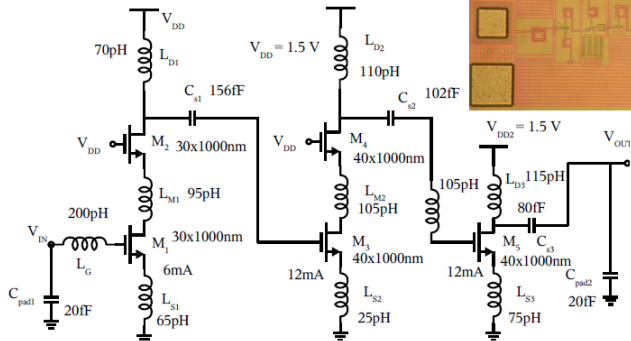
2-Stage Cascode PA with CS Output Stage in 90nm CMOS (1)



  2-Stage Cascode PA with CS Output Stage in 90nm CMOS (2)



  2-Stage Cascode PA with CS Output Stage in 90nm CMOS (3)



Other PA Concepts (Read in the Textbook)

- ▶ Non-idealities in PA
 - ▶ Drain inductance
 - ▶ Thermal runaway in Bipolar PAs
 - ▶ Avalanche breakdown
- ▶ Efficiency enhancement techniques
 - ▶ Dynamic biasing
 - ▶ PA subbranging
 - ▶ Envelope tracking
 - ▶ PWM modulated class-E PA with envelop restoration
 - ▶ Doherty amplifier
 - ▶ Dephasing
 - ▶ Digital Predistortion

Other PA Concepts (Read in the Textbook)

- ▶ Power combining techniques
 - ▶ Transformer based power combining
 - ▶ Series stacking of transistors (super-cascode)
 - ▶ Spatial power combining

References

- ▶ S. Voinigescu, "High-Frequency Integrated Circuits," The Cambridge RF and Microwave Engineering Series, 1st ed., 2013.