

# Homework 1

## ECE 5/413 – Radio Frequency IC Design

The following problems are intended to review analog circuits material from the pre-requisite courses.

**Problem 1:** Find small-signal voltage gain ( $A_v = \frac{v_{out}}{v_{in}}$ ) of the amplifier stages shown in Fig. 1 in terms of transistor small-signal parameters ( $g_{m1}$ ,  $g_{m2}$ ,  $r_{o1}$ ,  $r_{o2}$ , etc.) and circuit parameters ( $R_s$ ,  $R_D$ , etc.). Here,  $V_{b1}$ ,  $V_{b2}$ , etc., are DC bias voltages. Assume that all transistors are in saturation.

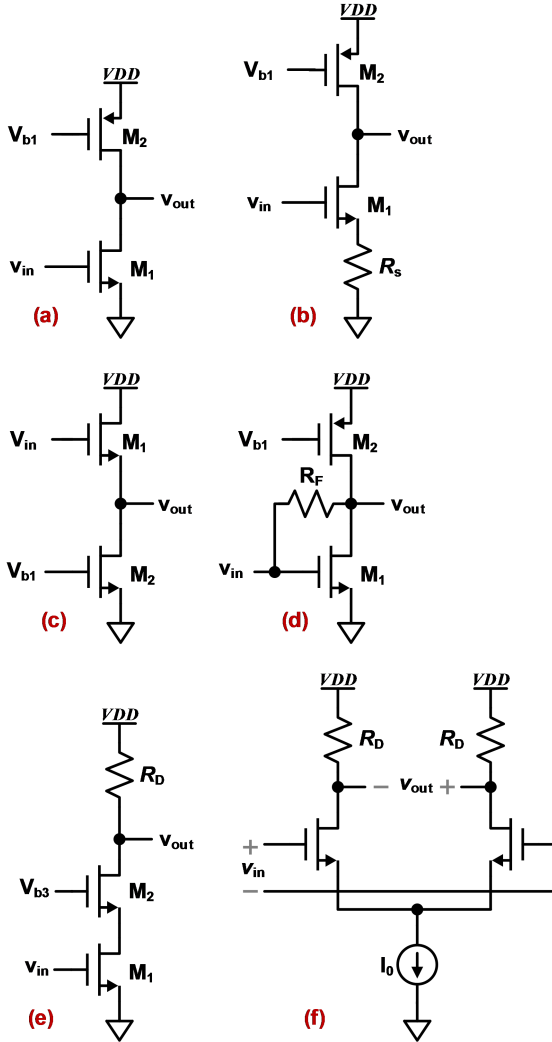


Figure 1