
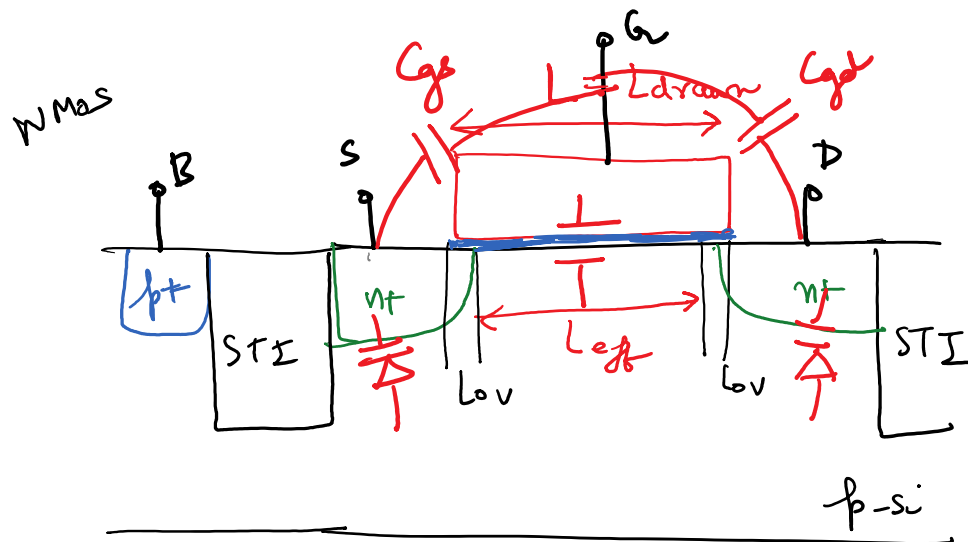


ECE 513 - lecture 14

Thursday, October 4, 2018 9:29 AM

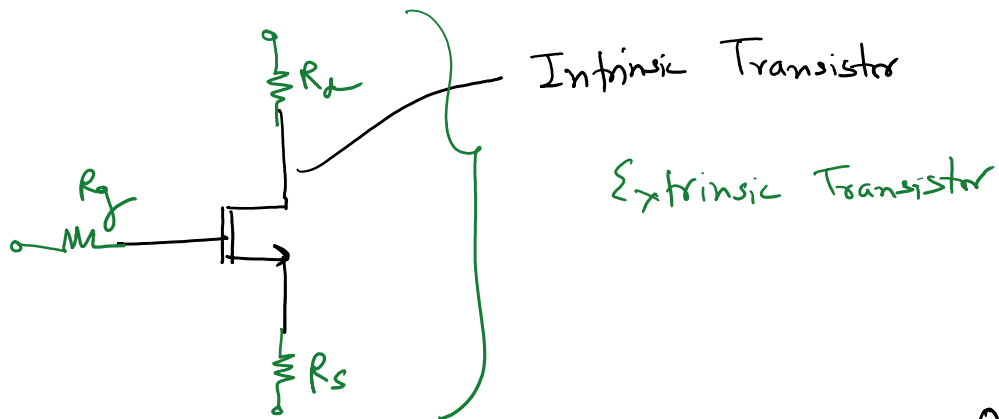


Overlap Capacitances

No channel

$$C_{gs} = C_{gd} = C_{ox} \cdot L_{ov} \cdot W$$

$$C_{gs} = C_{GS0} \cdot W$$

$$C_{gd} = C_{GD0} \cdot W$$

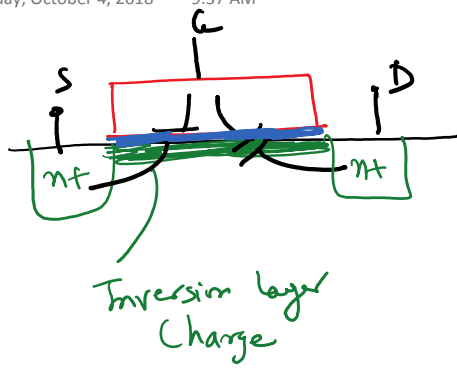

Triode :


$$C_{gs} \approx C_{gd} = \frac{1}{2} C_{ox}' W (L - L_{ov}) + C_{ox}' W L_{ov} \\ \approx \frac{1}{2} C_{ox}' W L$$



Saturation :

$$C_{gs} \approx \frac{2}{3} C_{ox}' W L$$

$$C_{gd} = C_{GD0} \cdot W$$


$$C_{gs} \gg C_{gd}$$

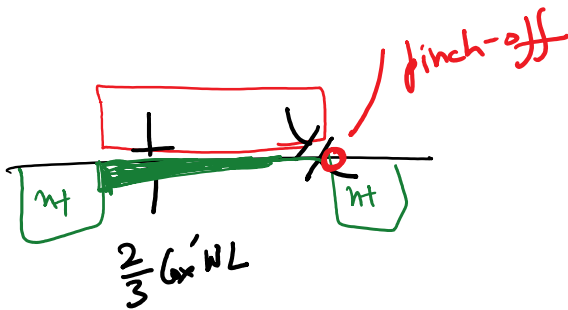

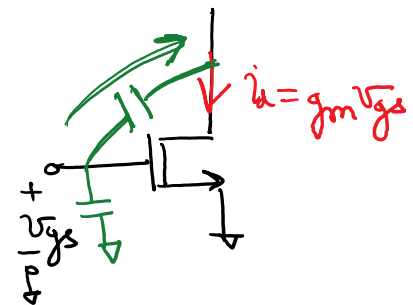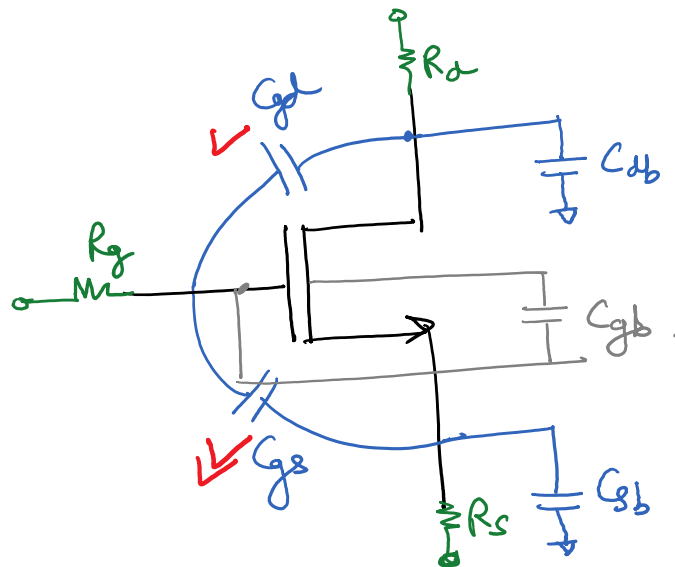

Simplified Small-Signal model

Intrinsic Transistor Model

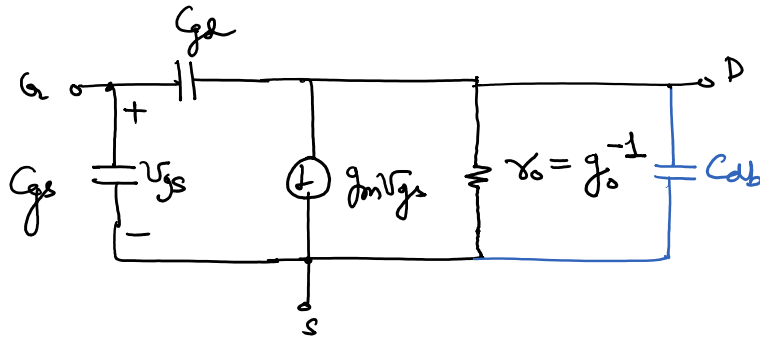

$$r_o = g_o^{-1} = g_{DS}^{-1}$$

No R_s, R_d or R_g here

$$r_i = 0$$


$$r_o = 0$$

Simplified Y-parameter matrix for unit width

$$\left[\frac{y}{w} \right] = \begin{bmatrix} j\omega C_{gs}' + j\omega C_{gd}' & -j\omega C_{gd}' \\ g_m' - j\omega C_{gd}' & g_o' + j\omega (C_{ds}' + C_{gd}') \end{bmatrix}$$

* $g_m', g_o', C_{gs}', C_{gd}', C_{ds}'$ are technology dependent parameters per unit width

Extrinsic Transistor Model

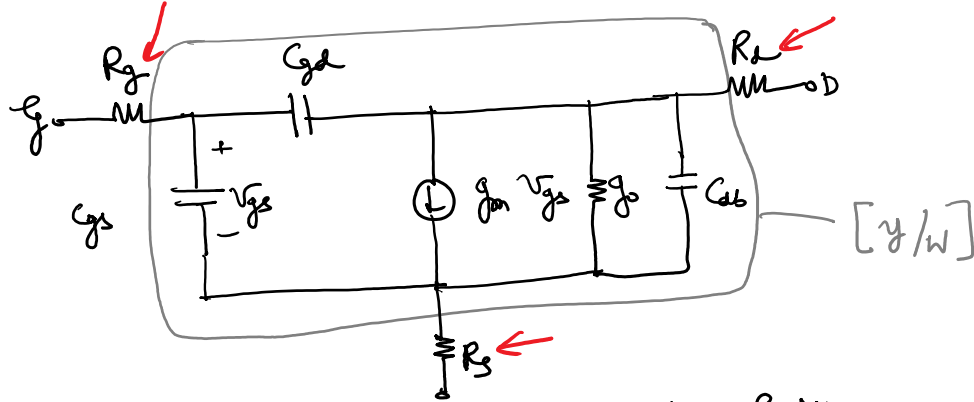

$$Y_{11} = \frac{y_{11} + (R_s + R_d) \Delta y}{N}$$

$$Y_{12} = \frac{y_{12} - R_s \Delta y}{N}$$


$$Y_{21} = \frac{y_{21} - R_s \Delta y}{N}$$

$$Y_{22} = \frac{y_{22} + (R_s + R_d) \Delta y}{N}$$

where $N = 1 + R_s (y_{11} + y_{12} + y_{21} + y_{22}) + R_d y_{22} + R_g y_{11} + \Delta y R_s^2$

$$\Delta y = y_{11} y_{22} - y_{21} y_{12}$$

9:50 AM

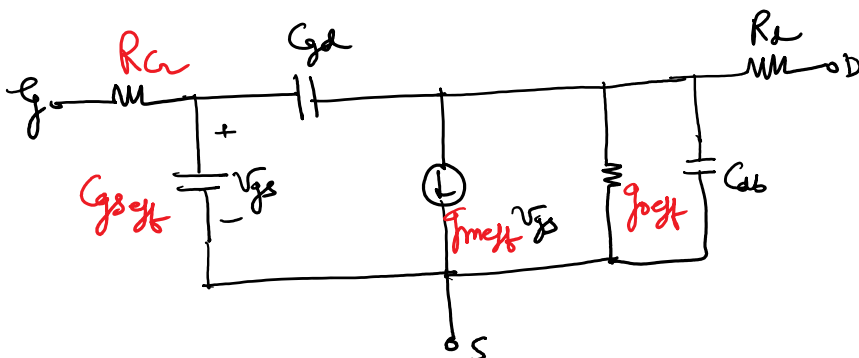

Source Degeneration

$$g_{m,eff} = \frac{g_m}{1 + g_m R_S}$$

$$g_{o,eff} = \frac{g_o}{1 + g_m R_S}$$

$$C_{gs,eff} = \frac{C_{gs}}{1 + g_m R_S}$$

$$R_{G_L} = R_G + R_S$$

High-Frequency figures of merit

Thursday, October 4, 2018

9:57 AM

- Cutoff frequency, f_T , (ω_T)
- Maximum oscillation frequency, f_{max} , (ω_{max})
- g_m/I_D

80-85%

$$f_T = \frac{1}{2\pi} \left[\frac{g_m}{C_{gs} + C_{gd}} \right] \parallel \left[\frac{1}{(R_s + R_d) C_{gd}} \right] \approx \frac{g_m}{2\pi C_{gs}}$$

Simplified
Expression

→
current gain cutoff metric
* More relevant for low-frequency
analog design

$C_{gs} \gg C_{gd}$
 $R_s = R_d \approx 0$


Maximum Oscillation frequency (f_{max})

Thursday, October 4, 2018 10:10 AM

- * In higher frequency circuits, power gain is more important than voltage or current gain
- * Maximum available (power) gain MAG
$$MAG(f=f_{max}) = 1 \text{ or } 0dB$$
- * Definition of MAG implies conjugate matched input and output impedances
↳ we need to know the input and output impedance to define input and output power as well as achieve max transfer matching condition.

Simplified model with R_g

Thursday, October 4, 2018 10:15 AM

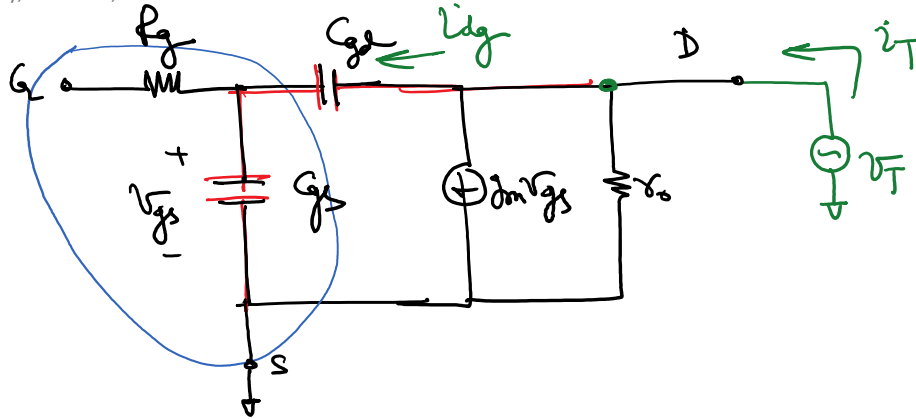

$$Z_{out} = \frac{V_T}{I_T}$$

Input impedance

$$* Z_{in} = \underline{R_g + \frac{1}{j\omega C_{gs}}} \quad \underline{\approx R_g} \text{ at high frequencies as } \left(\frac{1}{j\omega C_{gs}} \right) \approx 0$$

$$* Z_{out} \Rightarrow I_T = \frac{V_T}{r_o} + g_m V_{gs} + I_{dg}$$


Assuming $I_{dg} \ll g_m V_{gs}$

$$\leftarrow \frac{V_{gs}}{V_T} = \frac{C_{gd}}{C_{gd} + C_{gs}}$$

$$Z_{out} = \frac{1}{\frac{1}{r_o} + \frac{g_m C_{gd}}{C_{gd} + C_{gs}}}$$

$$= \underline{r_o \parallel \frac{C_T}{g_m C_{gd}}}, \quad \text{where } C_T = C_{gd} + C_{gs}$$


Conjugate Match at the input

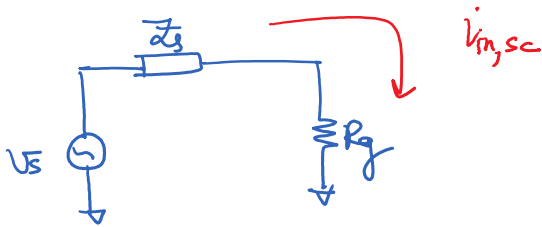

$$Z_s = R_g$$

$$\Rightarrow v_{in,sc} = \frac{V_s}{2R_g} \rightarrow \textcircled{1}$$

Conjugate Match at the output

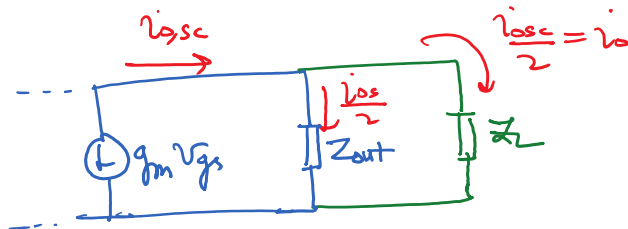

$$Z_{out} = Z_L$$

$$\Rightarrow R_{out} = R_L$$

$$i_o = \frac{i_{o,sc}}{2} \rightarrow \textcircled{2}$$

$$MAG = \frac{\frac{1}{2} i_o^2 R_{out}}{\frac{1}{2} i_{in}^2 R_{in}} \triangleq \frac{1}{4} \left(\frac{i_{o,sc}}{i_{in,sc}} \right)^2 \cdot \frac{R_L}{R_g}$$

$$P = \frac{1}{2} I^2 R$$

we used this ratio
to derive f_T

$$= \frac{1}{4} \left(\frac{f_T}{f} \right)^2 \frac{R_L}{R_g}$$

$$\omega \approx f_T$$

$$\frac{i_{o,sc}}{i_{in,sc}} \approx \frac{f_T}{f}$$

$$MAG \Big|_{f=f_{max}} = 1$$

$$\Rightarrow f_{max} = \frac{1}{2} f_T \sqrt{\frac{R_L}{R_g}}$$

$$R_L = R_{out} = \frac{1}{\frac{1}{r_o} + \frac{g_m C_{gd}}{g_m + g_d}}$$

$$= \frac{1}{\frac{1}{r_o} + 2\pi f_T C_{gd}}$$

$$f_{max} = \frac{1}{2} \frac{f_T}{\sqrt{2\pi f_T R_g C_{gd} + \frac{R_g}{r_o}}}$$

(A)

u. . .

$$\sqrt{2\pi f_T K_g C_{gd} + \frac{K_g}{r_o}}$$

→ (A)

Book Eq 4.125

Including R_s and R_g

$$f_{\max} = \frac{1}{2} \frac{f_T}{\sqrt{2\pi f_T C_{gs} (R_g + R_s) + (R_g + R_s) g_{os}}} \rightarrow \textcircled{B}$$

Simplifications

$$\frac{1}{r_o} \ll \frac{g_m C_{gs}}{C_{gs} + C_{gd}}$$

$$f_{\max} \approx \frac{1}{2} f_T \sqrt{\frac{R_g}{R_g + R_s}} = \frac{1}{2} f_T \sqrt{\frac{r_o}{R_g + R_s}}$$

$$f_{\max} \approx \frac{f_T}{2 \sqrt{(R_s + R_g) g_{os}}} \rightarrow \textcircled{C}$$

for several transistor technologies Denominator < 1
 $\frac{(R_s + R_g)}{r_{o,eff}} < 1$



$$f_{\max} > f_T$$

$$Y_{s,opt} = g_{s,opt} + jB_{s,opt} \Rightarrow F_{min}$$

Two-port Transistor Noise Model:

Van Der Ziel

Ignoring R_g

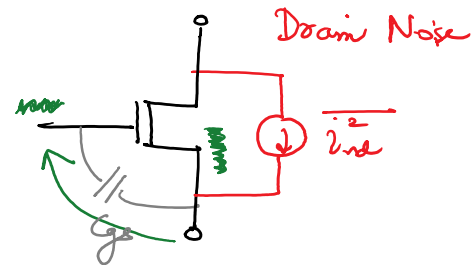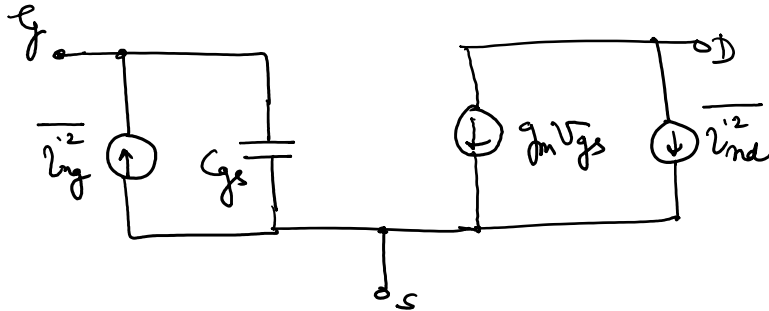

This gate noise is much higher than the thermal noise from R_g

$$\overline{i_{nd}^2} = 4kT\gamma g_{ds0}\Delta f$$

\rightarrow g_{ds} of transistor at $V_{DS}=0$

Excess noise parameter
technology dependent


$$g_{ds0} = k_n \frac{W}{L} (V_{GS} - V_{THN}) \triangleq g_m \text{ for long-channel}$$

$\gamma = 2/3$ for long channel
 $\gamma \uparrow$ with $W/L \downarrow$

$$\overline{i_{ng}^2} = 4kT\delta g_g \Delta f$$

$$g_g = \frac{\omega^2 C_{gs}^2}{5 g_{ds0}}$$

blue noise

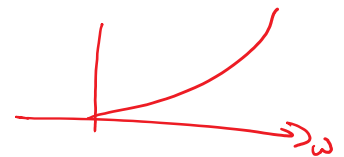

Correlated

$$C \triangleq \frac{\overline{i_{ng} i_{nd}^*}}{\sqrt{\overline{i_{ng}^2} \overline{i_{nd}^2}}}$$

$$= -j0.395 \approx -j0.4 \text{ for long-channel CMOS}$$