
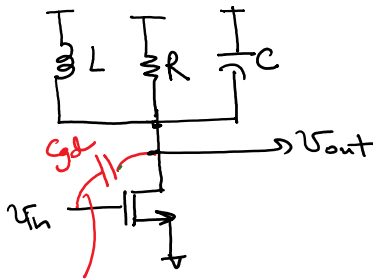


ECE 513- Lecture 18

Thursday, October 18, 2018 9:30 AM

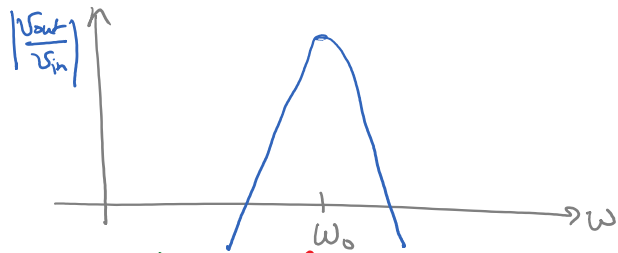


$$\omega_0 = \frac{1}{\sqrt{LC}}$$



Miller Capacitance

↳ shorts input & output at higher frequencies

Miller Effect

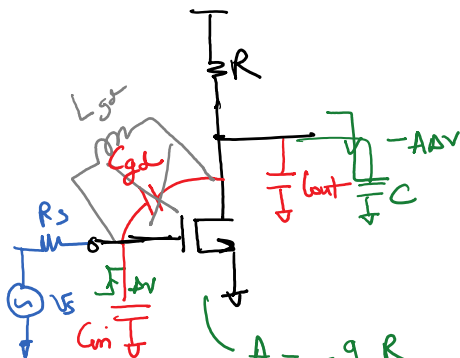

$$A = -g_m R$$

$$\text{Net charge across } C_{gd} = (1 + |A|) \Delta V$$

$$C_{in} = C_{gd} (1 + |A|)$$

$$C_{out} = C_{gd} \left(1 + \frac{1}{|A|}\right) \approx C_{gd} \quad \text{approximation}$$

@ higher frequencies, C_{gd} shorts input & output \Rightarrow zero in the frequency response.

* Can shift the resonance frequency away from ω_0

$$\text{Use } C \gg C_{gd} \Rightarrow \text{GBW} = \frac{g_m}{C} \downarrow$$

* R_{in} can have a negative real part at frequencies where the LC tank is inductive ($\omega \geq \omega_0$)

↳ resistance with negative real part can set oscillations

... .. oscillation of C_{gd}

... ..


Oscillations

* Need to mitigate the deleterious effects of C_{gd} (Lee's book)

↳ neutralization → cancel the effect/role of C_{gd}

↳ unilaterization $|S_{12}| \approx 0$

Cascode
CS Amplifier

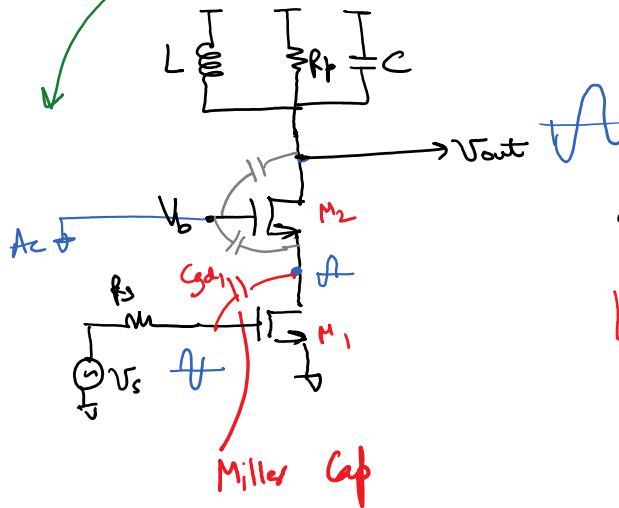


gain seen across M_1 is small
 ≈ -1


↳ effect of Miller cap is mitigated as the gain across $C_{gd} \approx -1$
(Miller killer)

Tuned CS Amplifier Analysis :

Thursday, October 18, 2018 9:54 AM

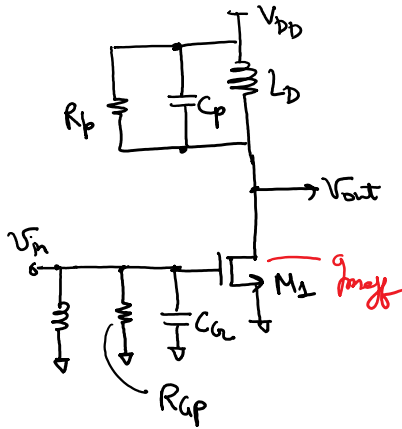

Baseband Equivalent

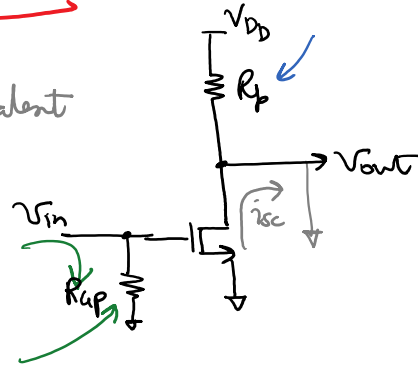

$$g_{meff} = \frac{g_m}{1 + g_m R_s}$$

Theorem (see Razavi Analog Book)

$$A_v = -g_{mi} R_{out} \quad \leftarrow \text{o/p resistance}$$

↳ short circuit g_m

$$* R_{out}(\omega_0) = R_p$$


$$* R_{in}(\omega_0) = R_{sp}$$

Output short circuit current

$$* I_{sc}(\omega_0) = -g_{meff} V_{in}$$

$$* \text{Voltage gain: } A_v(\omega_0) = -g_m \cdot R_{out} = -\frac{I_{sc}}{V_{in}} \cdot R_{out} = -g_{meff} \cdot R_p$$

Power gain

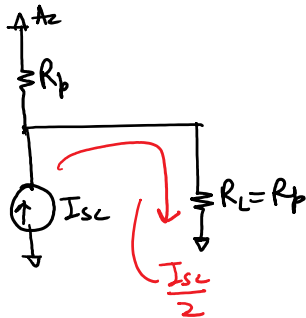

$$I_{sc} = -g_{meff} V_{in}$$

"Assume the input & output ports are conjugate matched"

$$I_{load} = \frac{I_{sc}}{2} = -\frac{g_{meff} V_{in}}{2} \quad \text{--- (1)}$$

$$V_{out} = \frac{I_{sc}}{2} \cdot R_p = -\frac{g_{meff} V_{in}}{2} \cdot R_p \quad \text{--- (2)}$$

Power delivered to the "matched" load

$$P_{load} = V_{out} \times I_{load} = \frac{g_{meff} R_p}{4} \cdot V_{in}^2 \quad \text{--- (3)}$$

Power delivered from the signal source

$$P_{in} = V_{in} \times I_{in} = V_{in} \cdot \left(\frac{V_{in}}{R_{sp}} \right) = \frac{V_{in}^2}{R_{sp}} \quad \text{--- (4)}$$

power gain


$$g = \frac{P_{load}}{P_{in}} = \boxed{\frac{g_m^2 R_p R_{ap}}{4}}$$

Now, assuming that we have ideal inductors (infinite Q) for tuning the input and output. $R_p = r_{o,eff}$ ← effective output resistance of the NMOSFET

* At the input side

$$R_{ap} \leq (R_g + R_s) Q^2$$
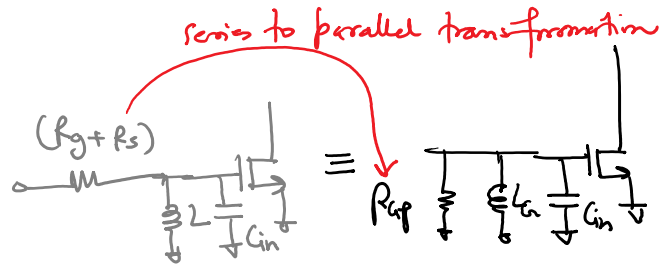
$$= \frac{(R_g + R_s)}{\omega_o^2 (R_g + R_s)^2 C_{in}^2} = \frac{1}{(R_g + R_s) \omega_o^2 C_{in}^2}$$




$$g(f) = \frac{g_m^2 r_o}{4 \omega^2 C_{in}^2 (R_g + R_s)} \leq \frac{f_T^2}{4 f^2} \cdot \frac{r_o}{R_g + R_s} = \boxed{\frac{f_{MAX}^2}{f^2}}$$

$$\text{where } f_{MAX} = \frac{f_T}{2} \sqrt{\frac{R_{out}}{R_{in}}}$$

available power gain $\propto \frac{1}{f^2}$

No power gain beyond $f = f_{MAX}$

$$f_{MAX} > f_T$$

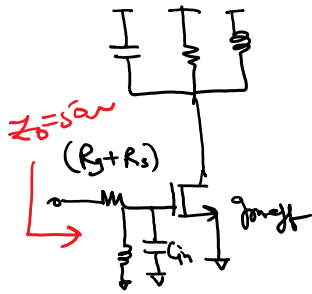



$R_{in} = R_g + R_s$ with input tank tuning

$$\Rightarrow \frac{1}{j\omega C_{gs}} + (R_g + R_s)$$


$R_g, R_s \downarrow$ for $f_{max} \uparrow$

Need 'Real' impedance at the input without degrading NF or BW.

CS with Inductive Degeneration

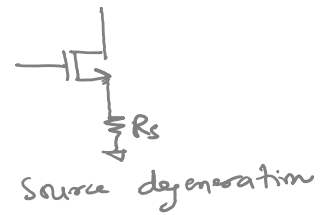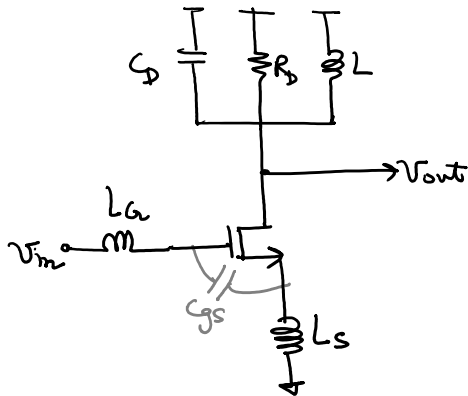

HF MOSFET Model

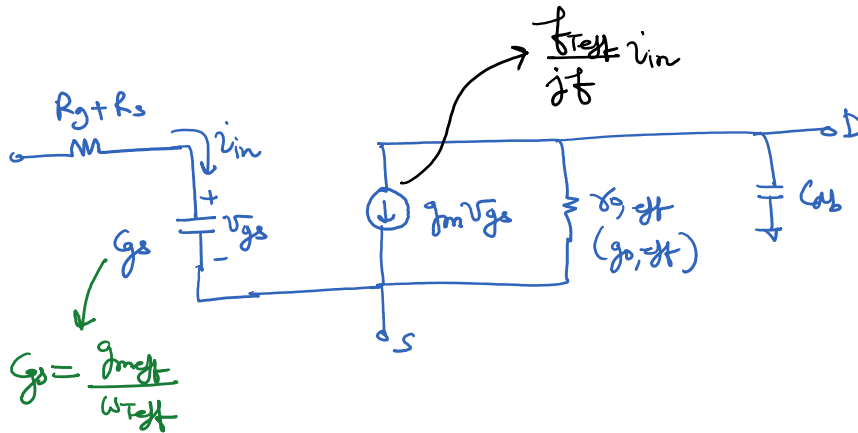


$$\omega_{Teff} = \frac{g_{m,eff}}{2\pi C_{gs}}$$

Experimental / Simulation based values for

$g_{m,eff}, \omega_{Teff}$

These include the impact of C_{gd}

$\rightarrow \pm 15\%$ error at 100 GHz

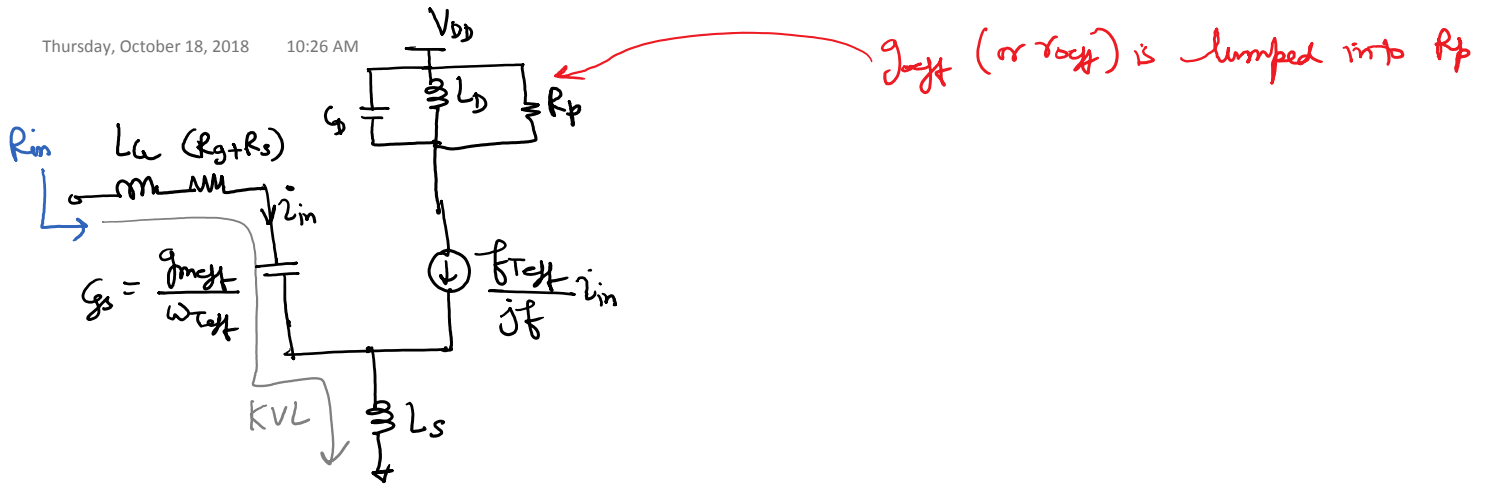

Step 1: Calculate R_{in} (KVL)

$$V_{in} = i_{in} \left(j\omega L_G + R_P + R_S + \frac{\omega T_{eff}}{j\omega g_{meff}} + j\omega L_S \right) + j\omega L_S \cdot \frac{\omega T_{eff}}{j\omega} i_{in}$$

$$\Rightarrow \underline{Z}_{in} = \frac{V_{in}}{i_{in}} = \underbrace{R_P + R_S + \omega T_{eff} L_S}_{R_e} + j \underbrace{\left[\omega (L_G + L_S) - \frac{\omega T_{eff}}{\omega g_{meff}} \right]}_{Z_m} \longrightarrow \textcircled{1}$$

Step 2: Output short circuit current

$$I_{sc} = - \frac{\beta_{Teff}}{jf} i_{in} = j \frac{\beta_{Teff}}{f} i_{in} \longrightarrow \textcircled{2}$$

Step 3: To match the input to a signal source with real impedance

Z_0

→ The imaginary part of Z_{in} is cancelled by a proper choice of L_G

$$L_G = \frac{\omega T_{eff}}{\omega^2 g_{meff}} - L_S$$

→ Z_{in} is made equal to the source impedance Z_0 by choosing appropriate value for L_S

$$L_S = \frac{Z_0 - (R_P + R_S)}{\omega T_{eff}}$$

Step 4: Power gain

$$V_{out} = \frac{I_{sc}}{2} \times R_p = \frac{f_{Teff}^2 R_p}{4f^2} v_{in}$$

$$I_{load} = \frac{I_{sc}}{2} = \frac{f_{Teff}^2}{2f} v_{in}$$


$$P_{load} = V_{out} \cdot I_{load}^* = \frac{f_{Teff}^2 R_p}{4f^2} |v_{in}|^2 \longrightarrow \textcircled{3}$$

$$P_{in} = V_{in} \cdot i_{in}^* = v_{in} \cdot R_{in} \cdot v_{in}^* = R_{in} |v_{in}|^2 \longrightarrow \textcircled{4}$$


$$g = \frac{P_{load}}{P_{in}} = \frac{f_{Teff}^2}{4f^2} \cdot \frac{R_p}{R_{in}} \quad \checkmark$$

Normally $R_p = R_{in} = Z_0$ (matched to Z_0)

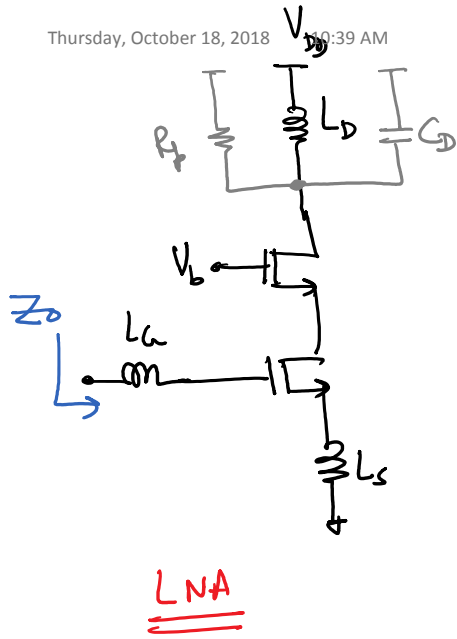
$$\Rightarrow g = \frac{f_{Teff}^2}{4f^2} \quad \checkmark$$



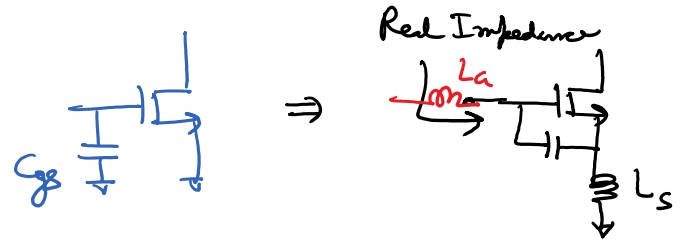Power Match vs Noise Match
 $Z_S = Z_{S,opt}$



Tuned Amplifiers

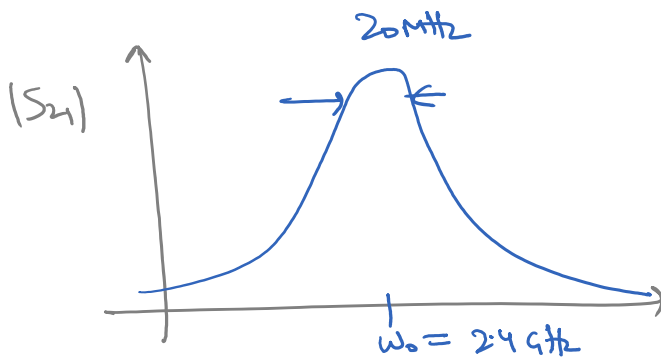

Broadband Amplifier

