

ECE 513- Lecture 21

Tuesday, October 30, 2018 9:34 AM

Data from

Table 7.1 in Textbook

* 6 GHz LNA Design Example:

Also, $k_i = 0.5$

$$X_{s\text{opt}} = \frac{1.15 W_T}{\omega g_{m\text{eff}}}$$

* 180nm CMOS

* load inductor has a fixed $Q=10$

* output of the LNA is terminated on a matched load

* Determine transistor sizes, bias current, L_s & L_u and estimate the power gain for the CMOS cascode LNA

* Assume that the best finger width for minimum noise is $W_f = 2\mu\text{m}$.

6 GHz LNA Design:

$$W_f = 2\mu\text{m}, \quad I_{\text{opt}} = 0.15 \frac{\text{mA}}{\mu\text{m}}$$

* from process characterization

$$* \quad \overset{\text{from Table}}{g'_{m\text{eff}}} = \frac{g'_m}{1 + g'_m R'_s} \Rightarrow g'_m = \frac{g_{m\text{eff}}}{1 - R'_s g_{m\text{eff}}} = \frac{0.4 \frac{\text{mS}}{\mu\text{m}}}{1 - 200\mu\text{m} \times 0.4 \frac{\text{mS}}{\mu\text{m}}}$$

$$g'_m = 0.434 \frac{\text{mS}}{\mu\text{m}}$$

$$\frac{\text{mA}}{V_{\mu\text{m}}}$$

① Size the transistors in the cascode st. $R_{\text{sopt}} = Z_0 = 50\Omega$

$$\Rightarrow N_f = \frac{f_{\text{Teff}}}{f Z_0 W_f g'_{m\text{eff}}} \cdot \sqrt{\frac{g'_m R'_s + W_f g'_m R'_g(W_f)}{R_L}} \quad \rightarrow R'_g = f(W_f)$$

$$= \frac{35 \text{ GHz}}{6 \text{ GHz} \cdot 50 \cdot 2 \mu\text{m} \times \frac{0.4 \text{ mS}}{\mu\text{m}}} \cdot \sqrt{\frac{0.43 \times 0.2 + 2 \times 0.43 \times 10^{-3} \times 75}{0.5}}$$

$$\leq 71$$


$$\Rightarrow W = N_f W_f = \underline{142 \mu\text{m}}, \quad L = 180 \text{ nm}$$

* if we biasing at $J_{\text{opt}} \Rightarrow$

$$\text{drain current, } I_D = J_{\text{opt}} \times W = \frac{0.15 \text{ mA}}{\mu\text{m}} \times 142 \mu\text{m} = \underline{21.3 \text{ mA}}$$

$$* g_{m\text{eff}} = 0.4 \frac{\text{mS}}{\mu\text{m}} \times 142 \mu\text{m} = \underline{56.8 \text{ mS}}$$

②

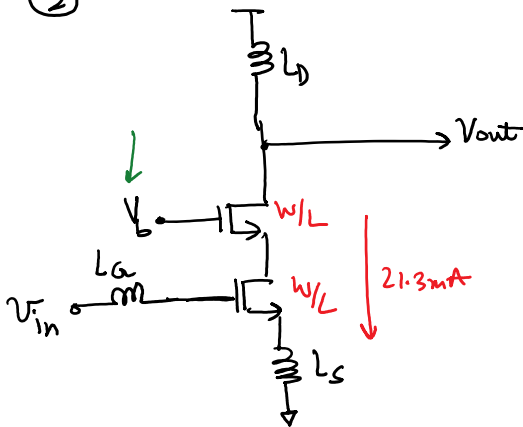


$$* L_S = \frac{Z_0 - R_g - R_s}{\omega_T} = \frac{50 - \frac{75 \Omega}{71} - \frac{100 \Omega}{71}}{2\pi \times 35 \times 10^9} \approx 217 \text{ pH}$$


$$* L_G + L_S = \frac{\omega_T}{\omega_c^2 g_{m\text{eff}}} = \frac{\omega_T}{(2\pi f_c)^2 W g_{m\text{eff}}} = 2.72 \text{ nH}$$

$$L_G = 2.72 \text{ nH} - 217 \text{ pH} = \underline{2.5 \text{ nH}}$$

Tuesday, October 30, 2018 9:54 AM

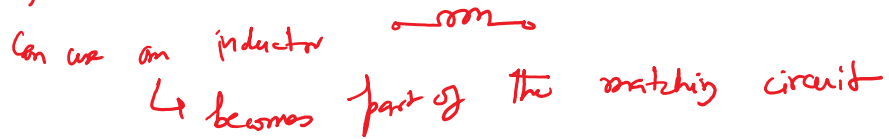

$Q=10$
output is matched

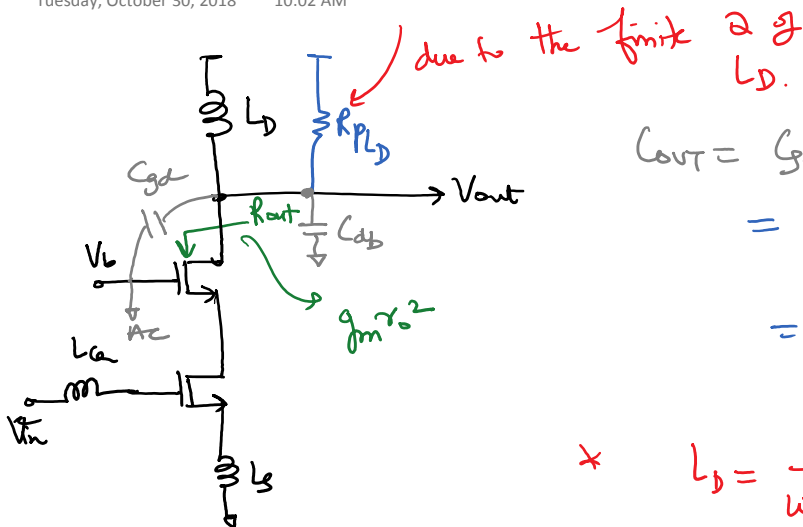

$$C_{out} = C_{gs} + C_{db}$$

$$= (C_{db}' + C_{gs}) \cdot W$$

$$= (1.1 + 0.4) \frac{fF}{\mu m} \times 142 \mu m = 213 fF$$


$$\begin{aligned} * L_D &= \frac{1}{\omega_0^2 C_{out}} = \frac{1}{(2\pi \cdot 64Hz)^2 \cdot 213 fF} \quad \left(\omega_0 = \frac{1}{\sqrt{LC}} \right) \\ &= \underline{3.3 nH} \end{aligned}$$

\Rightarrow for a parallel RLC

$$Q = \frac{R_p}{\omega_0 L_p} \Rightarrow R_p = Q \cdot 2\pi f_0 \cdot L_D = \underline{1.244 k\Omega}$$

\Rightarrow Resistance looking into the drain of the Cascode
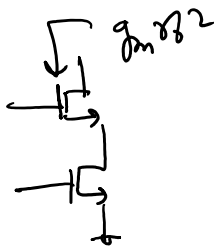
$$R_{out} = g_{m2} r_{o2}^2 = \frac{g_{m2}}{g_{o2}} = \underline{1.76 k\Omega}$$



\Rightarrow Total output resistance

$$R_p = R_{pL_D} \parallel R_{out} = 1.244 k\Omega \parallel 1.76 k\Omega = \underline{728 \Omega}$$

\therefore the output is matched


$$\Rightarrow R_L = R_p$$

$$\Rightarrow \text{Power gain} \Rightarrow G = \frac{1}{4} \frac{R_p}{Z_0} \rightarrow \epsilon_t \approx 7.25 \text{ in the Textbook}$$

$$= 126$$

$$= \underline{\underline{21 \text{ dB}}}$$

Parasitic Capacitance of the Bond Pad :

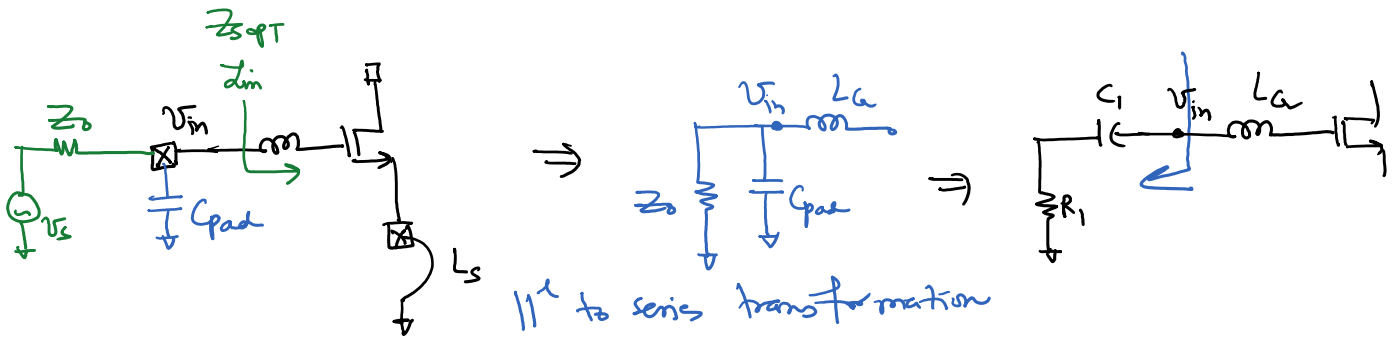

\Rightarrow $||^L$ to series transformation

$$R_1 = \frac{Z_0}{1+Q^2} \quad \text{and} \quad C_1 = \left(\frac{Q^2+1}{Q^2} \right) C_{pad}$$

$$Q = \omega_0 R_p C_p = \frac{R_p}{\omega_0 L_p} \rightarrow \omega_0 Z_0 C_{pad}$$

$$\Rightarrow R_1 = \frac{Z_0}{k}$$

$$C_1 = \frac{k}{k-1} C_{pad}, \quad k = 1+Q^2 = 1+\omega^2 C_{pad}^2 Z_0^2$$

* The new source impedance is complex instead of Z_0

\hookrightarrow real part (R_1) is frequency dependent

\Rightarrow Adjust our matching.

for noise match, we set $R_{sopt} = \frac{Z_0}{k} \leftarrow$ correction factor

$$L_s = \frac{\frac{Z_0}{k} - R_j - R_s}{\omega_T}$$

$$Ex. \quad f_0 = 65 \text{ GHz in } 65 \text{ nm CMOS}$$

$$k = 1.166$$


_____.

Techniques to Maximize Bandwidth (BW Extension Techniques) :

Tuesday, October 30, 2018 10:24 AM


(Chapter 5)

* Bandwidth of an Amplifier Cascade:

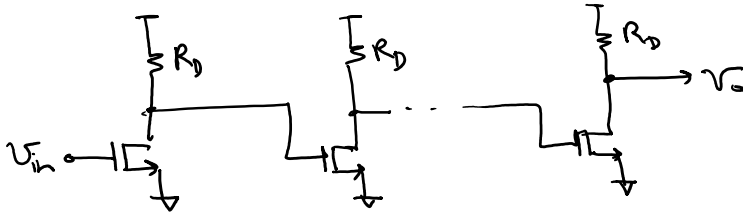

↳ If the voltage gain of each stage is a single pole response

$$A(s) = \frac{A_0}{(1 + s/\omega_p)}$$

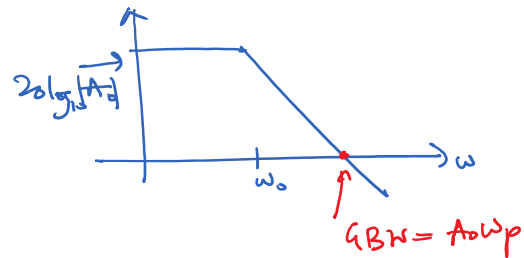

* For a cascade of n -identical single-pole stages

$$A_{tot}(s) = A(s)^n = \frac{A_0^n}{(1 + s/\omega_p)^n}$$

⇒ 3dB bandwidth of the chain

$$A_{tot}(s = j\omega_{3dB}) = \frac{[A_0]^n}{\sqrt{2}}$$

$$\Rightarrow \left| 1 + \frac{j\omega_{3dB}}{\omega_p} \right| = 2^{1/2n}$$

$$\Rightarrow 1 + \frac{\omega_{3dB}^2}{\omega_p^2} = 2^{1/n}$$

$$\Rightarrow \omega_{3dB} = \omega_p \sqrt{2^{1/n} - 1} \leq \omega_p$$

⇒

$$\omega_{3dB} = \underbrace{\omega_p \sqrt{2^{1/n} - 1}} \leq \omega_p$$

Overall BW shrinks!

⇒ gain bandwidth

$$g_{BW_{tot}} = A_0^n \omega_p \sqrt{2^{1/n} - 1} = A_{tot} \omega_p \sqrt{2^{1/n} - 1}$$

* Ratio of GBW of the entire cascade to that of the individual stage



$$\frac{g_{BW_{tot}}}{g_{BW_s}} = A_{tot}^{1-1/n} \times \sqrt{2^{1/n} - 1}$$

$$\frac{\partial}{\partial n} \left(\frac{g_{BW_{tot}}}{g_{BW_s}} \right) = 0 \Rightarrow n_{opt} \approx 2 \ln(A_{tot})$$

* See Ex. 5.5 in the Textbook

* How to increase the BW of the individual stages?

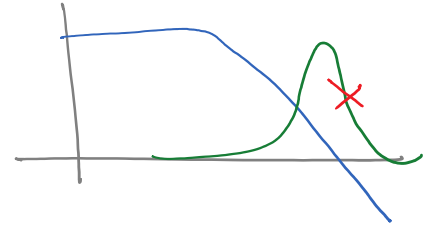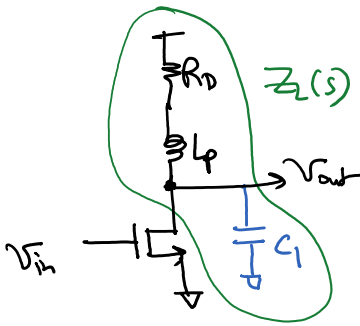Shunt peaking: (Broadband stages, not tuned stages)



* A zero is introduced by adding an inductor to the load
 ↳ the zero partly compensates for the pole's response

↳ inductor also introduces a second pole

Voltage gain

$$A_v(s) = -g_m \cdot Z_L(s)$$

$$Z_L = \frac{R_D + sL_p}{1 + sR_D C_L + s^2 L_p C_L}$$

$$= -g_m \cdot R_D \cdot \frac{1 + \frac{sL_p}{R_D}}{1 + sR_D C_L + s^2 L_p C_L}$$

$$\rightarrow A_v(s) = A_0 \frac{(1 + s\omega_z) \leftarrow \text{zero}}{1 + \frac{s}{Q\omega_0} + \frac{s^2}{\omega_0^2} \leftarrow \text{2nd order Denominator}}$$

$$A_0 = -g_m R_D, \quad \omega_0 = \frac{1}{\sqrt{L_p C_L}}, \quad \omega_z = \frac{R_D}{L_p} = \frac{\omega_0}{Q}$$

(parallel)

7.10 - 1st 3g

$$\sqrt{L_p C_1} \quad \sim \quad L_p \quad \omega$$

$$Q = \frac{1}{R_D} \sqrt{\frac{L_p}{C_1}}$$

(parallel
RLC tank
circuit)

